

# CMOS Differential Amplifier

## 1. Current Equations of Differential Amplifier

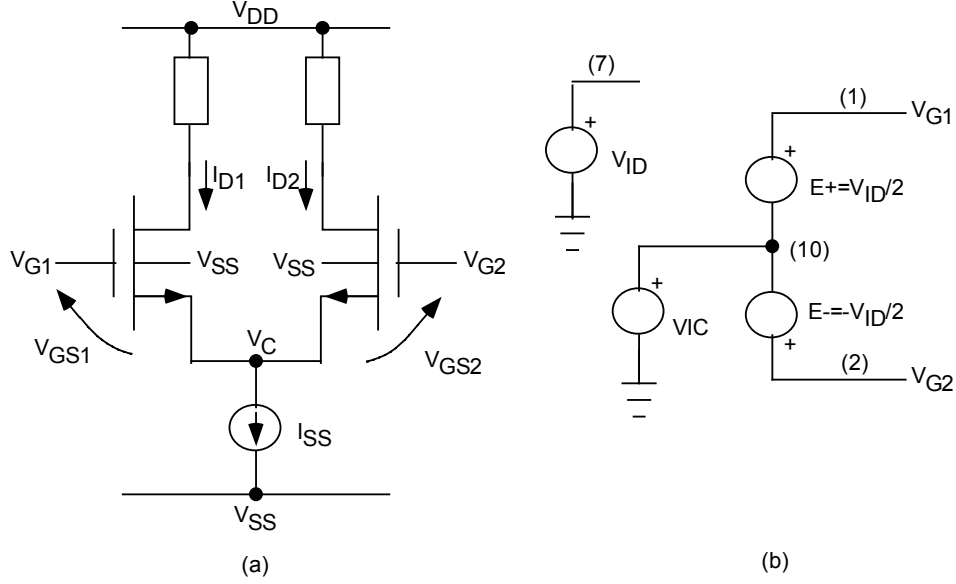


Figure 1. General MOS Differential Amplifier: (a) Schematic Diagram, (b) Input Gate Voltages Implementation.

Figure 1(a) shows the schematic diagram of a typical differential amplifier. The differential input is given by:

$$V_{ID} = V_{G1} - V_{G2} = (V_{GS1} + V_C) - (V_{GS2} + V_C) \quad --(1)$$

$$V_{ID} = V_{GS1} - V_{GS2} = (V_{GS1} - V_{TN}) - (V_{GS2} - V_{TN}) = \sqrt{\frac{2I_{D1}}{\beta_1}} - \sqrt{\frac{2I_{D2}}{\beta_2}} \quad --(2)$$

The common-mode input signal is given by:

$$V_{IC} = \frac{V_{G1} + V_{G2}}{2} \quad --(3)$$

The input voltages in term of  $V_{ID}$  and  $V_{IC}$  are given by

$$V_{G1} = V_{IC} + V_{ID}/2 \quad --(4)$$

$$V_{G2} = V_{IC} - V_{ID}/2 \quad --(5)$$

Figure 1(b) shows the implementation of the 2 gate voltages in terms of the differential and common mode voltages. Its PSpice implementation using voltage controlled voltage source is given below:

```
VID 7 0 DC 0V
E+ 1 10 7 0 0.5
E- 2 10 7 0 -0.5
VIC 10 0 DC 0V
```

Two special cases of input gate signals are of interests : pure differential and pure common mode input signals. Pure differential input signals mean  $V_{IC}=0$ , from equation (4) and (5);

$$V_{G1} = V_{ID} / 2$$

$$V_{G2} = -V_{ID} / 2$$

This case is of interest when studying the differential gain of differential amplifier, see Figure 2(a). Pure common-mode input signals mean  $V_{ID}=0$ , from equation (4) and (5);

$$V_{G1} = V_{IC}$$

$$V_{G2} = V_{IC}$$

This case is of interest when studying the common-mode gain of differential amplifier, see Figure 5(a).

Assume both transistor drivers are matched, that is:

$$\beta_1 = \beta_2 = \beta$$

$$V_{ID} = \sqrt{\frac{2I_{D1}}{\beta}} - \sqrt{\frac{2I_{D2}}{\beta}} \quad \text{--(6)}$$

$$\sqrt{\beta/2} V_{ID} = \sqrt{I_{D1}} - \sqrt{I_{D2}} \quad \text{--(7)}$$

The transistor currents satisfy the following equations:

$$I_{SS} = I_{D1} + I_{D2} \quad \text{--(8)}$$

$$I_{OD} = I_{D1} - I_{D2} \quad \text{--(9)}$$

$$I_{D1} = (I_{SS} + I_{OD}) / 2 \quad \text{--(10)}$$

$$I_{D2} = (I_{SS} - I_{OD}) / 2 \quad \text{--(11)}$$

Substituting Eq(10) and Eq(11) to Eq(7)

$$\sqrt{\beta/2} V_{ID} = \sqrt{(I_{SS} + I_{OD})/2} - \sqrt{(I_{SS} - I_{OD})/2} \quad \text{--(12)}$$

Normalizing by  $I_{SS}$

$$\sqrt{\frac{\beta}{I_{SS}}} V_{ID} = \left( \sqrt{1 + \frac{I_{OD}}{I_{SS}}} - \sqrt{1 - \frac{I_{OD}}{I_{SS}}} \right) \quad --(13)$$

To simplify the equation, let

$$x = \sqrt{\frac{\beta}{I_{SS}}} V_{ID}, \text{ and } y = \frac{I_{OD}}{I_{SS}} \quad --(14)$$

The equation reduces to:

$$x = \sqrt{1+y} - \sqrt{1-y}$$

Solve for y,

$$x^2 = (1+y) - 2\sqrt{(1+y)(1-y)} + (1-y) = 2 - 2\sqrt{1-y^2}$$

$$\sqrt{1-y^2} = 1 - \frac{x^2}{2}$$

$$1-y^2 = 1 - x^2 + \frac{x^4}{4}$$

$$y^2 = x^2 \left(1 - \frac{x^2}{4}\right)$$

The result is:

$$y = x \sqrt{1 - \frac{x^2}{4}}, \text{ provided } \left| \frac{x}{2} \right| \leq 1 \quad --(15)$$

Substituting for x and y, one obtains


$$\frac{I_{OD}}{I_{SS}} = \sqrt{\frac{\beta}{I_{SS}}} V_{ID} \sqrt{1 - \frac{\beta V_{ID}^2}{I_{SS}^4}} \quad --(16)$$

$$I_{OD} = I_{SS} \sqrt{\frac{\beta V_{ID}^2}{I_{SS}} - \frac{\beta V_{ID}^4}{4 I_{SS}^2}} \quad --(17)$$


$$I_{D1} = \frac{1}{2} I_{SS} + \frac{1}{2} I_{SS} \sqrt{\frac{\beta V_{ID}^2}{I_{SS}} - \frac{\beta V_{ID}^4}{4 I_{SS}^2}} \quad --(18)$$

$$I_{D2} = \frac{1}{2}I_{SS} - \frac{1}{2}I_{SS}\sqrt{\frac{\beta V_{ID}^2}{I_{SS}} - \frac{\beta V_{ID}^4}{4I_{SS}^2}}, \text{ provided } |V_{ID}| \leq \sqrt{\frac{2I_{SS}}{\beta}} \quad --(19)$$
 
## 2. Low Frequency Small Signal Equivalent Circuit With Pure Differential Input Signal



(a)

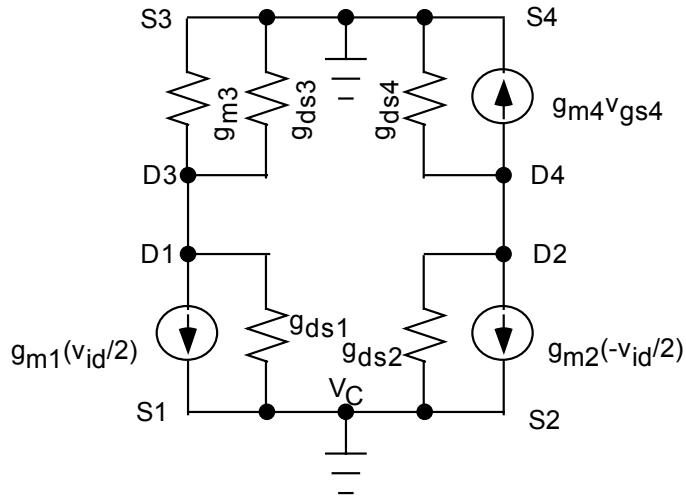

(b)

Figure 2. Differential Amplifier Implementation: (a) Differential Amplifier with PMOS current mirror load, (b) Small Signal Equivalent Circuit for Purely Differential Input Signal.

An active load acts as a current source. Thus it must be biased such that their currents add up exactly to  $I_{SS}$ . In practice this is quite difficult. Thus a feedback circuit is required to ensure this equality. This is achieved by using a current mirror circuit as load, as in Figure 2. The current mirror consists of transistor M3 and M4. One transistor (M3) is always connected as diode and drives the other transistor (M4). Since  $V_{GS3}=V_{GS4}$ , if both transistors have the same  $\beta$ , then the current  $I_{D3}$  is mirrored to  $I_{D4}$ , i.e.,  $I_{D3}=I_{D4}$ .

The advantage of this configuration is that the differential output signal is converted to a single ended output signal with no extra components required. In this circuit, the output voltage or current is taken from the drains of M2 and M4. The operation of this circuit is as follows. If a differential voltage,  $V_{ID}=V_{G1}-V_{G2}$ , is applied between the gates, then half is applied to the gate-source of M1 and half to the gate-source of M2. The result is to increase  $I_{D1}$  and decrease  $I_{D2}$  by equal increment,  $\Delta I$ . The  $\Delta I$  increase  $I_{D1}$  is mirrored through M3-M4 as an increase in  $I_{D4}$  of  $\Delta I$ . As a consequence of the  $\Delta I$  increase in  $I_{D4}$  and the  $\Delta I$  decrease in  $I_{D2}$ , the output must sink a current of  $2\Delta I$ . The sum of the changes in  $I_{D1}$  and  $I_{D2}$  at the common node  $V_C$  is zero. That is, the node  $V_C$  is at an ac ground, see Figure 2(b). From Eq(4) and Eq(5) for pure differential input signal means the common-mode signal  $V_{IC}$  is zero. That is, the input signals are  $V_{G1}=V_{ID}/2$  and  $V_{G2}=-V_{ID}/2$ . This is shown in Figure 2(a). The transconductance of the differential amplifier is given by:

$$g_{mD} = \frac{\Delta I_O}{\Delta V_{ID}} = \frac{2\Delta I}{\Delta V_{ID}} = \frac{\Delta I}{\Delta V_{ID} / 2} = \frac{\Delta I}{V_{gs1}} = g_{m1}$$

That is, the differential amplifier has the same transconductance as a single stage common source amplifier.

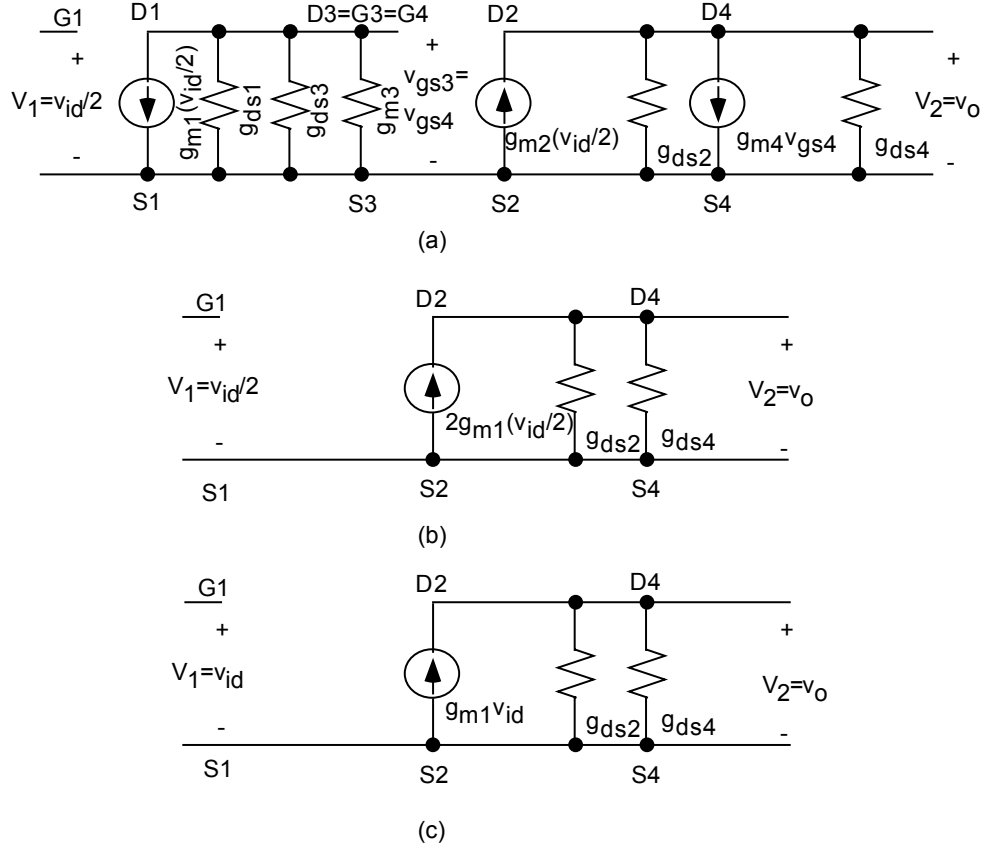


Figure 3. Differential Amplifier Operating in Purely Differential Input Signal: (a) Original Equivalent Circuit, (b) Reduction to Two-port Network, and (c) Changing Input Port Variable to  $V_1=V_{id}$ .

The derivation of the small signal equivalent circuit is shown in Figure 2. The simplification is based on the symmetry of the circuit. In Figure 2(b), each transistor equivalent circuit is drawn. Figure 3(a) redraws the equivalent circuit in Figure 2(b) in a form suitable for two-port analysis. The further reduction is obtained after the two-port parameters are obtained.

From Figure 3(a), the following two-port variables and load are obtained.

$$\begin{aligned}
 Y_L &= 0 \\
 V_1 &= V_{ID}/2 \\
 \text{and} \\
 V_2 &= V_O
 \end{aligned}$$

The port current equations are derived to obtain the Y parameters:

$$I_1 = 0 \quad \text{--(20)}$$

$$I_2 = -g_{m2} V_1 + g_{m4} V_{gs4} + (g_{ds2} + g_{ds4}) V_2 \quad \text{--(21)}$$

$$V_{gs4} = -\frac{g_{m1}}{g_{ds1} + g_{ds3} + g_{m3}} V_1 \quad --(22)$$

Substitute eq(22) to eq(21)

$$\begin{aligned} I_2 &= -g_{m2} V_1 - \frac{g_{m1} g_{m4}}{g_{ds1} + g_{ds3} + g_{m3}} V_1 + (g_{ds2} + g_{ds4}) V_2 \\ &= -(g_{m2} + \frac{g_{m1} g_{m4}}{g_{ds1} + g_{ds3} + g_{m3}}) V_1 + (g_{ds2} + g_{ds4}) V_2 \\ &= -2g_{m1} V_1 + (g_{ds2} + g_{ds4}) V_2 \end{aligned} \quad --(23)$$

assuming  $g_{m1} = g_{m2}$   $g_{m3} = g_{m4}$   $g_{m3} \gg g_{ds1} + g_{ds3}$

The resulting Y-parameter matrix is:

$$Y = \begin{bmatrix} 0 & 0 \\ -2g_{m1} & g_{ds2} + g_{ds4} \end{bmatrix}$$

The dc voltage gain is,

$$A_{VD02} = \frac{V_2}{V_1} = \frac{V_O}{V_{id}/2} = -\frac{y_{21}}{y_{22} + Y_L} = \frac{2g_{m1}}{g_{ds2} + g_{ds4}}$$

Instead of half differential input, dc gain with respect to full differential input is desired. That is,

$$A_{VDO} = \frac{V_2}{V_1} = \frac{V_O}{V_{id}} = \frac{g_{m1}}{g_{ds2} + g_{ds4}} = \frac{g_{m2}}{g_{ds2} + g_{ds4}} \quad --(24)$$






```

+ TOX=0.05U LD=0.5U CJ=5E-4 CJSW=10E-10
+ U0=200 MJ=0.5 MJSW=0.5 CGSO=0.4E-9 CGDO=0.4E-9
.DC VID -2.5 2.5 0.05V
.TF V(6) VID
.PROBE
.END

```

 

The operating point current is determined by the source current  $I_{SS}$ , which is split between the two PMOS current loaded inverters.  $I_{DSQ1}=I_{DSQ2}=I_{SS}/2$ , and similarly  $I_{DSQ3}=I_{DSQ4}=I_{SS}/2$ . For the given differential amplifier  $I_{SS}=220\mu A$ . The voltage gain is computed as follows:

$$\beta_{N1} = \beta_{N2} = K_{N1} (W_{N1} / L_{N1}) = (40E-6)(9.6\mu / (5.4\mu - 2 * 0.5\mu)) = 87.3\mu A/V^2$$

$$\beta_{P3} = \beta_{P4} = K_{P3} (W_{P3} / L_{P3}) = (15E-6)(25.8\mu / (5.4\mu - 2 * 0.5\mu)) = 87.95\mu A/V^2$$

$$g_{m1} = g_{m2} = \sqrt{2\beta_{N1}I_{DSQ1}} = \sqrt{2(87.3E-6)(110E-6)} = 138.59\mu mho$$

$$g_{m3} = g_{m4} = \sqrt{2\beta_{P3}I_{DSQ3}} = \sqrt{2(87.95E-6)(110E-6)} = 139.1\mu mho$$

$$g_{ds2} = \lambda_{DS2}I_{DSQ2} = \lambda_N I_{DSQ1} = .02(110E-6) = 2.2\mu mho$$

$$g_{ds4} = \lambda_{DS4}I_{DSQ4} = \lambda_P I_{DSQ1} = .02(110E-6) = 2.2\mu mho$$

$$g_{ds5} = \lambda_{DS5}I_{DSQ} = \lambda_P I_{DSQ5} = .02(220E-6) = 4.4\mu mho$$

$$A_{VD} \approx \frac{g_{m1}}{g_{ds2} + g_{ds4}} = \frac{138.59E-6}{2.2E-6 + 2.2E-6} = 31.5$$

The low frequency input resistance  $R_{in} = \infty$ . The output resistance  $R_{out} = 1/(g_{ds2}+g_{ds4}) = 1/(2.2E-6+2.2E-6) = .2272M$ , see Figure 3(d), and the computation above. These calculations agree well with Pspice simulation results of:

\*\*\*\* SMALL-SIGNAL CHARACTERISTICS

V(6)/VID = 3.347E+01

INPUT RESISTANCE AT VID = 1.000E+20

OUTPUT RESISTANCE AT V(6) = 2.423E+05

### **3. Determination of the input common-mode range**

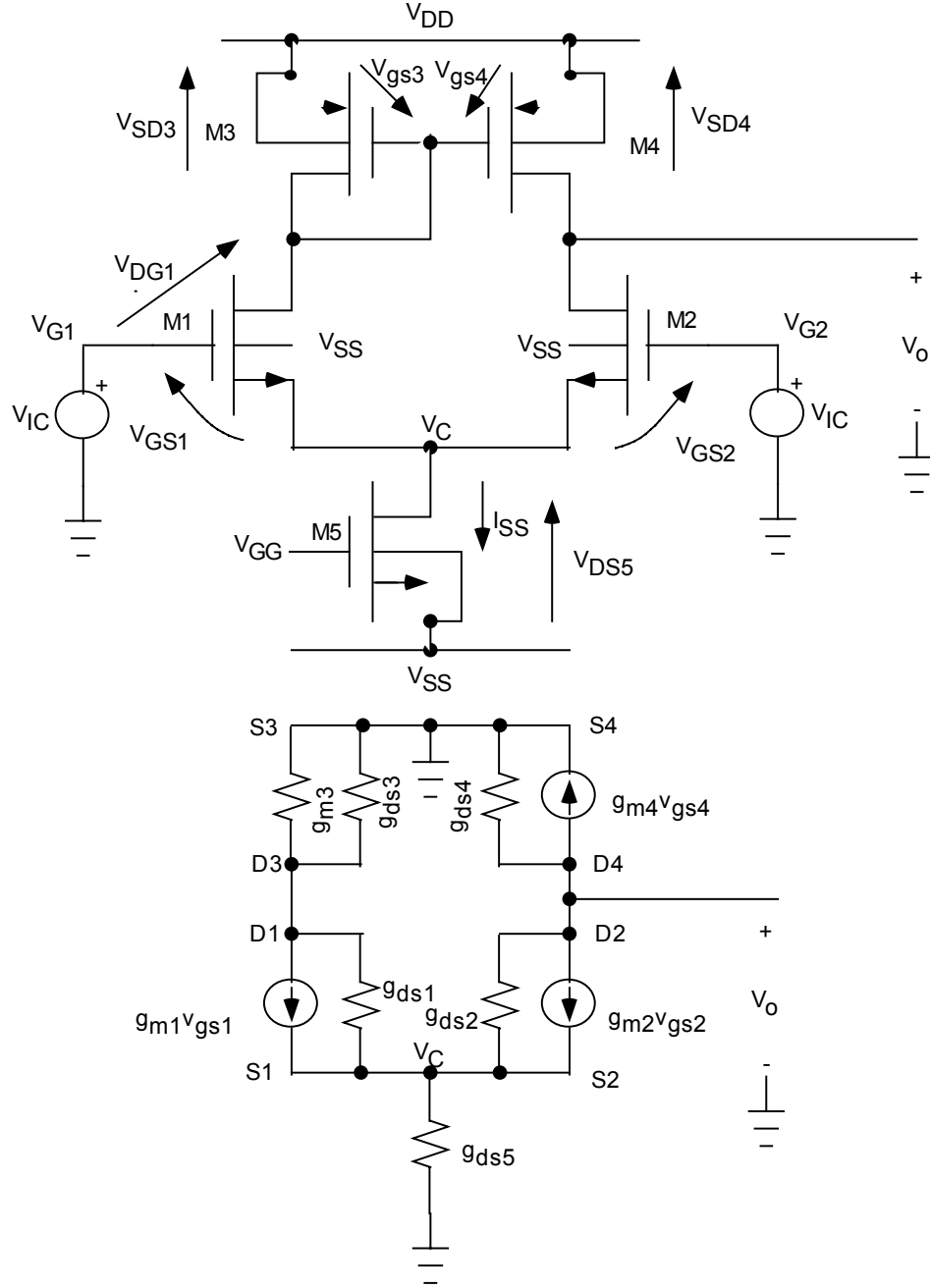


Figure 5. Differential Amplifier with Purely Common-mode Input Signal: (a) Schematic Diagram, and (b) Small Signal Equivalent Circuit.

The input common-mode range is the range of common-mode voltage  $V_{IC}=V_{G1}=V_{G2}$  in which all the transistors are operating in saturation region. To determine this a purely common-mode input is applied at both inputs, see Figure 5.

### 3.1 Maximum $V_{G1}$ or $V_{G2}$ Determination

As  $V_{G1}$  approaches  $V_{DD}$  transistor M1 and M2 go into the triode region.  $V_{G1}(\text{max})$  is the value of the input when it occurs. This can be determined from Figure 5 by writing the KVL equation from  $V_{DD}$  toward  $V_{G1}$ .

$$\begin{aligned} V_{G1} &= V_{DD} - V_{SD3} - V_{DG1} \\ &= V_{DD} - V_{SG3} - V_{DG1}, \quad \text{since } D = G \end{aligned}$$

$$V_{SG3} = (|V_{GS3}| - |V_{TP3}|) + |V_{TP3}| = \sqrt{\frac{2|I_{DS3}|}{\beta_{P3}}} + |V_{TP3}|$$

$$V_{G1} = V_{DD} - \sqrt{\frac{2|I_{DS3}|}{\beta_{P3}}} - |V_{TP3}| - V_{DG1}$$

From Figure 5(a),  $V_{DG1}$  can be determined in term of the commonly known transistor voltages of M1.

$$V_{DG1} = V_{DS1} - V_{GS1}$$

or

$$V_{DS1} = V_{GS1} + V_{DG1}$$

Transistor M1 is on saturation when the following condition holds.

$$V_{GS1} - V_{TN1} \leq V_{DS1} = V_{GS1} + V_{DG1}$$

That is,

$$-V_{TN1} \leq V_{DG1}$$

The minimum value of  $V_{DG1}$  is achieved when transistor M1 is on the threshold of saturation. That is,

$$-V_{TN1} = V_{DG1}$$

The maximum input voltage is obtained when  $-V_{TN1} = V_{DG1}$ . That is,

$$\begin{aligned} V_{G1}(\text{max}) &= V_{DD} - \sqrt{\frac{2|I_{DS3}|}{\beta_{P3}}} - |V_{TP3}| + V_{TN1} \\ &= V_{DD} - \sqrt{\frac{2|I_{DS3}|}{\beta_{P3}}} = V_{DD} - \sqrt{\frac{I_{SS}}{\beta_{P3}}} \end{aligned} \quad \text{--(25)}$$

Assuming  $|V_{TP3}| \approx V_{TN1}$ .

### 3.2 Minimum $V_{G1}$ or $V_{G2}$ Determination

As  $V_{G1}$  approaches  $V_{SS}$ , M1 becomes cutoff. The minimum input voltage  $V_{G1}$  is determined when M5 is no longer in saturation. This is obtained by writing the KVL equation from  $V_{SS}$  to  $V_{G1}$ .

$$V_{G1} = V_{SS} + V_{DS5} + V_{GS1}$$

Transistor M5 is on saturation when,

$$V_{GS5} - V_{TN5} \leq V_{DS5}$$

M5 is at verge of saturation when,  $V_{GS5} - V_{TN5} = V_{DS5} = V_{DS5(SAT)}$

That is, the minimum input voltage occurs when,  $V_{GS5} - V_{TN5} = V_{DS5(SAT)}$ .

$$V_{G1}(\min) = V_{SS} + V_{DS5(SAT)} + V_{GS1} \quad \text{--(26)}$$

$$V_{G1}(\min) = V_{SS} + (V_{GS5} - V_{TN5}) + V_{GS1}$$

$$\begin{aligned} V_{G1}(\min) &= V_{SS} + (V_{GG} - V_{SS} - V_{TN5}) + (V_{GS1} - V_{TN1}) + V_{TN1} \\ &= V_{GG} - V_{TN5} + \sqrt{\frac{2I_{DS1}}{\beta_{N1}}} + V_{TN1} \\ &= V_{GG} + \sqrt{\frac{2I_{DS1}}{\beta_{N1}}} = V_{GG} + \sqrt{\frac{I_{SS}}{\beta_{N1}}} \end{aligned} \quad \text{--(27)}$$

Ignoring the bulk bias effect.

Using the SPICE parameters for the differential amplifier implemented in Figure 4.

From Eq(25),

$$V_{G1}(\max) = V_{DD} - \sqrt{\frac{I_{SS}}{\beta_{P3}}}$$

$$\beta_{P3} = K_P (W_3 / L_3) = (15E-6)(25.8u / (5.4u - 2 * 0.5u)) = 87.95 \mu A/V^2$$

$$V_{G1}(\max) = 2.5 - \sqrt{\frac{220E-6}{87.95E-6}} = 2.5 - 1.58 = 0.92 \text{ V}$$

and from Eq(27),

$$V_{G1}(\min) = \sqrt{\frac{I_{SS}}{\beta_{N1}}} + V_{GG} = \sqrt{\frac{220E-6}{87.3}} - 1.2 = 1.58 - 1.2 = 0.38 \text{ V}$$

To guarantee that the differential amplifier stays on the linear region of operation, set common-mode signal at half way the common-mode range. That is,  $V_{IC} = [V_{G1}(\max) + V_{G1}(\min)]/2 = [0.92 + 0.38]/2 = 0.65$ .

#### 4. Low Frequency Small Signal Equivalent Circuit With Pure Common-Mode Input Signal

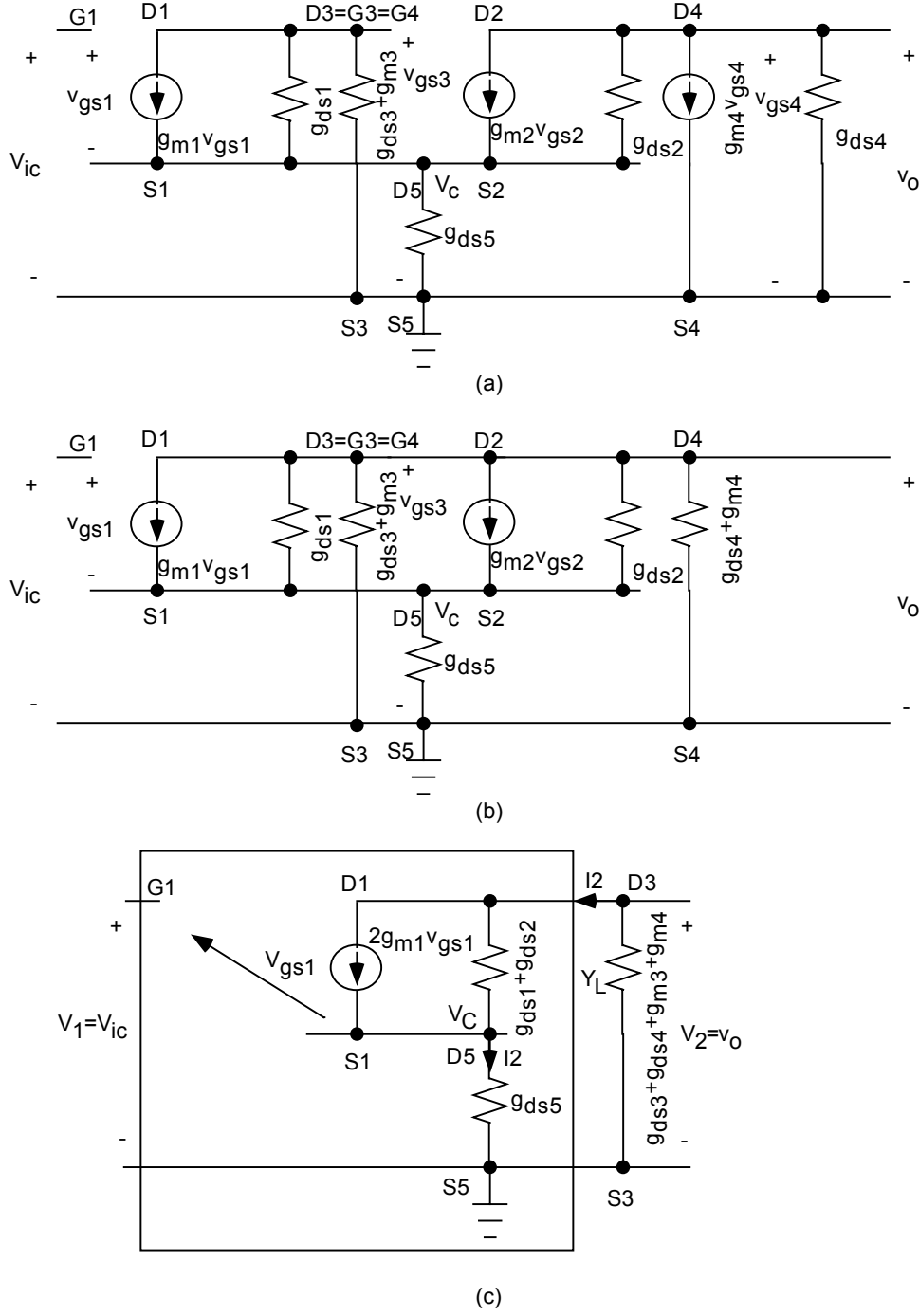


Figure 6. Small Signal Equivalent Circuit: (a) Original Small Signal Equivalent Circuit, (b) Accounting for Source Values and Polarities, and (c) Two-port Conversions.

Figure 5(a) shows the schematic when a purely common-mode input is applied at both inputs that is,  $V_{G1}=V_{G2}=V_{ic}$ . If  $V_{ic}$  increases both  $I_{D1}$  and  $I_{D2}$  increases. Their sum at the common node  $V_c$  also increases. Figure 5(b) shows that  $V_c$  is not at ac ground, unlike the pure differential input signal case shown in Figure 2(b). Due to signal symmetry when both inputs are the same,  $V_{DS3}=V_{DS4}$ . Since both G and S of  $M3$  and  $M4$  are connected to each other, means  $V_{GS3}=V_{GS4}$ .  $M3$  is diode connected with G and D connected, means  $V_{GS3}=V_{DS3}$ . From these expressions,  $V_{DS4}=V_{GS4}$  can be deduced. That is the voltage

across D and S of M4 can be labelled as  $V_{GS4}$ , see Figure 6(a). The current source of M4 is therefore reduced to conductance  $g_{m4}$ , see Figure 6(b). Since  $V_{DS3}=V_{DS4}$ , the D3 and D4 can be connected together. Figure 6(c) shows the final equivalent circuit after combining all components that are in parallel.

From Figure 6(c), the following two-port variables and load are obtained.

$$Y_L = g_{ds3} + g_{ds4} + g_{m3} + g_{m4} = 2g_{ds3} + 2g_{m3}$$

$$\text{assuming } g_{ds3} = g_{ds4} \quad g_{m3} = g_{m4}$$

$$V_1 = V_{IC}$$

and

$$V_2 = V_O$$

The two-port current equations are derived to obtain the Y parameters.

$$I_1 = 0$$

$$\begin{aligned} I_2 &= (g_{ds1} + g_{ds2})(V_2 - V_C) + 2g_{m1}(V_1 - V_C) \\ &= 2g_{m1}V_1 + (g_{ds1} + g_{ds2})V_2 - (g_{ds1} + g_{ds2} + 2g_{m1})V_C \end{aligned}$$

$$V_C = \frac{1}{g_{ds5}}I_2$$

$$I_2 = 2g_{m1}V_1 + (g_{ds1} + g_{ds2})V_2 - (g_{ds1} + g_{ds2} + 2g_{m1})\frac{1}{g_{ds5}}I_2$$

$$I_2 = \frac{2g_{m1}g_{ds5}}{g_{ds1} + g_{ds2} + g_{ds5} + 2g_{m1}}V_1 + \frac{(g_{ds1} + g_{ds2})g_{ds5}}{g_{ds1} + g_{ds2} + g_{ds5} + 2g_{m1}}V_2$$

The Y-parameter matrix is:

$$\begin{aligned} Y &= \begin{bmatrix} 0 & 0 \\ \frac{2g_{m1}g_{ds5}}{g_{ds1} + g_{ds2} + g_{ds5} + 2g_{m1}} & \frac{(g_{ds1} + g_{ds2})g_{ds5}}{g_{ds1} + g_{ds2} + g_{ds5} + 2g_{m1}} \end{bmatrix} \\ &= \begin{bmatrix} 0 & 0 \\ \frac{2g_{m1}g_{ds5}}{2g_{ds1} + g_{ds5} + 2g_{m1}} & \frac{2g_{ds1}g_{ds5}}{2g_{ds1} + g_{ds5} + 2g_{m1}} \end{bmatrix} \end{aligned}$$

$$\text{assuming } g_{ds1} = g_{ds2} \quad g_{m3} = g_{m4}$$

The dc common-mode voltage gain is,

$$\begin{aligned}
A_{VC0} &= \frac{-y_{21}}{y_{22} + Y_L} = \frac{-\frac{2g_{m1}g_{ds5}}{2g_{ds1} + g_{ds5} + 2g_{m1}}}{\frac{2g_{ds1}g_{ds5}}{2g_{ds1} + g_{ds5} + 2g_{m1}} + 2(g_{ds3} + g_{m3})} \\
&= \frac{-2g_{m1}g_{ds5}}{2g_{ds1}g_{ds5} + 2(g_{ds3} + g_{m3})(2g_{ds1} + g_{ds5} + 2g_{m1})} \\
&= \frac{-\frac{g_{m1}}{g_{m3}}}{\frac{g_{ds1}}{g_{m3}} + 1 + \frac{2g_{ds1} + 2g_{m1}}{g_{ds5}}} \approx \frac{-\frac{g_{m1}}{g_{m3}}}{1 + 2g_{m1}r_{ds5}} \approx \frac{-\frac{g_{m1}}{g_{m3}}}{2g_{m1}r_{ds5}} \approx \frac{-1}{2g_{m3}r_{ds5}}
\end{aligned}$$



assuming  $g_{m3} \gg g_{ds3}$ .

```

* Filename="diffvic.cir"
* MOS Diff Amp with Current Mirror Load
*DC Transfer Characteristics vs VIC
VID 7 0 DC 0V
E+ 1 10 7 0 0.5
E- 2 10 7 0 -0.5
VIC 10 0 DC 0V
VDD 3 0 DC 2.5VOLT
VSS 4 0 DC -2.5VOLT
M1 5 1 8 8 NMOS1 W=9.6U L=5.4U
M2 6 2 8 8 NMOS1 W=9.6U L=5.4U
M3 5 5 3 3 PMOS1 W=25.8U L=5.4U
M4 6 5 3 3 PMOS1 W=25.8U L=5.4U
M5 8 9 4 4 NMOS1 W=21.6U L=1.2U
M6 9 9 4 4 NMOS1 W=100.8U L=3.6U
M7 9 9 3 3 PMOS1 W=3.6U L=3.6U
.MODEL NMOS1 NMOS VTO=1 KP=40U
+ GAMMA=1.0 LAMBDA=0.02 PHI=0.6
+ TOX=0.05U LD=0.5U CJ=5E-4 CJSW=10E-10
+ U0=550 MJ=0.5 MJSW=0.5 CGSO=0.4E-9 CGDO=0.4E-9
.MODEL PMOS1 PMOS VTO=-1 KP=15U
+ GAMMA=0.6 LAMBDA=0.02 PHI=0.6
+ TOX=0.05U LD=0.5U CJ=5E-4 CJSW=10E-10
+ U0=200 MJ=0.5 MJSW=0.5 CGSO=0.4E-9 CGDO=0.4E-9
.OP
.DC VIC -2.5 2.5 0.05V
.TF V(6) VIC
.PROBE
.END

```



 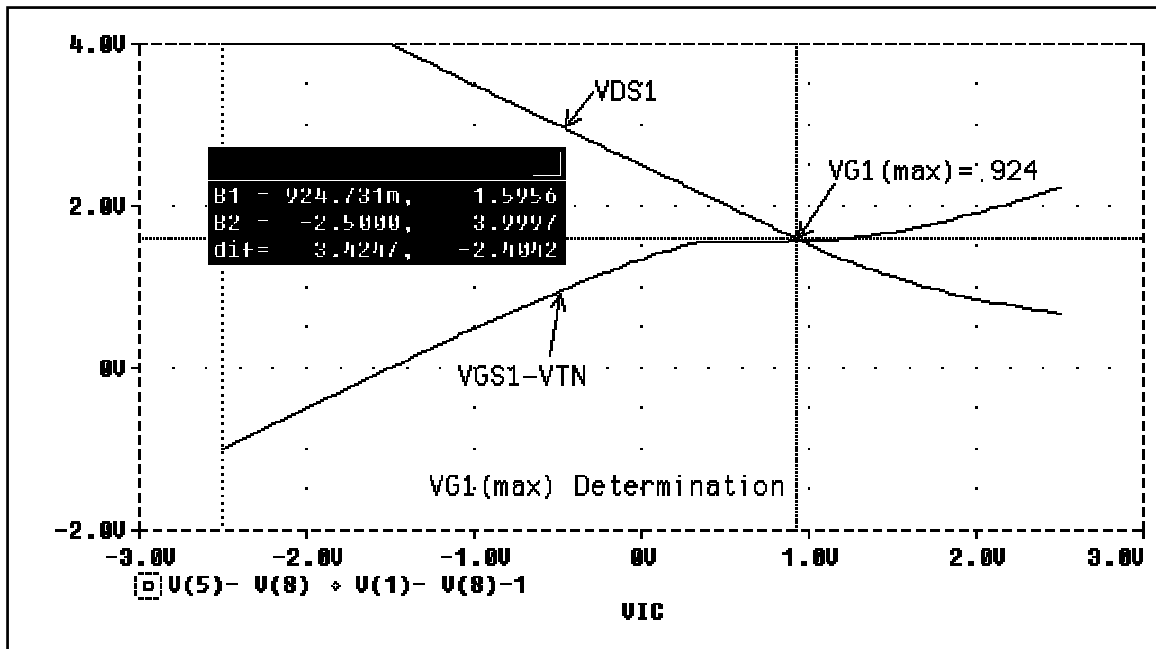

$$A_{VCO} = -\frac{1}{2g_{m3}r_{ds5}} = -\frac{1}{2(139.1E-6)(.2272E6)} = -0.01582$$

This is very closed to the PSpice simulation result.

\*\*\*\* SMALL-SIGNAL CHARACTERISTICS

$$V(6)/VIC = -1.459E-02$$

$$\text{INPUT RESISTANCE AT VIC} = 1.000E+20$$

$$\text{OUTPUT RESISTANCE AT V(6)} = 2.386E+05$$

The goal of differential amplifier is to amplify the difference signal and to reject common-mode signal. A figure of merit called common-mode rejection ration (CMRR) is defined as:

$$\text{CMRR} = \left| \frac{A_{VD}}{A_{VC}} \right| = \left| \frac{31.5}{-0.01582} \right| = 1991.15$$

## **5. Differential Gain Frequency Response**

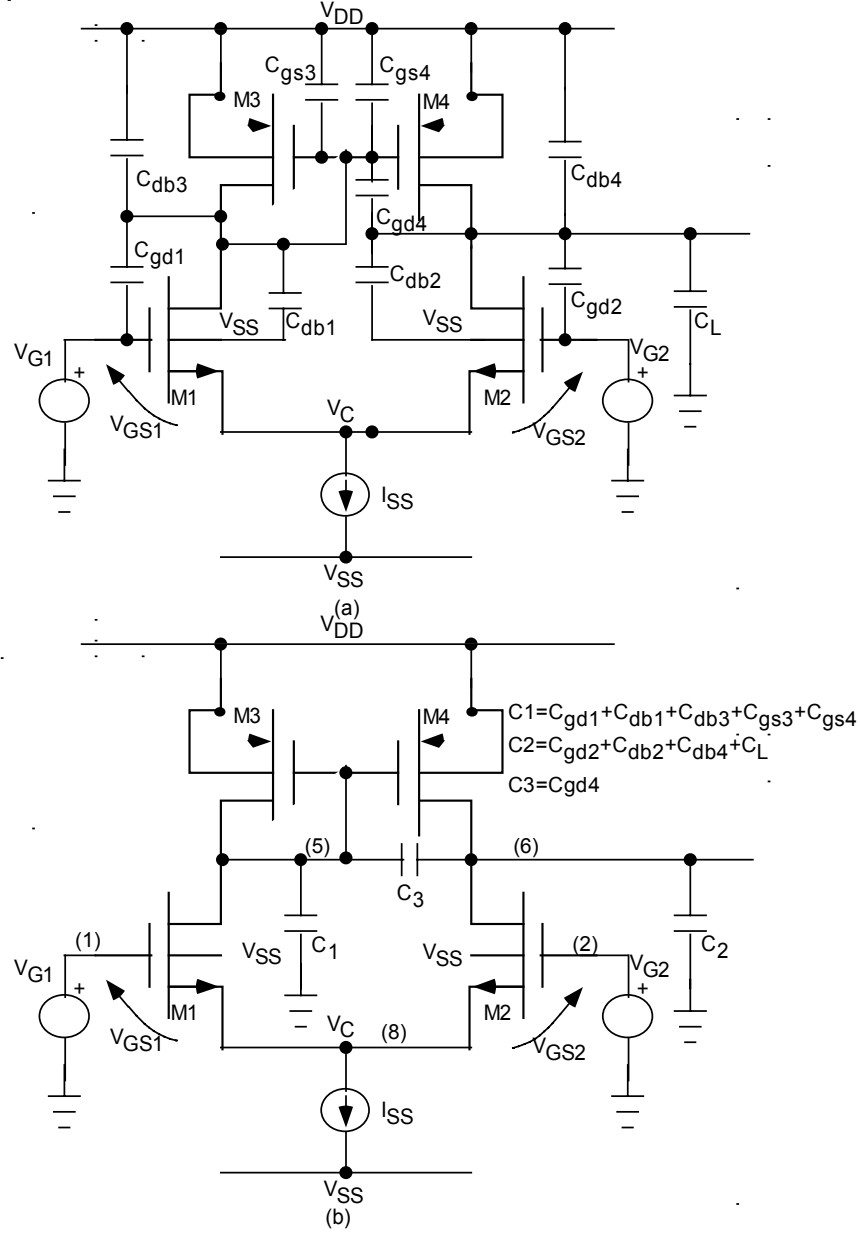



Figure 7. Parasitic Capacitances of Differential Amplifier Operating in Purely Differential Input Signal: (a) Parasitic Capacitances of each Transistor, (b) Lumped Parasitic Capacitances.

Figure 7(a) shows all the parasitic capacitances of the differential amplifier with purely differential input signals. Since both inputs are voltage sources, they are at ac ground when considering the effects of gate capacitances. Figure 7(b) shows that there are basically three capacitances. These are:

$$C_1 = C_{gd1} + C_{db1} + C_{db3} + C_{gs3} + C_{gs4}$$

$$C_2 = C_{gd2} + C_{db2} + C_{db4} + C_L$$

$$C_3 = C_{gd4}$$

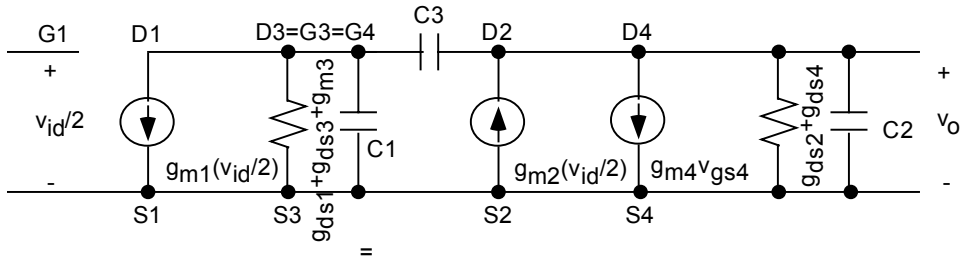


$$C1 = C_{gd1} + C_{db1} + C_{db3} + C_{gs3} + C_{gs4}$$

$$C2 = C_{gd2} + C_{db2} + C_{db4} + C_L$$

$$C3 = C_{gd4}$$

(a)

 

(b)  $g_{m1} = g_{m2}$

Figure 8. High Frequency Small Signal Equivalent Circuit: (a) Small Signal Equivalent Circuit Showing Lumped Capacitances, (b) Small Signal Equivalent Circuit Combining Capacitance and Resistance to Admittance.

**NOTE**  $C_3$  is not a miller capacitance, it is connected between the outputs of the two inverter amplifiers, and not between an output and an input terminals of an amplifier.  $C_3$  in this case is normally small and can be ignored. Figure 8(b) shows that the three admittances are given by:

$$Y_1 = g_{ds1} + g_{ds3} + g_{m3} + sC_1$$

$$Y_2 = g_{ds2} + g_{ds4} + sC_2$$

$$Y_3 = sC_3 = sC_{gd4}$$

The two-port Y parameters are to be determined. Figure 8(b) shows that the two-port variables are:

$$Y_L = 0$$

$$V_1 = v_{id}/2$$

and

$$V_2 = v_o$$

$$I_1 = 0$$

$$\begin{aligned} I_2 &= Y_3(V_2 - V_{gs4}) - g_{m1}V_1 + g_{m4}V_{gs4} + Y_2V_2 \\ &= -g_{m1}V_1 + (Y_2 + Y_3)V_2 + (-Y_3 + g_{m4})V_{gs4} \end{aligned}$$

At node D3

$$I_3 + g_{m1}V_1 - Y_3(V_2 - V_{gs4}) = 0$$

$$I_3 = Y_1V_{gs4}$$

$$Y_1V_{gs4} + g_{m1}V_1 - Y_3(V_2 - V_{gs4}) = 0$$

Solve for  $V_{gs4}$

$$V_{gs4} = \frac{-g_{m1}}{Y_1 + Y_3}V_1 + \frac{Y_3}{Y_1 + Y_3}V_2$$

$$\begin{aligned} I_2 &= -g_{m1}V_1 + (Y_2 + Y_3)V_2 + (-Y_3 + g_{m4})\left(\frac{-g_{m1}}{Y_1 + Y_3}V_1 + \frac{Y_3}{Y_1 + Y_3}V_2\right) \\ &= \frac{-g_{m1}Y_1 - g_{m1}g_{m4}}{Y_1 + Y_3}V_1 + \frac{Y_1Y_2 + Y_1Y_3 + Y_2Y_3 + g_{m1}Y_3}{Y_1 + Y_3}V_2 \end{aligned}$$

The Y-parameter matrix is:

$$Y = \begin{bmatrix} 0 & 0 \\ \frac{-g_{m1}Y_1 - g_{m1}g_{m4}}{Y_1 + Y_3} & \frac{Y_1Y_2 + Y_1Y_3 + Y_2Y_3 + g_{m1}Y_3}{Y_1 + Y_3} \end{bmatrix}$$

For differential amplifier the assumption that  $Y_3$  or  $C_3$  is approximately 0 is valid. That is,

$$Y = \begin{bmatrix} 0 & 0 \\ -g_{m1} - \frac{g_{m1}g_{m4}}{Y_1} & Y_2 \end{bmatrix}$$

The differential gain is given by:

$$\begin{aligned}
A_{VD2} &= \frac{V_2}{V_1} = \frac{-y_{21}}{y_{22} + Y_L} = \frac{g_{m1} + \frac{g_{m1}g_{m4}}{Y_1}}{Y_2} = \frac{g_{m1}(1 + \frac{g_{m4}}{Y_1})}{Y_2} \\
&= \frac{g_{m1}(1 + \frac{g_{m4}}{g_{ds1} + g_{ds3} + g_{m3} + sC_1})}{(g_{ds2} + g_{ds4} + sC_2)} = \frac{g_{m1}(g_{ds1} + g_{ds3} + g_{m3} + g_{m4} + sC_1)}{(g_{ds1} + g_{ds3} + g_{m3} + sC_1)(g_{ds2} + g_{ds4} + sC_2)} \\
&= \left( \frac{g_{m1}}{g_{ds2} + g_{ds4}} \right) \frac{(g_{ds1} + g_{ds3} + g_{m3} + g_{m4}) \left( 1 + s \frac{C_1}{g_{ds1} + g_{ds3} + g_{m3} + g_{m4}} \right)}{(g_{ds1} + g_{ds3} + g_{m3}) \left( 1 + s \frac{C_1}{g_{ds1} + g_{ds3} + g_{m3}} \right) \left( 1 + s \frac{C_2}{g_{ds2} + g_{ds4}} \right)} \\
&= 2 \left( \frac{g_{m1}}{g_{ds2} + g_{ds4}} \right) \frac{\left( 1 + s \frac{C_1}{g_{ds1} + g_{ds3} + g_{m3} + g_{m4}} \right)}{\left( 1 + s \frac{C_1}{g_{ds1} + g_{ds3} + g_{m3}} \right) \left( 1 + s \frac{C_2}{g_{ds2} + g_{ds4}} \right)}
\end{aligned}$$

The differential gain when the input voltage  $V_1$  is changed to  $V_{ID}$  is:

$$\begin{aligned}
A_{VD} &= \frac{V_O}{V_{id}} = \left( \frac{g_{m1}}{g_{ds2} + g_{ds4}} \right) \frac{\left( 1 + s \frac{C_1}{g_{ds1} + g_{ds3} + g_{m3} + g_{m4}} \right)}{\left( 1 + s \frac{C_1}{g_{ds1} + g_{ds3} + g_{m3}} \right) \left( 1 + s \frac{C_2}{g_{ds2} + g_{ds4}} \right)} \\
&= A_{VDO} \frac{(1 - \frac{s}{z})}{(1 - \frac{s}{p_2})(1 - \frac{s}{p_1})}
\end{aligned}$$

where :

$$\begin{aligned}
p_1 &= -\frac{g_{ds2} + g_{ds4}}{C_2} \\
p_2 &= -\frac{g_{ds1} + g_{ds3} + g_{m3}}{C_1} \approx -\frac{g_{m3}}{C_1} \\
z &= -\frac{g_{ds1} + g_{ds3} + g_{m3} + g_{m4}}{C_1} \approx -\frac{2g_{m3}}{C_1}
\end{aligned}$$

$$p_1 \ll p_2 \ll z$$


NOTE the differential voltage gain has pole-zero doublets. That is, the zero  $z$  is double that of the non-dominant pole  $p_2$ . The dominant (lowest frequency) pole  $p_1$  occurs at the output node. The above transfer function can also be obtained by noting that each pole correspond to a node in the differential amplifier.

Each node is at a finite impedance with respect to ground. That is, each node there is a resistance  $R_n$  (or conductance) and capacitance  $C_n$  to ground. To determine which poles are dominant (or more significant), the impedance levels must be monitored. The parasitic capacitances  $C_n$  are of approximately the same magnitude, but  $R_n$  usually vary considerably. When the resistance (conductance) is high (low), a dominant pole is generated. The impedance levels are summarized in the following table:

Node(From Netlist)	Resistance	Capacitance	Pole
1	0 (ac ground)		X
2	0 (ac ground)		X
5	$R_5=1/(g_{ds1}+g_{ds3}+g_{m3})$	$C_1$	$p_2=1/(R_5C_1)^*$
6	$R_6=1/(g_{ds2}+g_{ds4})$	$C_2$	$p_1=1/(R_6C_2)$
8	0 (ac ground)		X

The derivation shows that the pole  $p_2$  create a zero doublet.

```
* Filename="diffreq.cir"
* MOS Diff Amp with Current Mirror Load
*DC Transfer Characteristics vs VID
VID 7 0 DC 0V AC 1V
E+ 1 10 7 0 0.5
E- 2 10 7 0 -0.5
VIC 10 0 DC 0.65V
VDD 3 0 DC 2.5VOLT
VSS 4 0 DC -2.5VOLT
M1 5 1 8 8 NMOS1 W=9.6U L=5.4U
M2 6 2 8 8 NMOS1 W=9.6U L=5.4U
M3 5 5 3 3 PMOS1 W=25.8U L=5.4U
M4 6 5 3 3 PMOS1 W=25.8U L=5.4U
M5 8 9 4 4 NMOS1 W=21.6U L=1.2U
M6 9 9 4 4 NMOS1 W=100.8U L=3.6U
M7 9 9 3 3 PMOS1 W=3.6U L=3.6U
.MODEL NMOS1 NMOS VTO=1 KP=40U
+ GAMMA=1.0 LAMBDA=0.02 PHI=0.6
+ TOX=0.05U LD=0.5U CJ=5E-4 CJSW=10E-10
+ U0=550 MJ=0.5 MJSW=0.5 CGSO=0.4E-9 CGDO=0.4E-9
.MODEL PMOS1 PMOS VTO=-1 KP=15U
+ GAMMA=0.6 LAMBDA=0.02 PHI=0.6
+ TOX=0.05U LD=0.5U CJ=5E-4 CJSW=10E-10
+ U0=200 MJ=0.5 MJSW=0.5 CGSO=0.4E-9 CGDO=0.4E-9
.AC DEC 100 1HZ 100000GHZ
.PROBE
.END
```

 

## 6. Common-Mode Frequency Response



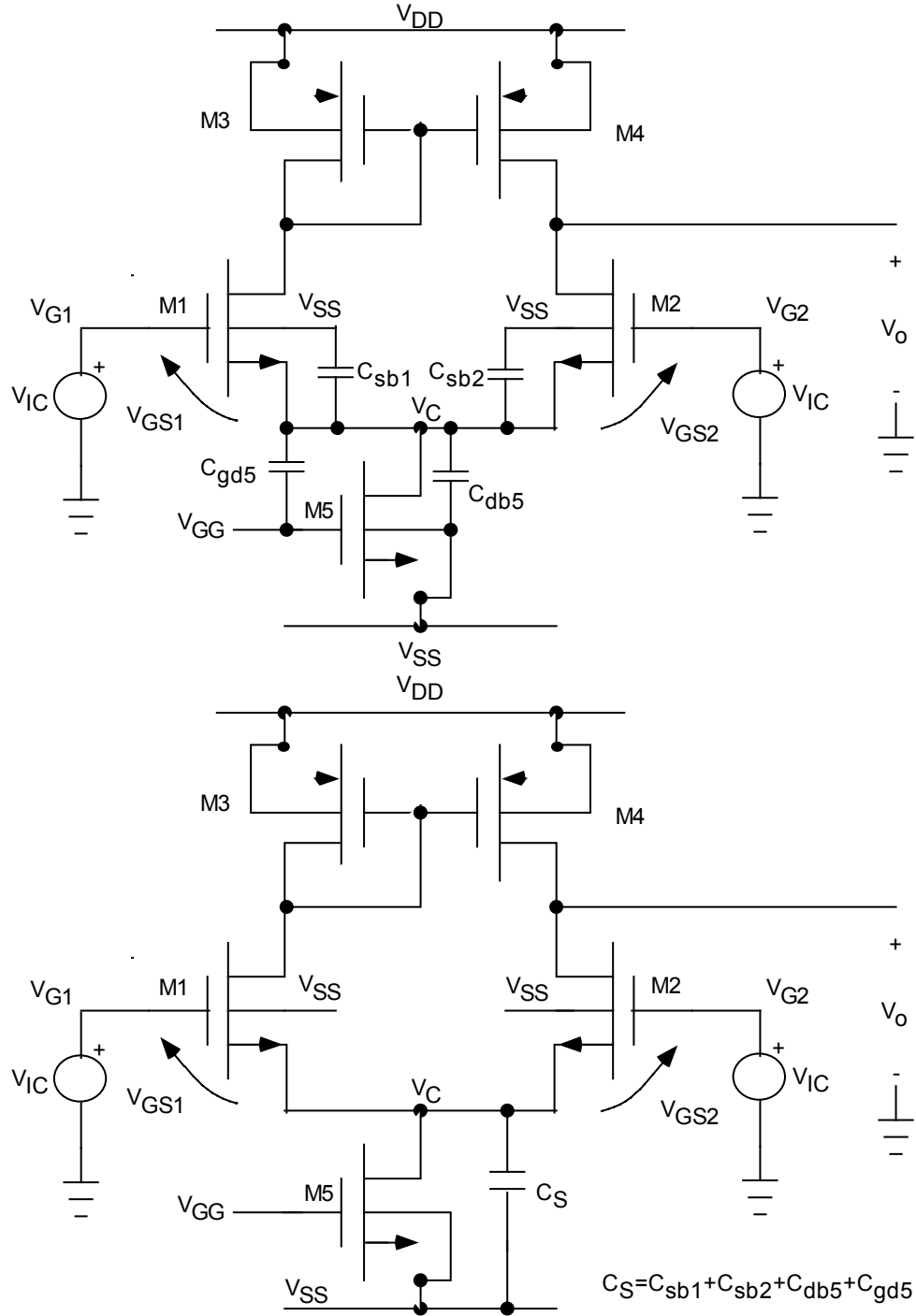


Figure 9. Differential Amplifier Operating in Pure Common-Mode Input Signal: (a) All Parasitic Capacitances at Common Node  $V_C$ , (b) Total Capacitances Across the Drain and Source of  $M_5$ .

From the expression of the dc common-mode gain, it is primarily a function of  $g_{m3}$  and  $r_{ds5}$ . The first order frequency response analysis can be simplified by ignoring all parasitic capacitances except the capacitance  $C_S$  across  $r_{ds5}$ , see Figure 9. That is  $r_{ds5}$  is replaced by  $z_{ds5}$  in the common-mode gain expression to account for frequency dependency.


$$z_{ds5} = (r_{ds5} // C_S) = \frac{r_{ds5}}{1 + sr_{ds5} C_S}$$

$$A_{VC} = \frac{-1}{2g_{m3} z_{ds5}} = \frac{-1}{2g_{m3} \frac{r_{ds5}}{1 + sr_{ds5} C_S}} = \frac{-(1 + sr_{ds5} C_S)}{2g_{m3} r_{ds5}}$$

where :

$$C_S = C_{sb1} + C_{sb2} + C_{db5} + C_{gd5}$$

```
* Filename="diffreqc.cir"
* MOS Diff Amp with Current Mirror Load
*DC Transfer Characteristics vs VIC
VID 7 0 DC 0V
E+ 1 10 7 0 0.5
E- 2 10 7 0 -0.5
VIC 10 0 DC 0.65V AC 1V
VDD 3 0 DC 2.5VOLT
VSS 4 0 DC -2.5VOLT
M1 5 1 8 8 NMOS1 W=9.6U L=5.4U
M2 6 2 8 8 NMOS1 W=9.6U L=5.4U
M3 5 5 3 3 PMOS1 W=25.8U L=5.4U
M4 6 5 3 3 PMOS1 W=25.8U L=5.4U
M5 8 9 4 4 NMOS1 W=21.6U L=1.2U
M6 9 9 4 4 NMOS1 W=100.8U L=3.6U
M7 9 9 3 3 PMOS1 W=3.6U L=3.6U
.MODEL NMOS1 NMOS VTO=1 KP=40U
+ GAMMA=1.0 LAMBDA=0.02 PHI=0.6
+ TOX=0.05U LD=0.5U CJ=5E-4 CJSW=10E-10
+ U0=550 MJ=0.5 MJSW=0.5 CGSO=0.4E-9 CGDO=0.4E-9
.MODEL PMOS1 PMOS VTO=-1 KP=15U
+ GAMMA=0.6 LAMBDA=0.02 PHI=0.6
+ TOX=0.05U LD=0.5U CJ=5E-4 CJSW=10E-10
+ U0=200 MJ=0.5 MJSW=0.5 CGSO=0.4E-9 CGDO=0.4E-9
.AC DEC 100 1HZ 100000GHZ
.PROBE
.END
```

 

The differential-mode voltage gain decreases with increasing frequency but common-mode voltage increases. Therefore, CMRR decreases with increasing frequency.

## 7. Designing Differential Amplifier With Specified CMR

Given a common-mode range of  $-0.75 \leq V_{IC} \leq 0.75$ ,  $V_{GG} = -1$ ,  $I_{SS} = I_{DS5} = 100 \mu A$ ,  $L_{min} = 5.4 \mu m$ ,  $\Delta V = V_{GS} - V_{TN} = 0.5$ . Determine the size of each transistor in the differential amplifier circuit, see Figure 4.

1. Determine the  $(W/L)_5$  to sink  $100 \mu A$ .

$$I_{DS5} = \frac{\beta_{N5}}{2} (V_{GS5} - V_{TN5})^2 = \frac{K_N}{2} \left( \frac{W}{L} \right)_5 (V_{GS5} - V_{TN5})^2$$

$$\left( \frac{W}{L} \right)_5 = \frac{2I_{DS5}}{K_N (V_{GS5} - V_{TN5})^2} = \frac{2I_{DS5}}{K_N (V_{GG} - V_{SS} - V_{TN5})^2}$$

$$= \frac{2(100E-6)}{(40E-6)[-1 - (-2.5) - 1]^2} = 20 = \left( \frac{108 \mu}{5.4 \mu} \right)$$

2. Determine  $(W/L)_1 = (W/L)_2$  from  $V_{IC(min)} = V_{G1(min)}$  specification

From Eq(26),

$$V_{IC} = V_{G1}(\min) = V_{SS} + V_{DS5(SAT)} + V_{GS1} \geq -0.75$$

$$V_{GS1} \geq -0.75 - V_{SS} - V_{DS5(SAT)} = -0.75 - (-2.5) - 0.5 = 1.25$$

$$\left(\frac{W}{L}\right)_1 = \left(\frac{W}{L}\right)_2 = \frac{2I_{DS1}}{K_N(V_{GS1} - V_{TN})^2} = \frac{2(50E-6)}{(40E-6)(1.25-1)^2} = 40 = \left(\frac{216u}{5.4u}\right)$$

3. Determine (W/L)<sub>3</sub>=(W/L)<sub>4</sub> from V<sub>IC</sub>(max)=V<sub>G1</sub>(max) specification

From Eq(25),

$$V_{IC}(\max) = V_{G1}(\max) = V_{DD} - \sqrt{\frac{2|I_{DS3}|}{\beta_{P3}}}$$

$$|I_{DS3}| = \frac{\beta_{P3}}{2}(V_{DD} - V_{G1}(\max))^2 = \frac{K_P}{2}\left(\frac{W}{L}\right)_3(V_{DD} - V_{G1}(\max))^2$$

$$\left(\frac{W}{L}\right)_3 = \frac{2|I_{DS3}|}{K_P(V_{DD} - V_{G1}(\max))^2} = \frac{2(50E-6)}{(15E-6)(2.5-0.75)^2} = 2.177 = \left(\frac{11.75u}{5.4u}\right)$$

The above is simulated using PSpice. The results agree well with the calculations.

```
* Filename="diffcmr.cir"
* MOS Diff Amp with Current Mirror Load
*DC Transfer Characteristics vs VIC
VID 7 0 DC 0V
E+ 1 10 7 0 0.5
E- 2 10 7 0 -0.5
VIC 10 0 DC 0V
VDD 3 0 DC 2.5VOLT
VSS 4 0 DC -2.5VOLT
M1 5 1 8 8 NMOS1 W=216U L=5.4U
M2 6 2 8 8 NMOS1 W=216U L=5.4U
M3 5 5 3 3 PMOS1 W=11.75U L=5.4U
M4 6 5 3 3 PMOS1 W=11.75U L=5.4U
M5 8 9 4 4 NMOS1 W=108U L=5.4U
VGG 9 0 DC -1V
.MODEL NMOS1 NMOS VTO=1 KP=40U
+ GAMMA=1.0 LAMBDA=0.02 PHI=0.6
+ TOX=0.05U LD=0.5U CJ=5E-4 CJSW=10E-10
+ U0=550 MJ=0.5 MJSW=0.5 CGSO=0.4E-9 CGDO=0.4E-9
.MODEL PMOS1 PMOS VTO=-1 KP=15U
+ GAMMA=0.6 LAMBDA=0.02 PHI=0.6
+ TOX=0.05U LD=0.5U CJ=5E-4 CJSW=10E-10
+ U0=200 MJ=0.5 MJSW=0.5 CGSO=0.4E-9 CGDO=0.4E-9
.DC VIC -2.5 2.5 0.05V
.TF V(6) VIC
.PROBE
.END
```

