

Summary inf3410



- CMOS amplifiers
 - Continuous time
 - Integrated modern technology
 - Single stage amps
 - Two-stage amps
 - Frequency response
 - Feedback topologies

TSL inf3410

1

MOS models



- Transistor operating regions
 - Drain-source biasing
 - Triode (linear) region $V_{DS} < V_{DS-sat} = V_{GS} - V_{th} = V_{eff}$
 - Active (saturation) region $V_{DS} > V_{DS-sat} = V_{GS} - V_{th} = V_{eff}$
 - Gate biasing in active region
 - Weak inversion/subthreshold $V_{GS} < V_{th}$
 - Strong inversion $V_{GS} > V_{th}$
 - Mobility degradation
 - At high current densities

TSL inf3410

2

MOS modeling




- Small signal models

- Active region

- Low frequencies

- Medium frequencies

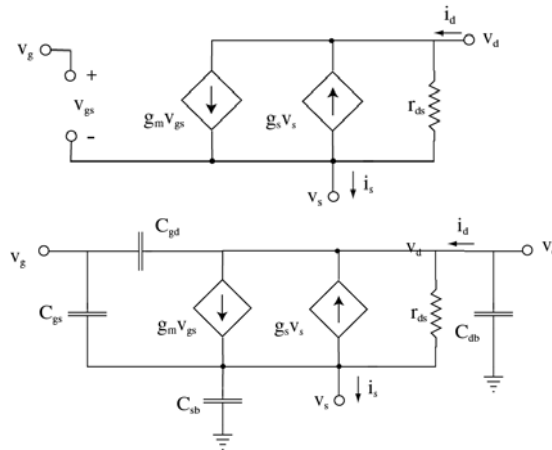


TSL inf3410

3

CS-stage with passive load




- Simple analysis

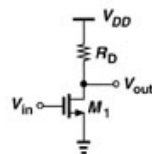

$$g_m = \sqrt{2\mu_n C_{ox} \frac{W}{L} I_D}$$

- Normally in saturation region

- Small-signal gain:

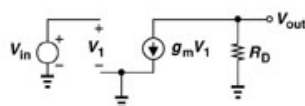

Inverting amplifier


$$A_v = -g_m R_D$$

4

CS-stage with current load



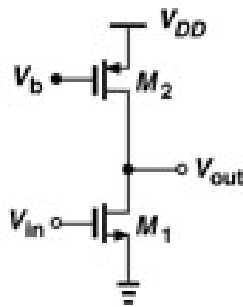- Small signal gain
 - Dominated by output impedance



$$A_v = -g_m r_{o1} \parallel r_{o2}$$

$$r_o = \frac{1}{\lambda I_D}$$

Assuming r_{o2} large,


$$A_v = -g_m r_{o1} = -\sqrt{2\mu_n C_{ox} I_D \left(\frac{W}{L}\right)_1} \frac{1}{\lambda I_D}$$

5

CS-stage with source degeneration



- Improve linearity by weaker source

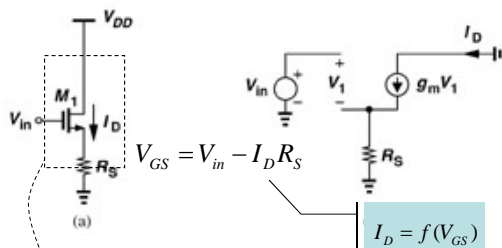

$$G_m = \left(1 - R_S \frac{\partial I_D}{\partial V_{in}}\right) \frac{\partial f}{\partial V_{GS}}$$

$$G_m = g_m$$

$$G_m = \frac{\partial I_D}{\partial V_{in}} = \frac{\partial f}{\partial V_{GS}} \frac{\partial V_{GS}}{\partial V_{in}}$$

$$I_D = f(V_{GS})$$

$$G_m = \frac{g_m}{1 + g_m R_S}$$

$$\frac{\partial I_D}{\partial V_{GS}} = g_m$$

$$\frac{\partial V_{GS}}{\partial V_{in}} = 1 - R_S \frac{\partial I_D}{\partial V_{in}}$$

When $R_S \gg 1/g_m \rightarrow G_m \approx 1/R_S$

giving lower gain and even more noise....



6

CD-stage voltage gain



Voltage follower

- Source follower

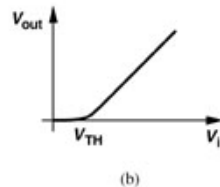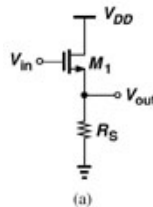

- Assuming saturation



$$\Rightarrow A_v = \frac{g_m R_S}{1 + (g_m + g_{mb}) R_S}$$

7

Follower behavior



- Voltage offset dependant on current

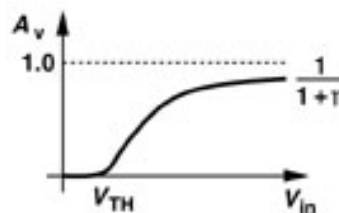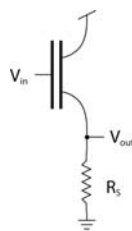

$$V_{out} = V_{in} - V_{GS} \Rightarrow$$

$$V_{out} = V_{in} - \left(V_{in} + \sqrt{\frac{2}{\mu_n C_{ox} (W/L)}} \cdot \sqrt{I_D} \right)$$

- 1. order approximation w/o body-effect and channel length modulation
- Current through resistor changes linear with voltage


TSL inf3410

8

Common-gate stage (CG)



- Main configuration

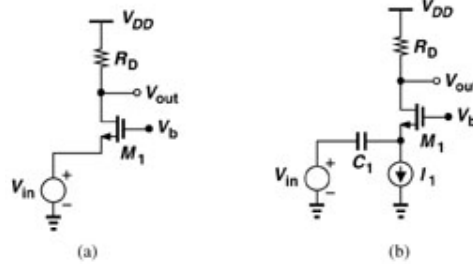


- Input at source
- Output at drain
- Gate at some suitable bias voltage

TSL inf3410

9

CG- stage main equations

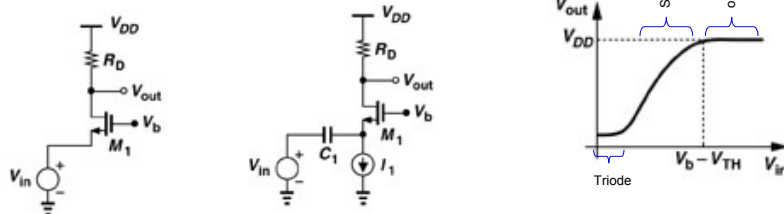


$$V_{out} = V_{DD} - \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_b - V_{in} - V_{TH})^2 R_D$$

$$A_V = g_m (1 + \eta) R_D$$




$$A_V = \frac{\partial V_{out}}{\partial V_{in}} = -\mu_n C_{ox} \frac{W}{L} (V_b - V_{in} - V_{TH}) \left(-1 - \frac{\partial V_{TH}}{\partial V_{in}} \right) R_D \quad \eta$$
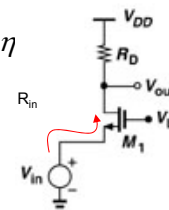
$$\frac{V_{in}}{I_{in}} = R_{in} = \frac{1}{g_m + g_{mb}} = \frac{1}{g_m (1 + \eta)}$$



Single transistor amps

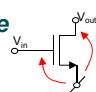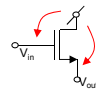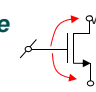


| | Common Source  | Common Drain  | Common Gate  |
|-----------------------|---|--|---|
| A_v | high $A_v = -g_m(r_o \parallel R_D)$ | ≈ 1 $A_v = \frac{g_m}{g_m + g_{mb}}$ | high $(g_m + g_{mb})(r_o \parallel R_D)$ |
| A_i | "infinite" | "infinite" | =1 |
| R_{in} | "infinite" | "infinite" | low $\frac{1}{g_m + g_{mb}}$ |
| R_o | high $r_o \parallel R_D$ | low $\frac{1}{g_m + g_{mb}}$ | high $r_o \parallel R_D$ |

Cascode stage







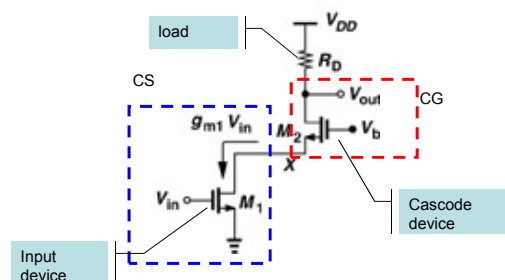
- Combining CS- and CG-stages
 - Cascaded CS and CG = cascode
 - CS → current
 - CG buffer current to load



Folded cascode



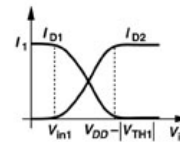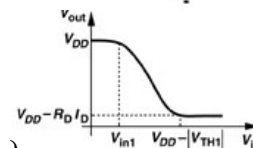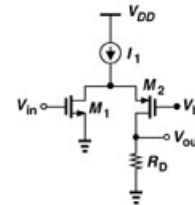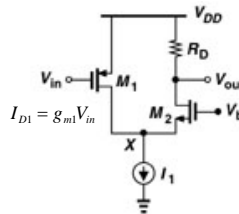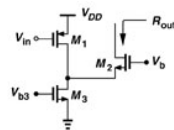- Combining nMOS CS-stage with pMOS CG-stage
 - Or vice versa
 - Same first-order behavior
 - Must feed both devices with current source



$$A_v = g_{m1} \cdot \{[(g_{m2} + g_{mb2})r_{o2}]r_{o1} \parallel R_D\}$$

- Increased bias current for same performance
- No DC offset, important for low supply voltage

13


Small signal gain



- Apply small input signal
 - Assuming saturation
 - In equilibrium
 - Split tail current

$$G_{m-\max} = \sqrt{\mu_n C_{ox} \frac{W}{L} I_{SS}} \quad \left. \vphantom{G_{m-\max}} \right\} \text{Must be valid for small signals}$$

$$I_{SS} = 2I_{M1,2}$$

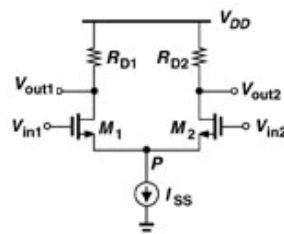

$$G_{m-\max} = g_m = \sqrt{2\mu_n C_{ox} \frac{W}{L} I_{M1,2}} \quad \text{Common-source topology}$$

TSL inf3410

14

Current mirrors



- Current controlled current source

- Equal transistor sizes with same gate voltage
 - Give same current


$$I_{out} = I_{in}$$

- Sink or source
- Assuming active region
- Ignoring channel shortening

- Fixed gain current amplifier

- Different transistor sizes
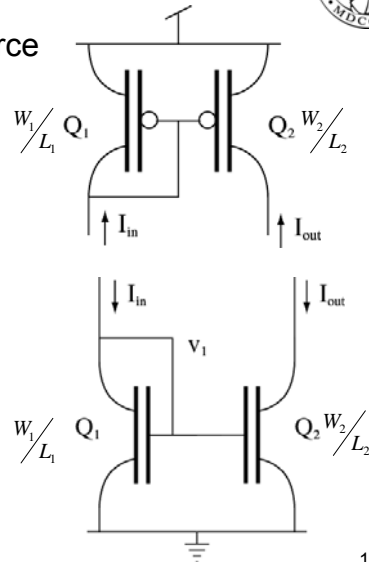
$$I_{out} = \frac{W_2 L_1}{W_1 L_2} I_{in}$$




TSL inf3410

15

Differential amp



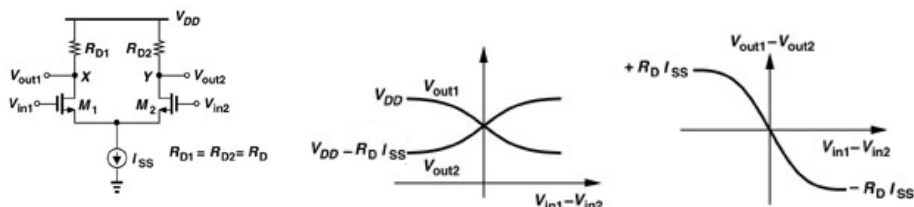- Output peak values well-defined
 - Independent of CM level
- Maximum gain at $V_{in1} = V_{in2}$
 - Non-linear for large signals




TSL inf3410

16

Diff pair small signal



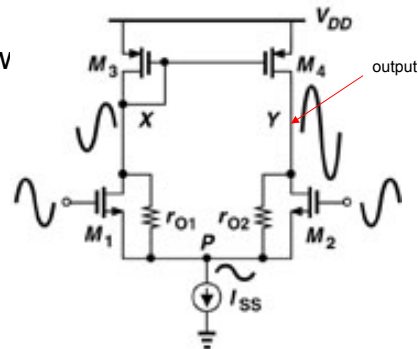- Signal swing differ
 - X node much less signal sw
 - Nonlinear load (diode)
 - Affecting symmetry
 - Must be analyzed
 - compensated



$$A_{v-Y} \approx G_m R_{out}$$


TSL inf3410

17

Frequency response



- Assuming one pole for each node

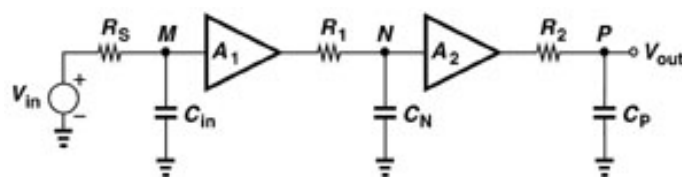

- Total gain by multiplying each stage gain

$$\frac{V_{out}}{V_{in}}(s) = \frac{A_1}{1 + sR_s C_{in}} \cdot \frac{A_2}{1 + sR_1 C_N} \cdot \frac{1}{1 + sR_2 C_P}$$

Simple and easy 1. order approximation

TSL inf3410

18



Poles and zeros

$$H(s) = K \frac{(s+z_1)(s+z_2)\dots(s+z_m)}{(s+\omega_1)(s+\omega_2)\dots(s+\omega_n)} = a \frac{\left(1+\frac{s}{z_1}\right)\left(1+\frac{s}{z_2}\right)\dots\left(1+\frac{s}{z_m}\right)}{\left(1+\frac{s}{\omega_1}\right)\left(1+\frac{s}{\omega_2}\right)\dots\left(1+\frac{s}{\omega_n}\right)}$$

- Poles and zeros are real or complex conjugates
- The actual roots are the *negatives* of the poles and zeros
- Referred to as a positive frequency

• Magnitude and phase

Euler's formula

– Sinusoidal: $x_{in}(t) = A_{in} \cos(\omega_m t) = A_{in} \frac{e^{j\omega_m t} + e^{-j\omega_m t}}{2}$

- Frequency domain two solutions $s = j\omega_m$ and $s = -j\omega_m$
- May find for particular $s = j\omega_m$:

$$x_{out}(t) = \frac{A_{in}}{2} |H(j\omega_m)| (e^{j(\omega_m t + \phi)} + e^{-j(\omega_m t + \phi)}) = A_{in} |H(j\omega_m)| \cos(\omega_m t + \phi)$$

- Where magnitude is $|H(j\omega_m)|$ and phase $\phi = \angle H(j\omega_m)$

19



2. order transfer

$$H(s) = \frac{K\omega_0^2}{\omega_0^2 + s\frac{\omega_0}{Q} + s^2}$$

• Analyze some cases

- May equate denominators

$$D(s) = \omega_0^2 + s\frac{\omega_0}{Q} + s^2 = (s + \omega_{p1})(s + \omega_{p2}) = \omega_{p1}\omega_{p2} + s(\omega_{p1} + \omega_{p2}) + s^2$$

- Equating coefficients: $\omega_0^2 = \omega_{p1}\omega_{p2}$ $\frac{\omega_0}{Q} = (\omega_{p1} + \omega_{p2})$

- Solving yields

$$\omega_{p1}, \omega_{p2} = \frac{\omega_0}{2Q} (1 \pm \sqrt{1 - 4Q^2})$$

- Assuming roots $\omega_{p1} \ll \omega_{p2}$ giving $Q \ll 1$ and $\sqrt{1 - 4Q^2} \cong 1 - 2Q^2$

$$\omega_{p1} \approx \omega_0 Q \quad \omega_{p2} \approx \frac{\omega_0}{Q}$$

20



Slur rate

- Frequency \rightarrow time

- 1. order LP filter

- Applied step response

$$X_{out}(s) = A_{in} \frac{1}{s} \frac{A_0}{1 + \frac{s}{\omega_0}}$$

- Residue method

$$X_{out}(s) = A_{in} A_0 \left[\frac{1}{s} - \frac{1}{s + \omega_0} \right]$$

- Inverse Laplace give time domain



$$x_{out}(t) = u(t) A_{in} A_0 \left(1 - e^{-\frac{t}{\tau}} \right) \quad \tau = \frac{1}{\omega_0}$$

21



Bandwidth

- Example: determine time-constant

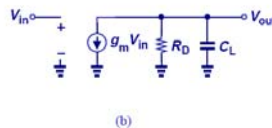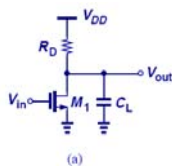


$$H(s) = \frac{V_{out}}{V_{in}}(s) = -g_m (R_D \parallel \frac{1}{C_L s})$$

$$= \frac{-g_m R_D}{R_D C_L s + 1}$$

$$s = j\omega \rightarrow \left| \frac{V_{out}}{V_{in}} \right| = \frac{g_m R_D}{\sqrt{R_D^2 C_L^2 \omega^2 + 1}}$$

$$\omega = 1/(R_D C_L) \quad \left| \frac{V_{out}}{V_{in}} \right| = \frac{g_m R_D}{\sqrt{2}}$$

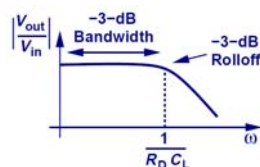

Time constant or -3dB bandwidth

22



Frequency response

- Basic amp circuits
 - CS stage
 - CD stage
 - CG stage
 - Diff pair
 - Cascode


TSL inf3410

23



Feedback principle

- Formal definition

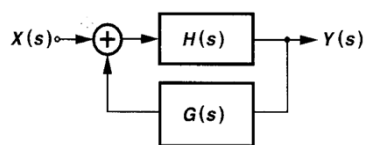


$$Y(s) = H(s)[X(s) + G(s)Y(s)]$$

$$\frac{Y(s)}{X(s)} = \frac{H(s)}{1 - G(s)H(s)}$$

-- Closed-loop transfer function

$H(s)$ -- Open-loop transfer function


- Negative feedback

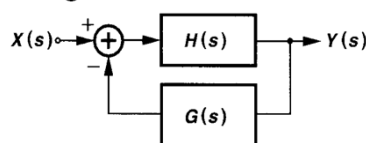

$$Y(s) = H(s)[X(s) - G(s)Y(s)]$$

$$\frac{Y(s)}{X(s)} = \frac{H(s)}{1 + G(s)H(s)}$$

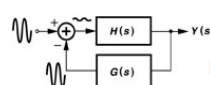1. Feed forward amplifier
2. Output sensing
3. Feedback network
4. Finding feedback error



Minimizing error by correct feedback

TSL inf3410

24


Negative feedback properties



- Gain desensitization

- CS example


$$A_V = g_{m1} r_{o1}$$

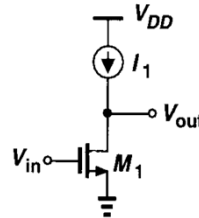

- Gain poorly defined

- Temperature, mismatch

- CS with feedback

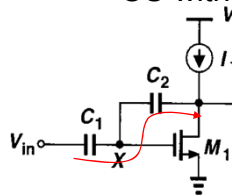

$$\frac{V_{OUT}}{V_X} = -g_{m1} r_{o1}$$

(disregard C_2 output load)

$$\frac{V_{OUT}}{V_{IN}} = - \frac{1}{\left(1 + \frac{1}{g_{m1} r_{o1}}\right) \frac{C_2}{C_1} + \frac{1}{g_{m1} r_{o1}}} \approx - \frac{C_1}{C_2} \quad (1/g_{m1} r_{o1} \approx 0)$$

$$(V_{OUT} - V_X) C_2 s = (V_X - V_{in}) C_1 s$$

TSL inf3410


Gain determined by capacitive ratio
- high precision devices

25

Gain desensitization



- Negative feedback major advantage

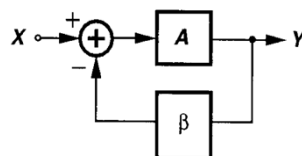

$$A_{CL} = \frac{Y}{X} = \frac{A}{1 + A\beta} = \frac{1}{\beta} \cdot \frac{A\beta}{1 + A\beta} \approx \frac{1}{\beta} \cdot \left(1 - \frac{1}{A\beta}\right) \quad A\beta \gg 1$$

- Feedback factor β and βA is loop gain

- Major reduction of gain errors
- Trading gain for precision


TSL inf3410

26

Feedback and bandwidth

- Open loop

- high gain and low frequency roll-off

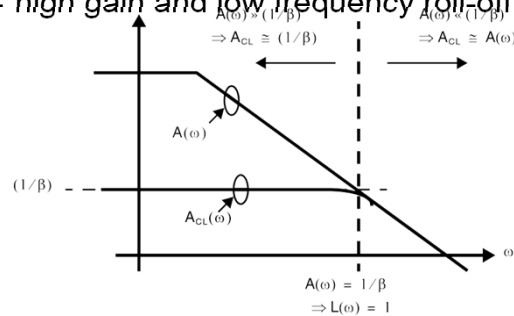

- Closed loop

- Reduced gain and increased bandwidth


$$\rightarrow A(s) = \frac{1}{\beta}$$

TSL inf3410


27

Typical feedback amp

- Bode plot

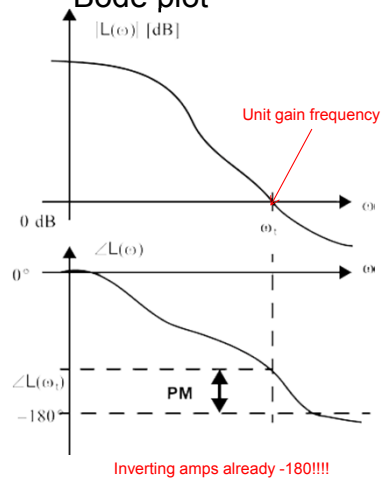

- Polar plot

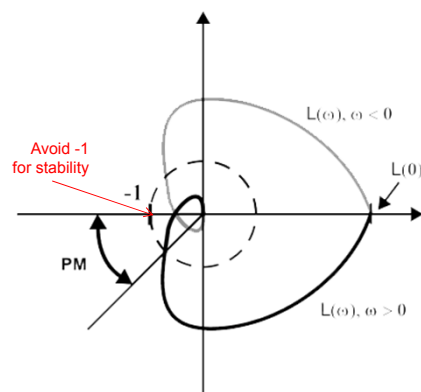


Stable if $\angle L(\omega_t) > -180$ at unit-gain frequency
 -180 degrees due to inverting amp = -360

TSL inf3410

Phase margins

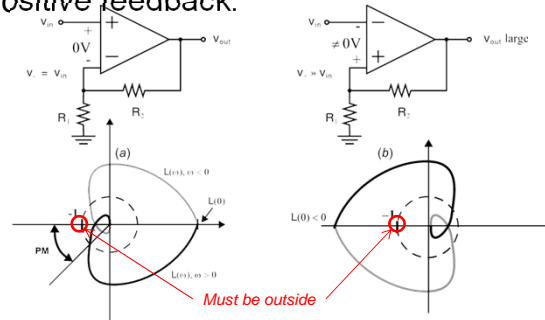- Measure of stability $PM = \angle L(\omega_t) + 180$
 - Must account for variations and need margins
- Positive feedback:




- Never positive feedback in amps!
 - Fine in oscillators

TSL inf3410

29

Frequency compensation

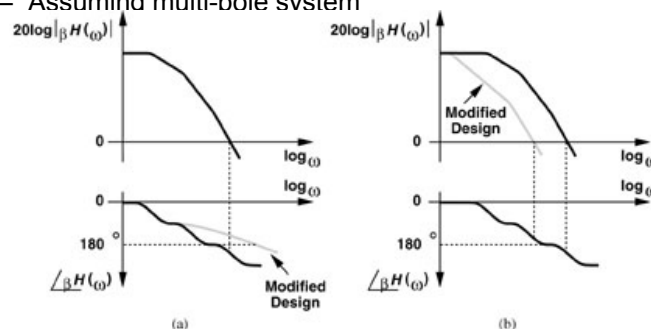
- Improving phase margins
 - Assuming multi-pole system



1. Reduce phase shift for sufficient PM
 - Hard since we must reduce number of poles \rightarrow lower gain
2. Reduce gain for sufficient PM
 - Maintain gain and signal swing at LF, but reduce bandwidth

30

Miller Theorem

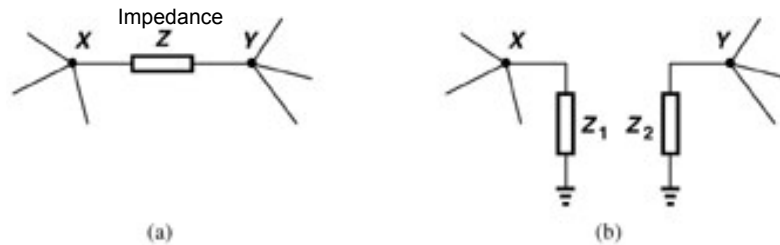

- If circuit (a) is converted to (b) then:

$$Z_1 = \frac{Z}{1 - A_v} \quad Z_2 = \frac{Z}{\left(1 - \frac{1}{A_v}\right)} \quad A_v = \frac{V_Y}{V_X}$$


Approximation!

31

Op Amp performance parameters



- Gain
 - May vary depending on application, but high gain is usually good
- Small-signal bandwidth
 - Gain drops with increased frequency
 - Unity-gain bandwidth; recurring measure
- Large-signal bandwidth
 - May introduce instability
 - Hard to analyze
- Output swing
 - “Rail-to-rail” operation
 - Differential topologies popular
- Linearity
- Noise and offset
- Supply rejection
 - Important in mixed-mode systems
 - Digital switching noise is showing up all over!

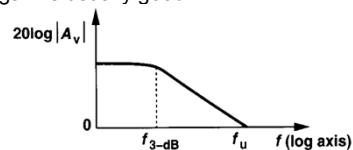


*Trading off performance parameters
According to application and technology*

32

Single-stage diff amplifiers




- Any diff amp may do...

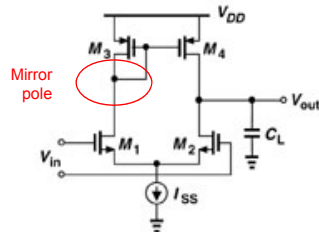

$$A_v = g_{m1,2}(r_{o2} \parallel r_{o4})$$

Single ended output

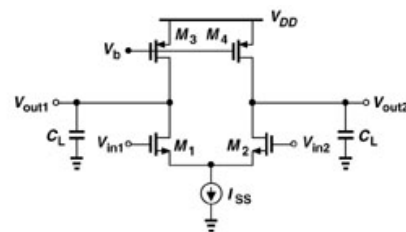

$$A_v = g_{m1,2}(r_{o2} \parallel r_{o4})$$

Differential output

- Output load capacitance determine bandwidth
- Gain around 20-50
- How do we improve?

TSL inf3410

33

Advanced mirrors and opamps




- Two-stage OPAMP
 - Compensation
- Advanced Current Mirrors
 - Wide-Swing Current Mirrors
 - Enhanced Output-Impedance Current Mirrors
- Advanced OTAs
 - Folded-Cascode OTA
 - Current-Mirror OTA
 - Fully Differential OTAs
 - Folded-Cascode
 - Current-Mirror
 - Common-Mode Feedback Circuits

TSL inf3410

34

CMOS OPAMP topology

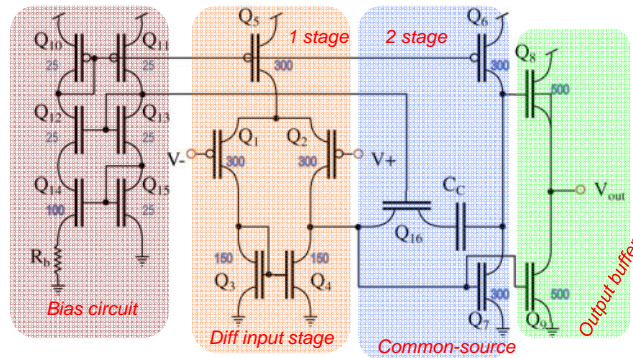

- PMOS diff input stage
- Numbers realistic transistor widths
 - Length 1-2 times minimum
- Output buffer drop for capacitive loads

TSL inf3410


35

Opamp compensation

$$\omega_t \approx \beta \omega_{ta}$$



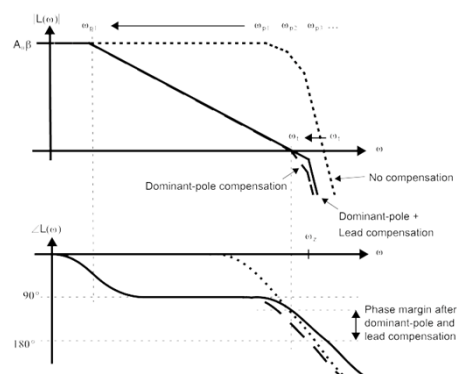- Dominant-pole compensation
 - Forcing a feedback system to have 1. order response up to loop unit-gain frequency ω_t
 - Stable system with increased PM
- Lead compensation
 - Adding zero, ω_z , just above ω_t
 - May improve PM with 20°



TSL inf3410

36

Two stage opamp compensation



- Dominant pole compensation

- Setting the ω_{p1} and ω_t since

$$\omega_t = A_0 \omega_0$$

- Q_{16} operate in triode region


- Resistive element

$$R_C = r_{DS16} = \frac{1}{\mu_n C_{ox} \frac{W}{L} V_{eff16}}$$

- Resistive element ensures left half-plane zero

- Damping element

- *Lead compensation*

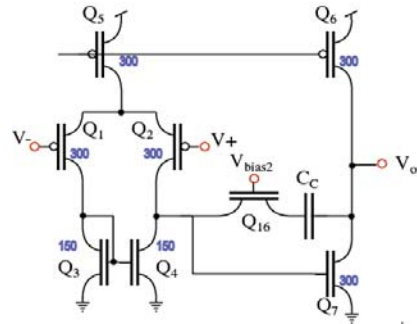

TSL inf3410

37

Topology comparison



| | Gain | Output Swing | Speed | Power dissipation | Noise |
|----------------|--------|--------------|---------|-------------------|--------|
| Telescopic | Medium | Medium | Highest | Low | Low |
| Folded Cascode | Medium | Medium | High | Medium | Medium |
| Two-stage | High | Highest | Low | Medium | Low |
| Gain Boosted | High | Medium | Medium | High | Medium |


TSL inf3410

38

Biasing and refs



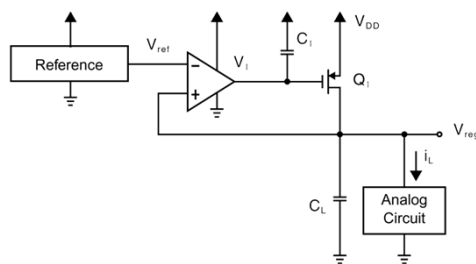- Distribute as current
- Combine mirrors and resistor for ref voltage
- Temperature compensate
 - Combine positive and negative temperature dependencies
- Low dropout reference



TSL inf3410

39

That's it!



- Good luck!

TSL inf3410

40