

1999 Power Electronics Specialists Conference

Advances in Averaged Switch Modeling and Simulation

Dragan Maksimovic* and Robert Erickson

Colorado Power Electronics Center

CoPEC

<http://ece-www.colorado.edu/~pwrelect>

* Acknowledgment: the work by Dragan Maksimovic was supported in part by the National Science Foundation CAREER Award, Grant No. ECS-9703449.

Outline

- 1. Introduction: converter modeling approaches and objectives**
- 2. Averaged switch modeling of PWM converters operating in the continuous conduction mode (CCM)**
 - Basics of averaged switch modeling
 - Switch network steady-state and small-signal models
 - Using averaged-switch model to predict converter steady-state characteristics and small-signal dynamics in CCM
 - PSpice implementation of the averaged switch model
 - Application examples: small-signal dynamics, conduction losses and efficiency of a Sepic converter
 - Averaged switch modeling exercise: include switching losses

Outline

continued

- 3. Averaged switch modeling of PWM converters operating in discontinuous conduction mode (DCM)**
- Averaged switch model in DCM
 - Switch network steady-state and small-signal models in DCM
 - Using averaged-switch model to predict converter steady-state characteristics and small-signal dynamics in DCM
 - Combined CCM/DCM averaged switch model
 - PSpice implementation of combined CCM/DCM models
 - Application examples:
 - Large-signal transient response of a SEPIC
 - Flyback converter small-signal frequency responses in CCM and DCM

Outline

continued

4. Averaged modeling of PWM converters with current-programmed mode (CPM) control

- Averaged switch model in CCM and DCM
- Steady-state and AC models in CCM and DCM
- Large-signal averaged CCM/DCM model for CPM controller
- PSpice implementation of the CPM controller model
- Application example: buck converter with CPM controller

5. Single-phase low-harmonic rectifiers

- The ideal rectifier
- Averaged models of rectifiers
- Application examples:
 - DCM boost rectifier
 - SEPIC rectifier with nonlinear-carrier control

6. Summary

7. Bibliography

On-Line Materials

- ***<http://ece-www.colorado.edu/~pwrelect/publications>***
seminar slides, collection of simulation examples, library of PSpice models used in the examples, and many other CoPEC publications and presentation materials
- ***<http://ece-www.colorado.edu/~pwrelect/>*** is the CoPEC home page
- ***<http://ece-www.colorado.edu/~pwrelect/book/bookdir.html>***
is the home page for the Textbook: R.W.Erickson, *Fundamentals of Power Electronics*
- **Power Electronics courses at the University of Colorado:**
 - *Power Electronics 1: <http://ece-www.colorado.edu/~ecen5797>*
 - *Power Electronics 2: [http:// ece-www.colorado.edu/~ecen5807](http://ece-www.colorado.edu/~ecen5807)*
 - *Power Electronics Lab: <http:// ece-www.colorado.edu/~ecen4517>*
- All simulation examples completed using free PSpice evaluation version available from: ***<http://www.orcad.com>***

1. Introduction

Engineering design based on converter modeling:

- Predict converter system behavior, validate models by experiments
- Use the model to predict performance under worst-case conditions
- Improve design until worst-case behavior meets specifications
(or until reliability and production yield are acceptably high)

Models:

- Circuit models that yield design-oriented, analytical results
- Models for computer simulation

Results of interest:

- Steady-state characteristics
- Component stresses, losses, efficiency
- Large and small-signal dynamic responses

Seminar Objectives

- Describe basic averaged switch modeling approach
- Develop averaged models for
 - Converters in continuous conduction mode (CCM)
 - Converters in discontinuous conduction mode (DCM)
 - Converters with Current-Programmed Mode (CPM) controller
 - Single-phase power-factor correctors
- Summarize analytical results for steady-state and dynamic responses
- Demonstrate PSpice implementations of averaged-switch models and controllers
- Present application examples
 - Large-signal transient responses and small-signal dynamics of DC-DC converters and single-phase power-factor correctors

Averaged switch modeling



- Switch network is replaced by averaged circuit model. Switching harmonics are removed, and low-frequency components of waveforms are modeled in a simple way.
- A very general approach to modeling converter losses, efficiency, and dynamics.
- Yields an intuitive understanding of converter behavior in CCM, DCM, current-programmed mode, etc.
- Applicable to all types of converters: dc-dc converters, as well as dc-ac inverters, ac-dc low-harmonic rectifiers, ac-ac matrix converters.
- Well-suited to simulation
- Well developed and understood technique, easily taught to students.
- Main reference for the material in this seminar:
R.W.Erickson, *Fundamentals of Power Electronics*, Chapman and Hall, 1997.

Bibliography has a large collection of other selected references

Averaged switch modeling




simulation model

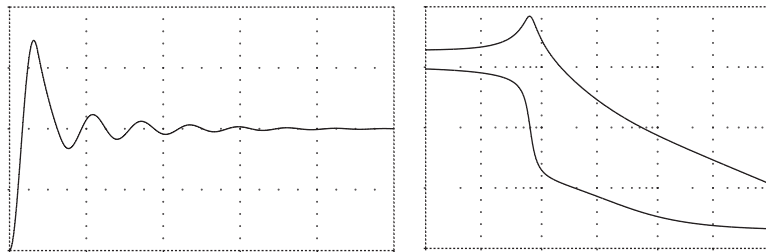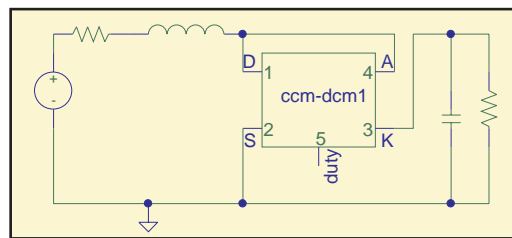

DC, AC and Transient simulation

linearization

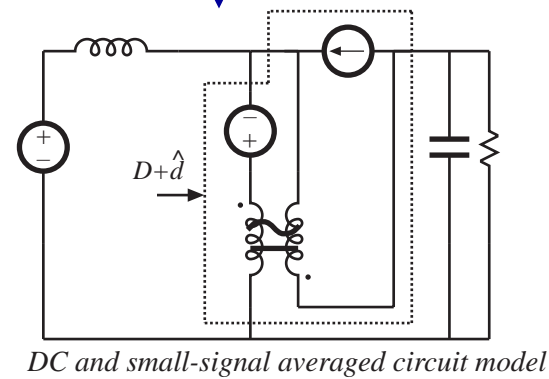

$$G_c(s) = G_{co} \frac{1 - s/w_s}{1 + (1/Q)s/w_o + (s/w_o)^2}$$

Analytical results:
steady-state characteristics
and small-signal dynamics


2. Averaged switch modeling of PWM converters operating in the continuous conduction mode

- **Basics of averaged switch modeling**
- **Switch network steady-state and small-signal models**
- **Using averaged-switch model to predict converter steady-state characteristics and small-signal dynamics in CCM**
- **PSpice implementation of averaged switch models**
 - ideal switches (ccm1)
 - switches with conduction losses (ccm2)
 - switches in converters with isolation transformer (ccm3)
 - switch with conduction losses in converters with (possibly) isolation transformer (ccm4)
- **Application example:**
 - SEPIC small-signal frequency response, conduction losses and efficiency
- **Averaged switch modeling exercise: include switching losses**

Averaged switch modeling

Basic approach

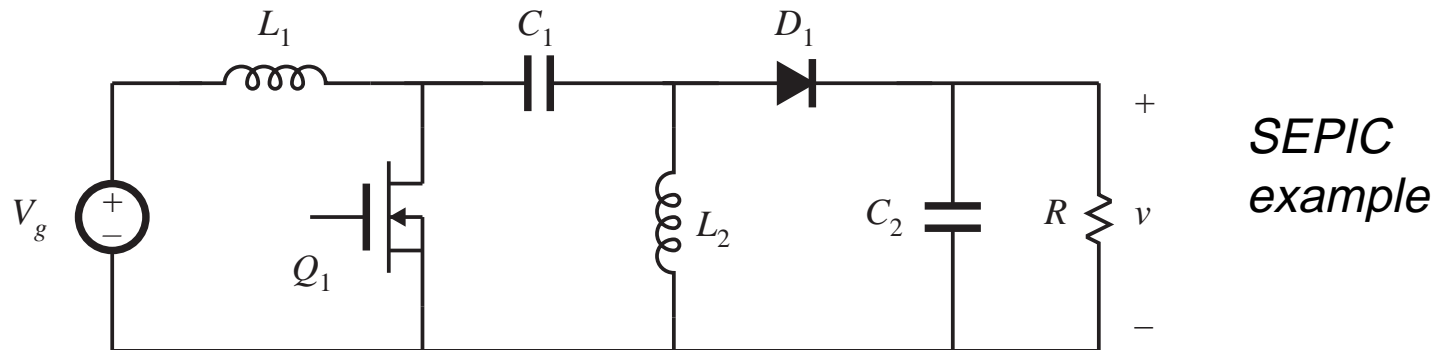
Given a PWM converter operating in continuous conduction mode:




Separate the switching elements from the remainder of the converter...

Definition of switch network, SEPIC example

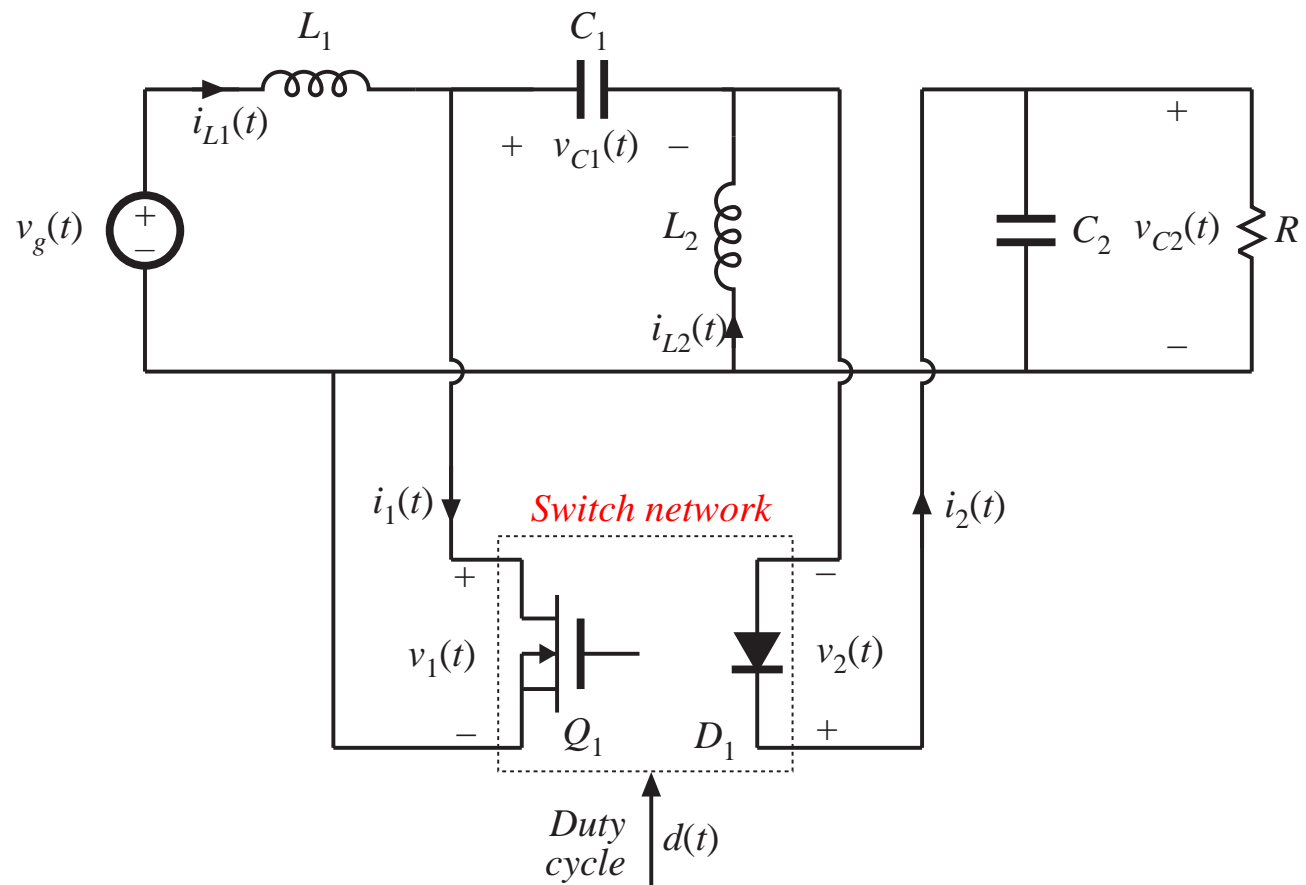- Define a switch network, containing all of the converter switching elements.
- The remainder of the converter is linear and time-invariant.
- The terminal voltages and currents of the switch network can be arbitrarily defined.



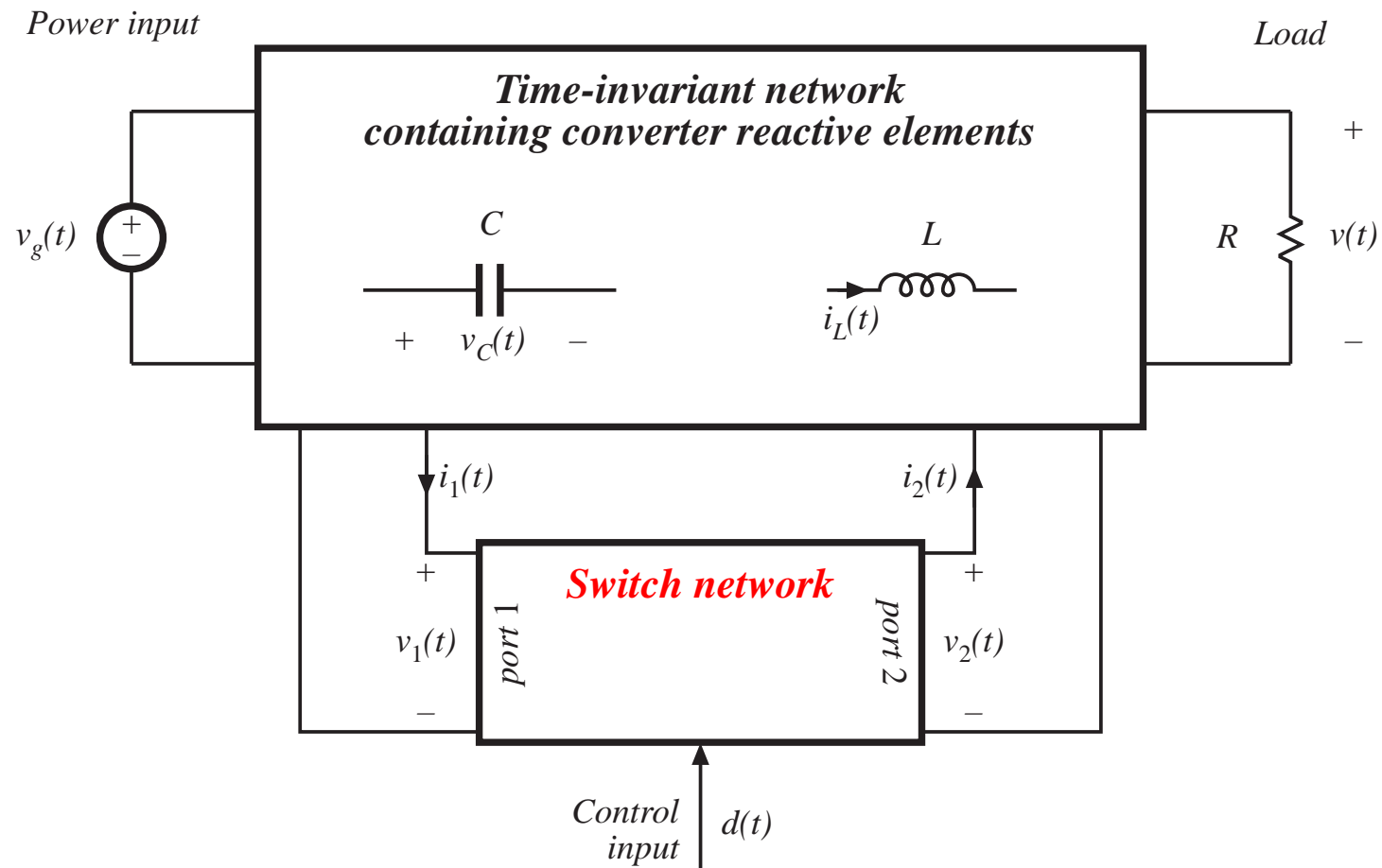Switching converter system with switch network explicitly defined



Discussion

- The number of ports in the switch network is less than or equal to the number of SPST switches in the converter
- Simple dc-dc case, in which converter contains two SPST switches: switch network contains two ports







The switch network terminal waveforms are then the port voltages and currents: $v_1(t)$, $i_1(t)$, $v_2(t)$, and $i_2(t)$.

Two of these waveforms can be taken as independent inputs to the switch network; the remaining two waveforms are then viewed as dependent outputs of the switch network.

Switch network also includes control input $d(t)$

- Definition of the switch network terminal quantities is not unique. Different definitions lead equivalent results having different forms

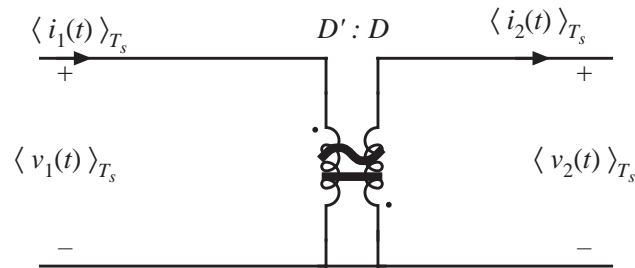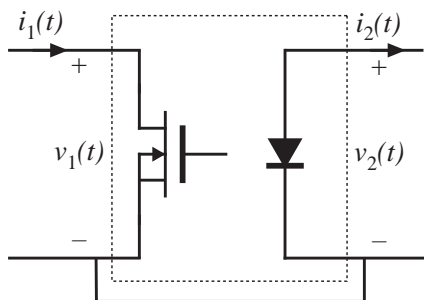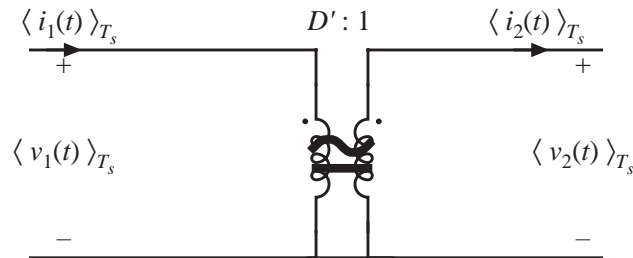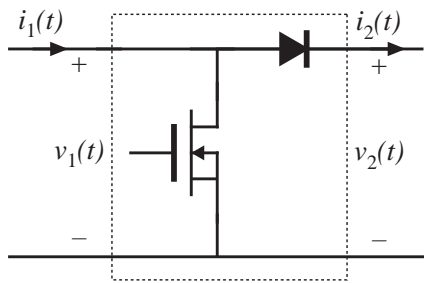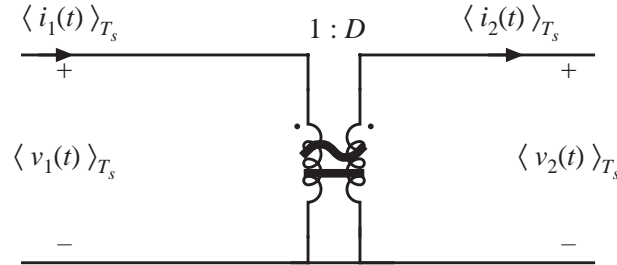
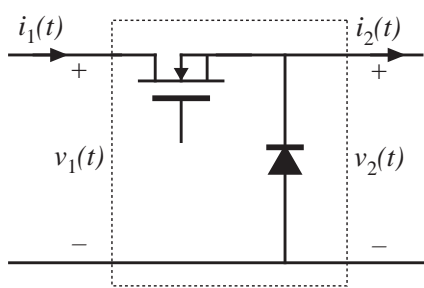
Several ways to define the PWM switch network, and the corresponding CCM models



A few points regarding averaged switch modeling

- The switch network can be defined arbitrarily, as long as its terminal voltages and currents are independent, and the switch network contains no reactive elements.
- It is **not** necessary that some of the switch network terminal quantities coincide with inductor currents or capacitor voltages of the converter, or be nonpulsating.
- The object is simply to write the averaged equations of the switch network; i.e., to express the average values of half of the switch network terminal waveforms as functions of
 - the average values of the remaining switch network terminal waveforms,
 - and
 - the control input.


Terminal waveforms of the switch network

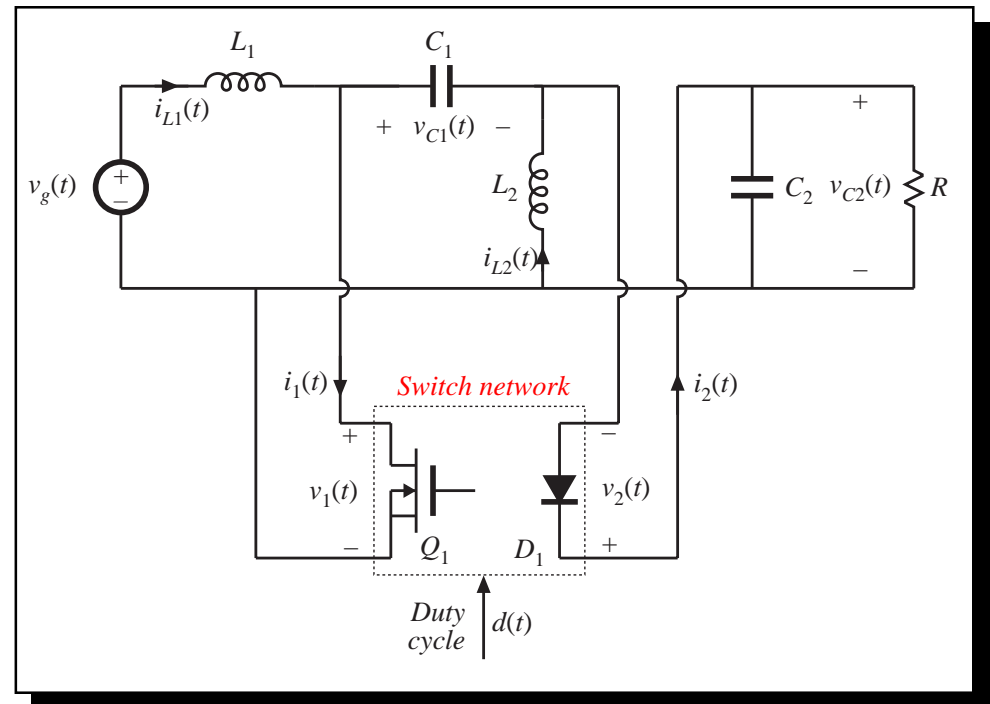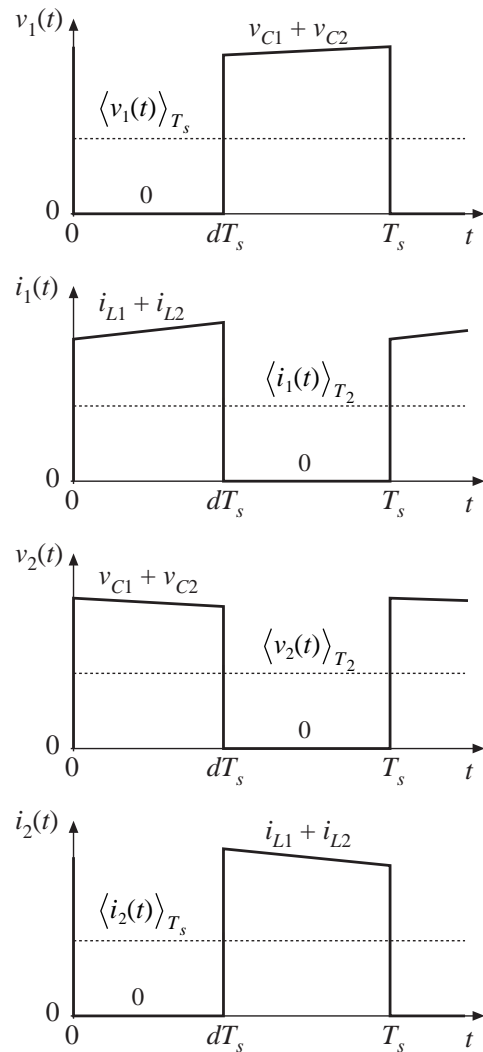

The averaging step

$$\langle x(t) \rangle_{T_s} = \frac{1}{T_s} \int_t^{t+T_s} x(t) dt$$

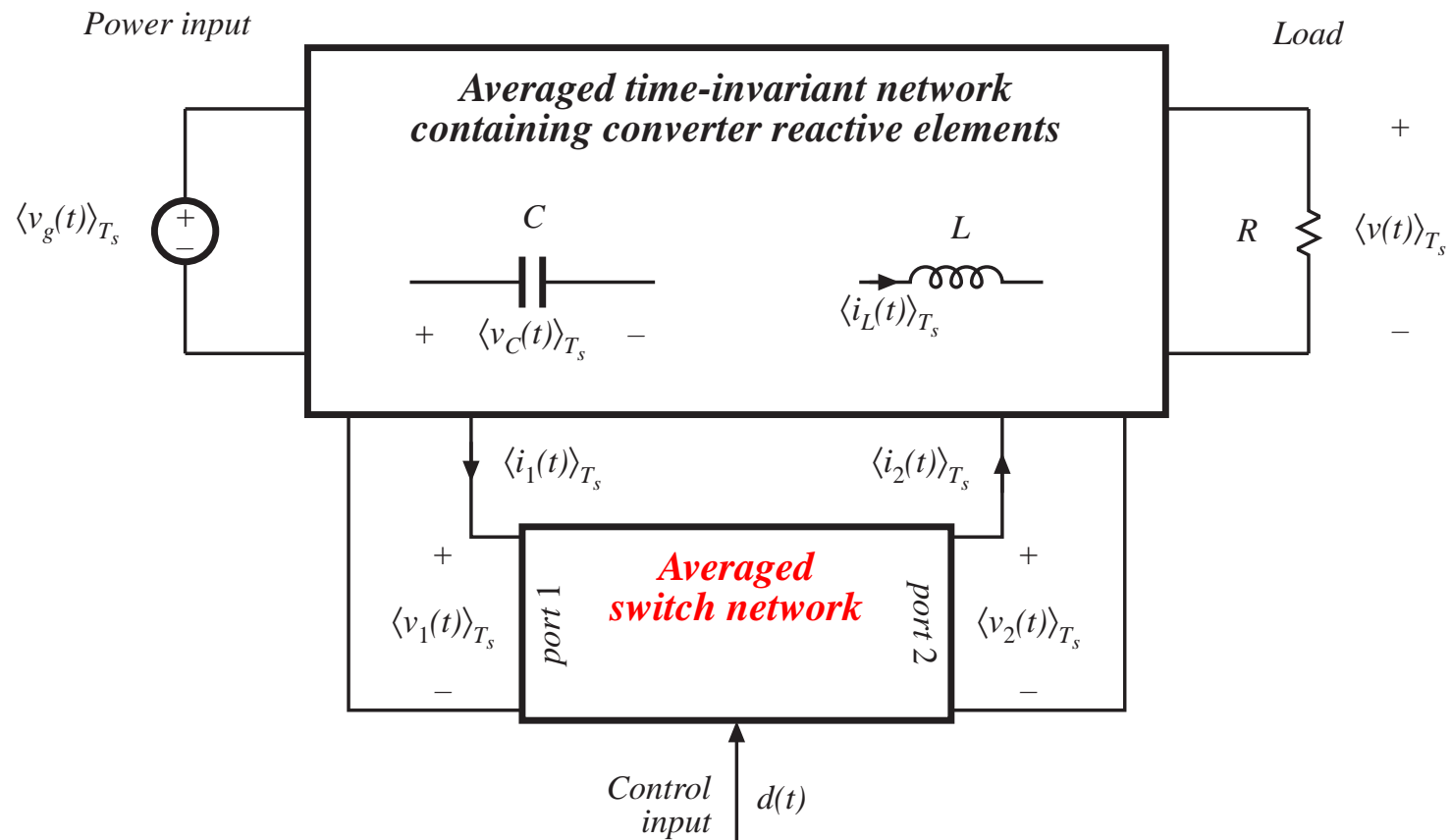Now average all waveforms over one switching period:



The averaging step

The basic assumption is made that the natural time constants of the converter are much longer than the switching period, so that the converter contains low-pass filtering of the switching harmonics:

One may average the waveforms over an interval that is short compared to the system natural time constants, without significantly altering the system response.


In particular, averaging over the switching period T_s removes the switching harmonics, while preserving the low-frequency components of the waveforms.

This step removes the small but mathematically-complicated switching harmonics, leading to a relatively simple and tractable converter model.


In practice, the only work needed for this step is to average the switch dependent waveforms.

Averaged terminal equations of the switch network


(small switching ripple is neglected)

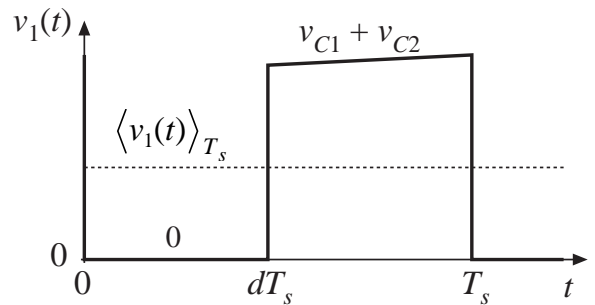

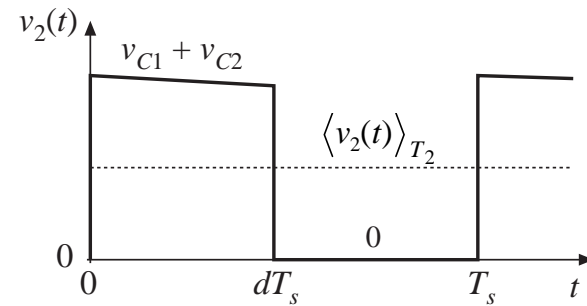
$$\langle v_1(t) \rangle_{T_s} = d'(t) \left(\langle v_{C1}(t) \rangle_{T_s} + \langle v_{C2}(t) \rangle_{T_s} \right)$$


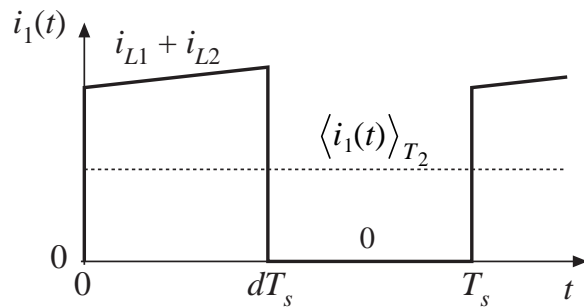
$$\langle v_2(t) \rangle_{T_s} = d(t) \left(\langle v_{C1}(t) \rangle_{T_s} + \langle v_{C2}(t) \rangle_{T_s} \right)$$


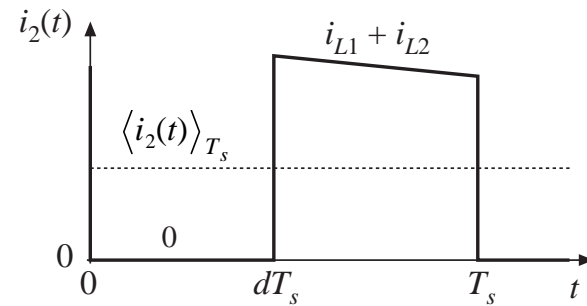
$$\langle i_1(t) \rangle_{T_s} = d(t) \left(\langle i_{L1}(t) \rangle_{T_s} + \langle i_{L2}(t) \rangle_{T_s} \right)$$



$$\langle i_2(t) \rangle_{T_s} = d'(t) \left(\langle i_{L1}(t) \rangle_{T_s} + \langle i_{L2}(t) \rangle_{T_s} \right)$$

Derivation of switch network equations (Algebra steps)

We can write


$$\langle i_{L1}(t) \rangle_{T_s} + \langle i_{L2}(t) \rangle_{T_s} = \frac{\langle i_1(t) \rangle_{T_s}}{d(t)}$$

$$\langle v_{C1}(t) \rangle_{T_s} + \langle v_{C2}(t) \rangle_{T_s} = \frac{\langle v_2(t) \rangle_{T_s}}{d(t)}$$

Hence



$$\langle v_1(t) \rangle_{T_s} = \frac{d'(t)}{d(t)} \langle v_2(t) \rangle_{T_s}$$
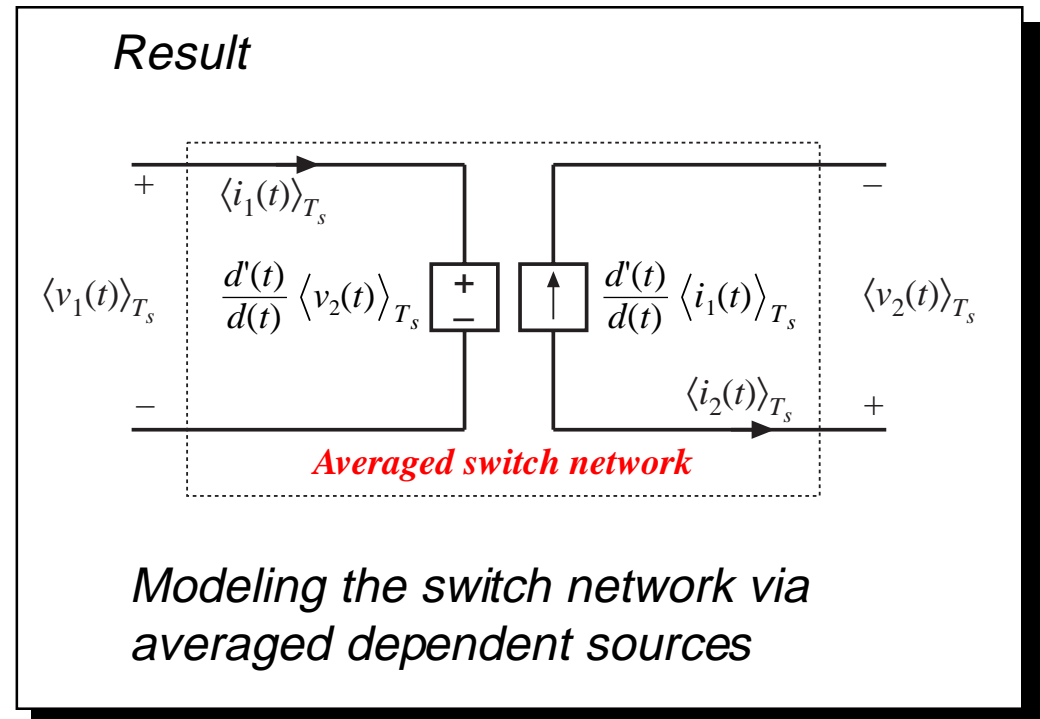
$$\langle i_2(t) \rangle_{T_s} = \frac{d'(t)}{d(t)} \langle i_1(t) \rangle_{T_s}$$




Steady-state switch model: Dc transformer model

Original switch network

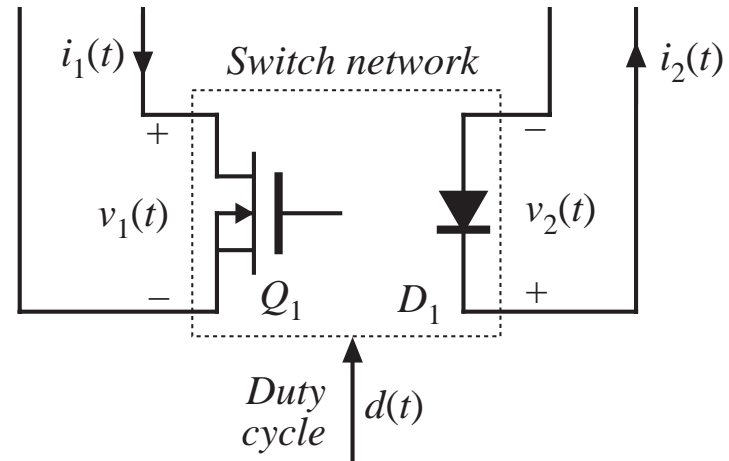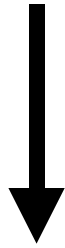


Averaged steady-state model:
"DC transformer"

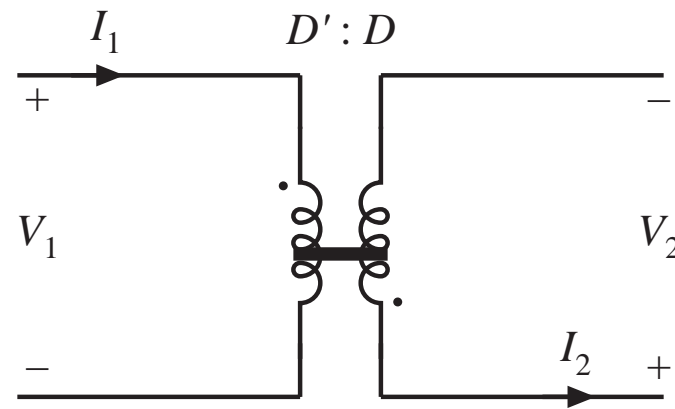- Correctly represents the relationships between the dc and low-frequency components of the terminal waveforms of the switch network



Steady-state CCM SEPIC model

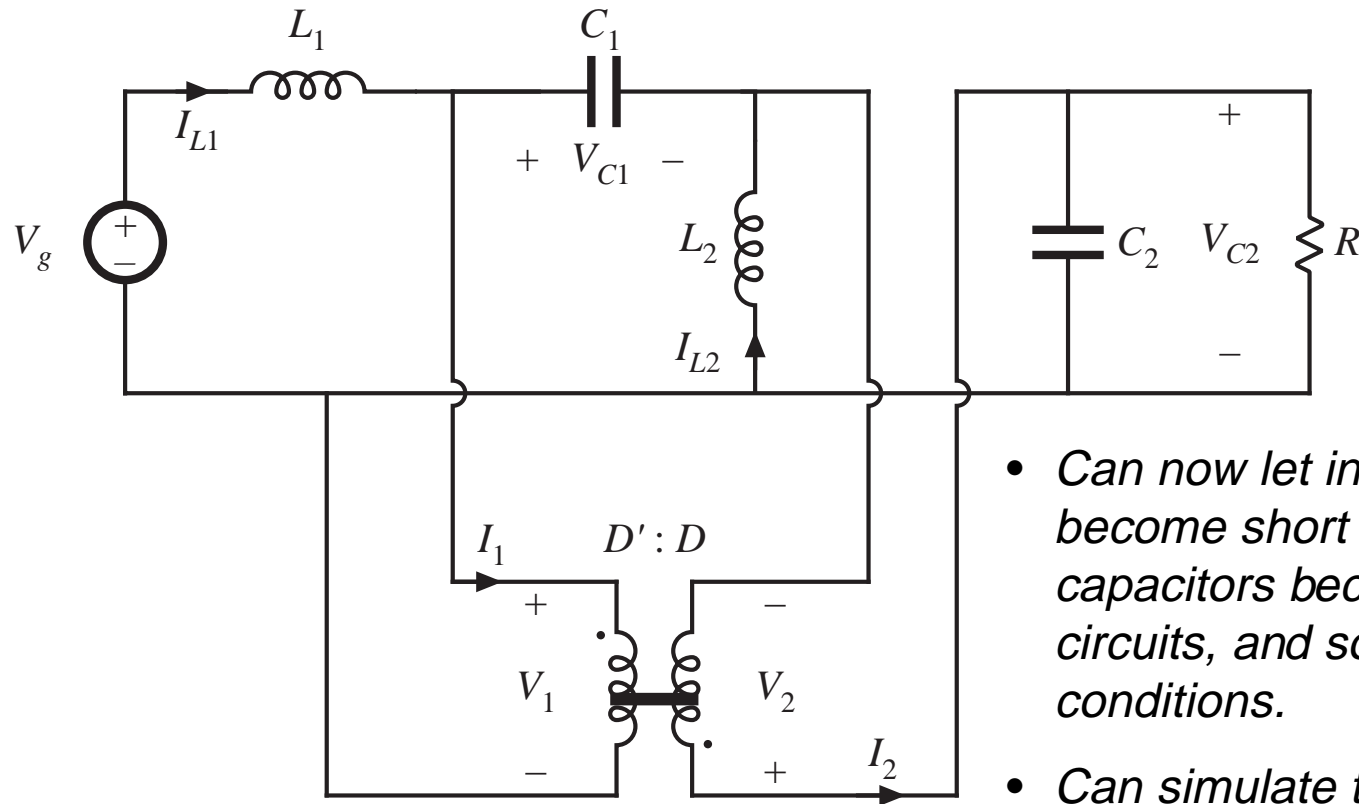Replace switch network with dc transformer model



- *Can now let inductors become short circuits, capacitors become open circuits, and solve for dc conditions.*
- *Can simulate this model using PSPICE, to find transient waveforms*

Modeling converter dynamics: Small-signal linearization of model

Perturb and linearize the switch network averaged waveforms about a quiescent operating point. Let:

$$d(t) = D + \hat{d}(t)$$

$$\langle v_1(t) \rangle_{T_s} = V_1 + \hat{v}_1(t)$$

$$\langle i_1(t) \rangle_{T_s} = I_1 + \hat{i}_1(t)$$

$$\langle v_2(t) \rangle_{T_s} = V_2 + \hat{v}_2(t)$$

$$\langle i_2(t) \rangle_{T_s} = I_2 + \hat{i}_2(t)$$

Voltage equation becomes

$$(D + \hat{d})(V_1 + \hat{v}_1) = (D' - \hat{d})(V_2 + \hat{v}_2)$$

Eliminate nonlinear terms and solve for v_1 terms:

$$\begin{aligned} (V_1 + \hat{v}_1) &= \frac{D'}{D} (V_2 + \hat{v}_2) - \hat{d} \left(\frac{V_1 + V_2}{D} \right) \\ &= \frac{D'}{D} (V_2 + \hat{v}_2) - \hat{d} \left(\frac{V_1}{DD'} \right) \end{aligned}$$

Linearization, continued

Current equation becomes


$$(D + \hat{d})(I_2 + \hat{i}_2) = (D' - \hat{d})(I_1 + \hat{i}_1)$$

Eliminate nonlinear terms
and solve for i_2 terms:

$$\begin{aligned}(I_2 + \hat{i}_2) &= \frac{D'}{D} (I_1 + \hat{i}_1) - \hat{d} \left(\frac{I_1 + I_2}{D} \right) \\ &= \frac{D'}{D} (I_1 + \hat{i}_1) - \hat{d} \left(\frac{I_2}{DD'} \right)\end{aligned}$$

Switch network: Small-signal ac model

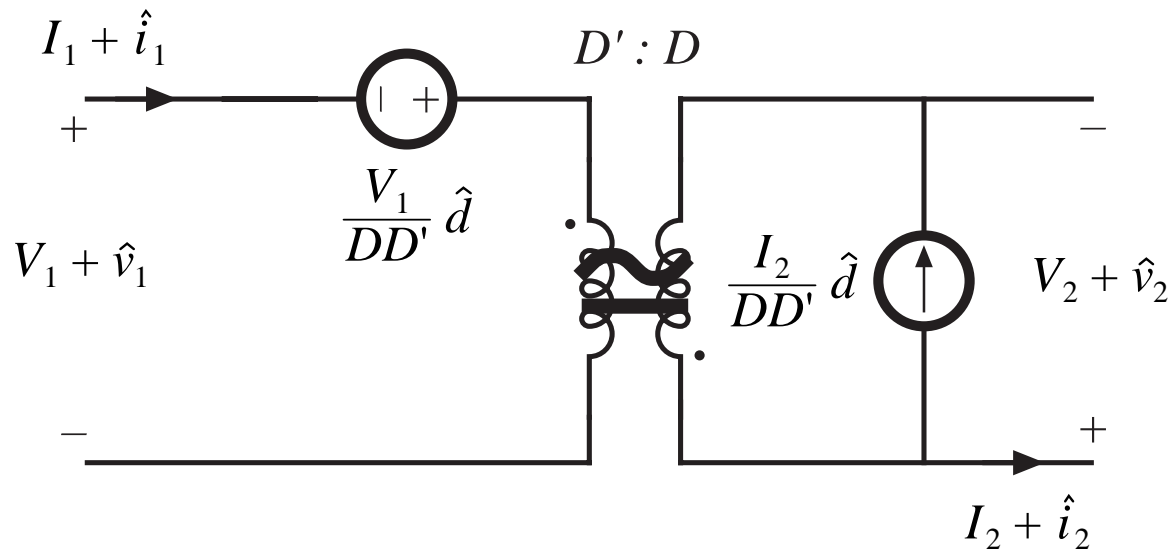Reconstruct an equivalent circuit that corresponds to these small-signal equations:




Transistor port

Diode port

A general small-signal ac model for the PWM switch network operating in CCM.

Small-signal ac model of the CCM SEPIC

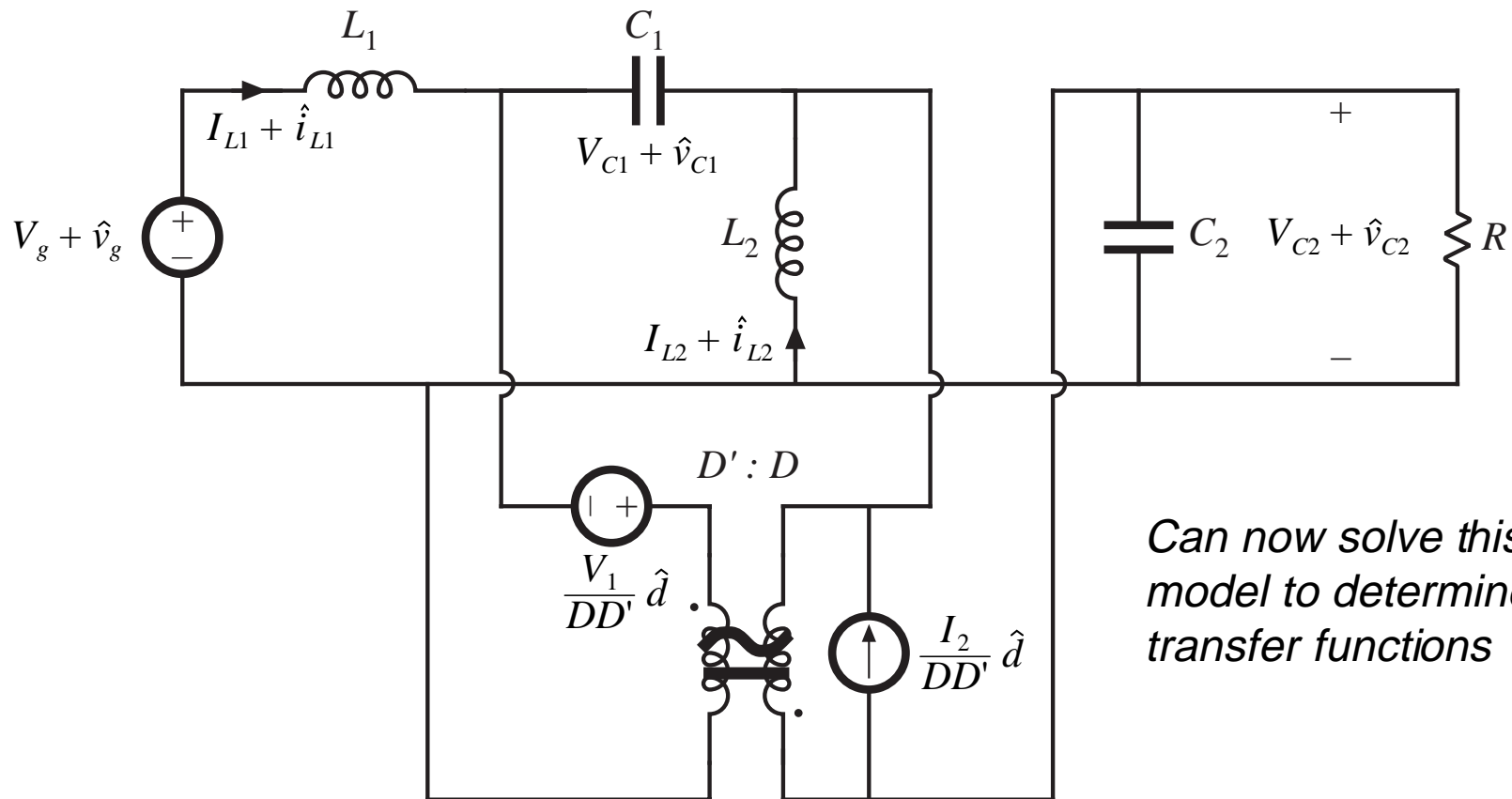Replace switch network with small-signal ac model:



Can now solve this model to determine ac transfer functions

Small-signal models of several basic switch networks

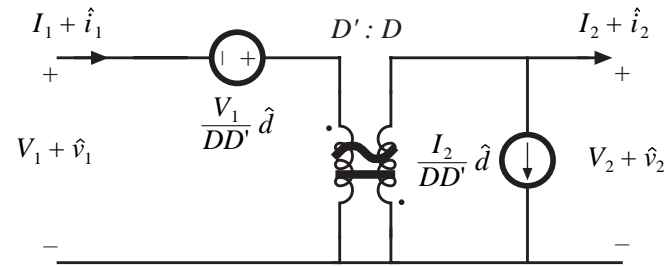
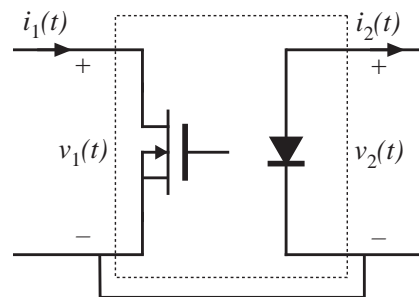
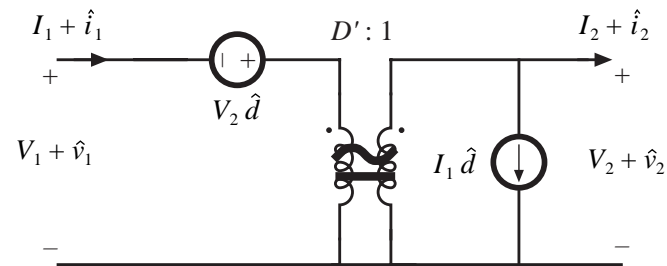
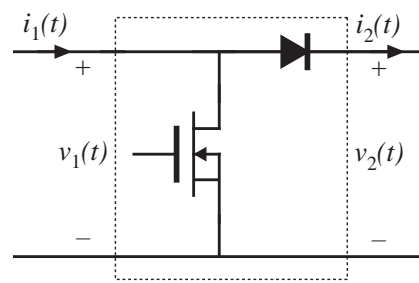
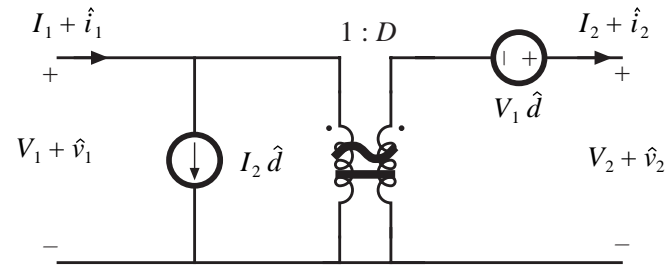
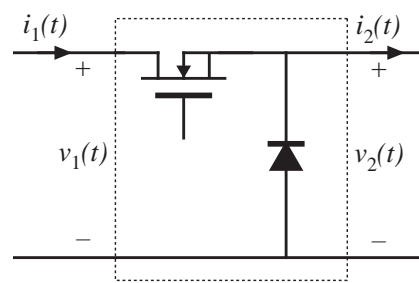


Table of results

Transfer functions of the basic buck, boost, and buck-boost converters

Control-to-output and line-to-output transfer functions $G_{vd}(s)$ and $G_{vg}(s)$


Converter	G_{g0}	G_{d0}	ω_0	Q	ω_z
<i>buck</i>	D	$\frac{V}{D}$	$\frac{1}{\sqrt{LC}}$	$R \sqrt{\frac{C}{L}}$	∞
<i>boost</i>	$\frac{1}{D'}$	$\frac{V}{D'}$	$\frac{D'}{\sqrt{LC}}$	$D'R \sqrt{\frac{C}{L}}$	$\frac{D'^2 R}{L}$
<i>buck-boost</i>	$-\frac{D}{D'}$	$\frac{V}{D D'^2}$	$\frac{D'}{\sqrt{LC}}$	$D'R \sqrt{\frac{C}{L}}$	$\frac{D'^2 R}{D L}$

where the transfer functions are written in the standard forms

$$G_{vd}(s) = G_{d0} \frac{\left(1 - \frac{s}{\omega_z}\right)}{\left(1 + \frac{s}{Q\omega_0} + \left(\frac{s}{\omega_0}\right)^2\right)}$$

$$G_{vg}(s) = G_{g0} \frac{1}{1 + \frac{s}{Q\omega_0} + \left(\frac{s}{\omega_0}\right)^2}$$


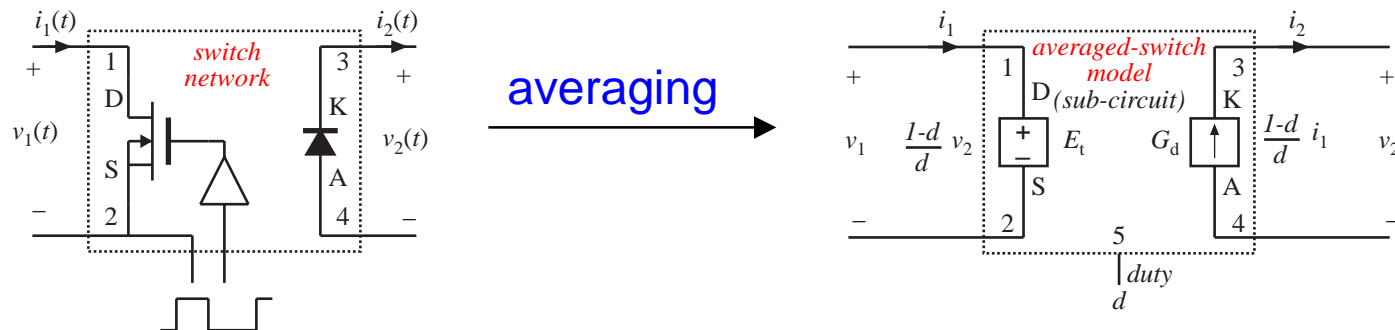
PSpice implementation of the basic CCM averaged switch model (ccm1)



- Controlled voltage source E_t replaces the transistor, controlled current source G_d replaces the diode
- Duty ratio d is input to the subcircuit
- Large-signal, nonlinear model suitable for DC, AC or Transient simulation
- The *same* model can be applied in *any* two-switch PWM converter (the transistor and the diode need not have a common node)
- Limitations: ideal switches, CCM only, valid for two-switch converters without isolation transformer

CCM Averaged-Switch Model

PSpice Implementation: `ccm1`

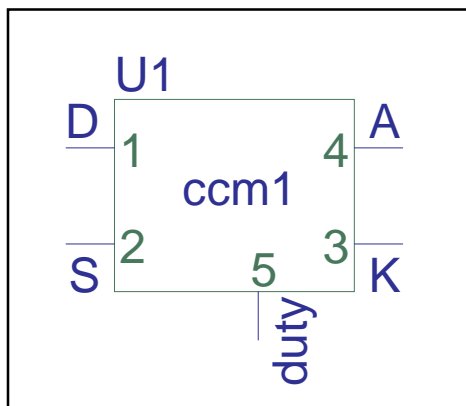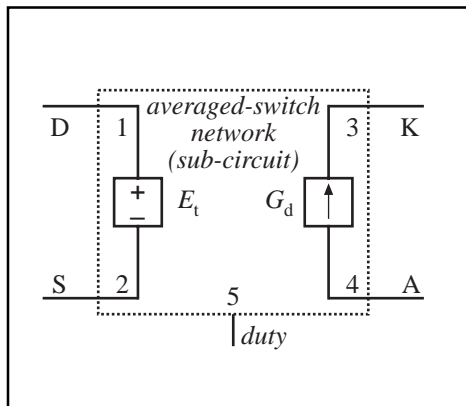

- * MODEL: `ccm1`
- * Application: two-switch PWM converters
- * Limitations: ideal switches, CCM only, no transformer


- * Parameters: none

* Nodes:

- * 1: transistor+ (D)
- * 2: transistor- (S)
- * 3: diode cathode (K)
- * 4: diode anode (A)
- * 5: duty ratio (duty)


```
.subckt ccm1 1 2 3 4 5
Et 1 2 value={(1-v(5))*v(3,4)/v(5)}
Gd 4 3 value={(1-v(5))*i(Et)/v(5)}
.ends
```

Sepic converter example using ccm1 model

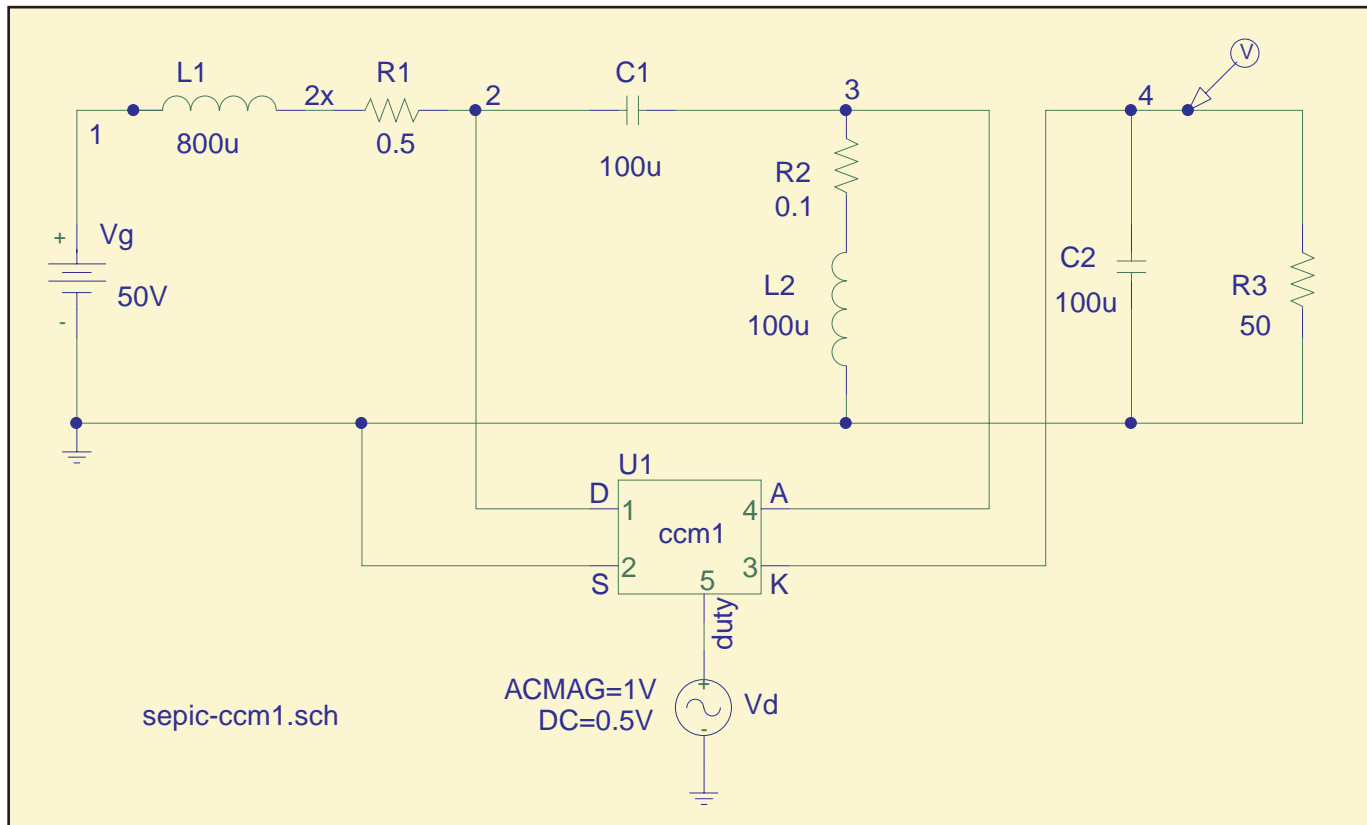

Objective: generate small-signal control-to-output frequency responses

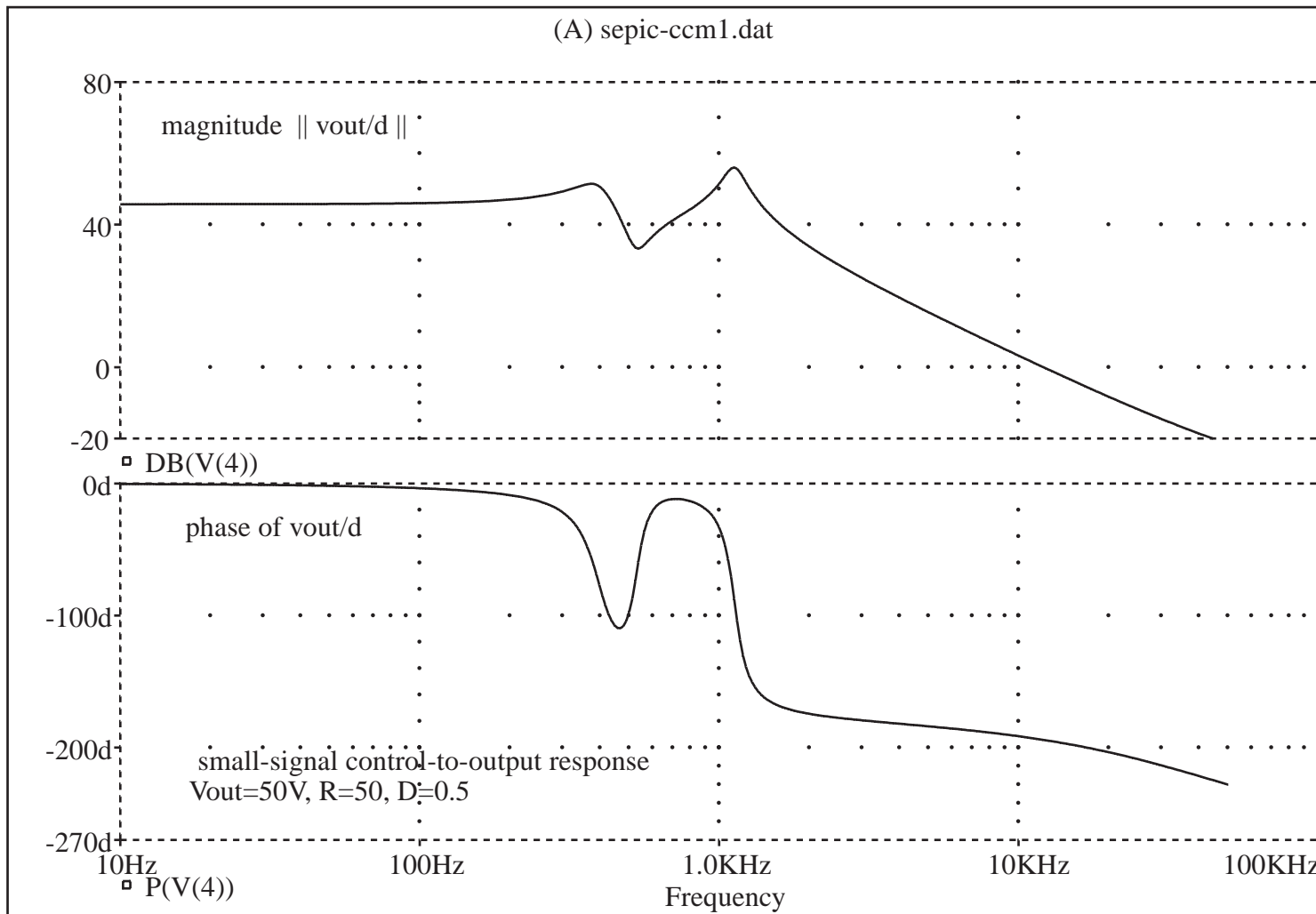Sepic converter example using ccm1 model: small-signal control-to-output response




Comments

- Subcircuit **ccm1** is implementation of a large-signal, nonlinear averaged model of the switch network
- Averaged circuit model of the converter is obtained simply by replacing switching devices with the averaged-switch subcircuit model
- Linearization and AC small-signal analysis are performed by the simulator
- Small-signal dynamic responses can be easily generated for different operating points or different sets of parameter values





CCM Averaged Switch Model That Includes Conduction Losses

- MOS transistor model: on-resistance R_{ON}
- Diode model: constant forward voltage drop V_D in series with R_d resistance


- Switch network

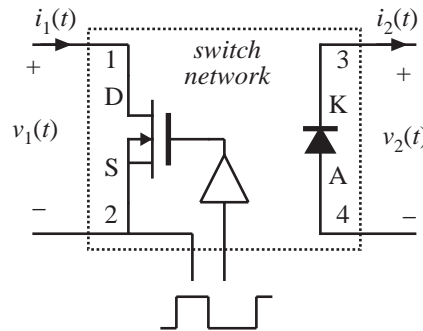

- Waveforms

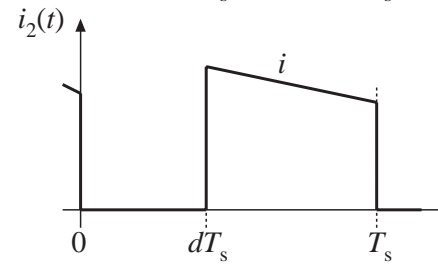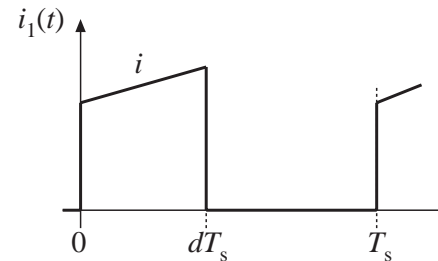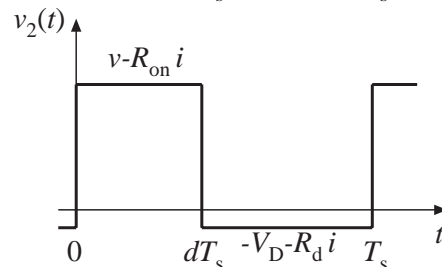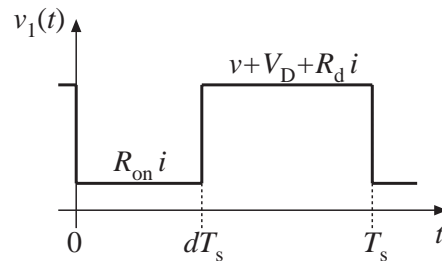

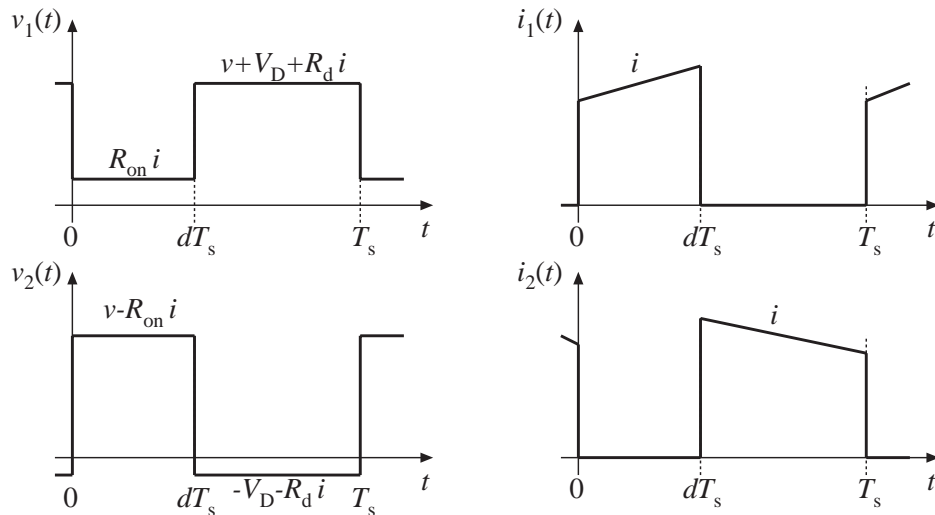CCM Averaged Switch Model ccm2 That Includes Conduction Losses



$$\langle i_1 \rangle_{T_s} = d \langle i \rangle_{T_s}$$

$$\langle i_2 \rangle_{T_s} = (1-d) \langle i \rangle_{T_s}$$

$$\langle i_2 \rangle_{T_s} = \frac{1-d}{d} \langle i_1 \rangle_{T_s}$$


$$\langle v_1 \rangle_{T_s} = d R_{on} \langle i \rangle_{T_s} + (1-d) (\langle v \rangle_{T_s} + V_D + R_d i)$$

$$\langle v_1 \rangle_{T_s} + \langle v_2 \rangle_{T_s} = \langle v \rangle_{T_s}$$


$$\langle v_1 \rangle_{T_s} = \frac{R_{on} \langle i_1 \rangle_{T_s}}{d} + \frac{(1-d) R_d \langle i_1 \rangle_{T_s}}{d^2} + \frac{1-d}{d} (\langle v_1 \rangle_{T_s} + V_D)$$

CCM Averaged-Switch Model

PSpice Implementation: `ccm2`

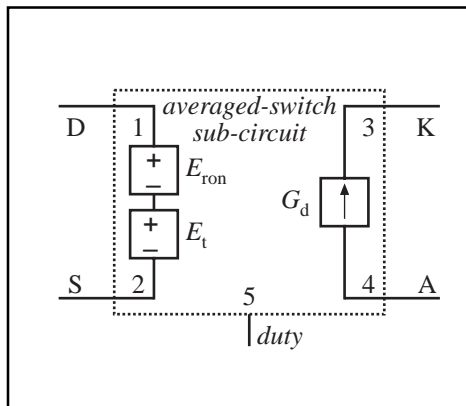

Subcircuit implementation

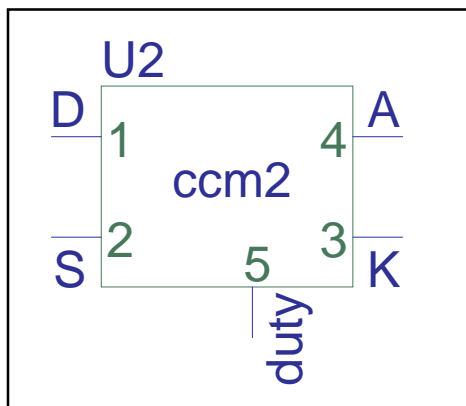


- * MODEL: `ccm2`
- * Application: two-switch PWM converters, includes conduction losses due to R_{on} , V_D , R_d
- * Limitations: CCM only, no transformer

- * Parameters:
- * R_{on} =transistor on resistance
- * V_D =diode forward voltage drop (constant)
- * R_d =diode on resistance

- * Nodes: (same as in `ccm1`)


```
.subckt ccm2 1 2 3 4 5
+params: Ron=0 VD=0 Rd=0
Eron 1 1x value={i(Et)*(Ron+(1-v(5))*Rd/v(5))/v(5)}
Et 1x 2 value={({1-v(5)}*(v(3,4)+VD)/v(5)}
Gd 4 3 value={({1-v(5)}*i(Et)/v(5)}
.ends
```

Sepic converter example using ccm2 model

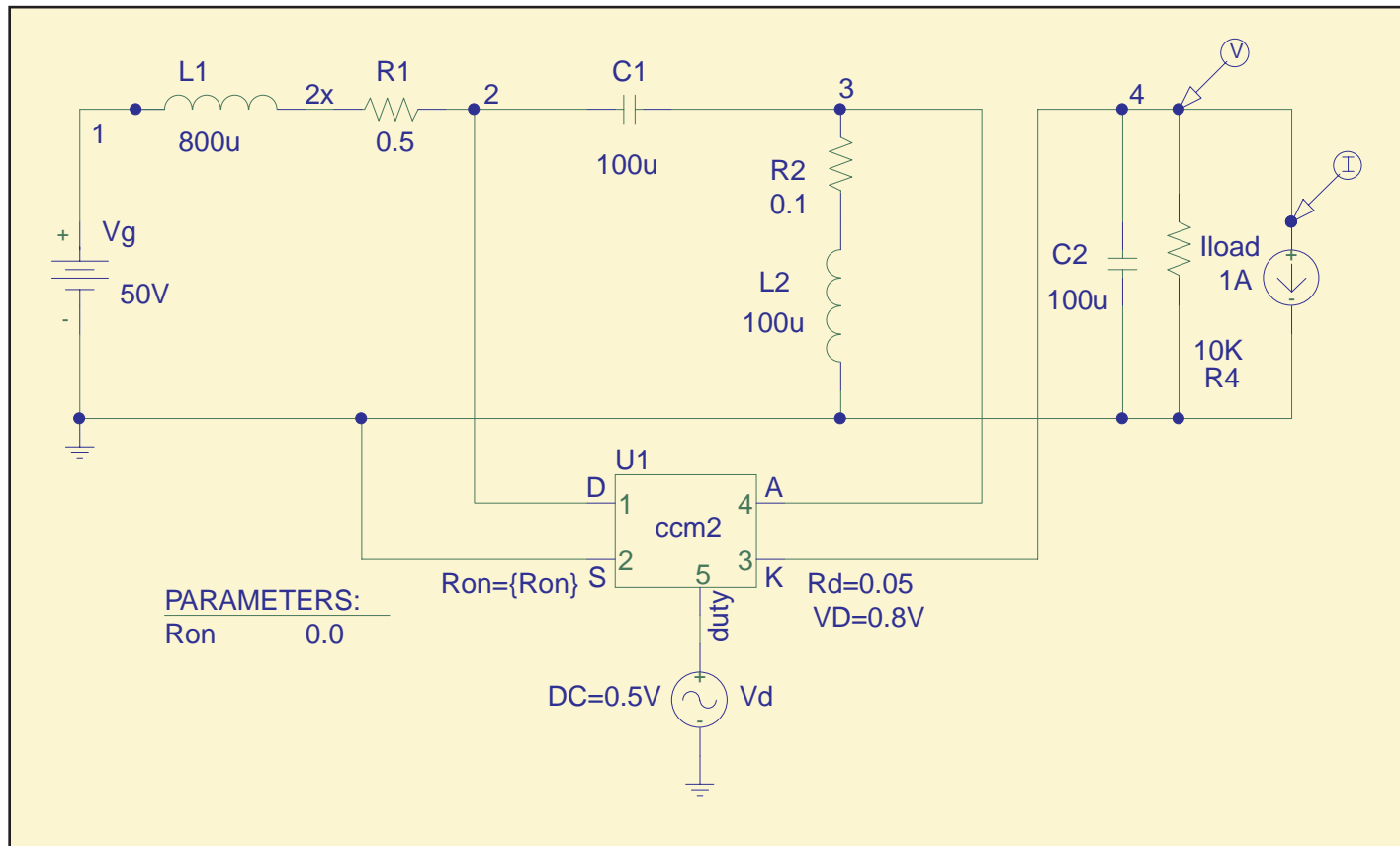


Objective: find converter efficiency as a function of the transistor on-resistance, for a range of loads

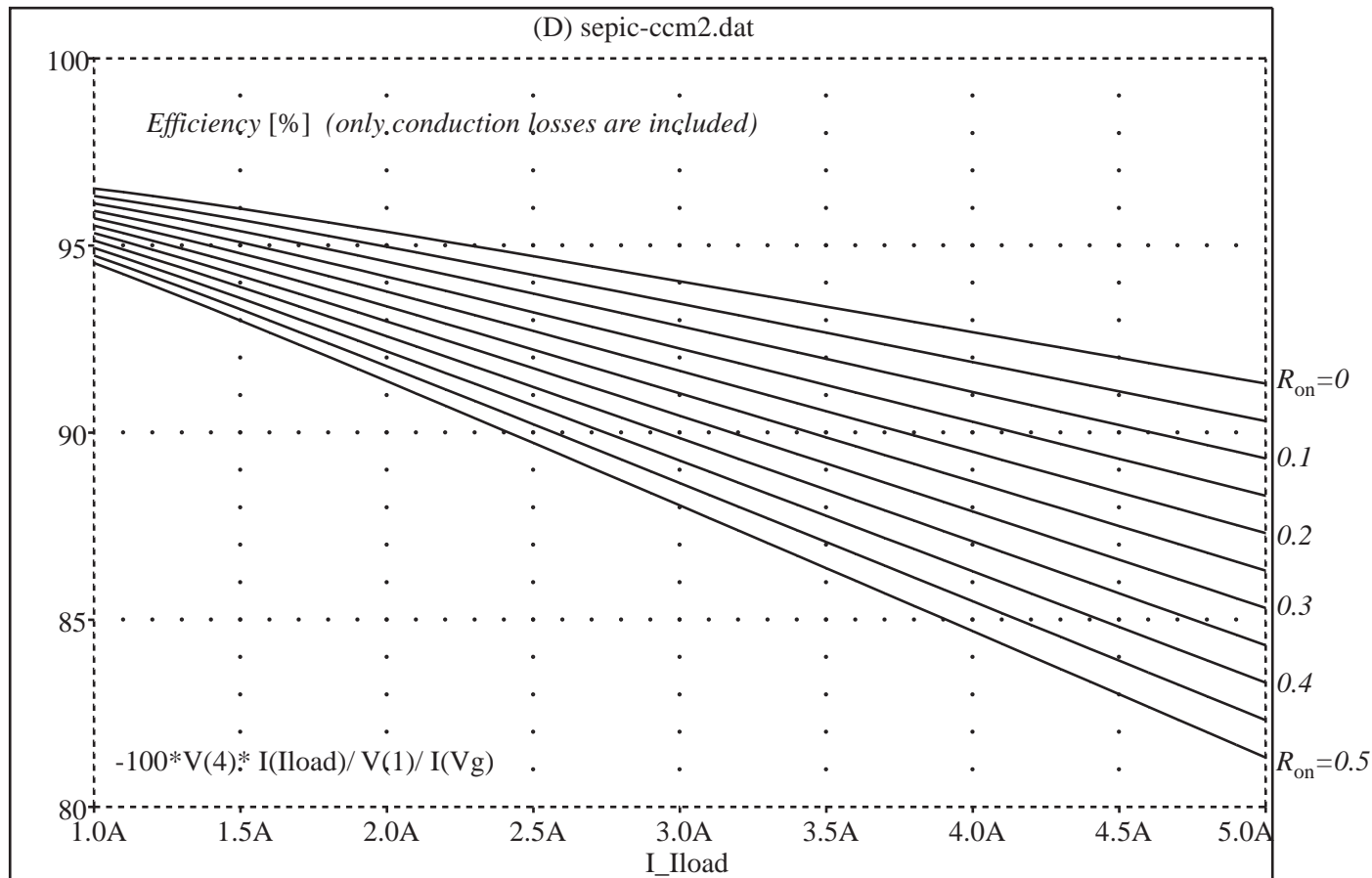Sepic converter example using ccm2 model: Efficiency vs. load current and Ron




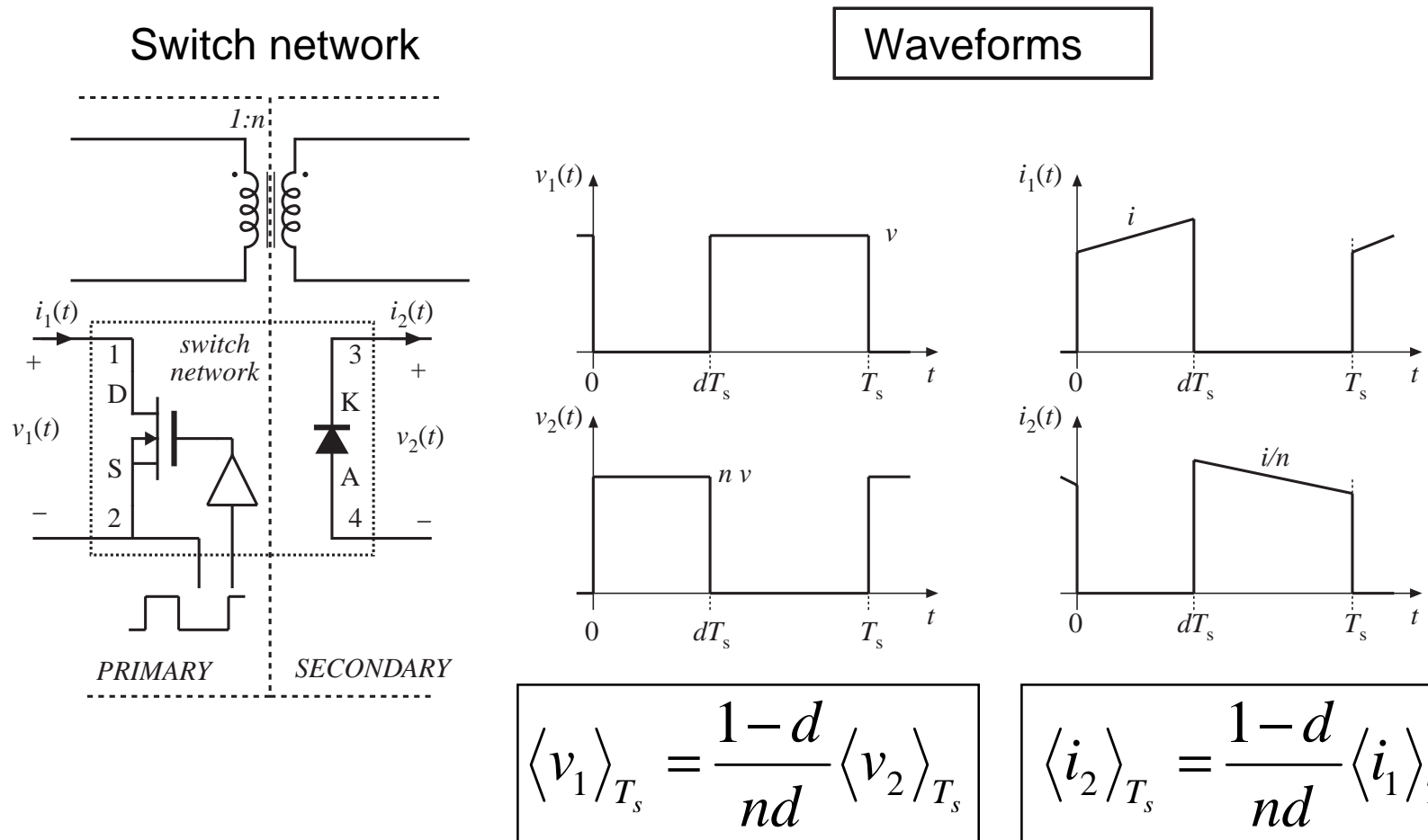
CCM Averaged Switch Model ccm3 For Converters With Isolation Transformer



- Converters: Flyback, Cuk, Sepic, Inverse Sepic (Zeta), with isolation transformer

CCM Averaged-Switch Model

PSpice Implementation: `ccm3`

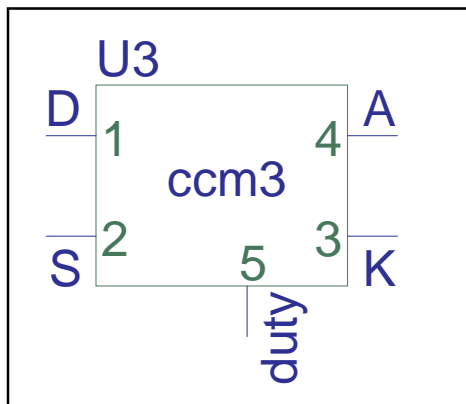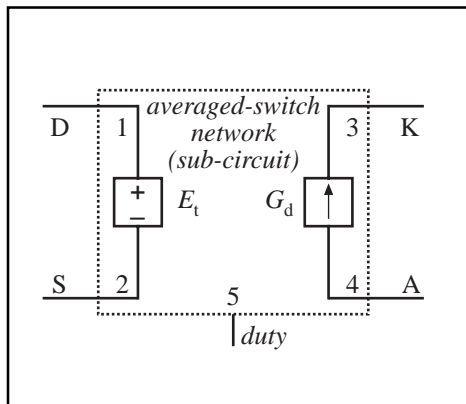

- * MODEL: `ccm3`
- * Application: two-switch PWM converters,
with (possibly) transformer
- * Limitations: ideal switches, CCM only

- * Parameters:
- * n =transformer turns ratio 1:n (primary:secondary)

- * Nodes: (same as in `ccm1`)


```
.subckt ccm3 1 2 3 4 5
+params: n=1
Et 1 2 value={{(1-v(5))*v(3,4)/v(5)/n}
Gd 4 3 value={{(1-v(5))*i(Et)/v(5)/n}
.ends
```

CCM Averaged Switch Model **ccm4** (Conduction Losses and Isolation Transformer)


- Combined **ccm2** and **ccm3** averaged-switch models
- Parameters:
 - Transistor on resistance R_{on}
 - Diode forward voltage drop V_D
 - Diode on resistance R_d
 - Transformer turns ratio n
- A general model implementation valid for all two-switch converters operating in CCM

CCM Averaged-Switch Model

PSpice Implementation: **ccm4**

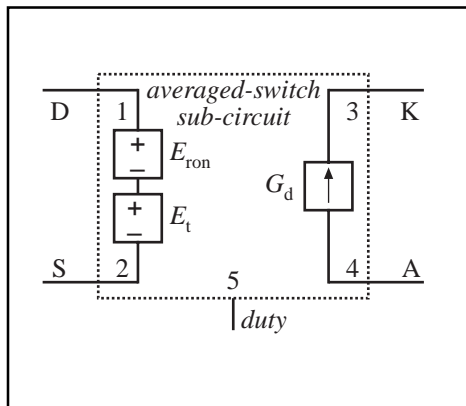

Subcircuit implementation

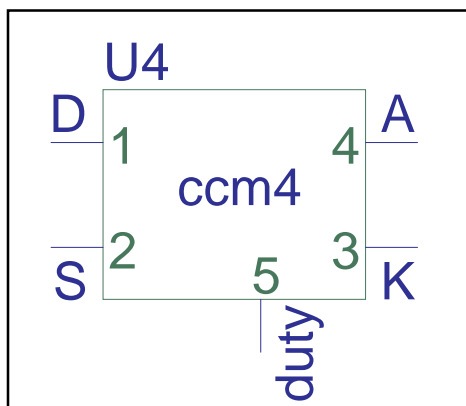

- * **MODEL:** ccm4
 - * **Application:** two-switch PWM converters, includes
 - * conduction losses due to R_{on} , V_D , R_d
 - * and (possibly) transformer
 - * **Limitations:** CCM only
 - *****
 - * **Parameters:**
 - * R_{on} =transistor on resistance
 - * V_D =diode forward voltage drop (constant)
 - * R_d =diode on resistance
 - * n =transformer turns ratio 1:n (primary:secondary)
 - *****
 - * **Nodes:** (same as in ccm1)
 - *****
- ```

.subckt ccm4 1 2 3 4 5
+params: Ron=0 VD=0 Rd=0 n=1
Eron 1 1x value={i(Et)*(Ron+(1-v(5))*Rd/n/n/v(5))/v(5)}
Et 1x 2 value={({1-v(5)}*(v(3,4)+VD)/v(5)/n}
Gd 4 3 value={({1-v(5)}*i(Et)/v(5)/n}
.ends

```


# Averaged-Switch Modeling Exercise: Include Switching Loss

---


- Use averaged-switch modeling approach to construct an averaged model that includes switching losses
- Loss mechanism example: diode reverse recovery

# Modeling switching loss

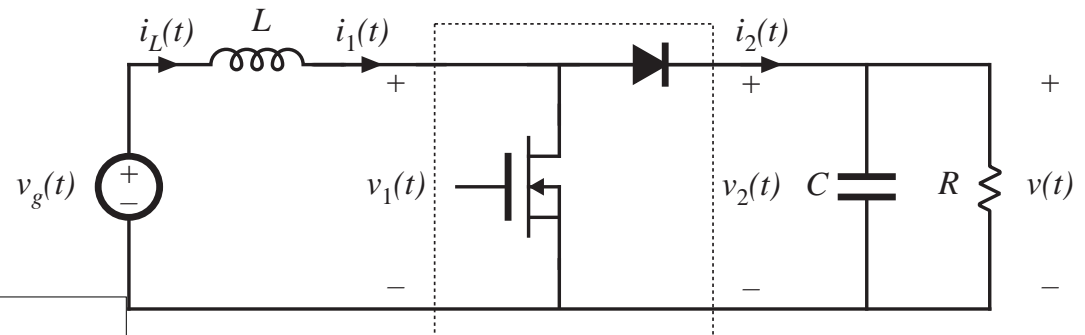Example: diode stored charge in boost converter



Waveforms:

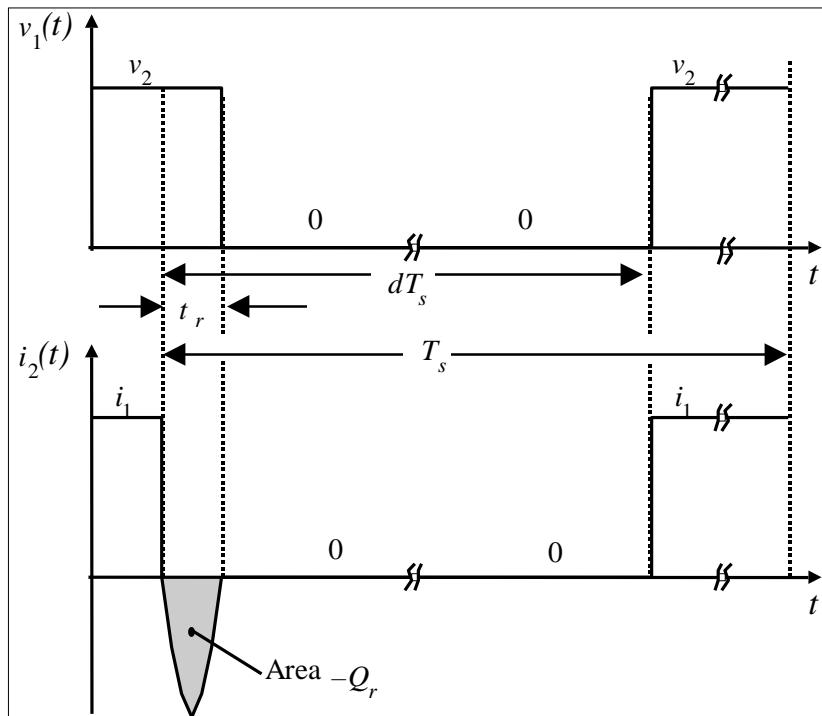

- Other switching loss mechanisms are ignored in this example; one can include other losses if desired, using a similar procedure
- Determine averaged terminal waveforms of switch network
- Construct averaged equivalent circuit model

# Expressions for average terminal waveforms


## Boost converter, switching loss example

$$\langle v_1(t) \rangle_{T_s} = \frac{1}{T_s} ((1-d)T_s + t_r) \langle v_2(t) \rangle_{T_s}$$


$$\langle i_2(t) \rangle_{T_s} = (1-d) \langle i_1(t) \rangle_{T_s} - \frac{Q_r}{T_s}$$

$t_r$  = diode reverse recovery time

$Q_r$  = diode recovered charge

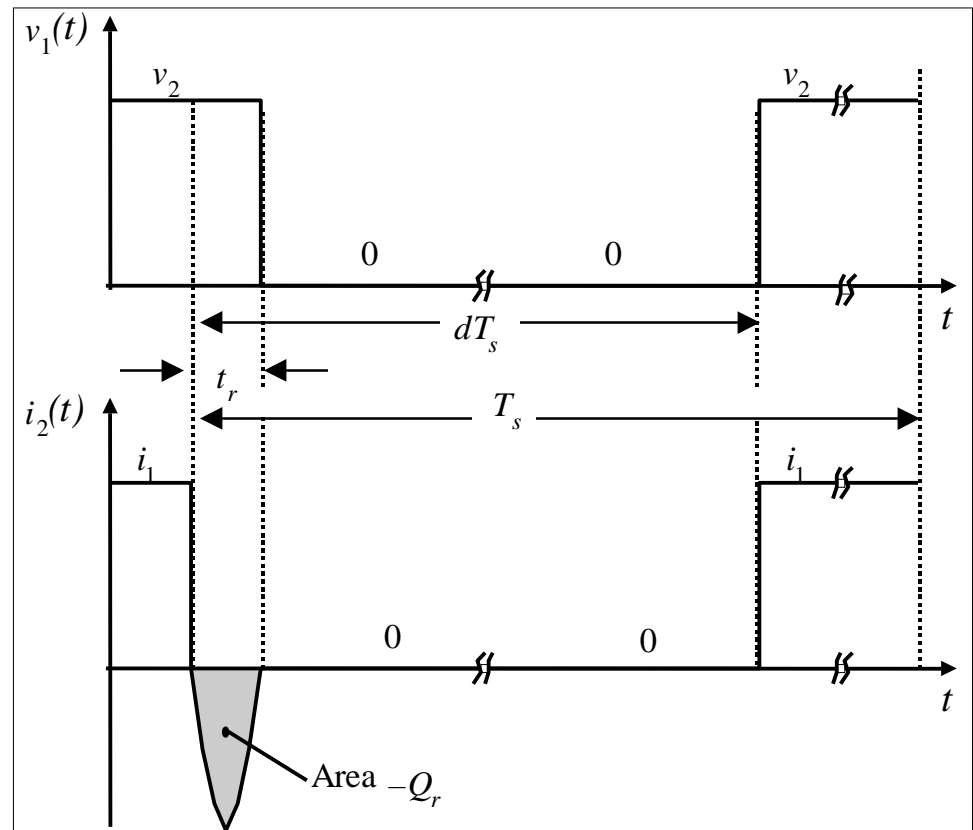

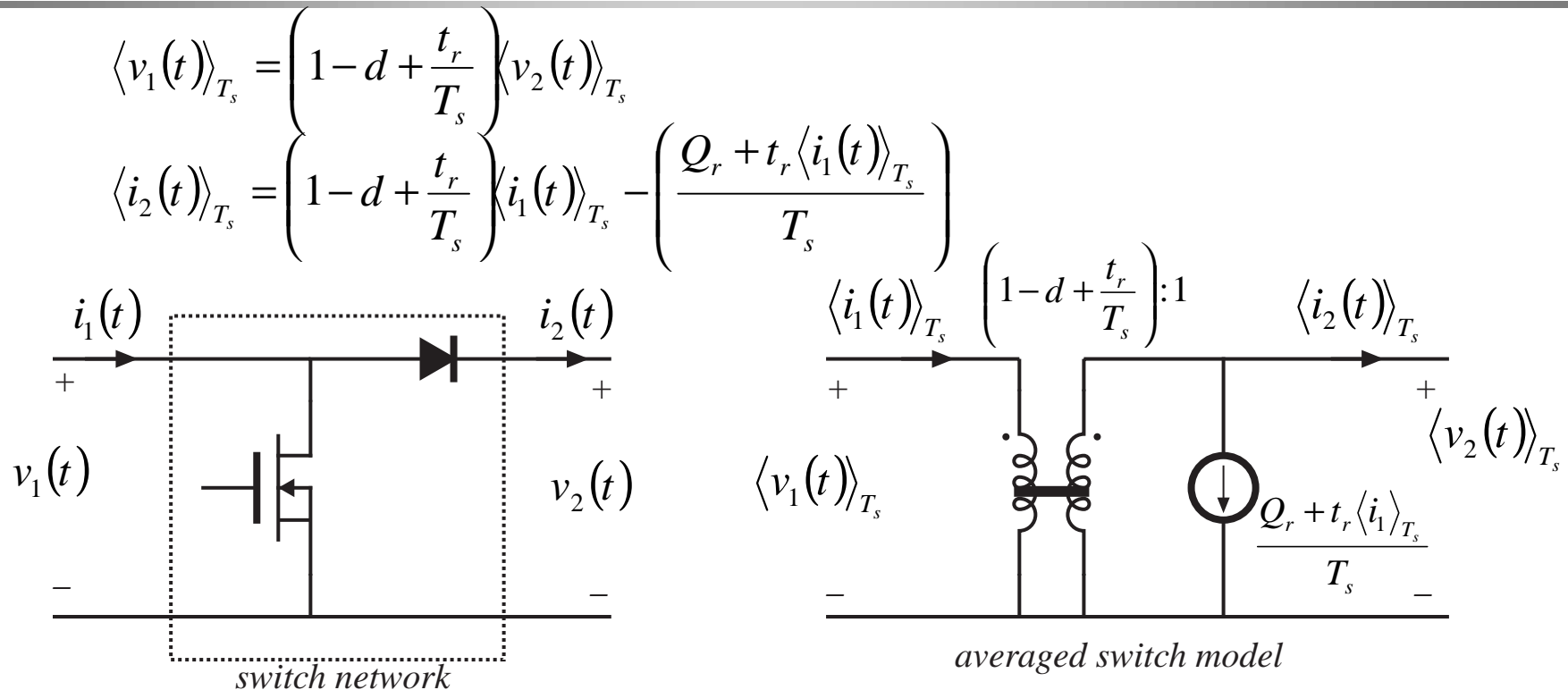
# Averaged equivalent circuit of switch network




- Diode reverse recovery time affects conversion ratio
- Stored charge leads to power loss, modeled by current sink

# Insert averaged switch model into converter circuit

*Original  
converter*

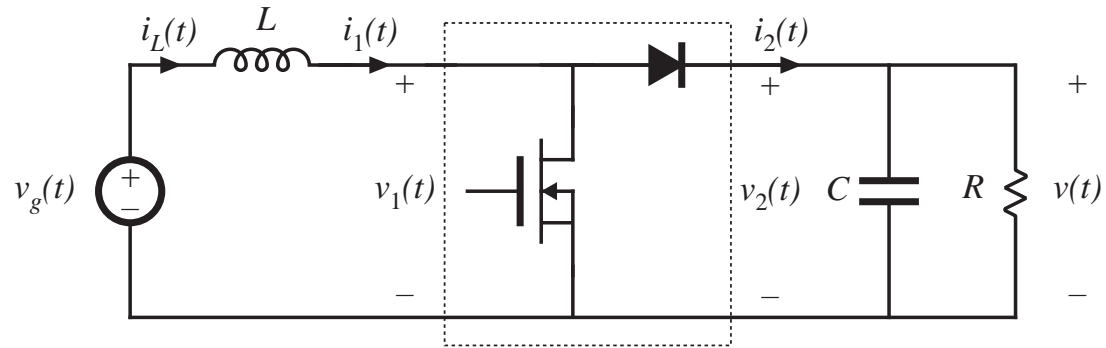

*Averaged  
model*

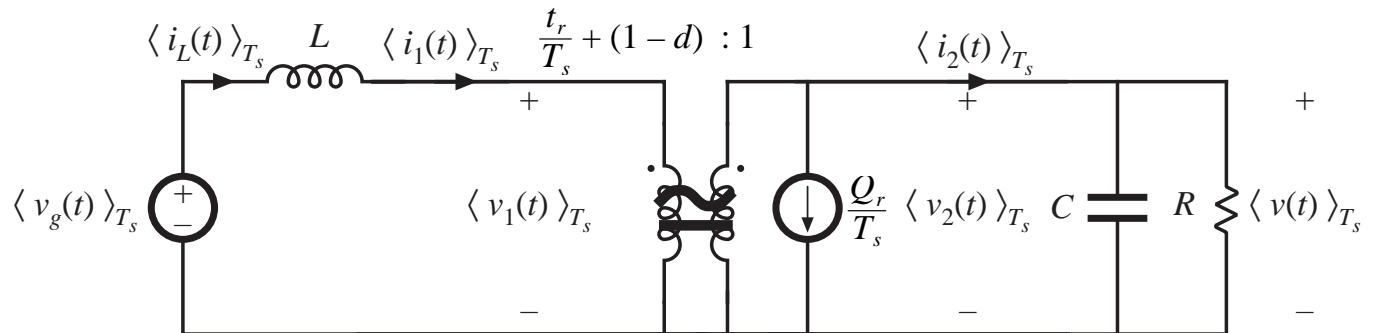

# Efficiency Analysis

## Boost converter, switching loss example

---

$$\eta = \frac{P_{out}}{P_{in}} = \frac{VI_2}{V_g I_1}$$

$$I_1 = \frac{I_2 + \frac{Q_r}{T_s}}{1-D}$$

$$V = \frac{V_g}{\frac{t_r}{T_s} + 1 - D}$$

$$\eta = \frac{VI_2}{V_g I_1} = \left( \frac{1-D}{1-D + \frac{t_r}{T_s}} \right) \left( \frac{I_2}{I_2 + \frac{Q_r}{T_s}} \right) = \left( \frac{1}{1 + \frac{t_r}{(1-D)T_s}} \right) \left( \frac{1}{1 + \frac{Q_r}{I_{load} T_s}} \right)$$

Efficiency due to diode reverse recovery. Other switching loss mechanisms can be included using a similar procedure.

# Summary of Part 2

---

- Basic idea of average-switch modeling:
  - Define a switch network, containing all of the converter switching elements
  - Average terminal waveforms over a switching period
  - Use controlled sources with values equal to average of the switch network terminal waveforms
  - The result is a large-signal, nonlinear, time-invariant model that can be inserted back into the converter network
- The choices of the switch network and the independent terminal waveforms are not unique - there are many ways to construct averaged switch models
- Averaged-switch model (suitable for circuit analysis or simulation) yields predictions of converter steady-state and low-frequency dynamic properties
- Next: apply the averaged-switch modeling approach to other cases of interest.

### 3. Averaged switch modeling of PWM converters operating in the discontinuous conduction mode

---

- **Averaged switch model in DCM**
- **Using averaged-switch model to predict converter steady-state characteristics and small-signal dynamics in DCM**
- **Combined CCM/DCM averaged switch model**
- **PSpice implementation of combined CCM/DCM models**
  - ideal switches (ccm-dcm1)
  - ideal switches in converters with isolation transformer (ccm-dcm2)
- **Application examples:**
  - comparison of transient simulation results in a SEPIC example using (1) switching circuit model and (2) averaged model
  - small-signal dynamic responses of a flyback converter operating in CCM or DCM
  - more converter examples using averaged-switch subcircuits

# Change in characteristics at the CCM/DCM boundary

---

- Steady-state output voltage becomes strongly load-dependent
- Simpler dynamics: one pole and the RHP zero are moved to very high frequency, and can normally be ignored
- Traditionally, boost and buck-boost converters are designed to operate in DCM at full load
- All converters may operate in DCM at light load


So we need equivalent circuits that model the steady-state and small-signal ac models of converters operating in DCM

The averaged switch approach yields an intuitive result that is relatively easy to solve


# Derivation of DCM averaged switch model
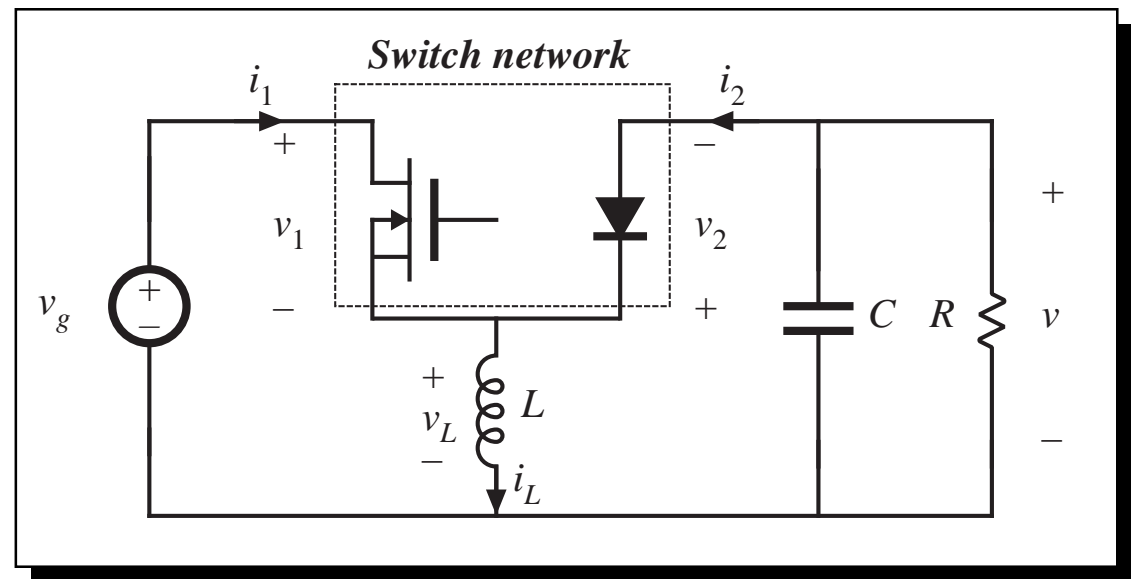
## Buck-boost example

- Define switch terminal quantities  $v_1$ ,  $i_1$ ,  $v_2$ ,  $i_2$ , as shown
- Let us find the averaged quantities  $\langle v_1 \rangle$ ,  $\langle i_1 \rangle$ ,  $\langle v_2 \rangle$ ,  $\langle i_2 \rangle$ , for operation in DCM, and determine the relations between them



# DCM waveforms

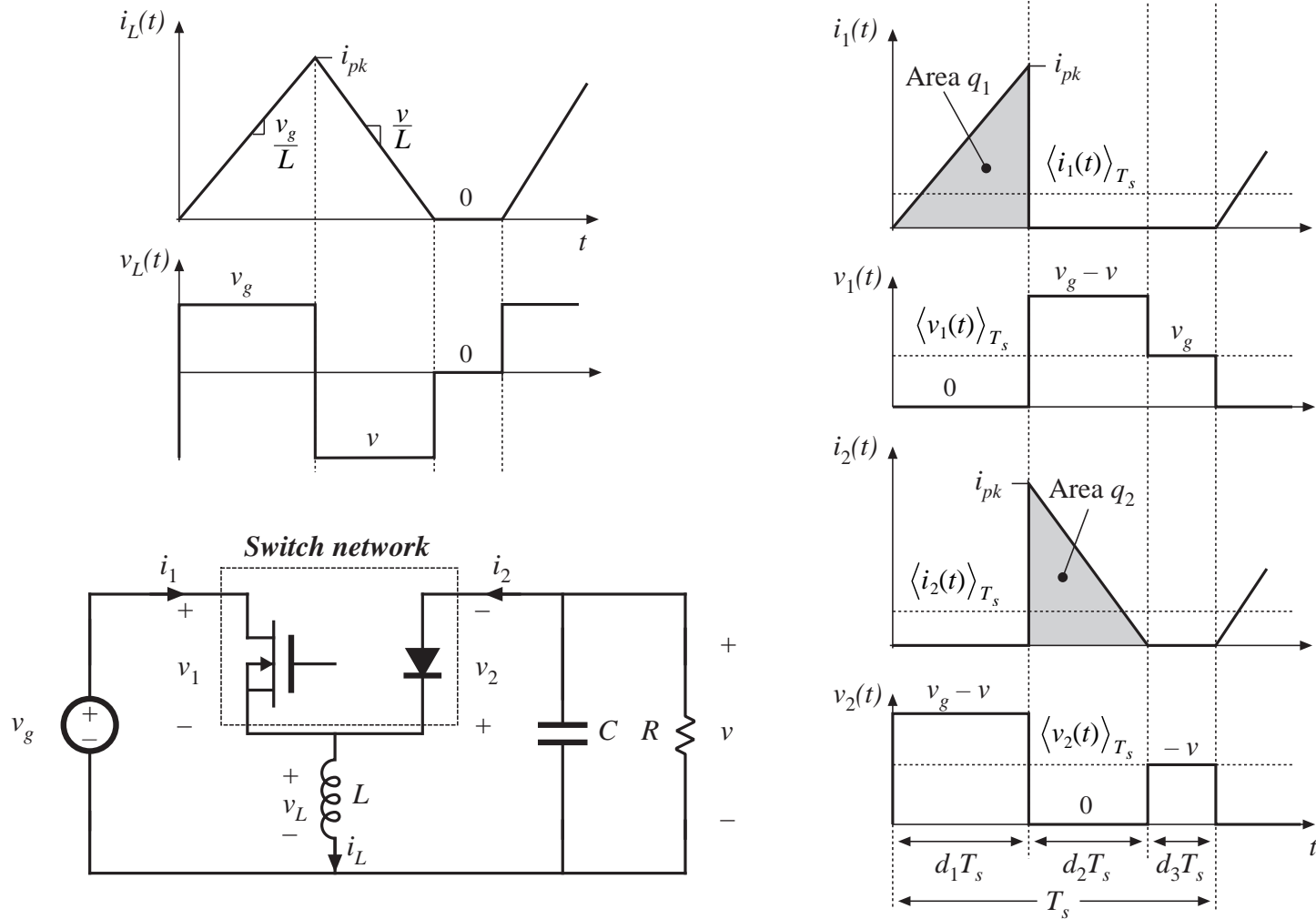

# Basic DCM equations

Peak inductor current:

$$i_{pk} = \frac{v_g}{L} d_1 T_s$$

Average inductor voltage:


$$\langle v_L(t) \rangle_{T_s} = d_1 \langle v_g(t) \rangle_{T_s} + d_2 \langle v(t) \rangle_{T_s} + d_3 \cdot 0$$

In DCM, the diode switches off when the inductor current reaches zero. Hence,  $i(0) = i(T_s) = 0$ , and the average inductor voltage is zero. This is true even during transients.

$$\langle v_L(t) \rangle_{T_s} = d_1(t) \langle v_g(t) \rangle_{T_s} + d_2(t) \langle v(t) \rangle_{T_s} = 0$$

Solve for  $d_2$ :
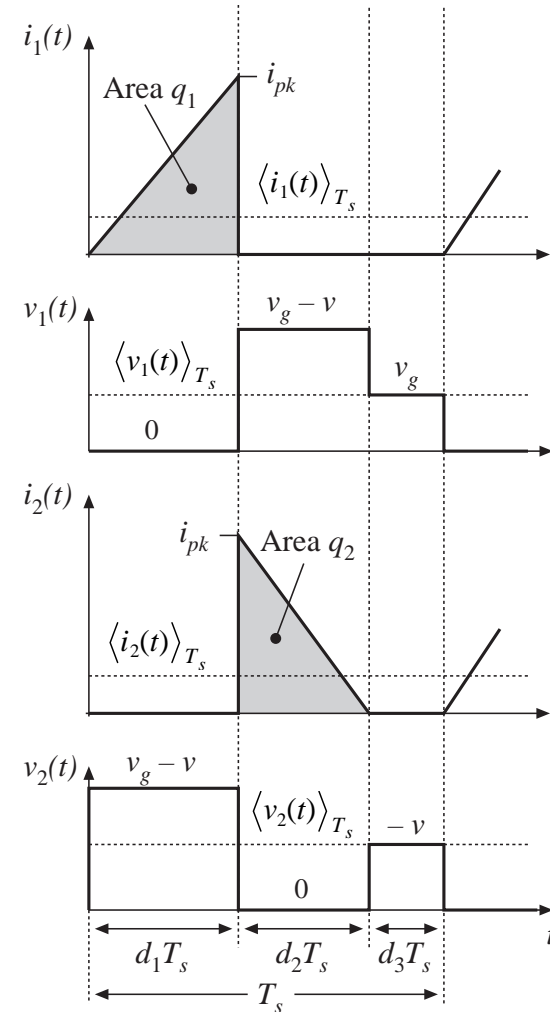
$$d_2(t) = -d_1(t) \frac{\langle v_g(t) \rangle_{T_s}}{\langle v(t) \rangle_{T_s}}$$



# Average switch network terminal voltages

Average the  $v_1(t)$  waveform:


$$\langle v_1(t) \rangle_{T_s} = d_1(t) \cdot 0 + d_2(t) \left( \langle v_g(t) \rangle_{T_s} - \langle v(t) \rangle_{T_s} \right) + d_3(t) \langle v_g(t) \rangle_{T_s}$$

Eliminate  $d_2$  and  $d_3$ :

$$\langle v_1(t) \rangle_{T_s} = \langle v_g(t) \rangle_{T_s}$$

Similar analysis for  $v_2(t)$  waveform leads to
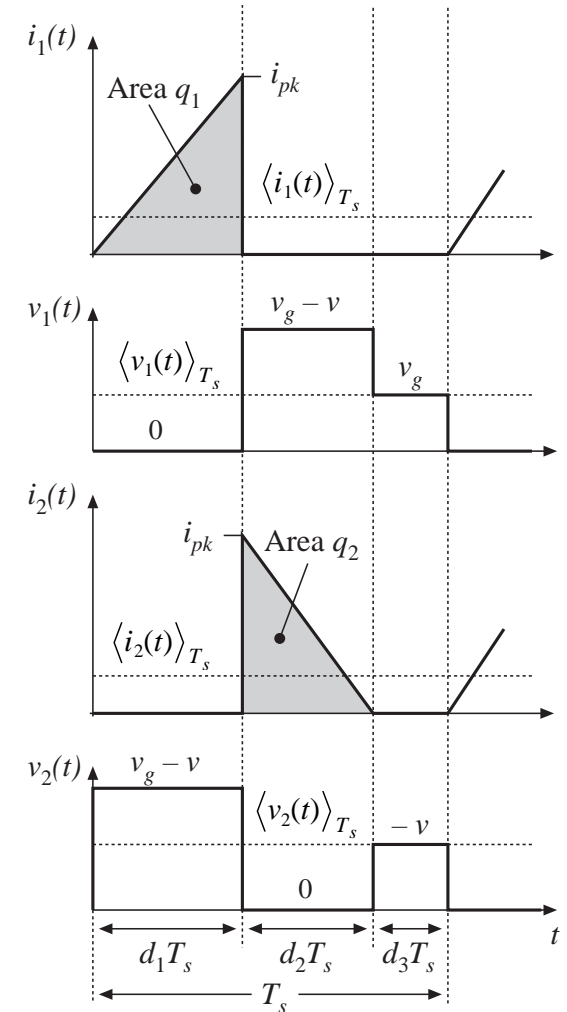
$$\begin{aligned} \langle v_2(t) \rangle_{T_s} &= d_1(t) \left( \langle v_g(t) \rangle_{T_s} - \langle v(t) \rangle_{T_s} \right) + d_2(t) \cdot 0 + d_3(t) \left( - \langle v(t) \rangle_{T_s} \right) \\ &= - \langle v(t) \rangle_{T_s} \end{aligned}$$



# Average switch network terminal currents

Average the  $i_1(t)$  waveform:

$$\langle i_1(t) \rangle_{T_s} = \frac{1}{T_s} \int_t^{t+T_s} i_1(t) dt = \frac{q_1}{T_s}$$

The integral  $q_1$  is the area under the  $i_1(t)$  waveform during first subinterval. Use triangle area formula:

$$q_1 = \int_t^{t+T_s} i_1(t) dt = \frac{1}{2} (d_1 T_s) (i_{pk})$$


Eliminate  $i_{pk}$ :

$$\langle i_1(t) \rangle_{T_s} = \frac{d_1^2(t) T_s}{2L} \langle v_1(t) \rangle_{T_s}$$

Note  $\langle i_1(t) \rangle_{T_s}$  is not equal to  $d \langle i_L(t) \rangle_{T_s}$  !

Similar analysis for  $i_2(t)$  waveform leads to
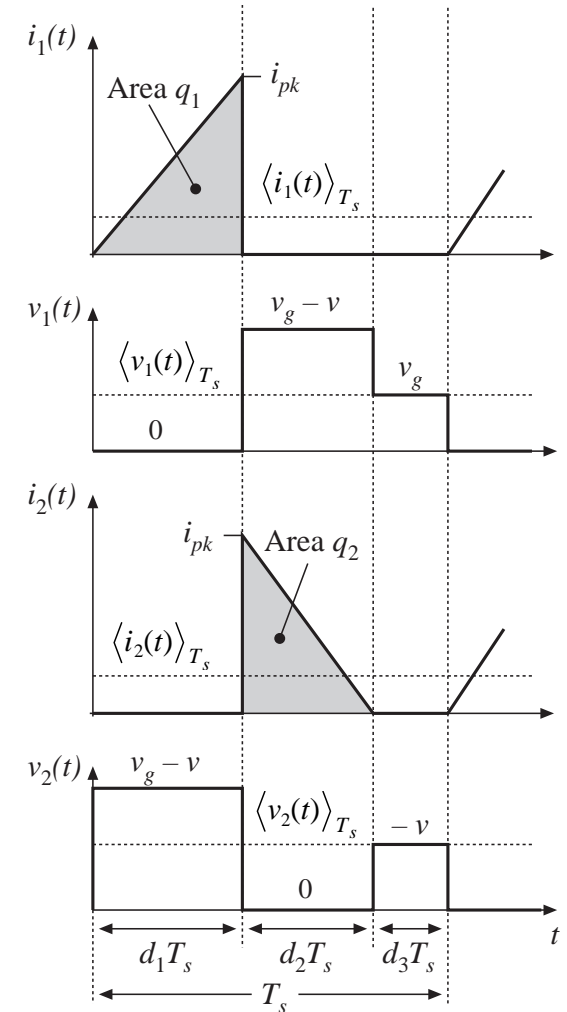
$$\langle i_2(t) \rangle_{T_s} = \frac{d_1^2(t) T_s}{2L} \frac{\langle v_1(t) \rangle_{T_s}^2}{\langle v_2(t) \rangle_{T_s}}$$




# Input port: Averaged equivalent circuit

---

$$\langle i_1(t) \rangle_{T_s} = \frac{d_1^2(t) T_s}{2L} \langle v_1(t) \rangle_{T_s}$$

$$\langle i_1(t) \rangle_{T_s} = \frac{\langle v_1(t) \rangle_{T_s}}{R_e(d_1)}$$

$$R_e(d_1) = \frac{2L}{d_1^2 T_s}$$

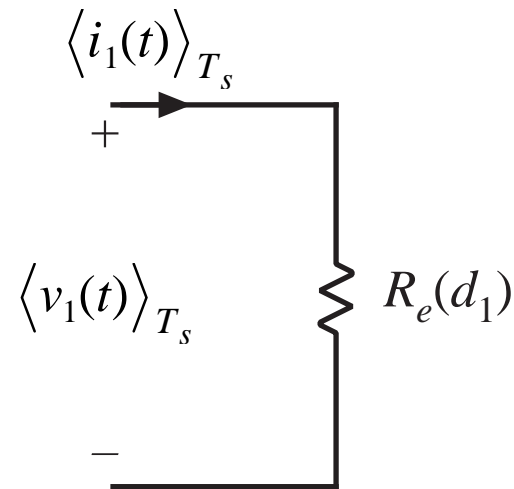


Low-frequency components of input port waveforms obey Ohm's law
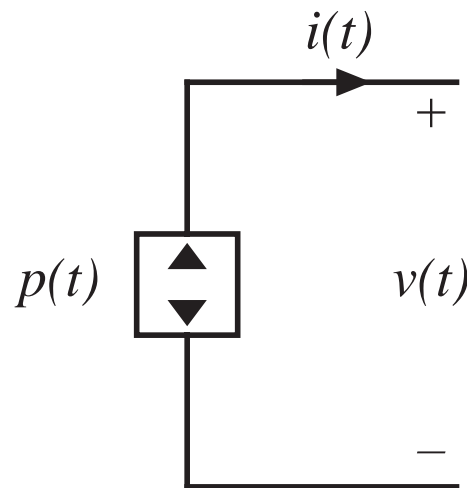
# Output port: Averaged equivalent circuit



$$\langle i_2(t) \rangle_{T_s} = \frac{d_1^2(t) T_s}{2L} \frac{\langle v_1(t) \rangle_{T_s}^2}{\langle v_2(t) \rangle_{T_s}}$$

$$\langle i_2(t) \rangle_{T_s} \langle v_2(t) \rangle_{T_s} = \frac{\langle v_1(t) \rangle_{T_s}^2}{R_e(d_1)} = \langle p(t) \rangle_{T_s}$$



- Output port is a source of power  $p(t)$
- Power  $p(t)$  is independent of load characteristics
- Power  $p(t)$  is dependent on (equal to) the power apparently consumed by the switch network input port

# The dependent power source

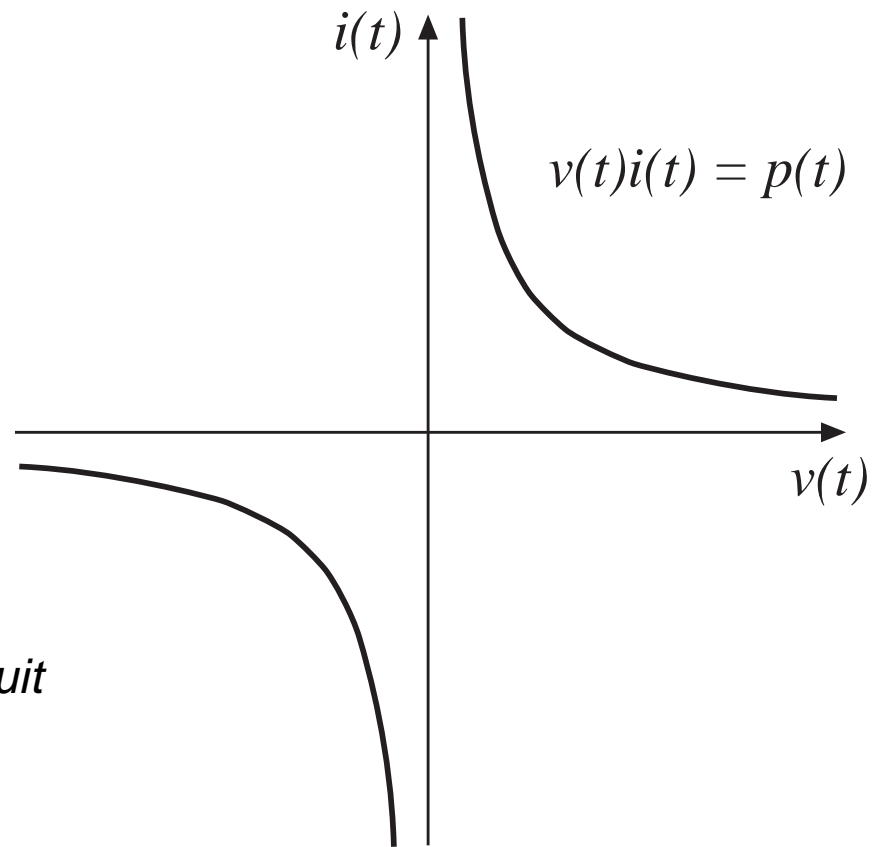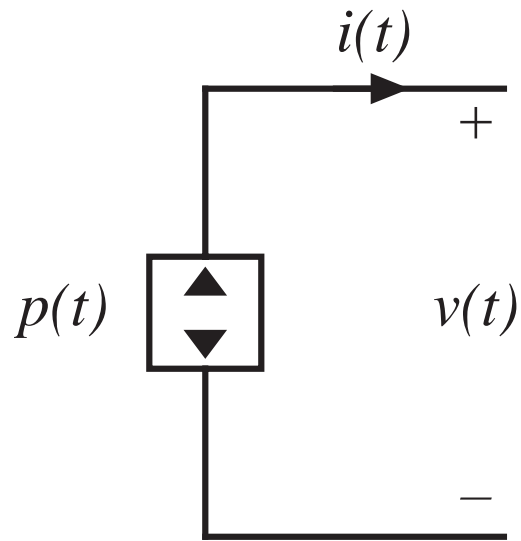

- *Must avoid open- and short-circuit connections of power sources*
- *Power sink: negative  $p(t)$*

# How the power source arises in lossless two-port networks

---

In a lossless two-port network without internal energy storage:  
instantaneous input power is equal to instantaneous output power


In all but a small number of special cases, the instantaneous power  
throughput is dependent on the applied external source and load

If the instantaneous power depends only on the external elements  
connected to one port, then the power is not dependent on the  
characteristics of the elements connected to the other port. The other  
port becomes a source of power, equal to the power flowing through  
the first port


A power source (or power sink) element is obtained
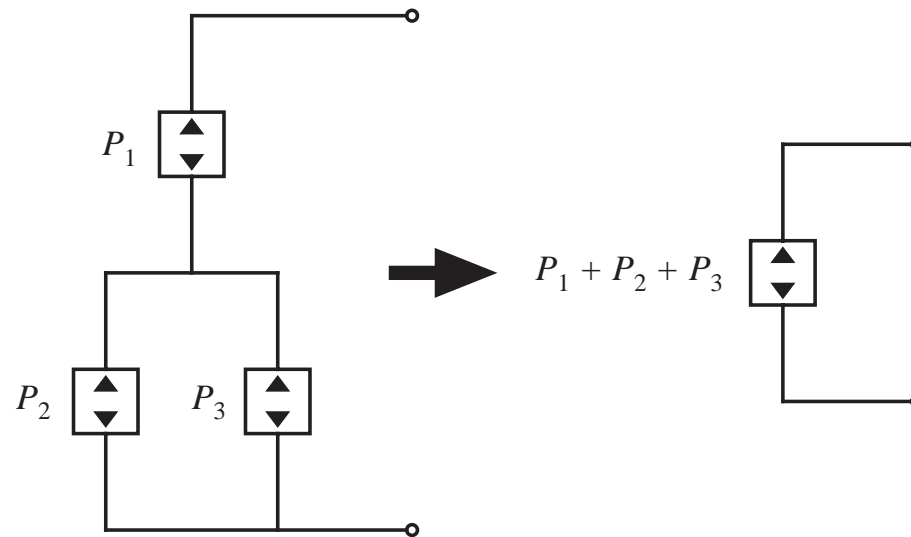
# Properties of power sources


*Series and parallel connection of power sources*



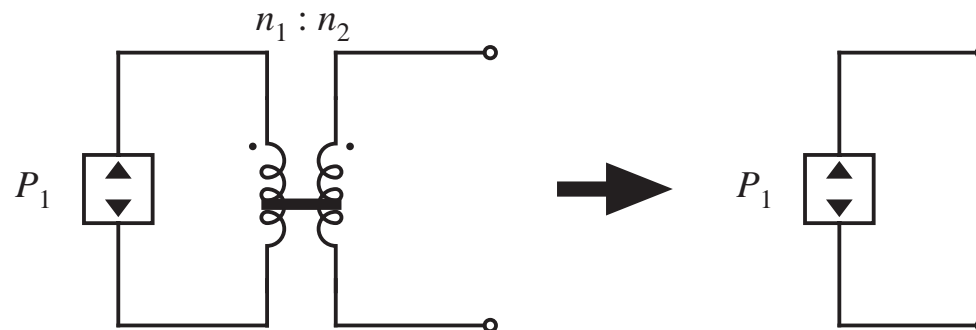*Reflection of power source through a transformer*



# The loss-free resistor (LFR)

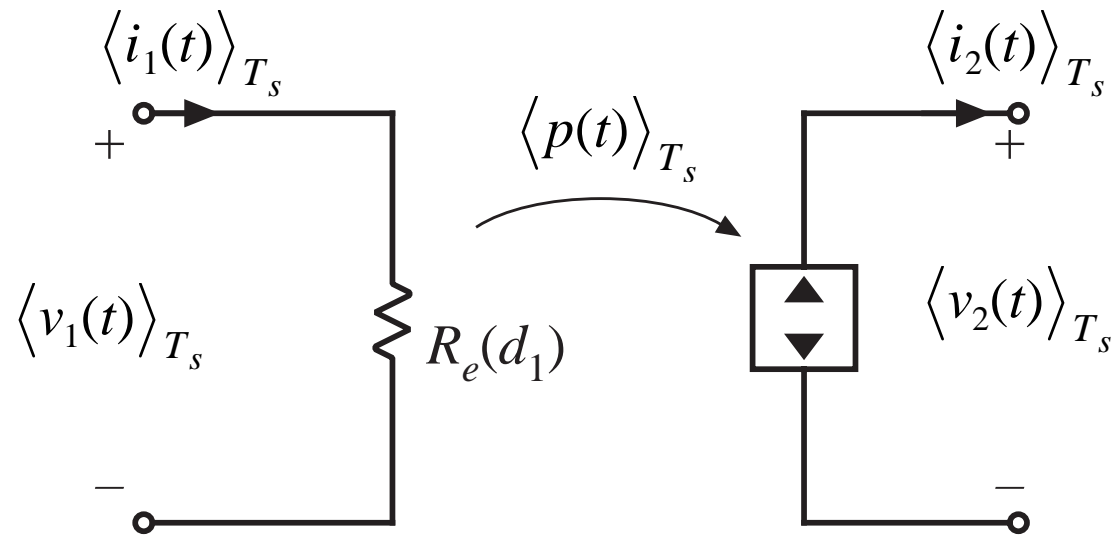


*A two-port lossless network*

*Input port obeys Ohm's Law*


*Power entering input port is transferred to output port*

# Averaged switch model: buck-boost example

*Original circuit*

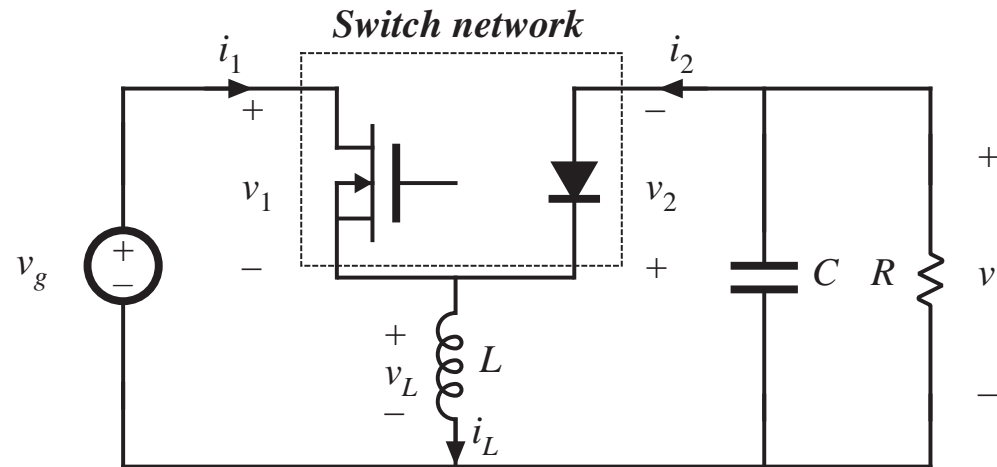

*Averaged model*

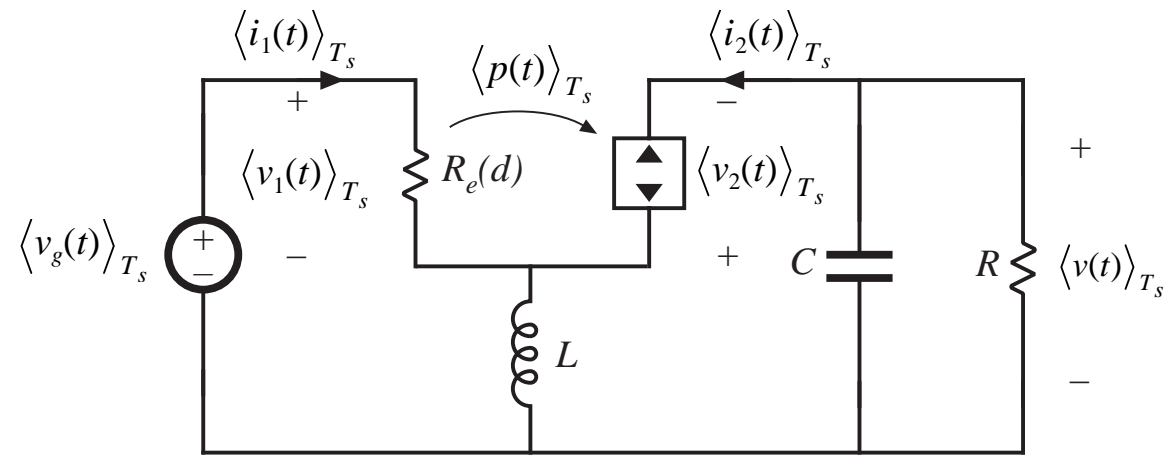


## Solution of averaged model: steady state

Let

$L \rightarrow$  short circuit

$C \rightarrow$  open circuit

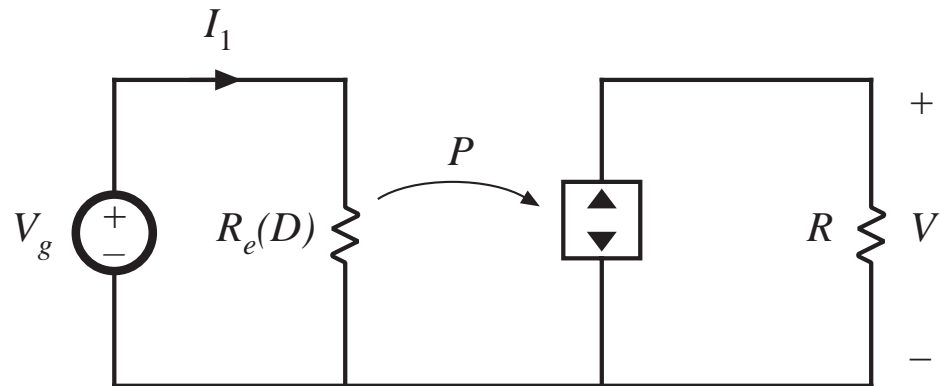

Converter input power:

$$P = \frac{V_g^2}{R_e}$$

Equate and solve:

$$P = \frac{V_g^2}{R_e} = \frac{V^2}{R}$$

Converter output power:

$$P = \frac{V^2}{R}$$

$$\frac{V}{V_g} = \pm \sqrt{\frac{R}{R_e}}$$

## Steady-state LFR solution

---

$$\frac{V}{V_g} = \pm \sqrt{\frac{R}{R_e}} \quad \text{is a general result, for any system that can be modeled as an LFR.}$$

For the buck-boost converter, we have

$$R_e(D) = \frac{2L}{D^2 T_s}$$


Eliminate  $R_e$ :

$$\frac{V}{V_g} = - \sqrt{\frac{D^2 T_s R}{2L}} = - \frac{D}{\sqrt{K}}$$

which agrees with the results of previous steady-state analyses.

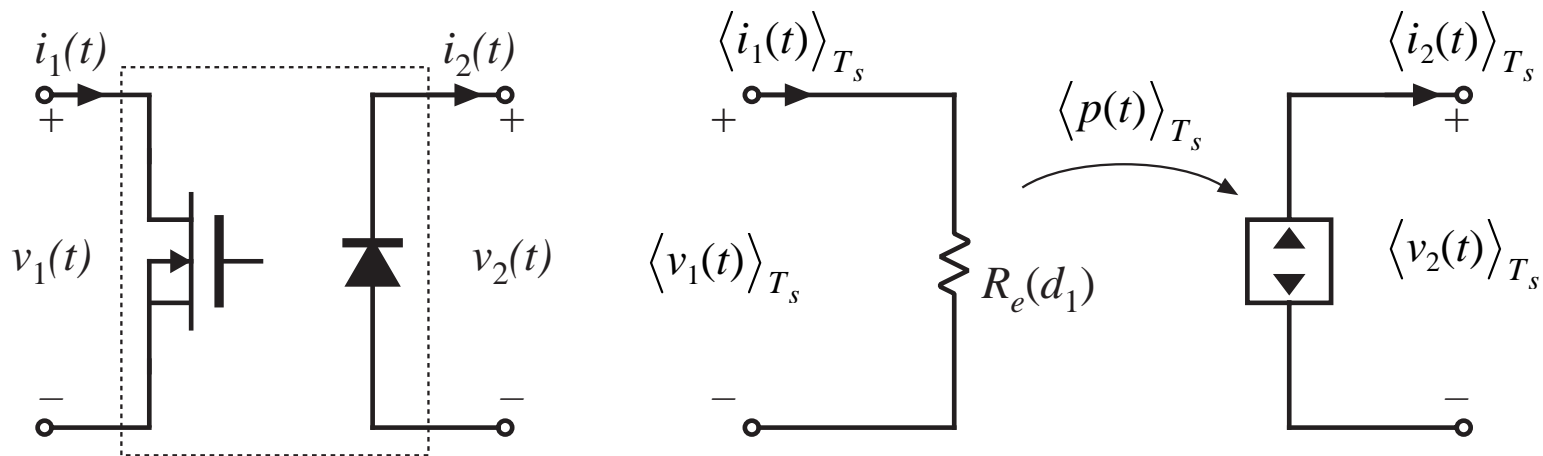
# Averaged models of other DCM converters

- Determine averaged terminal waveforms of switch network
- In each case, averaged transistor waveforms obey Ohm's law, while averaged diode waveforms behave as dependent power source
- **Can simply replace transistor and diode with the averaged model as follows:**




# DCM buck, boost

*Buck*

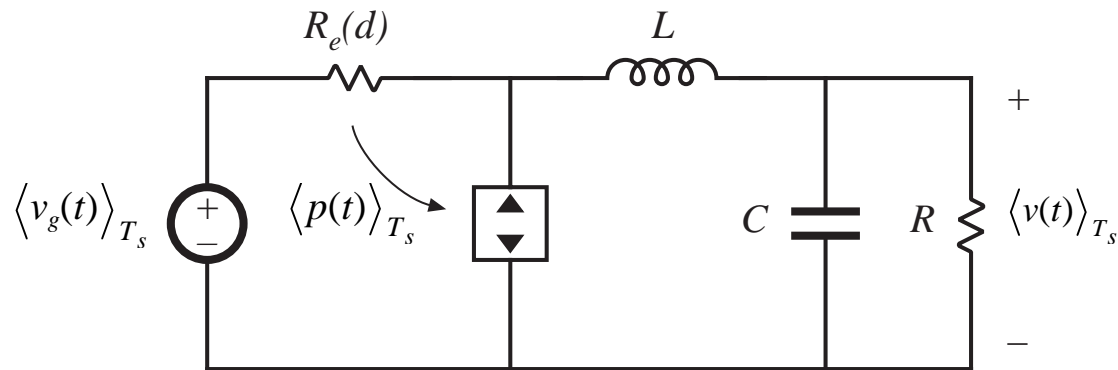


$$R_e = \frac{2L}{d^2 T_s}$$

*Boost*

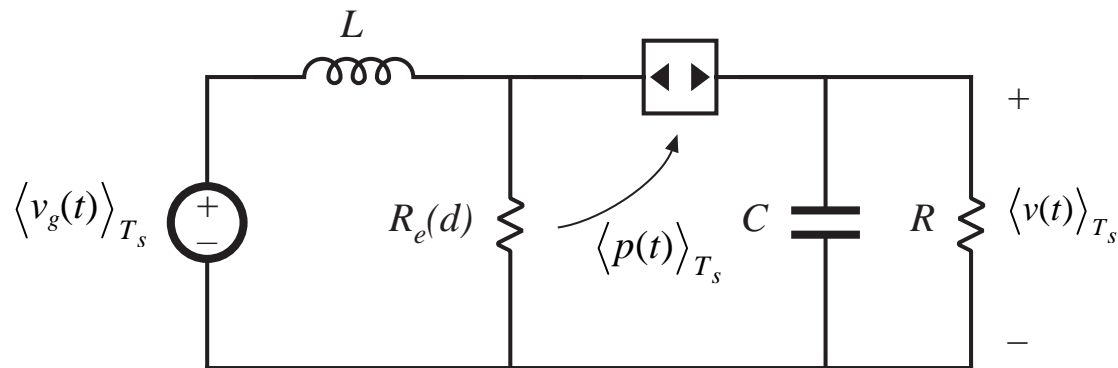


# DCM Cuk, SEPIC

*Cuk*

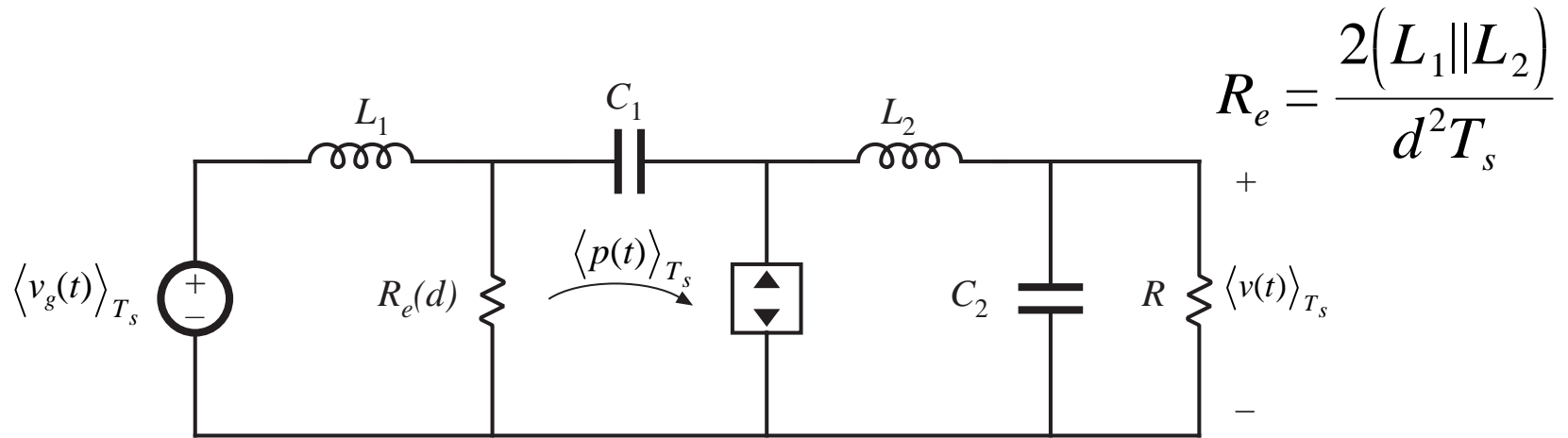

*SEPIC*

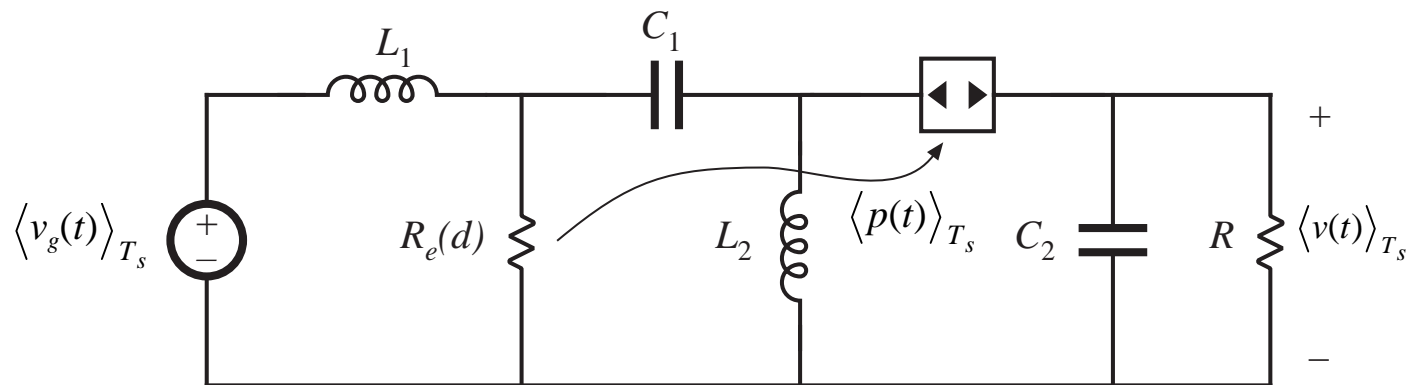


# Steady-state solution: DCM buck, boost


Let  $L \rightarrow$  short circuit

$C \rightarrow$  open circuit

*Buck*

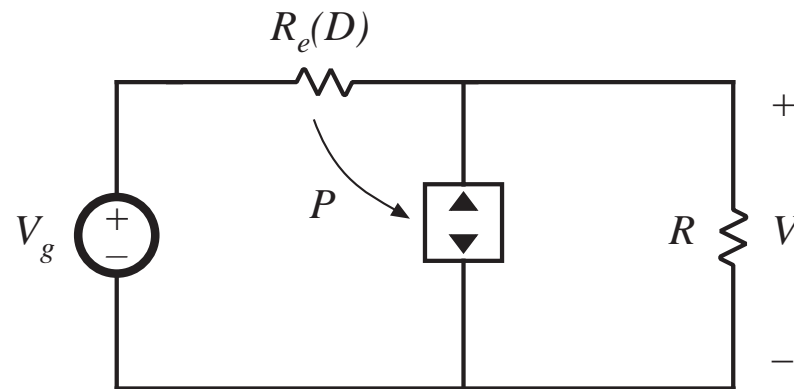

*Boost*

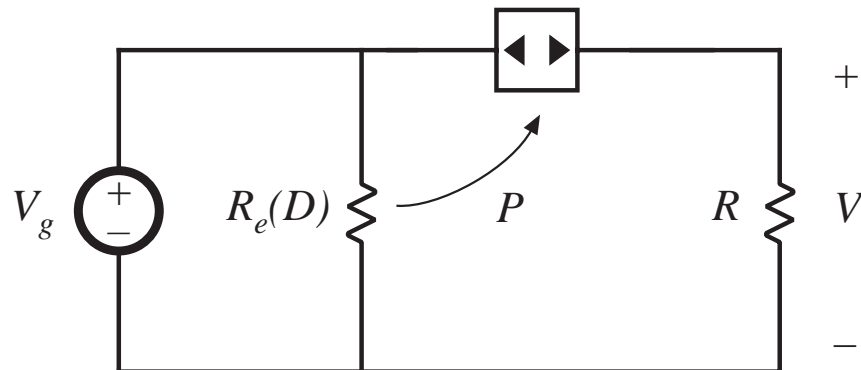

# Steady-state solution of DCM/LFR models


| Converter       | $M$ , CCM          | $M$ , DCM                         |
|-----------------|--------------------|-----------------------------------|
| Buck            | $D$                | $\frac{2}{1 + \sqrt{1 + 4R_e/R}}$ |
| Boost           | $\frac{1}{1 - D}$  | $\frac{1 + \sqrt{1 + 4R/R_e}}{2}$ |
| Buck-boost, Cuk | $\frac{-D}{1 - D}$ | $-\sqrt{\frac{R}{R_e}}$           |
| SEPIC           | $\frac{D}{1 - D}$  | $\sqrt{\frac{R}{R_e}}$            |

$I > I_{crit}$  for CCM  
 $I < I_{crit}$  for DCM

$$I_{crit} = \frac{1 - D}{D} \frac{V_g}{R_e(D)}$$

# Small-signal ac modeling of the DCM switch network

*Large-signal averaged model*

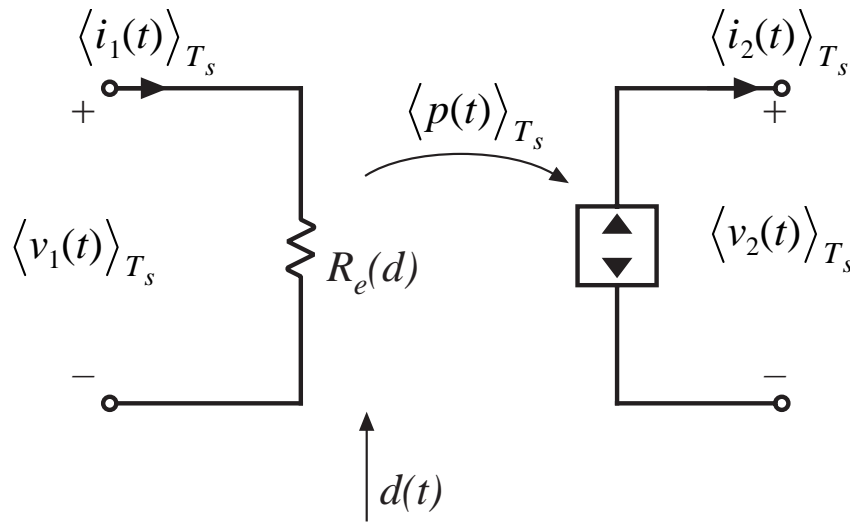

*Perturb and linearize: let*

$$d(t) = D + \hat{d}(t)$$

$$\langle v_1(t) \rangle_{T_s} = V_1 + \hat{v}_1(t)$$

$$\langle i_1(t) \rangle_{T_s} = I_1 + \hat{i}_1(t)$$

$$\langle v_2(t) \rangle_{T_s} = V_2 + \hat{v}_2(t)$$

$$\langle i_2(t) \rangle_{T_s} = I_2 + \hat{i}_2(t)$$



$$\langle i_1(t) \rangle_{T_s} = \frac{d_1^2(t) T_s}{2L} \langle v_1(t) \rangle_{T_s}$$

$$\langle i_2(t) \rangle_{T_s} = \frac{d_1^2(t) T_s}{2L} \frac{\langle v_1(t) \rangle_{T_s}^2}{\langle v_2(t) \rangle_{T_s}}$$


$$\hat{i}_1 = \frac{\hat{v}_1}{r_1} + j_1 \hat{d} + g_1 \hat{v}_2$$

$$\hat{i}_2 = -\frac{\hat{v}_2}{r_2} + j_2 \hat{d} + g_2 \hat{v}_1$$

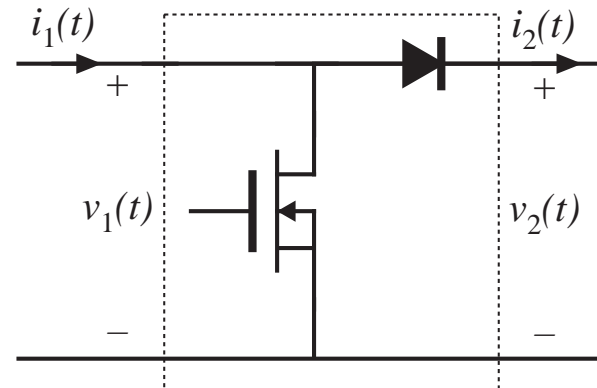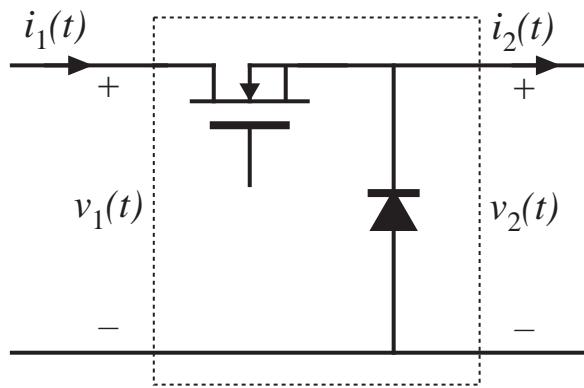
# A more convenient way to model the buck and boost small-signal DCM switch networks



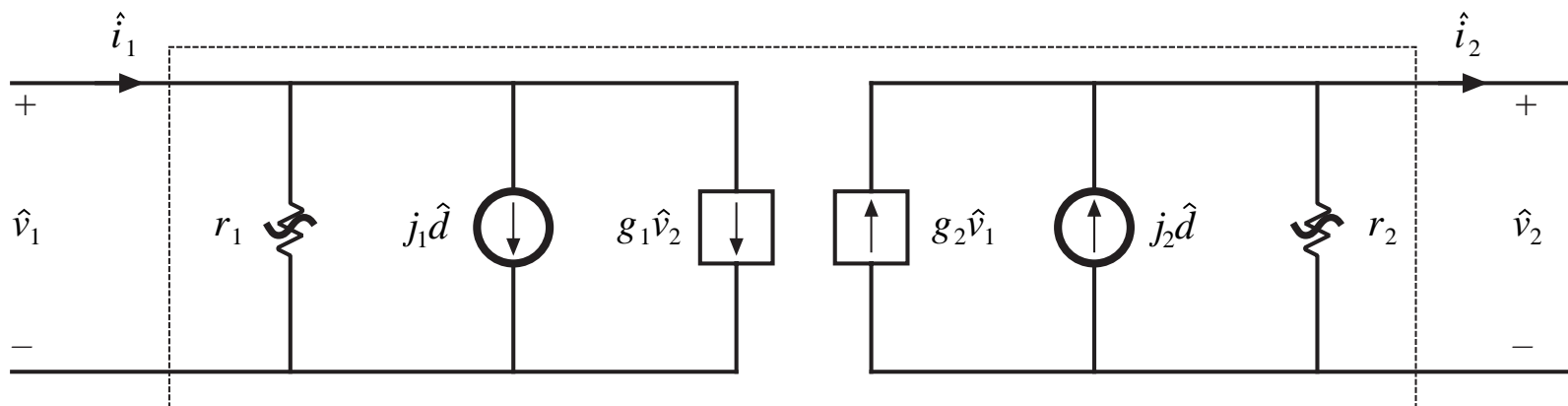In any event, a small-signal two-port model is used, of the form


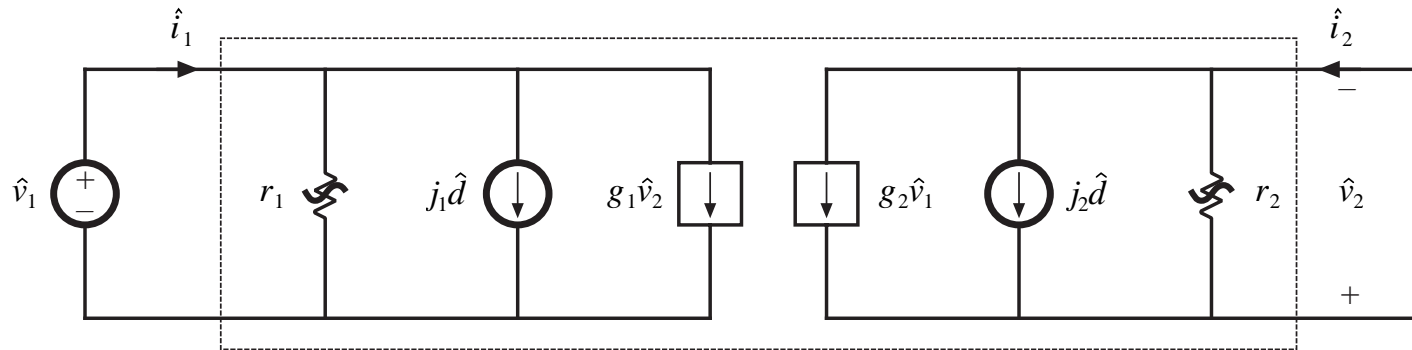
# Small-signal DCM switch model parameters



| Switch type                         | $g_1$                   | $j_1$                     | $r_1$                   | $g_2$                      | $j_2$                     | $r_2$         |
|-------------------------------------|-------------------------|---------------------------|-------------------------|----------------------------|---------------------------|---------------|
| Buck,<br><input type="text"/>       | $\frac{1}{R_e}$         | $\frac{2(1-M)V_1}{DR_e}$  | $R_e$                   | $\frac{2-M}{MR_e}$         | $\frac{2(1-M)V_1}{DMR_e}$ | $M^2R_e$      |
| Boost,<br><input type="text"/>      | $\frac{1}{(M-1)^2 R_e}$ | $\frac{2MV_1}{D(M-1)R_e}$ | $\frac{(M-1)^2}{M} R_e$ | $\frac{2M-1}{(M-1)^2 R_e}$ | $\frac{2V_1}{D(M-1)R_e}$  | $(M-1)^2 R_e$ |
| Buck-boost,<br><input type="text"/> | 0                       | $\frac{2V_1}{DR_e}$       | $R_e$                   | $\frac{2M}{R_e}$           | $\frac{2V_1}{DMR_e}$      | $M^2R_e$      |

# DCM small-signal transfer functions


---

- When expressed in terms of  $R$ ,  $L$ ,  $C$ , and  $M$  (not  $D$ ), the small-signal transfer functions are the same in DCM as in CCM
- Hence, DCM boost and buck-boost converters exhibit two poles and one RHP zero in control-to-output transfer functions
- **But**, value of  $L$  is small in DCM. Hence
  - RHP zero appears at high frequency, usually greater than switching frequency
  - Pole due to inductor dynamics appears at high frequency, near to or greater than switching frequency
  - So DCM buck, boost, and buck-boost converters exhibit essentially a single-pole response
- A simple approximation: let  $L \rightarrow 0$
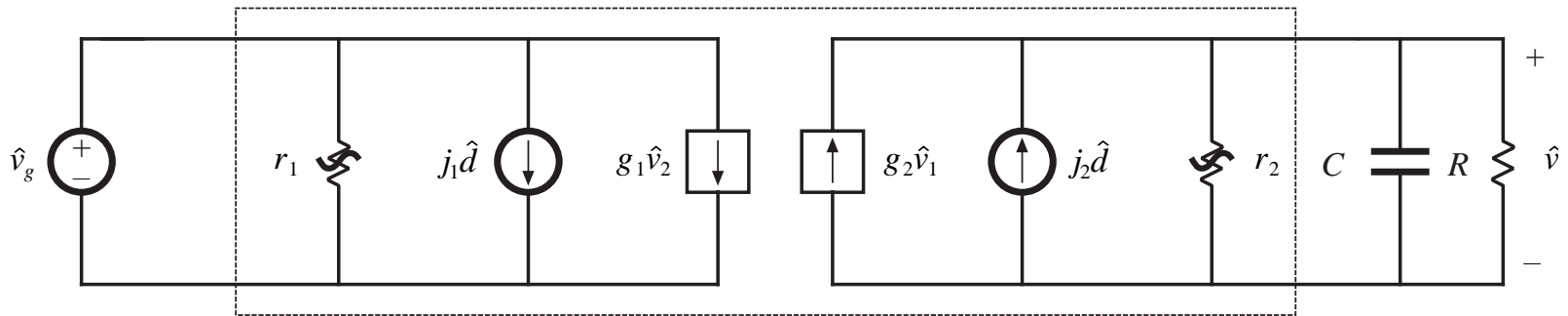
# The simple approximation $L \rightarrow 0$

Buck, boost, and buck-boost converter models all reduce to

*DCM switch network small-signal ac model*



Transfer functions

$$\begin{aligned}
 \text{control-to-output} \quad G_{vd}(s) &= \left. \frac{\hat{v}}{\hat{d}} \right|_{\hat{v}_g=0} = \frac{G_{d0}}{1 + \frac{s}{\omega_p}} & \text{with} & \quad G_{d0} = j_2 (R \parallel r_2) \\
 & & & \quad \omega_p = \frac{1}{(R \parallel r_2) C} \\
 \text{line-to-output} \quad G_{vg}(s) &= \left. \frac{\hat{v}}{\hat{v}_g} \right|_{\hat{d}=0} = \frac{G_{g0}}{1 + \frac{s}{\omega_p}} & & \quad G_{g0} = g_2 (R \parallel r_2) = M
 \end{aligned}$$

# Transfer function salient features

---

---

| Converter  | $G_{d0}$                        | $G_{g0}$ | $\omega_p$             |
|------------|---------------------------------|----------|------------------------|
| Buck       | $\frac{2V}{D} \frac{1-M}{2-M}$  | $M$      | $\frac{2-M}{(1-M)RC}$  |
| Boost      | $\frac{2V}{D} \frac{M-1}{2M-1}$ | $M$      | $\frac{2M-1}{(M-1)RC}$ |
| Buck-boost | $\frac{V}{D}$                   | $M$      | $\frac{2}{RC}$         |

---

# DCM boost example


## Control-to-output transfer function $G_{vd}(s)$

$$R = 12 \Omega$$

$$L = 5 \mu\text{H}$$

$$C = 470 \mu\text{F}$$

$$f_s = 100 \text{ kHz}$$

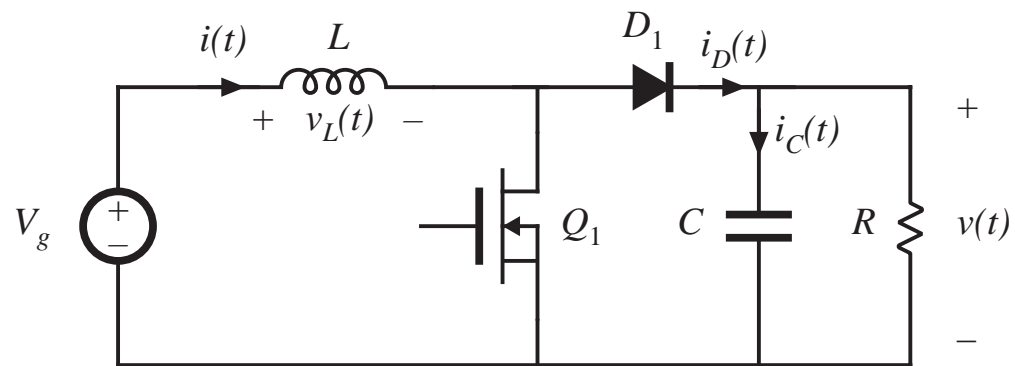

The output voltage is regulated to be  $V = 36 \text{ V}$ . It is desired to determine  $G_{vd}(s)$  at the operating point where the load current is  $I = 3 \text{ A}$  and the dc input voltage is  $V_g = 24 \text{ V}$ .

## Evaluate simple model parameters

---

$$P = I(V - V_g) = (3 \text{ A})(36 \text{ V} - 24 \text{ V}) = 36 \text{ W}$$


$$R_e = \frac{V_g^2}{P} = \frac{(24 \text{ V})^2}{36 \text{ W}} = 16 \Omega$$

$$D = \sqrt{\frac{2L}{R_e T_s}} = \sqrt{\frac{2(5 \mu\text{H})}{(16 \Omega)(10 \mu\text{s})}} = 0.25$$

$$G_{d0} = \frac{2V}{D} \frac{M-1}{2M-1} = \frac{2(36 \text{ V})}{(0.25)} \frac{\left(\frac{(36 \text{ V})}{(24 \text{ V})} - 1\right)}{\left(2 \frac{(36 \text{ V})}{(24 \text{ V})} - 1\right)} = 72 \text{ V} \Rightarrow 37 \text{ dBV}$$

$$f_p = \frac{\omega_p}{2\pi} = \frac{2M-1}{2\pi (M-1)RC} = \frac{\left(2 \frac{(36 \text{ V})}{(24 \text{ V})} - 1\right)}{2\pi \left(\frac{(36 \text{ V})}{(24 \text{ V})} - 1\right)(12 \Omega)(470 \mu\text{F})} = 112 \text{ Hz}$$
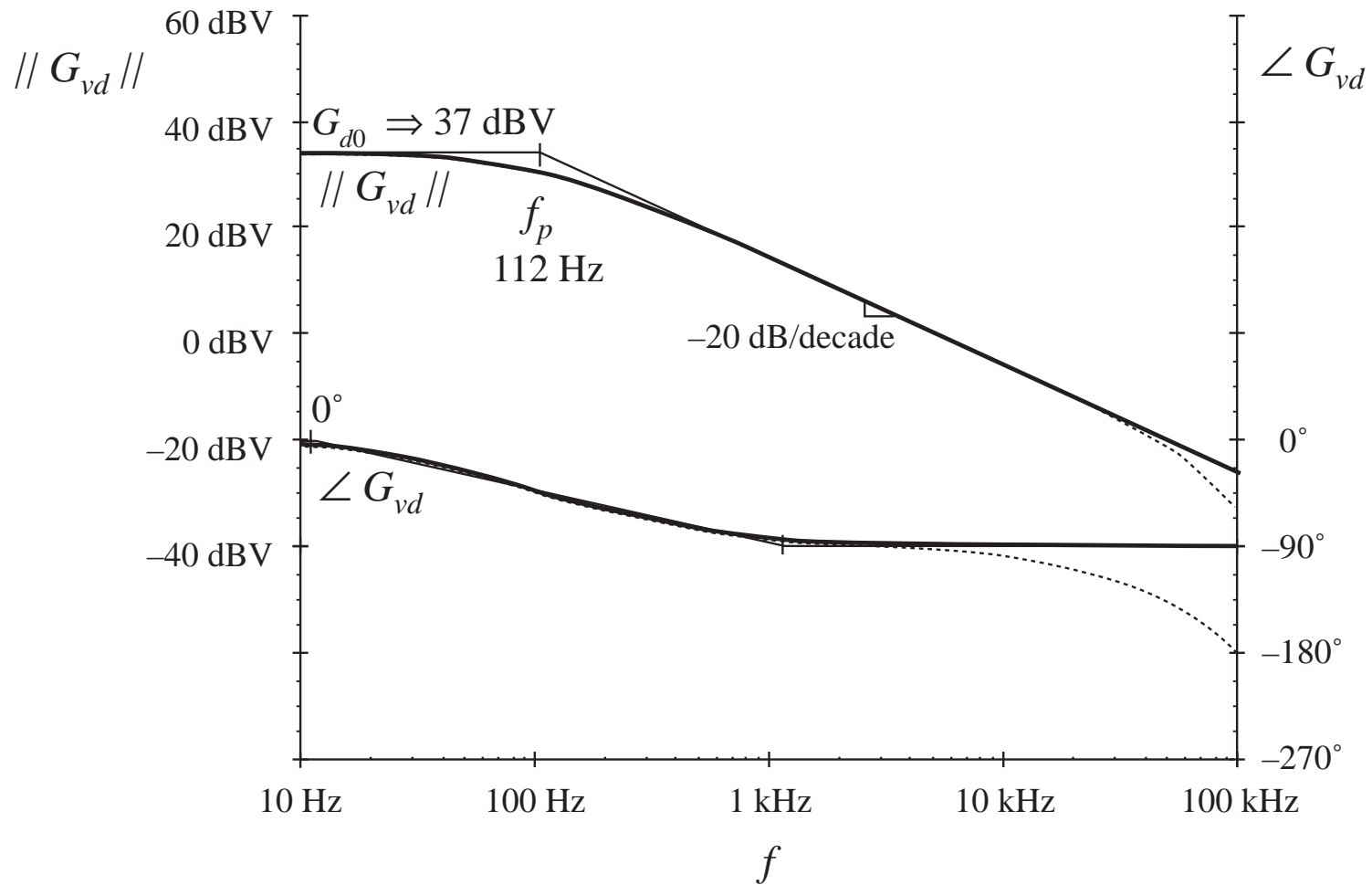
# Control-to-output transfer function, boost example



# A Note on High-Frequency Predictions of the Averaged Switch Model

---

- Observed high-frequency response due to inductor dynamics
- Averaged-switch model derivation used:

$$\langle v_L \rangle_{T_s} = 0$$

which is consistent with the fact that in DCM the inductor current starts from zero and ends at zero in each switching cycle, even in transients

- However, high-frequency dynamics due to the inductor indicates that the AC voltage across the inductor in the small-signal model is *not* zero
- *Model predictions at high frequencies are not quite correct*
- Corrected averaged models that *include the inductor* in the averaged switch model have recently been described

See References: [Sun et. al. PESC'99], [Ben-Yaakov et.al. PESC'94]


# Combined CCM/DCM Average Switch Model

---


## **Objective: a general large-signal averaged-switch model**

- Valid in CCM and DCM
- 5 terminals:
  - transistor port (2 terminals)
  - diode port (2 terminals)
  - duty ratio input (1 terminal)
- DCM/CCM boundary resolved within the model, based only on the terminal voltages/currents of the model
- Spice compatible

# Combined CCM/DCM Average Switch Model

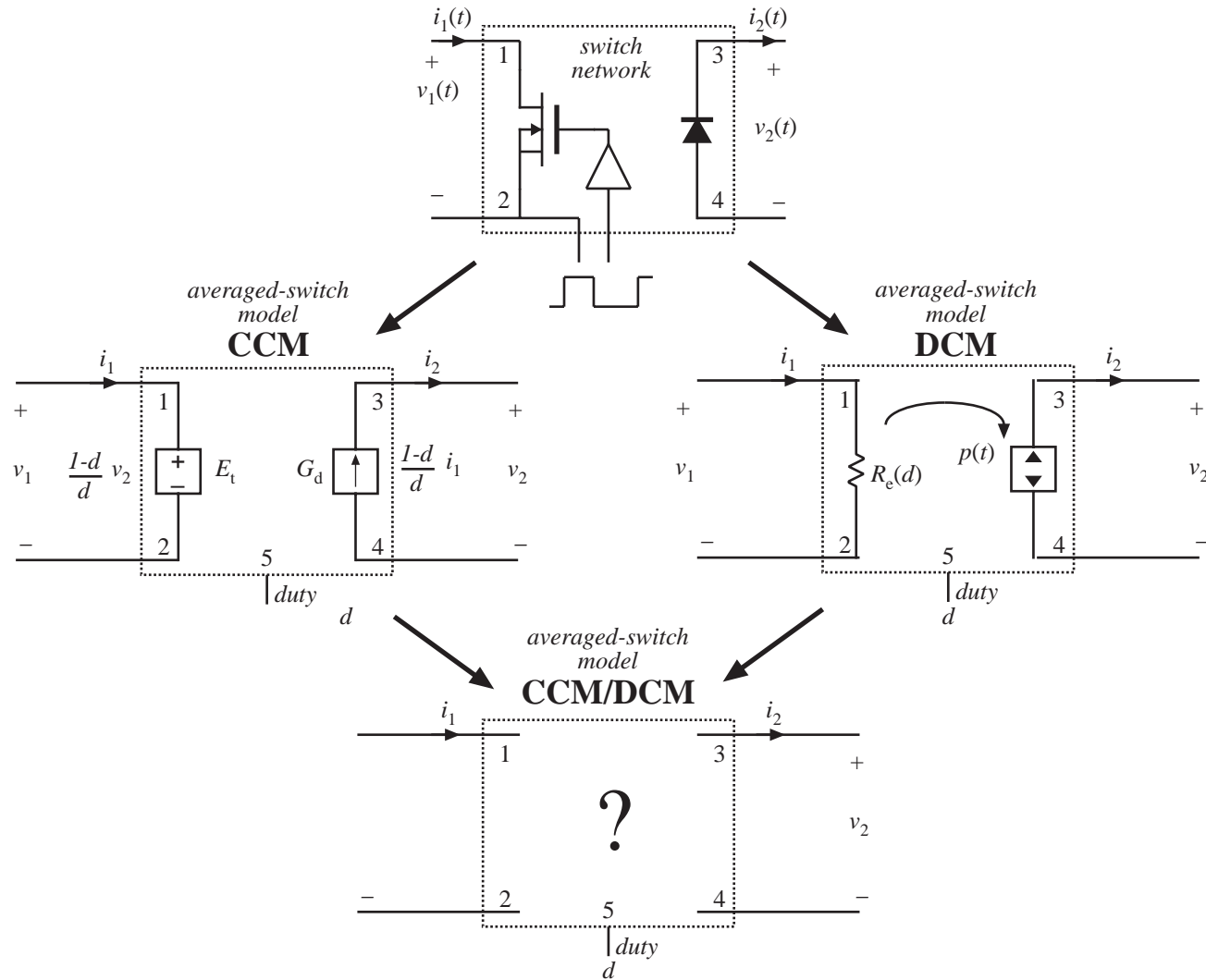

# Combined CCM/DCM Average Switch Model

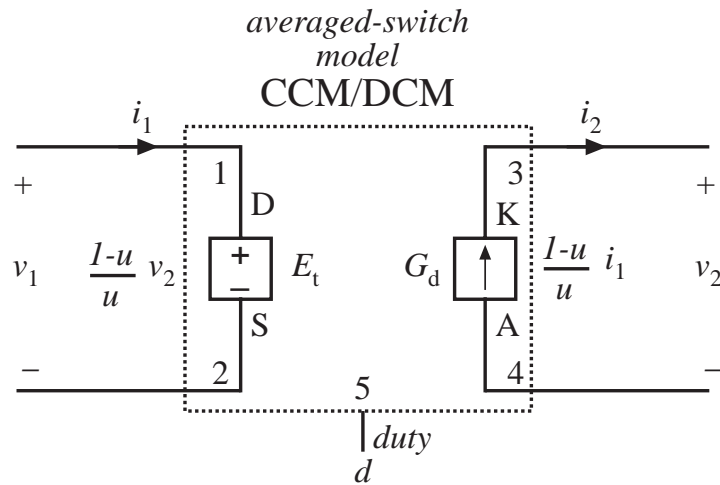

$$u = \begin{cases} d, & \text{CCM} \\ \frac{d^2}{d^2 + 2Lf_s \frac{i_1}{v_2}}, & \text{DCM} \end{cases}$$

CCM/DCM boundary:  $u = \text{MAX} \left( d, \frac{d^2}{d^2 + 2Lf_s \frac{i_1}{v_2}} \right)$

$u$  = equivalent switch duty ratio

# CCM/DCM Averaged-Switch Model

## PSpice Implementation: ccm-dcm1

---

```

* MODEL: ccm-dcm1
* Application: two-switch PWM converters, CCM or DCM
* Limitations: ideal switches, no transformer


* Parameters:
* L=equivalent inductance (relevant for DCM)
* fs=switching frequency

* Nodes: (same as in ccm1)

.subckt ccm-dcm1 1 2 3 4 5 params: L=1 fs=1E6
Et 1 2 value={({1-v(u)}*v(3,4)/v(u)}
Gd 4 3 value={({1-v(u)}*i(Et)/v(u)}
Ga 0 a value={MAX(i(Et),0)}
Va a b
Rdummy b 0 10
Eu u 0 table {MAX(v(5), v(5)*v(5)/(v(5)*v(5)+2*L*fs*i(Va)/v(3,4)))} (0 0) (1 1)
.ends

```
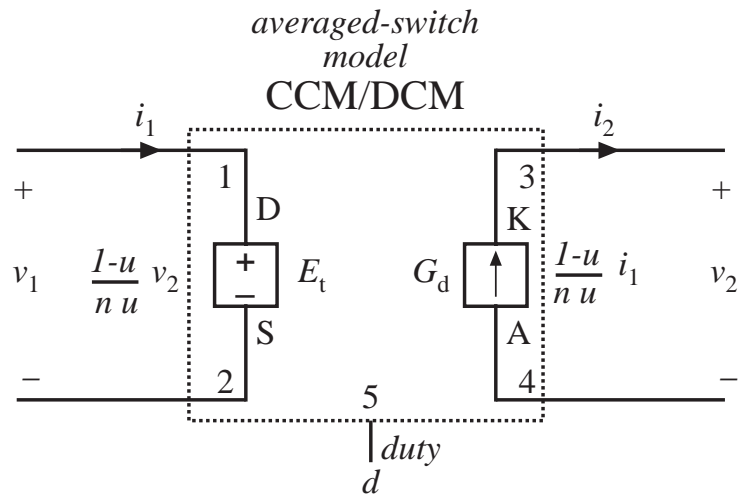
# Combined CCM/DCM Average Switch Model With Isolation Transformer



$$u = \begin{cases} d, & CCM \\ \frac{d^2}{d^2 + 2nLf_s \frac{i_1}{v_2}}, & DCM \end{cases}$$

$$CCM/DCM \text{ boundary: } u = \text{MAX} \left( d, \frac{d^2}{d^2 + 2nLf_s \frac{i_1}{v_2}} \right)$$

$u$  = equivalent switch duty ratio

# CCM/DCM Averaged-Switch Model

## PSpice Implementation: ccm-dcm2

---

- \* MODEL: ccm-dcm2
- \* Application: two-switch PWM converters, CCM or DCM with (possibly) transformer
- \* Limitations: ideal switches, no transformer

\*\*\*\*\*

### \* Parameters:

- \* L=equivalent inductance (relevant for DCM), referred to primary
- \* fs=switching frequency
- \* n=transformer turns ratio 1:n (primary:secondary)

\*\*\*\*\*

### \* Nodes: (same as in ccm1)

\*\*\*\*\*

```
.subckt ccm-dcm2 1 2 3 4 5 params: L=1 fs=1E6 n=1
```

```
Et 1 2 value={{(1-v(u))*v(3,4)/v(u)/n}}
```

```
Gd 4 3 value={{(1-v(u))*i(Et)/v(u)/n}}
```

```
Ga 0 a value={{MAX(i(Et),0)}}
```

```
Va a b
```

```
Rdummy b 0 10
```

```
Eu u 0 table {MAX(v(5), v(5)*v(5)/(v(5)*v(5)+2*L*n*fs*i(Va)/v(3,4)))} (0 0) (1 1)
```

```
.ends
```

\*\*\*\*\*


# CCM/DCM Model Applications

---

- **ccm-dcm1** (for non-isolated converters) and **ccm-dcm2** (for converters that may include isolation transformer) are general, large-signal averaged-switch models (PSpice subcircuits) valid for both CCM and DCM
- Can be applied to DC, AC, or Transient simulation of any two-switch PWM converter
- Limitations: ideal switches, no losses are modeled, but the model can be refined further to include conduction losses
- **Application examples:**
  - Comparison of Transient simulation results in a Sepic converter example using:
    - (1) switching circuit model
    - (2) ccm-dcm2 averaged switch model
  - AC simulation results for a flyback converter operating in CCM or DCM



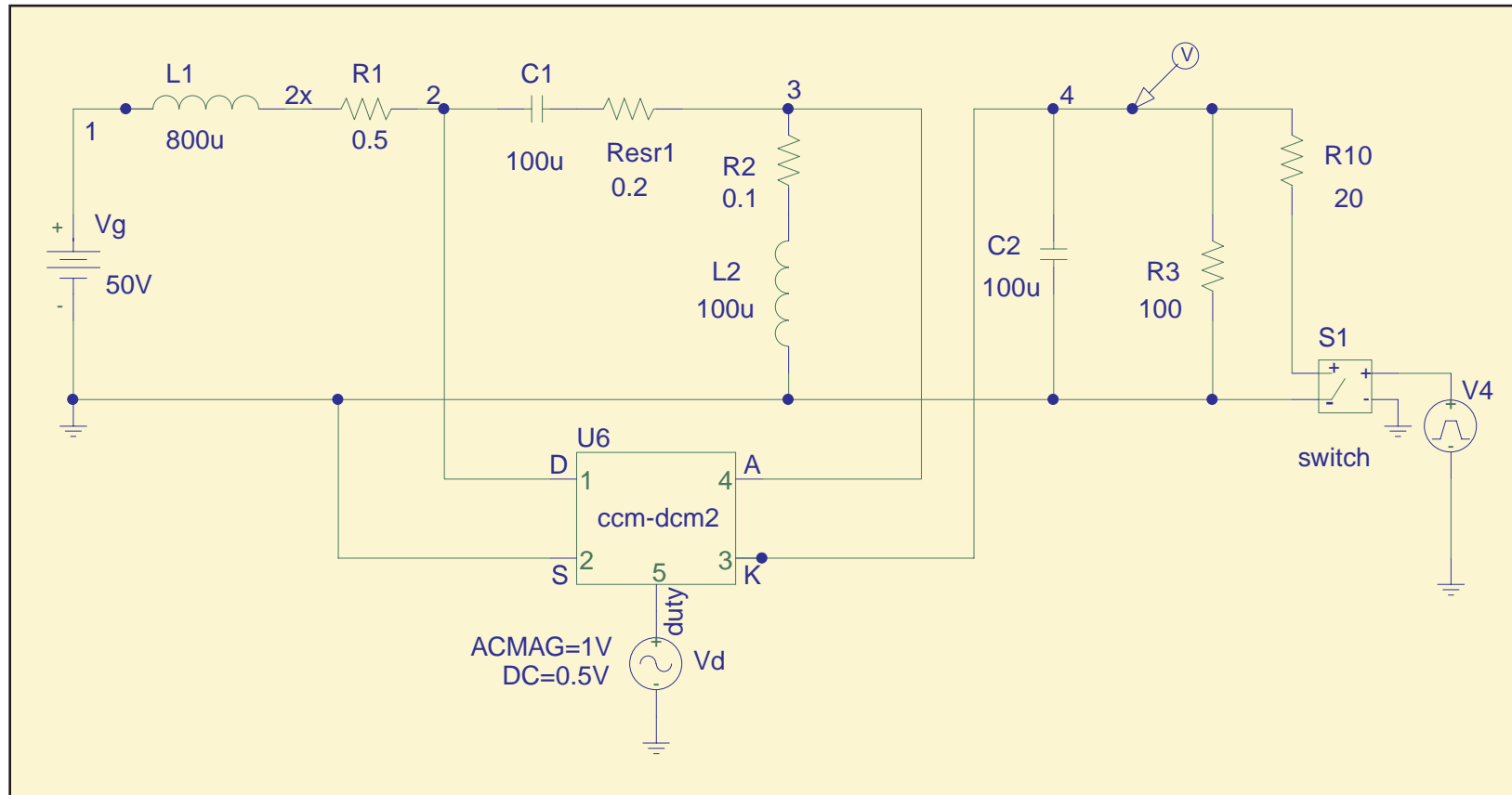
# Sepic converter example: averaged model using ccm-dcm2




Exactly the same PSpice circuit, except the MOSFET M1 and the diode D1 replaced by the **ccm-dcm2** subcircuit, and pulsating gate drive V3 replaced by a duty-ratio voltage source  $V_d$
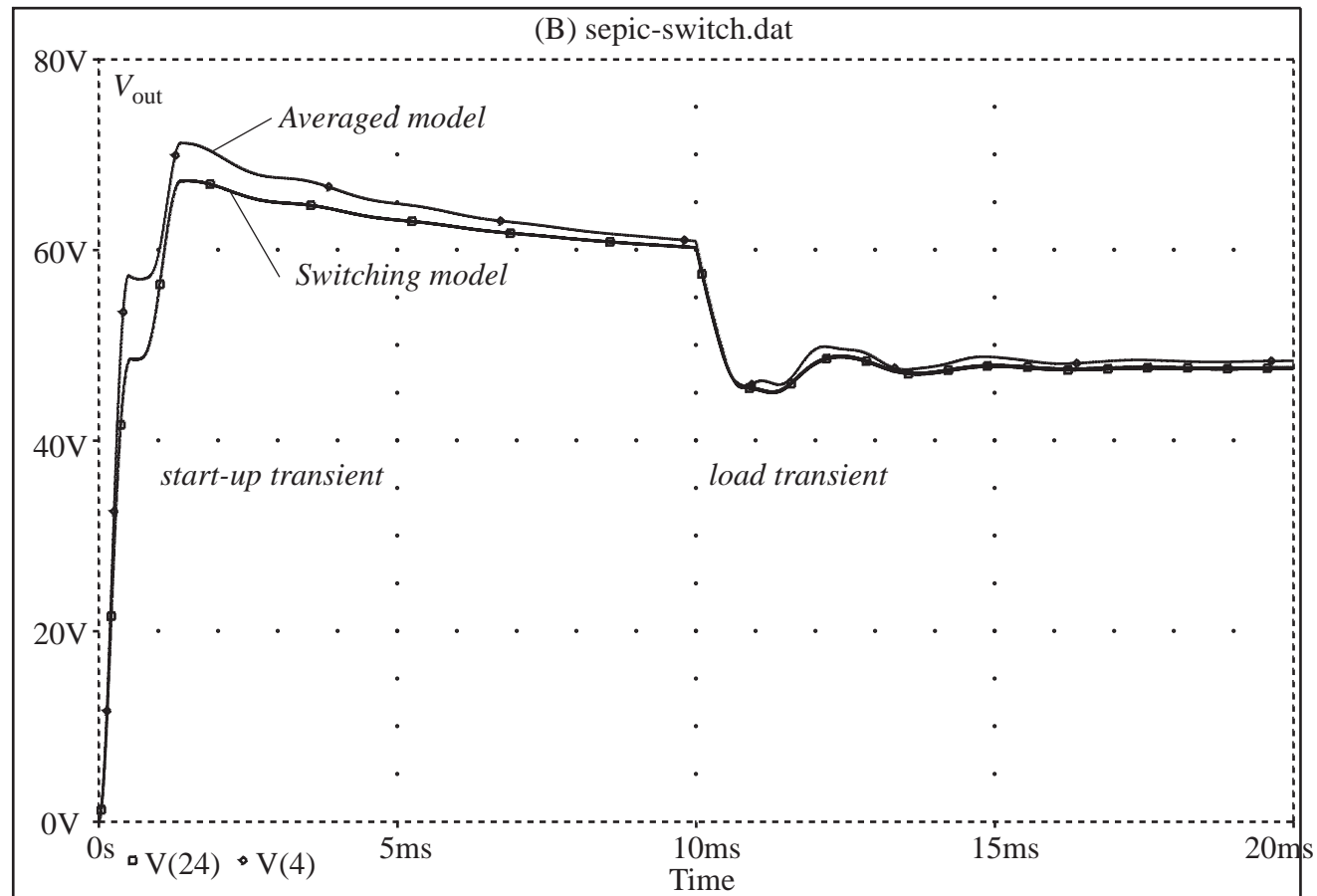
# Sepic converter example: averaged vs. switching model




Start-up and load transient response
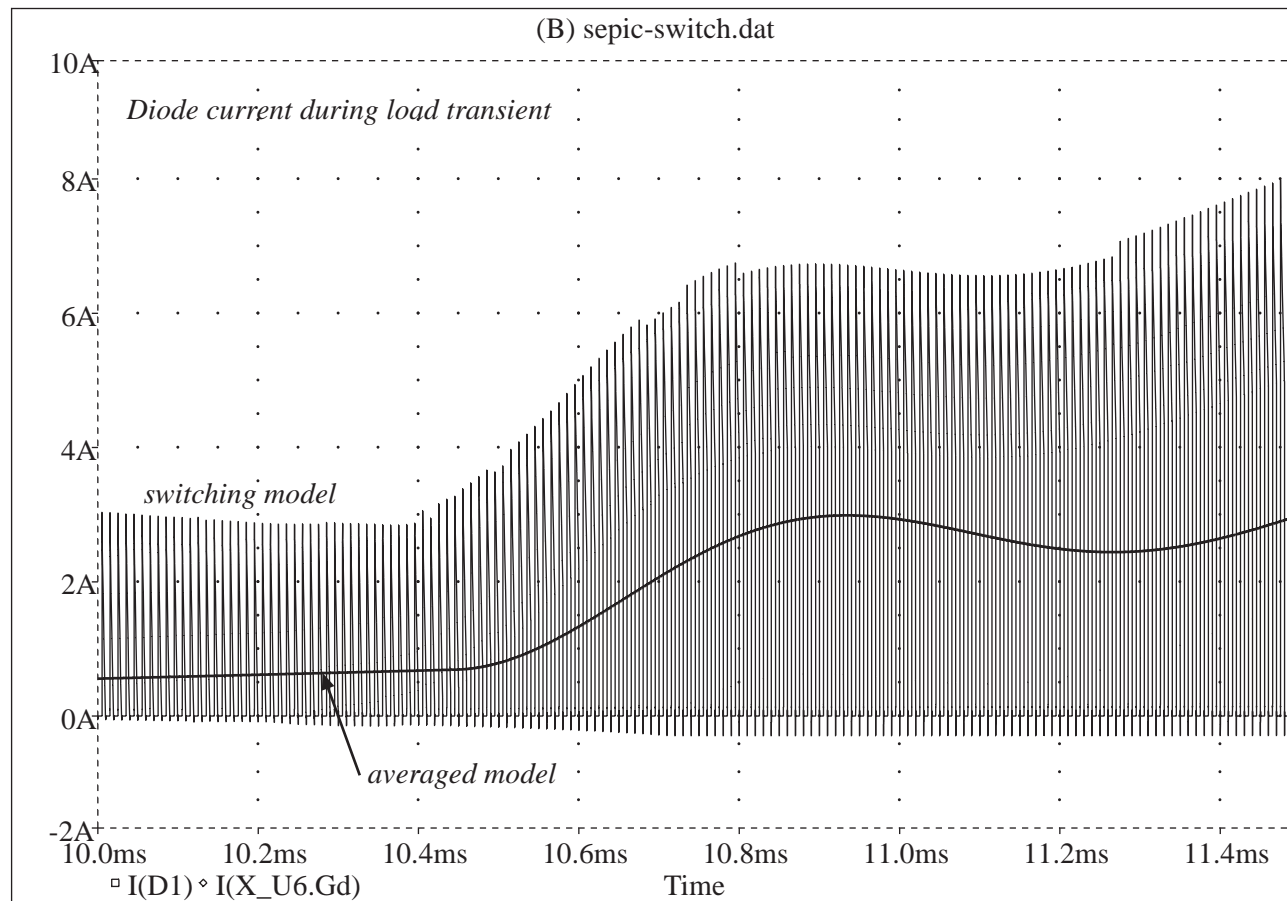
# Sepic converter example: averaged vs. switching model




Details of the diode current waveform around the load transient
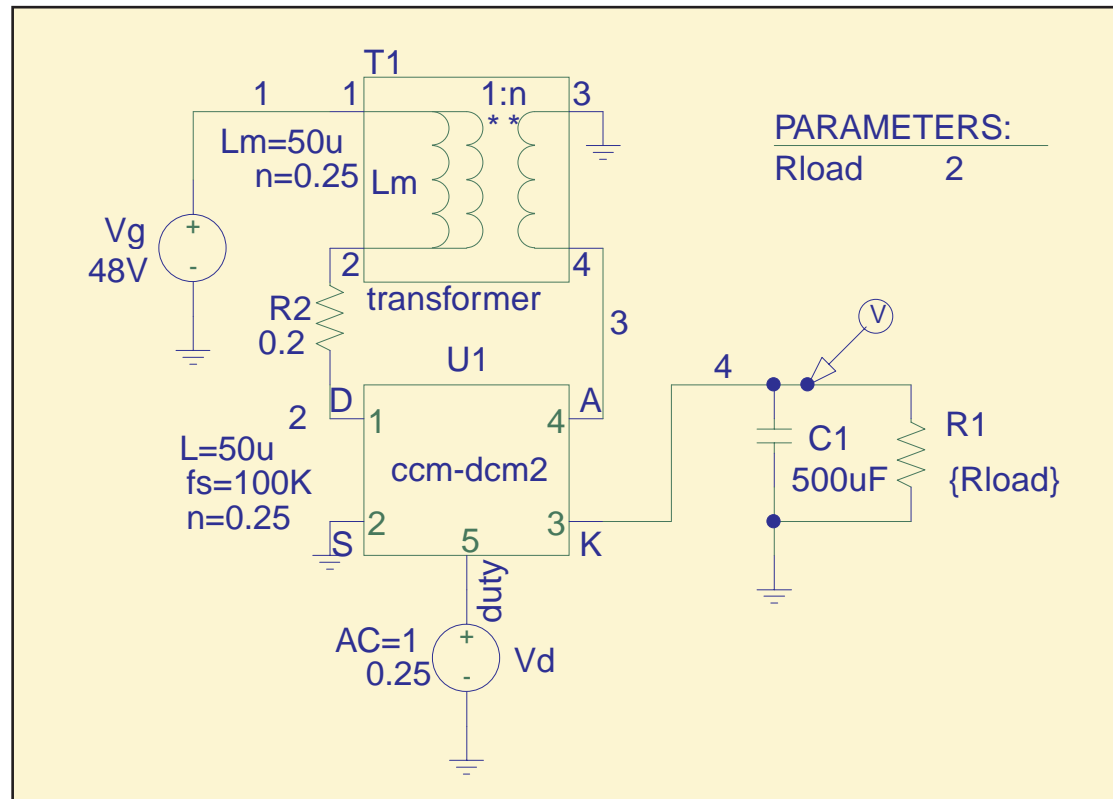
# Flyback converter example using ccm-dcm2 averaged-switch model




CCM for  $R_{load} = 1\ \Omega$ , DCM for  $R_{load} = 2\ \Omega$
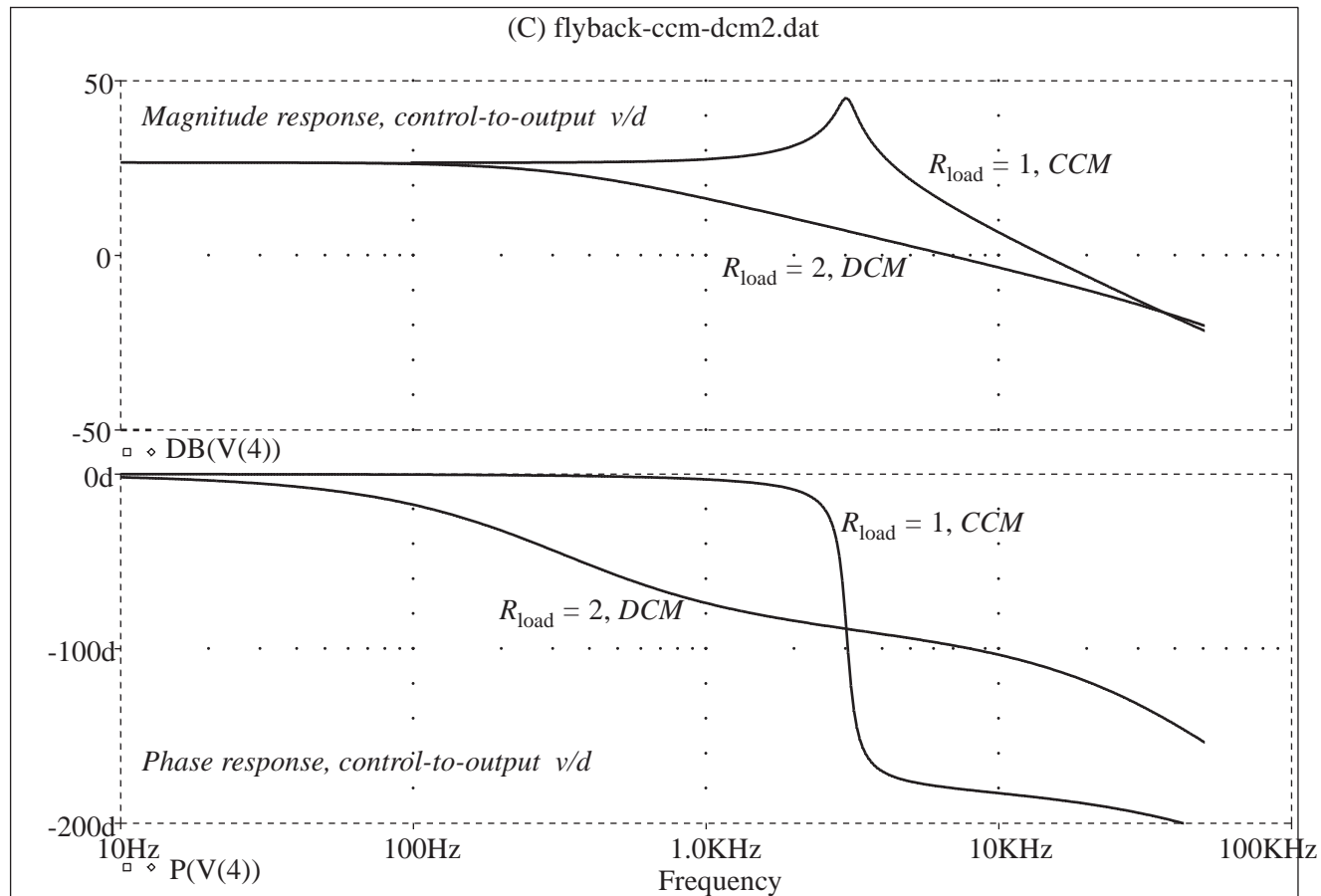
# Flyback converter example using ccm-dcm2 averaged-switch model



Frequency responses generated by PSpice AC analyses


# Other Converter Examples

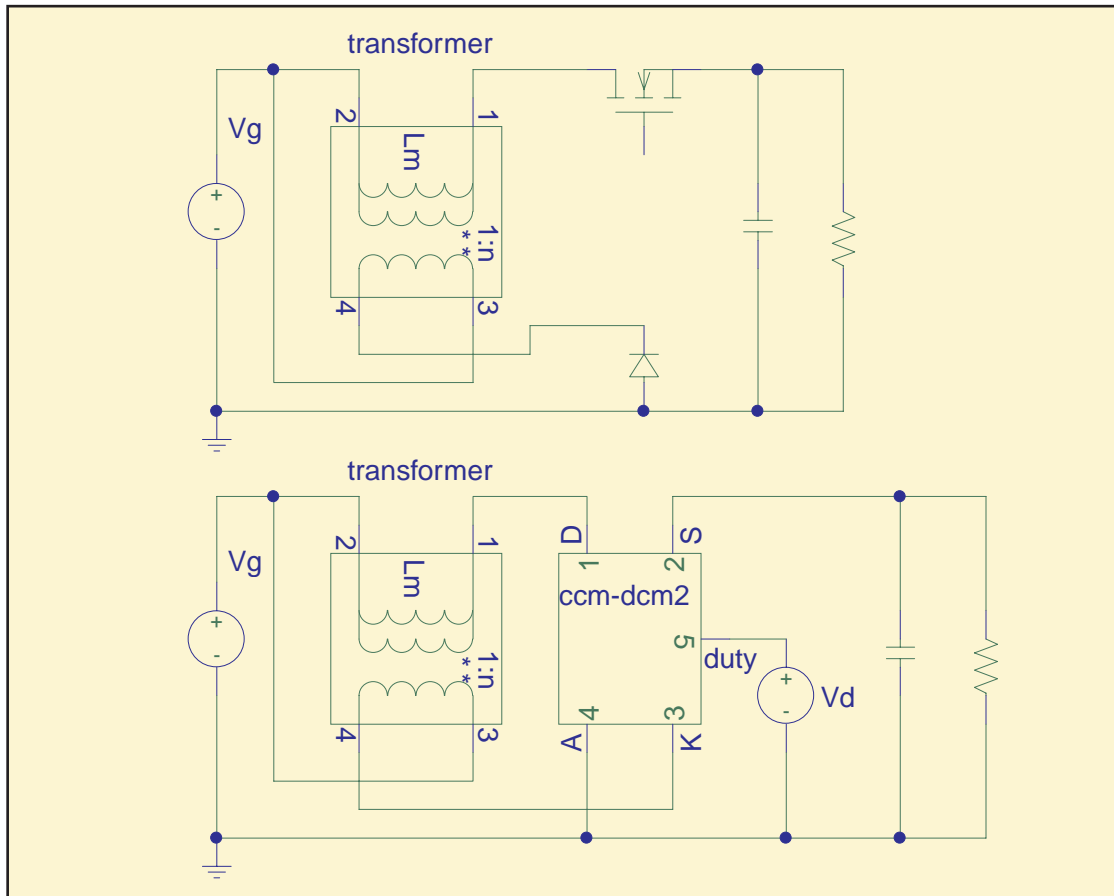

Watkins-Johnson converter

Pspice averaged circuit model  
using **ccm-dcm2**  
averaged-switch subcircuit

# Other Converter Examples

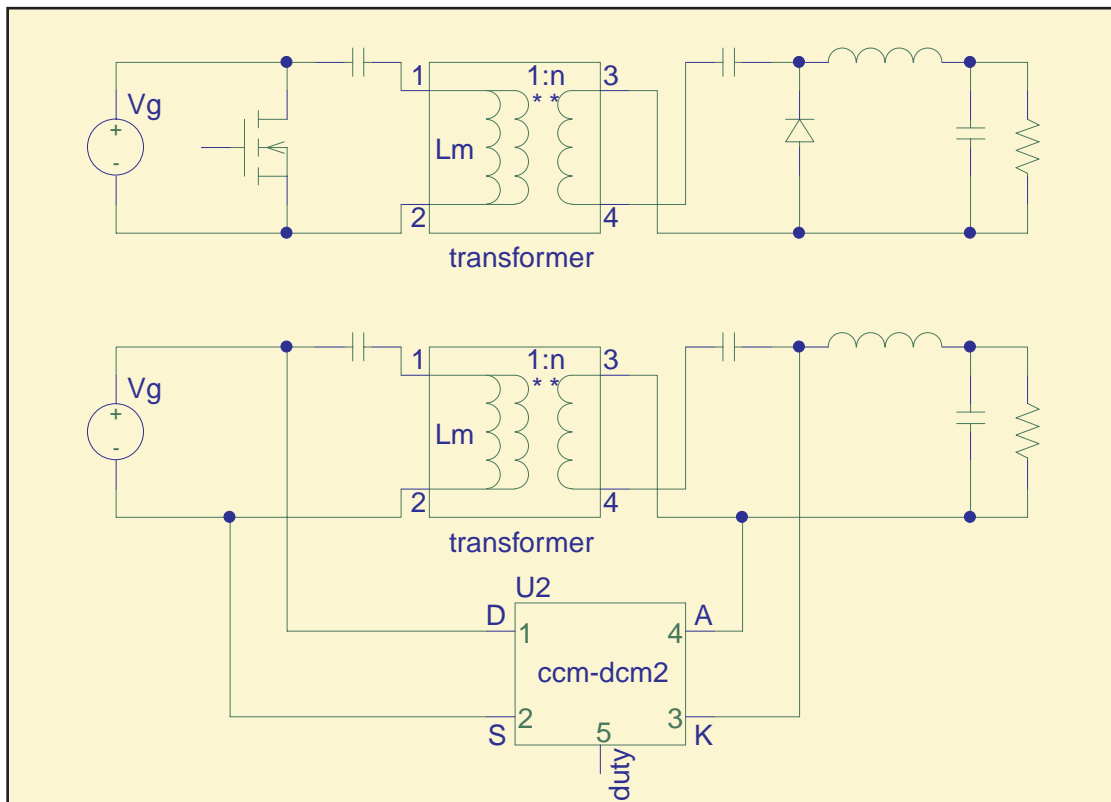

Cuk converter with  
isolation transformer


PSpice averaged circuit model  
using **ccm-dcm2**  
averaged-switch subcircuit

## 4. Averaged modeling of PWM converters with current-programmed mode (CPM) control


---

- **Averaged switch model for current-programmed mode (CPM) in CCM**
- **Steady-state and simple AC model in CCM**
- **Averaged switch model for CPM in DCM**
- **Steady-state and small-signal AC model in DCM**
- **Large-signal averaged CCM/DCM model for current-mode controller**
- **PSpice implementation of the averaged CPM controller model**
- **Application examples**
  - Buck converter with current-programmed mode controller

# Current-programmed control

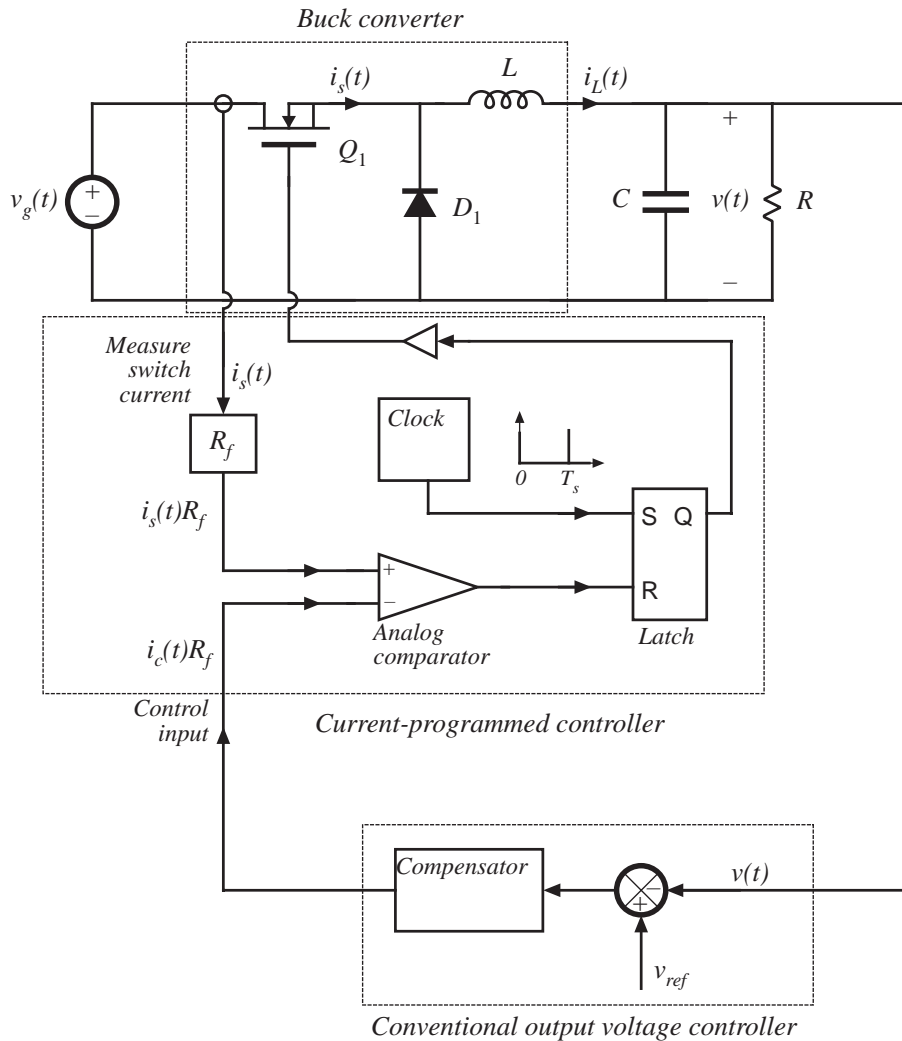

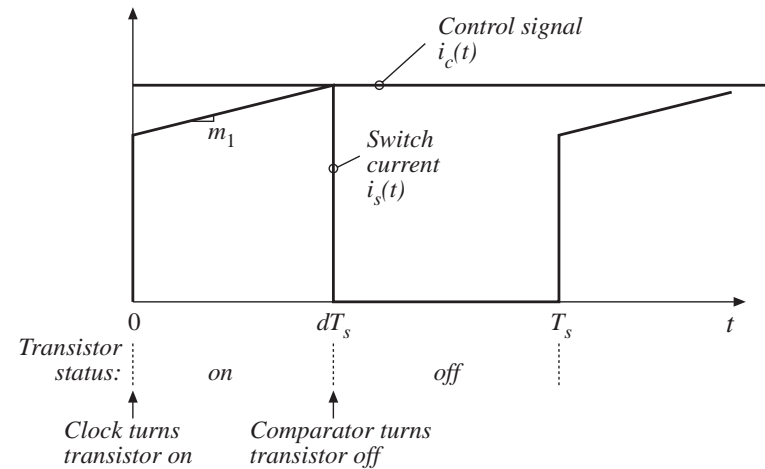The peak transistor current replaces the duty cycle as the converter control input.



# A simple approximation

---


$$\langle i_L(t) \rangle_{T_s} = i_c(t)$$

- Neglects switching ripple and artificial ramp (slope compensation)
- Yields physical insight and simple first-order model
- Accurate when converter operates well into CCM (so that switching ripple is small) and when the magnitude of the artificial ramp is not too large
- Well-accepted by practicing engineers
- Resulting small-signal relation:

$$\hat{i}_L(s) \approx \hat{i}_c(s)$$

# Averaged switch modeling with the simple approximation

*Buck converter example*

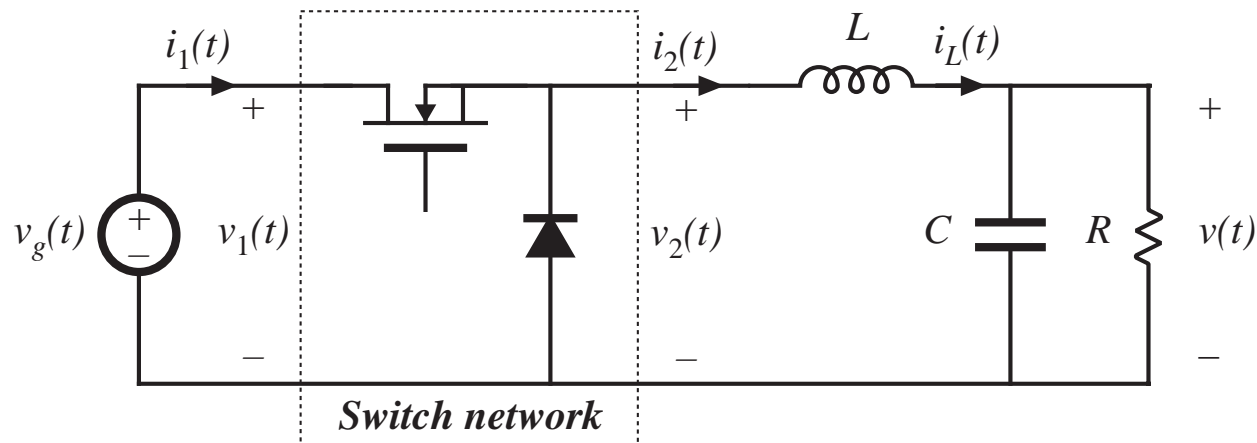

*Averaged terminal waveforms,  
CCM:*

$$\begin{aligned} \langle v_2(t) \rangle_{T_s} &= d(t) \langle v_1(t) \rangle_{T_s} \\ \langle i_1(t) \rangle_{T_s} &= d(t) \langle i_2(t) \rangle_{T_s} \end{aligned}$$

*The simple approximation:*

$$\langle i_2(t) \rangle_{T_s} \approx \langle i_c(t) \rangle_{T_s}$$

## CPM averaged switch equations

---

$$\begin{aligned}\langle v_2(t) \rangle_{T_s} &= d(t) \langle v_1(t) \rangle_{T_s} & \langle i_2(t) \rangle_{T_s} &\approx \langle i_c(t) \rangle_{T_s} \\ \langle i_1(t) \rangle_{T_s} &= d(t) \langle i_2(t) \rangle_{T_s}\end{aligned}$$

Eliminate duty cycle:


$$\langle i_1(t) \rangle_{T_s} = d(t) \langle i_c(t) \rangle_{T_s} = \frac{\langle v_2(t) \rangle_{T_s}}{\langle v_1(t) \rangle_{T_s}} \langle i_c(t) \rangle_{T_s}$$

$$\langle i_1(t) \rangle_{T_s} \langle v_1(t) \rangle_{T_s} = \langle i_c(t) \rangle_{T_s} \langle v_2(t) \rangle_{T_s} = \langle p(t) \rangle_{T_s}$$

So:


- Output port is a current source
- Input port is a dependent power sink

# CPM averaged switch model

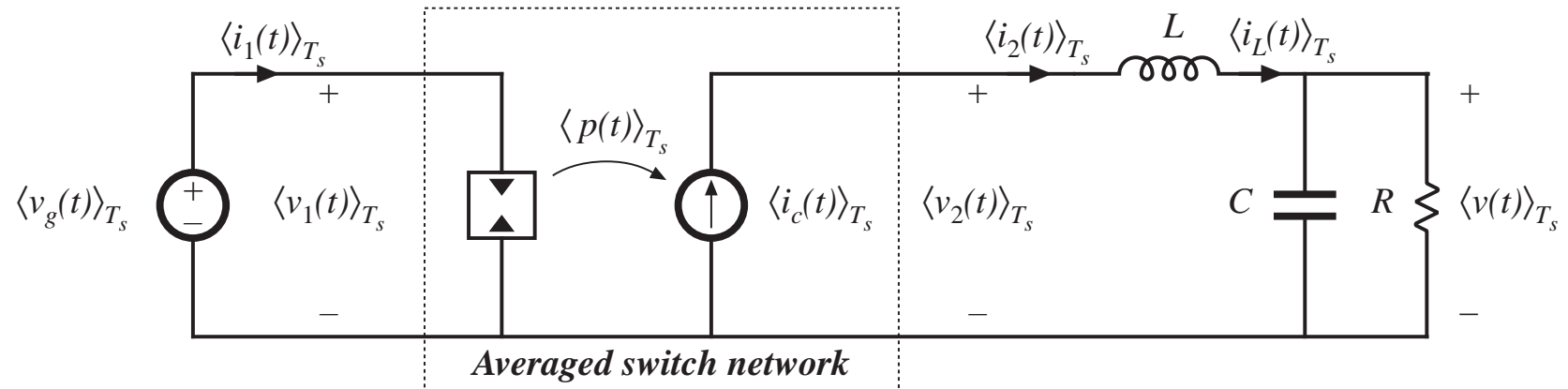


# Results for other converters

*Boost*

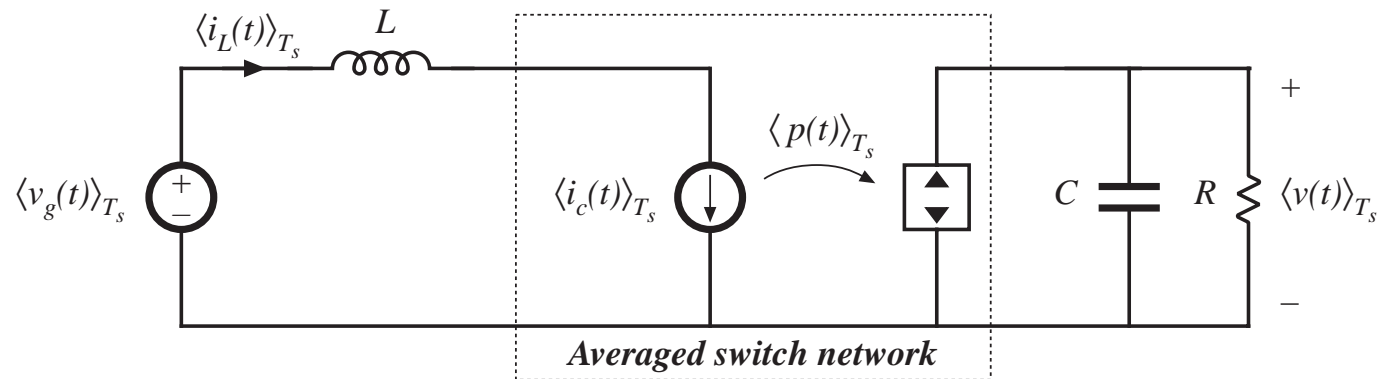

*Buck-boost*

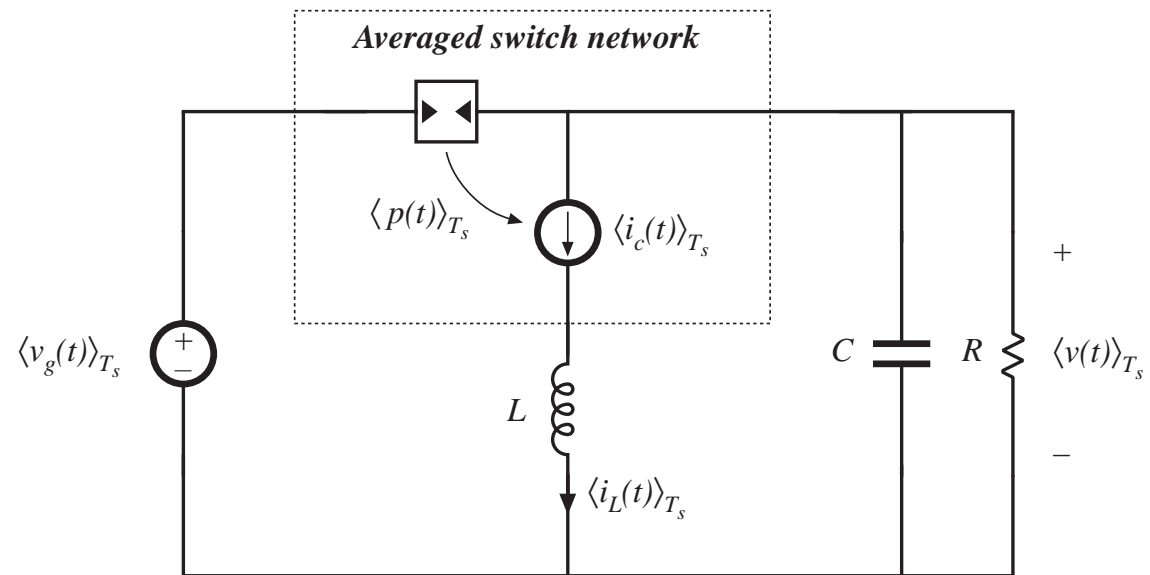

# Perturbation and linearization to construct small-signal model, CCM

---

Let

$$\langle v_1(t) \rangle_{T_s} = V_1 + \hat{v}_1(t)$$

$$\langle i_1(t) \rangle_{T_s} = I_1 + \hat{i}_1(t)$$

$$\langle v_2(t) \rangle_{T_s} = V_2 + \hat{v}_2(t)$$

$$\langle i_2(t) \rangle_{T_s} = I_2 + \hat{i}_2(t)$$

$$\langle i_c(t) \rangle_{T_s} = I_c + \hat{i}_c(t)$$

Resulting input port equation:

$$(V_1 + \hat{v}_1(t)) (I_1 + \hat{i}_1(t)) = (I_c + \hat{i}_c(t)) (V_2 + \hat{v}_2(t))$$

Small-signal result:


$$\hat{i}_1(t) = \hat{i}_c(t) \frac{V_2}{V_1} + \hat{v}_2(t) \frac{I_c}{V_1} - \hat{v}_1(t) \frac{I_1}{V_1}$$

Output port equation:

$$\hat{i}_2 = \hat{i}_c$$


# Resulting small-signal model

## Buck example

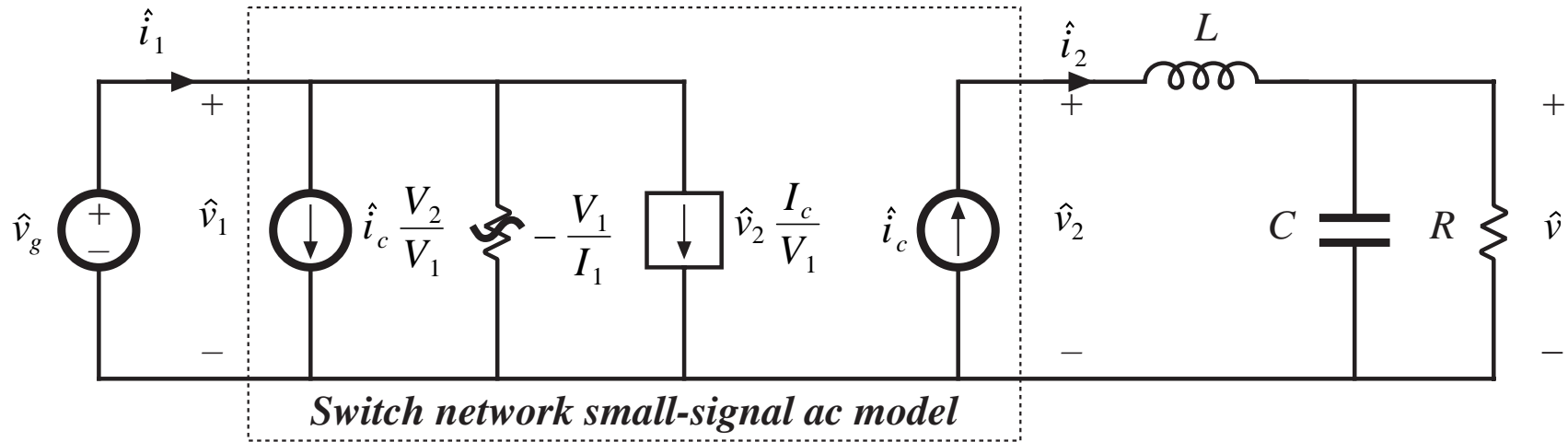

$$\hat{i}_1(t) = \hat{i}_c(t) \frac{V_2}{V_1} + \hat{v}_2(t) \frac{I_c}{V_1} - \hat{v}_1(t) \frac{I_1}{V_1}$$
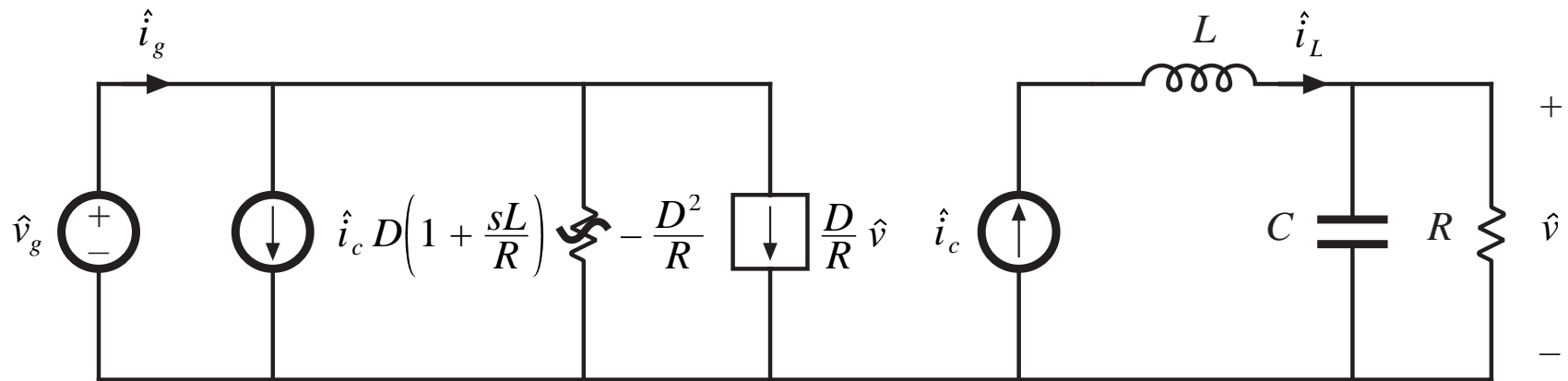
# Predicted transfer functions of the CPM buck converter




$$G_{vc}(s) = \left. \frac{\hat{v}(s)}{\hat{i}_c(s)} \right|_{\hat{v}_g=0} = \left( R \parallel \frac{1}{sC} \right)$$

$$G_{vg}(s) = \left. \frac{\hat{v}(s)}{\hat{v}_g(s)} \right|_{\hat{i}_c=0} = 0$$

# Table of results

## basic converters

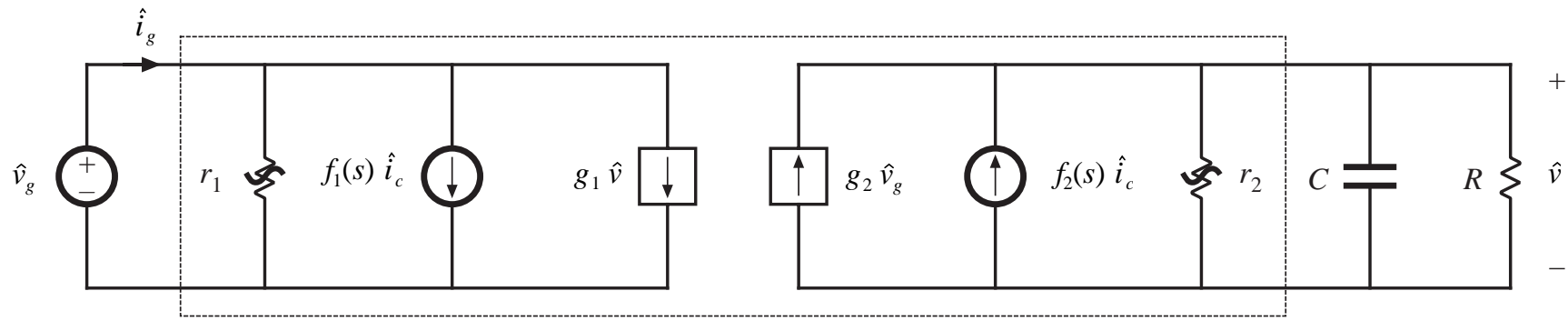



| Converter  | $g_1$          | $f_1$                                 | $r_1$              | $g_2$              | $f_2$                                       | $r_2$         |
|------------|----------------|---------------------------------------|--------------------|--------------------|---------------------------------------------|---------------|
| Buck       | $\frac{D}{R}$  | $D \left( 1 + \frac{sL}{R} \right)$   | $-\frac{R}{D^2}$   | 0                  | 1                                           | $\infty$      |
| Boost      | 0              | 1                                     | $\infty$           | $\frac{1}{D'R}$    | $D' \left( 1 - \frac{sL}{D'^2 R} \right)$   | $R$           |
| Buck-boost | $-\frac{D}{R}$ | $D \left( 1 + \frac{sL}{D'R} \right)$ | $-\frac{D'R}{D^2}$ | $-\frac{D^2}{D'R}$ | $-D' \left( 1 - \frac{sDL}{D'^2 R} \right)$ | $\frac{R}{D}$ |

# Discontinuous conduction mode in current-programmed converters

---

- Again, use averaged switch modeling approach
- Result: simply replace
  - Transistor by power sink
  - Diode by power source
- Inductor dynamics appear at high frequency, near to or greater than the switching frequency
- Small-signal transfer functions contain a single low frequency pole
- DCM CPM boost and buck-boost are stable without artificial ramp
- DCM CPM buck without artificial ramp is stable for  $D < 2/3$ . A small artificial ramp  $m_a \geq 0.086m_2$  leads to stability for all  $D$ .

# DCM CPM buck-boost example

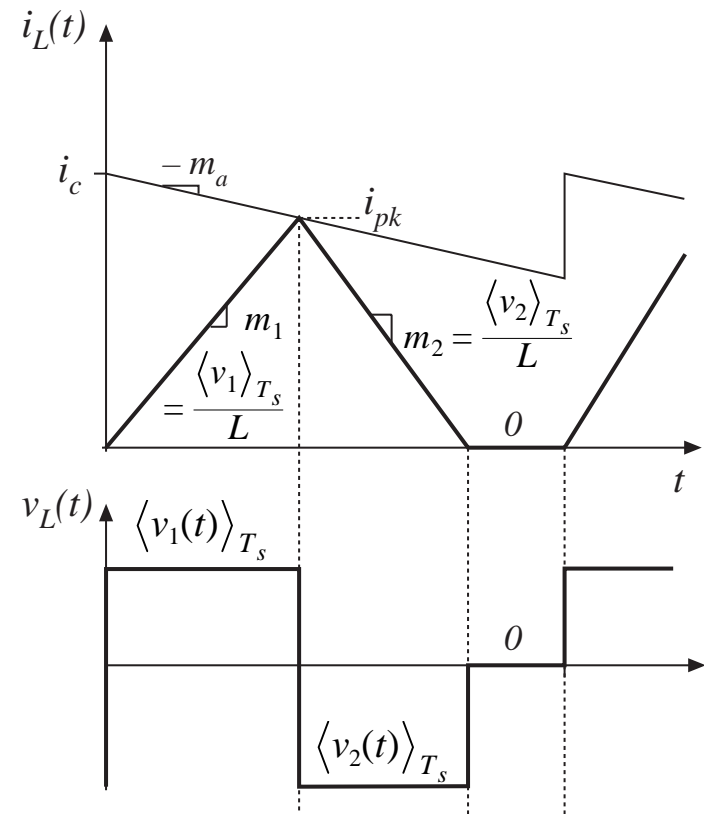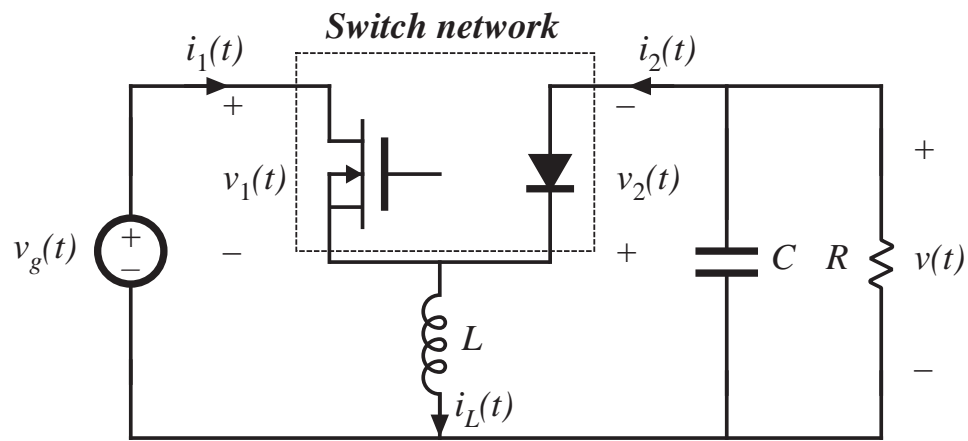


# Analysis

$$i_{pk} = m_1 d_1 T_s$$

$$m_1 = \frac{\langle v_1(t) \rangle_{T_s}}{L}$$

$$\begin{aligned} i_c &= i_{pk} + m_a d_1 T_s \\ &= (m_1 + m_a) d_1 T_s \end{aligned}$$
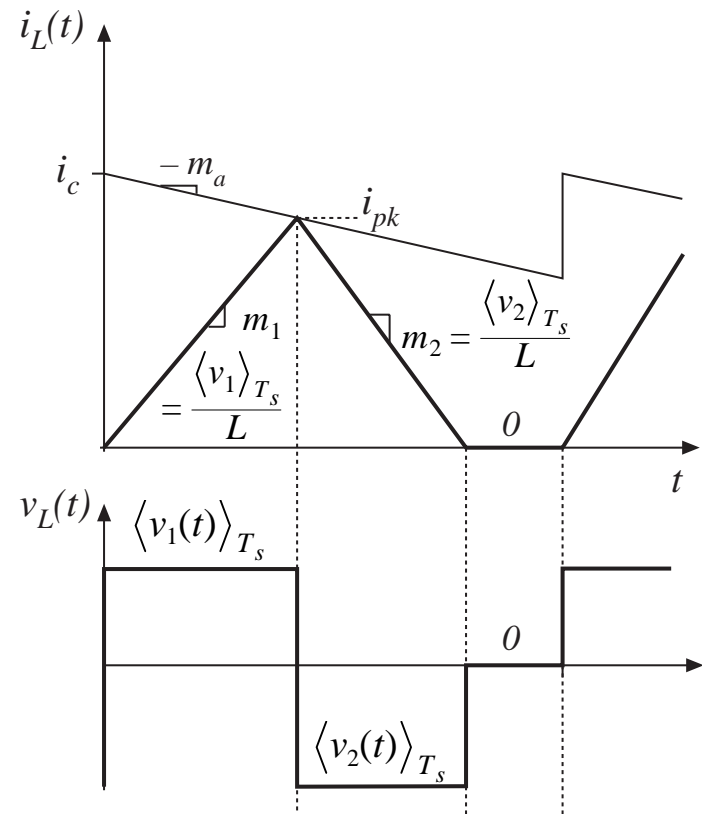
$$d_1(t) = \frac{i_c(t)}{(m_1 + m_a) T_s}$$



# Averaged switch input port equation


$$\langle i_1(t) \rangle_{T_s} = \frac{1}{T_s} \int_t^{t+T_s} i_1(\tau) d\tau = \frac{q_1}{T_s}$$

$$\langle i_1(t) \rangle_{T_s} = \frac{1}{2} i_{pk}(t) d_1(t)$$

$$\langle i_1(t) \rangle_{T_s} = \frac{1}{2} m_1 d_1^2(t) T_s$$

$$\langle i_1(t) \rangle_{T_s} = \frac{\frac{1}{2} L i_c^2 f_s}{\langle v_1(t) \rangle_{T_s} \left( 1 + \frac{m_a}{m_1} \right)^2}$$
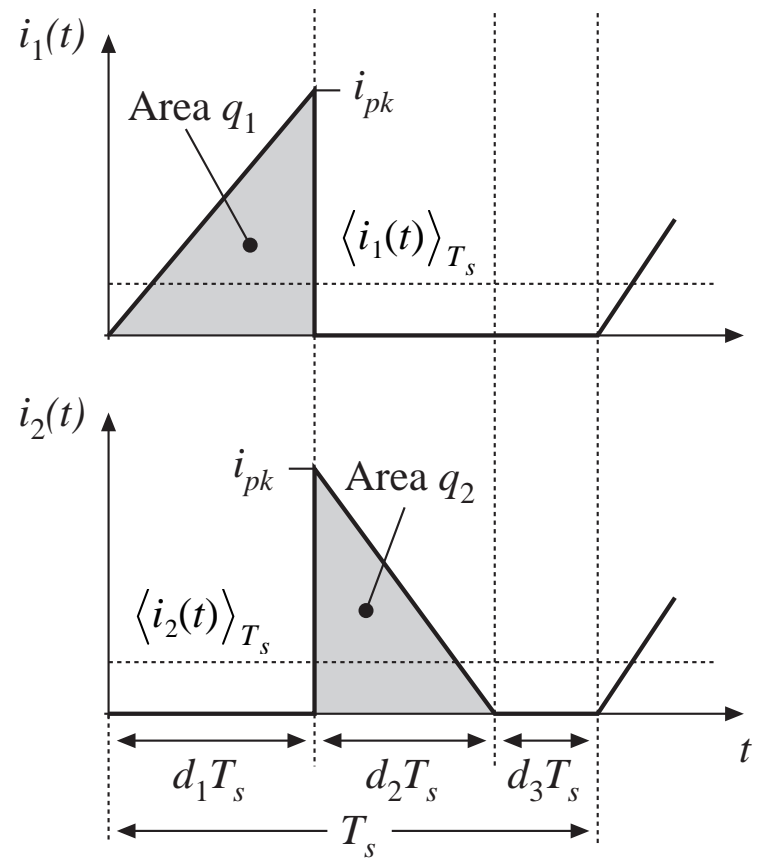
$$\langle i_1(t) \rangle_{T_s} \langle v_1(t) \rangle_{T_s} = \frac{\frac{1}{2} L i_c^2 f_s}{\left( 1 + \frac{m_a}{m_1} \right)^2} = \langle p(t) \rangle_{T_s}$$



## Discussion: switch network input port

---

- Averaged transistor waveforms obey a power sink characteristic
- During first subinterval, energy is transferred from input voltage source, through transistor, to inductor, equal to

$$W = \frac{1}{2} Li_{pk}^2$$

This energy transfer process accounts for power flow equal to

$$\langle p(t) \rangle_{T_s} = W f_s = \frac{1}{2} Li_{pk}^2 f_s$$

which is equal to the power sink expression of the previous slide.

# Averaged switch output port equation


$$\langle i_2(t) \rangle_{T_s} = \frac{1}{T_s} \int_t^{t+T_s} i_2(\tau) d\tau = \frac{q_2}{T_s}$$

$$q_2 = \frac{1}{2} i_{pk} d_2 T_s$$

$$d_2(t) = d_1(t) \frac{\langle v_1(t) \rangle_{T_s}}{\langle v_2(t) \rangle_{T_s}}$$

$$\langle i_2(t) \rangle_{T_s} = \frac{\langle p(t) \rangle_{T_s}}{\langle v_2(t) \rangle_{T_s}}$$
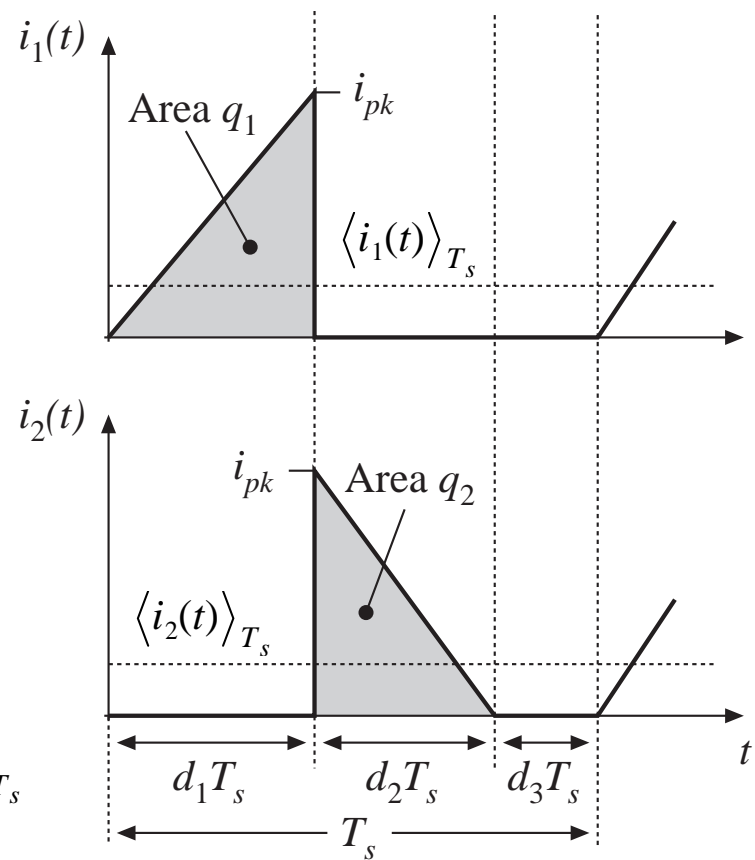
$$\langle i_2(t) \rangle_{T_s} \langle v_2(t) \rangle_{T_s} = \frac{\frac{1}{2} L i_c^2(t) f_s}{\left(1 + \frac{m_a}{m_1}\right)^2} = \langle p(t) \rangle_{T_s}$$




## Discussion: switch network output port


---

- Averaged diode waveforms obey a power sink characteristic
- During second subinterval, all stored energy in inductor is transferred, through diode, to load
- Hence, in averaged model, diode becomes a power source, having value equal to the power consumed by the transistor power sink element

# Averaged equivalent circuit

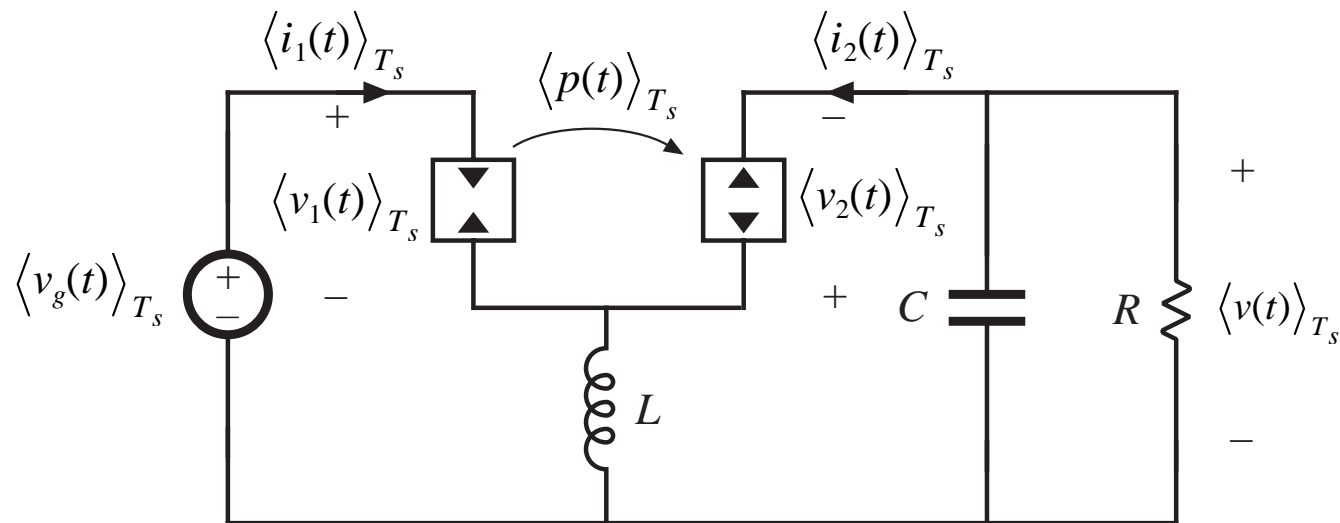

# Steady state model: DCM CPM buck-boost

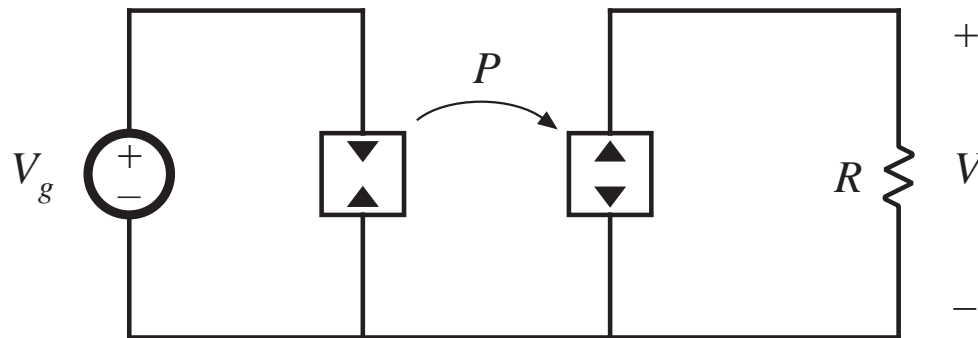

*Solution*

$$\frac{V^2}{R} = P$$


$$V = \sqrt{PR} = I_c \sqrt{\frac{RLf_s}{2 \left(1 + \frac{M_a}{M_1}\right)^2}}$$

$$P = \frac{\frac{1}{2} LI_c^2(t) f_s}{\left(1 + \frac{M_a}{M_1}\right)^2}$$


for a resistive load

# Models of buck and boost

*Buck*

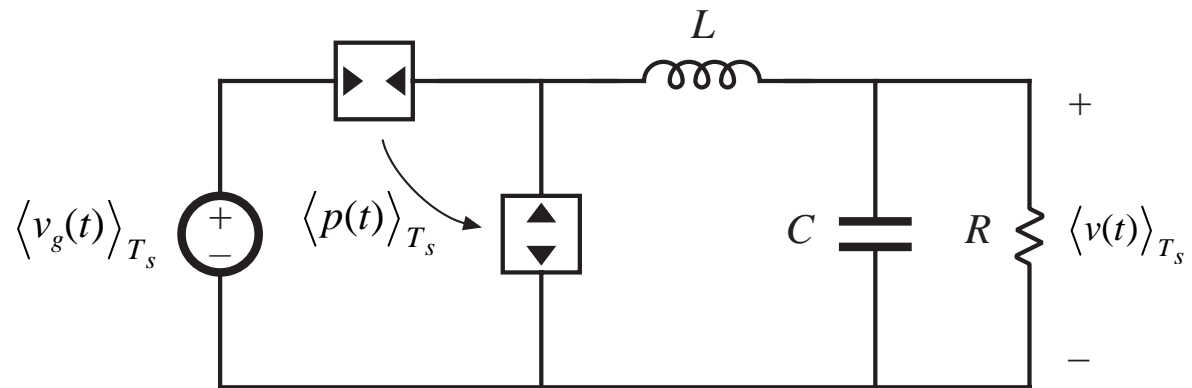

*Boost*

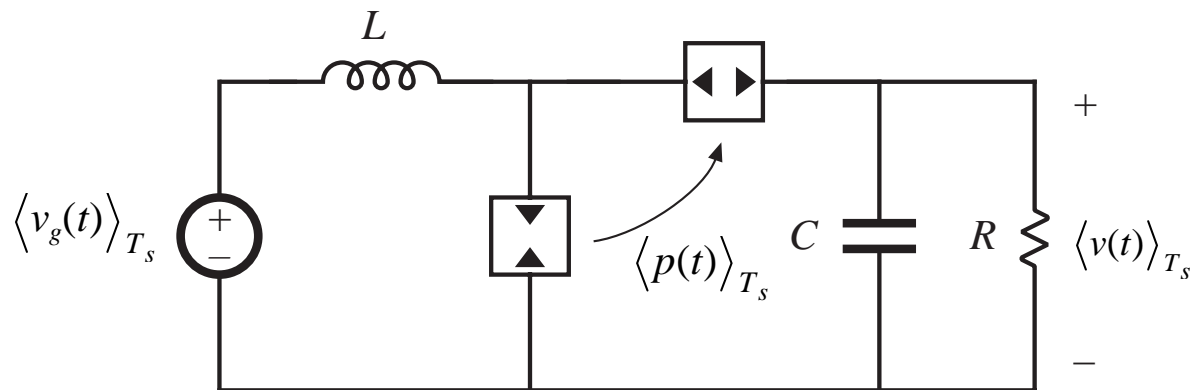

# Summary of steady-state DCM CPM characteristics


| Converter  | $M$                                               | $I_{crit}$                                                  | Stability range<br>when $m_a = 0$ |
|------------|---------------------------------------------------|-------------------------------------------------------------|-----------------------------------|
| Buck       | $\frac{P_{load} - P}{P_{load}}$                   | $\frac{1}{2} (I_c - M m_a T_s)$                             | $0 \leq M < \frac{2}{3}$          |
| Boost      | $\frac{P_{load}}{P_{load} - P}$                   | $\frac{\left( I_c - \frac{M-1}{M} m_a T_s \right)}{2M}$     | $0 \leq D \leq 1$                 |
| Buck-boost | Depends on load characteristic:<br>$P_{load} = P$ | $\frac{\left( I_c - \frac{M}{M-1} m_a T_s \right)}{2(M-1)}$ | $0 \leq D \leq 1$                 |

$$|I| > |I_{crit}| \quad \text{for CCM}$$


$$|I| < |I_{crit}| \quad \text{for DCM}$$

# Linearized small-signal models


*Buck*

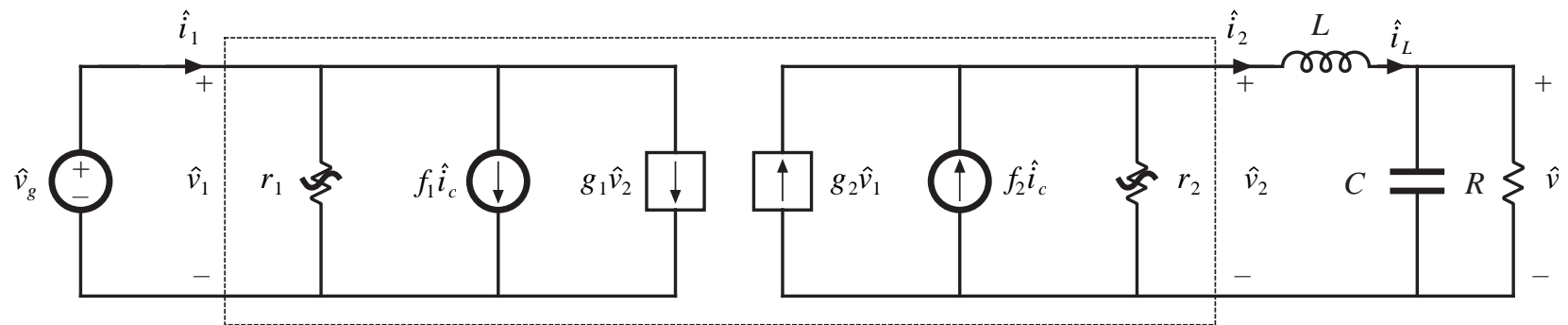

*Boost*

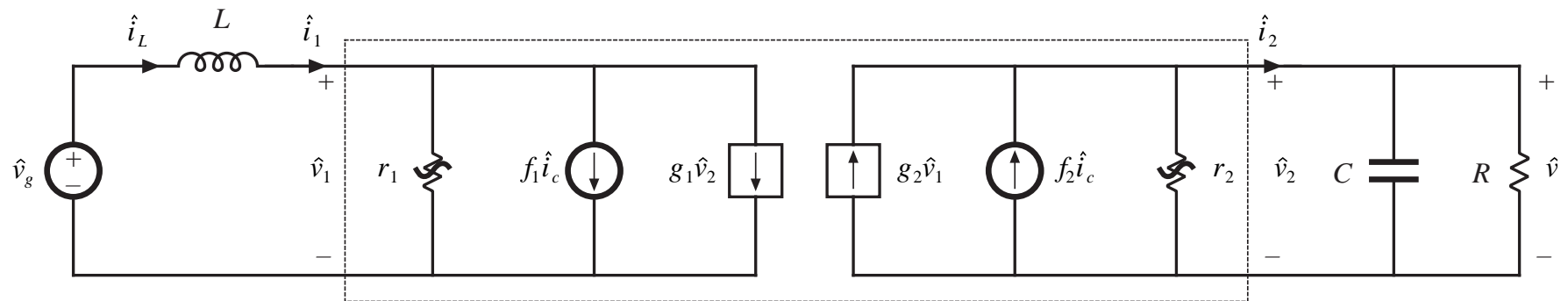
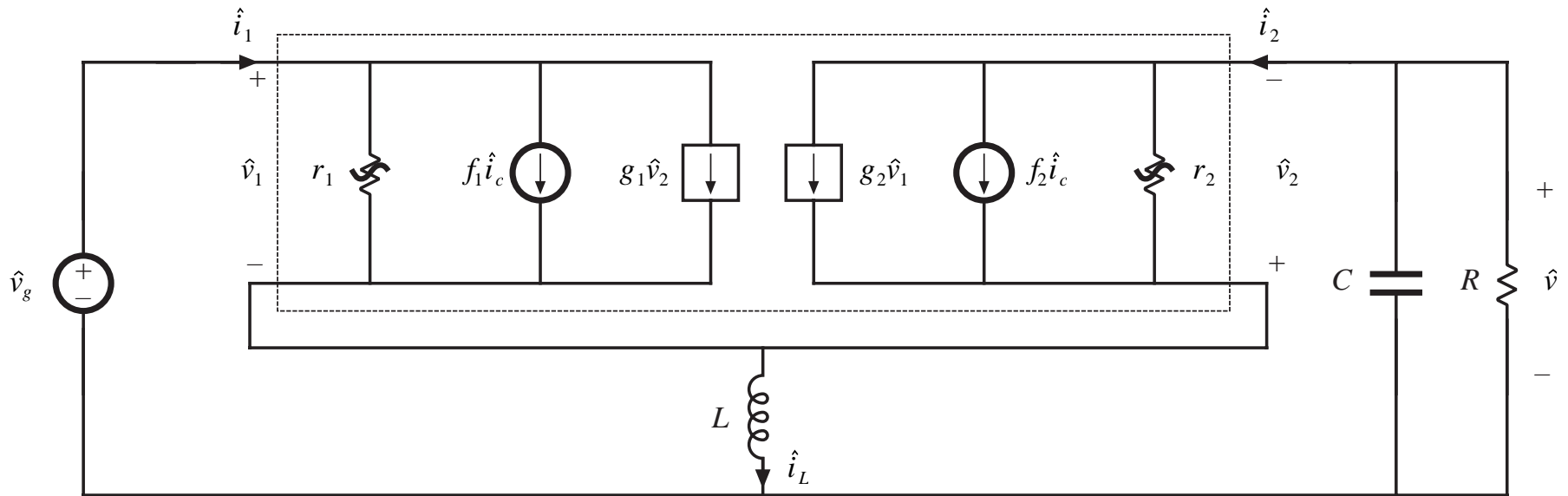
# Linearized small-signal models: Buck-boost



# DCM CPM small-signal parameters: input port


| Converter  | $g_1$                                                                                                                      | $f_1$               | $r_1$                                                                                                             |
|------------|----------------------------------------------------------------------------------------------------------------------------|---------------------|-------------------------------------------------------------------------------------------------------------------|
| Buck       | $\frac{1}{R} \left( \frac{M^2}{1-M} \right) \frac{\left( 1 - \frac{m_a}{m_1} \right)}{\left( 1 + \frac{m_a}{m_1} \right)}$ | $2 \frac{I_1}{I_c}$ | $-R \left( \frac{1-M}{M^2} \right) \frac{\left( 1 + \frac{m_a}{m_1} \right)}{\left( 1 - \frac{m_a}{m_1} \right)}$ |
| Boost      | $-\frac{1}{R} \left( \frac{M}{M-1} \right)$                                                                                | $2 \frac{I}{I_c}$   | $\frac{R}{M^2 \left( \frac{2-M}{M-1} + \frac{2 \frac{m_a}{m_1}}{1 + \frac{m_a}{m_1}} \right)}$                    |
| Buck-boost | 0                                                                                                                          | $2 \frac{I_1}{I_c}$ | $\frac{-R}{M^2} \frac{\left( 1 + \frac{m_a}{m_1} \right)}{\left( 1 - \frac{m_a}{m_1} \right)}$                    |

# DCM CPM small-signal parameters: output port

| Converter  | $g_2$                                                                                                                          | $f_2$               | $r_2$                                                                                        |
|------------|--------------------------------------------------------------------------------------------------------------------------------|---------------------|----------------------------------------------------------------------------------------------|
| Buck       | $\frac{1}{R} \left( \frac{M}{1-M} \right) \frac{\left( \frac{m_a}{m_1} (2-M) - M \right)}{\left( 1 + \frac{m_a}{m_1} \right)}$ | $2 \frac{I}{I_c}$   | $R \frac{(1-M) \left( 1 + \frac{m_a}{m_1} \right)}{\left( 1 - 2M + \frac{m_a}{m_1} \right)}$ |
| Boost      | $\frac{1}{R} \left( \frac{M}{M-1} \right)$                                                                                     | $2 \frac{I_2}{I_c}$ | $R \left( \frac{M-1}{M} \right)$                                                             |
| Buck-boost | $\frac{2M}{R} \frac{\left( \frac{m_a}{m_1} \right)}{\left( 1 + \frac{m_a}{m_1} \right)}$                                       | $2 \frac{I_2}{I_c}$ | $R$                                                                                          |

# Simplified DCM CPM model, with $L = 0$

*Buck, boost, buck-boost all become*

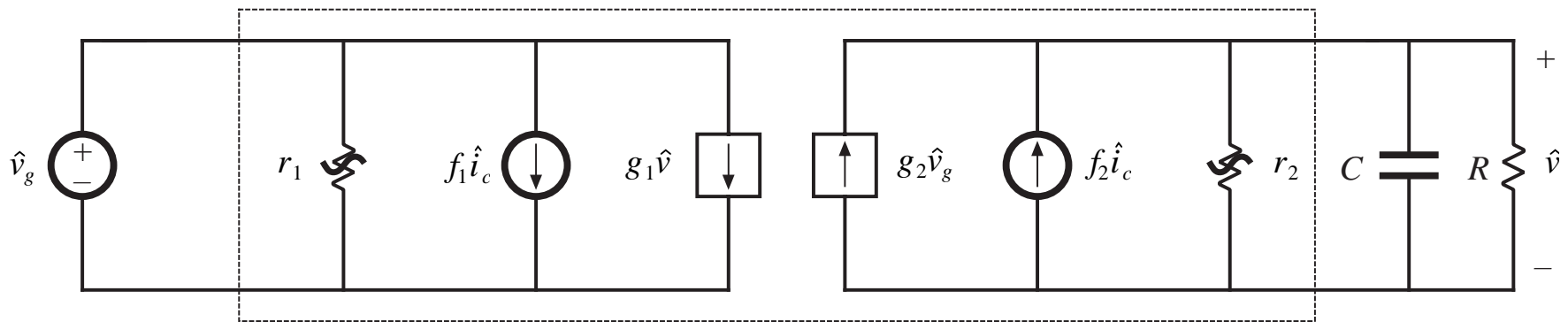

$$G_{vc}(s) = \left. \frac{\hat{v}}{\hat{i}_c} \right|_{\hat{v}_g=0} = \frac{G_{c0}}{1 + \frac{s}{\omega_p}}$$

$$G_{c0} = f_2 (R \parallel r_2)$$


$$\omega_p = \frac{1}{(R \parallel r_2) C}$$

$$G_{vg}(s) = \left. \frac{\hat{v}}{\hat{v}_g} \right|_{\hat{i}_c=0} = \frac{G_{g0}}{1 + \frac{s}{\omega_p}}$$

$$G_{g0} = g_2 (R \parallel r_2)$$

# Current-Programmed (CPM) Controller: Large-Signal CCM/DCM Averaged Model

$$i_{pk} = i_c - m_a d T_s$$

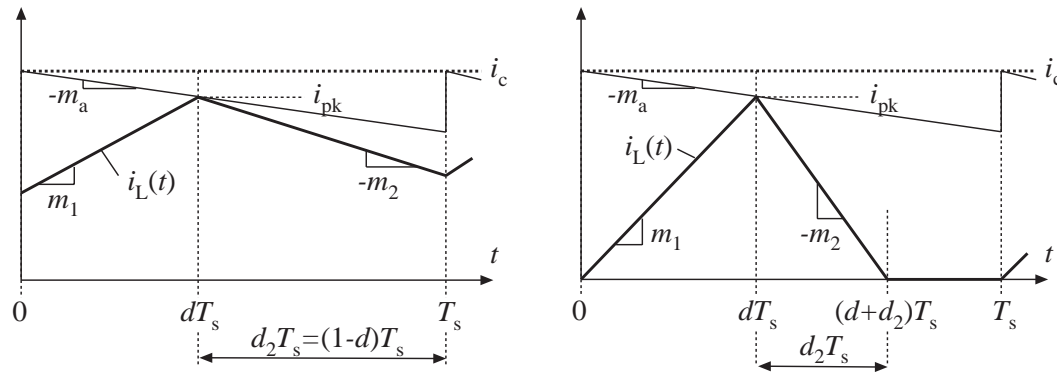


$$\langle i_L \rangle_{T_s} = d \left( i_{pk} - \frac{m_1 d T_s}{2} \right) + d_2 \left( i_{pk} - \frac{m_2 d_2 T_s}{2} \right)$$

$$d_2 = \begin{cases} 1-d & CCM \\ \frac{i_{pk}}{m_2 T_s} & DCM \end{cases}$$

$$CCM/DCM: \quad d_2 = \text{MIN} \left( 1-d, \frac{i_{pk}}{m_2 T_s} \right)$$

# CPM Controller: Large-Signal CCM/DCM Averaged Model

---

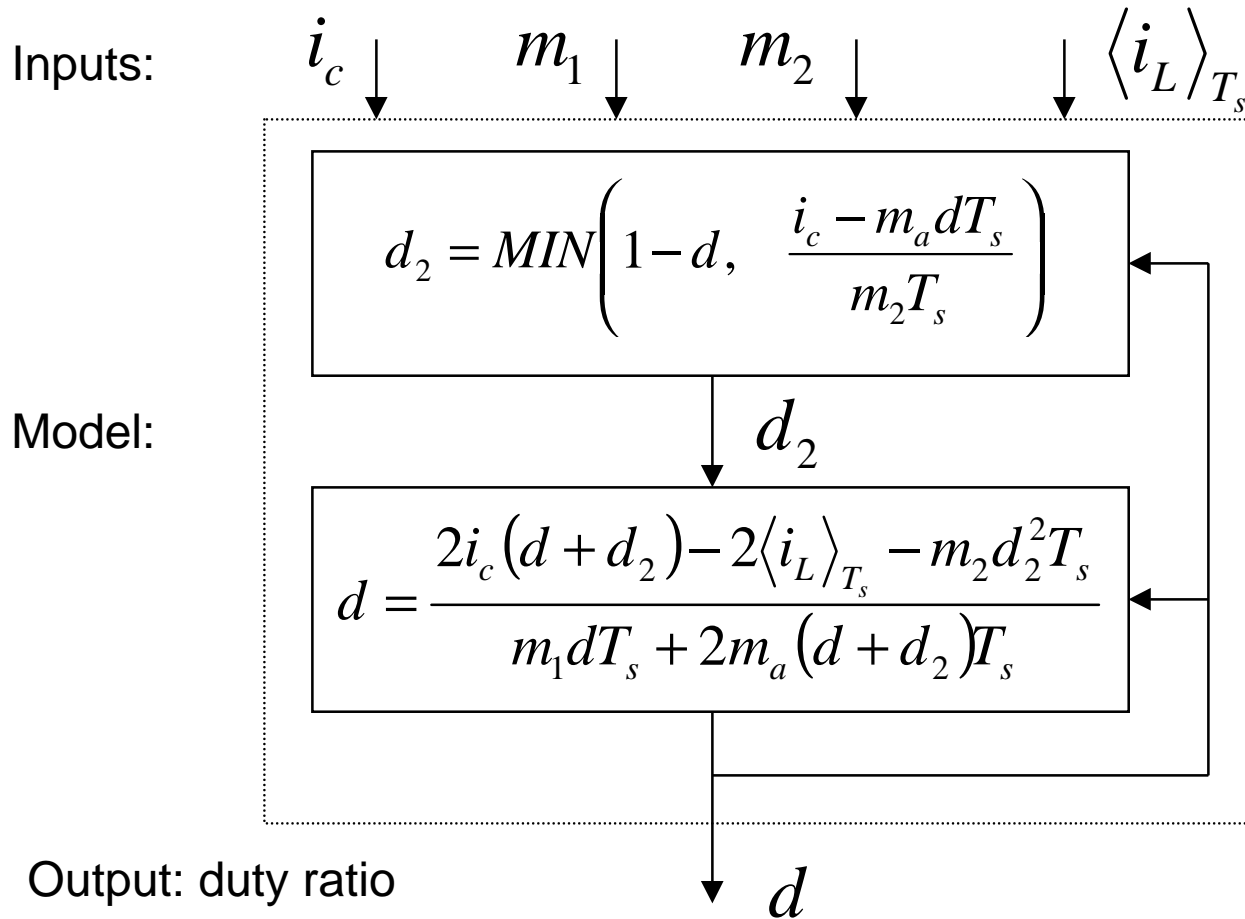

# CPM Large-Signal Averaged Model: PSpice Implementation

\*\*\*\*\*

\* MODEL: CPM  
 \* Current-Programmed-Mode CCM/DCM controller model.  
 \* All parameters and inputs are referred to  
 \* the primary side.

\*\*\*\*\*

\* Parameters:  
 \* L=equivalent inductance, referred to primary  
 \* fs=switching frequency  
 \* va=amplitude of the artificial ramp,  $va=Rf*ma/fs$   
 \* Rf=equivalent current-sense resistance

\*\*\*\*\*

\* Nodes:  
 \* ctr: control input,  $v(ctr)=Rf*ic$   
 \* current: sensed average inductor current  $v(current)=Rf*iL$   
 \* 1: voltage across L in interval 1, slope  $m1=v(1)/L$   
 \* 2: (-) voltage across L in interval 2, slope  $m2=v(2)/L$   
 \* d: duty ratio (output of the controller)

\*\*\*\*\*

.subckt CPM ctr current 1 2 d  
 +params: L=100e-6 fs=1e5 va=0.5 Rf=0.1  
 \*

\* generate d2 for CCM/DCM

Ed2 d2 0 table  
 + {MIN(  
 + L\*fs\*(v(ctr)-va\*v(d))/Rf/(v(2)),  
 + 1-v(d)  
 + )} (0,0) (1,1)

\*

Em1 m1 0 value={Rf\*v(1)/L/fs}  
 Em2 m2 0 value={Rf\*v(2)/L/fs}

\*

\* generate duty-ratio d (valid CCM and DCM operation)

\*

Eduty d 0 table  
 + {  
 + 2\*(v(ctr)\*(v(d)+v(d2))  
 + -v(current)-v(m2)\*v(d2)\*v(d2)/2  
 + /(v(m1)\*v(d)+2\*va\*(v(d)+v(d2)))  
 + } (0.01,0.01) (0.99,0.99)

\*

.ends ; end of subcircuit CPM

\*\*\*\*\*

# Application Example: Buck Converter with Current-Mode Control


---

- Demonstrate how CCM/DCM averaged-switch model can be used together with CCM/DCM averaged model of the current-mode controller
- Use DC sweep simulation to show steady-state characteristics including operation in DCM or CCM
- Use AC simulation to show control-to-output responses compared for duty-ratio control and current-mode control, in DCM or CCM
- Use parametric sweep simulation to find the amplitude of the artificial ramp to minimize input-to-output audio-susceptibility
- Specifications:
  - Input  $V_g = 28V$ , output  $V = 5-20V$ ,  $0.5-2A$
  - Switching frequency  $f_s = 100kHz$ , inductance  $L = 35\mu H$
  - Equivalent current-sense resistance  $R_f = 1$
  - Artificial-ramp amplitude  $V_a = 0-3V$



# Buck Converter with Current-Mode Control


## DC Sweep Simulation

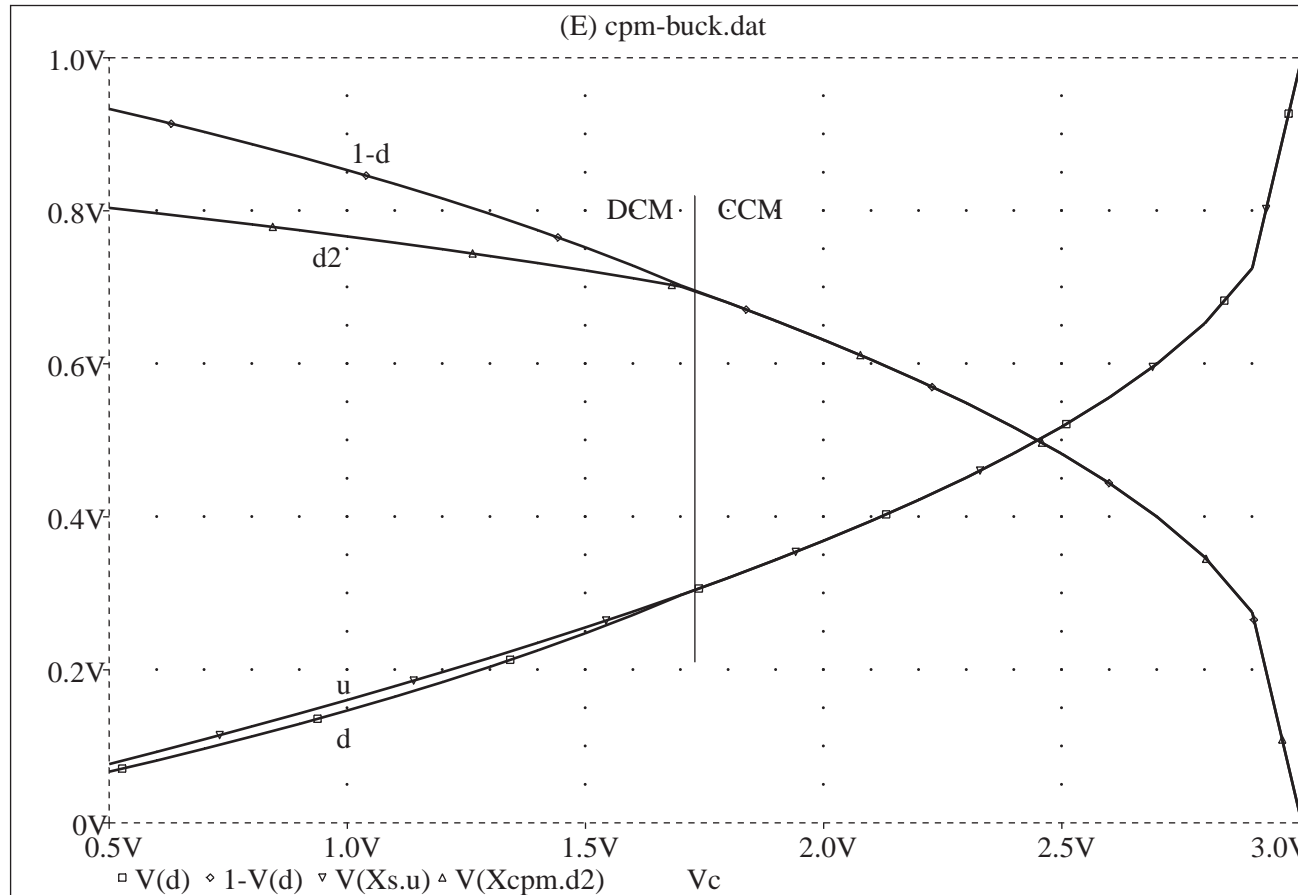

Duty ratio  $d$ , equivalent duty ratio  $u$ , and diode conduction interval  $d_2$  as functions of the control input  $V_c$

# Buck Converter with Current-Mode Control


## DC Sweep Simulation

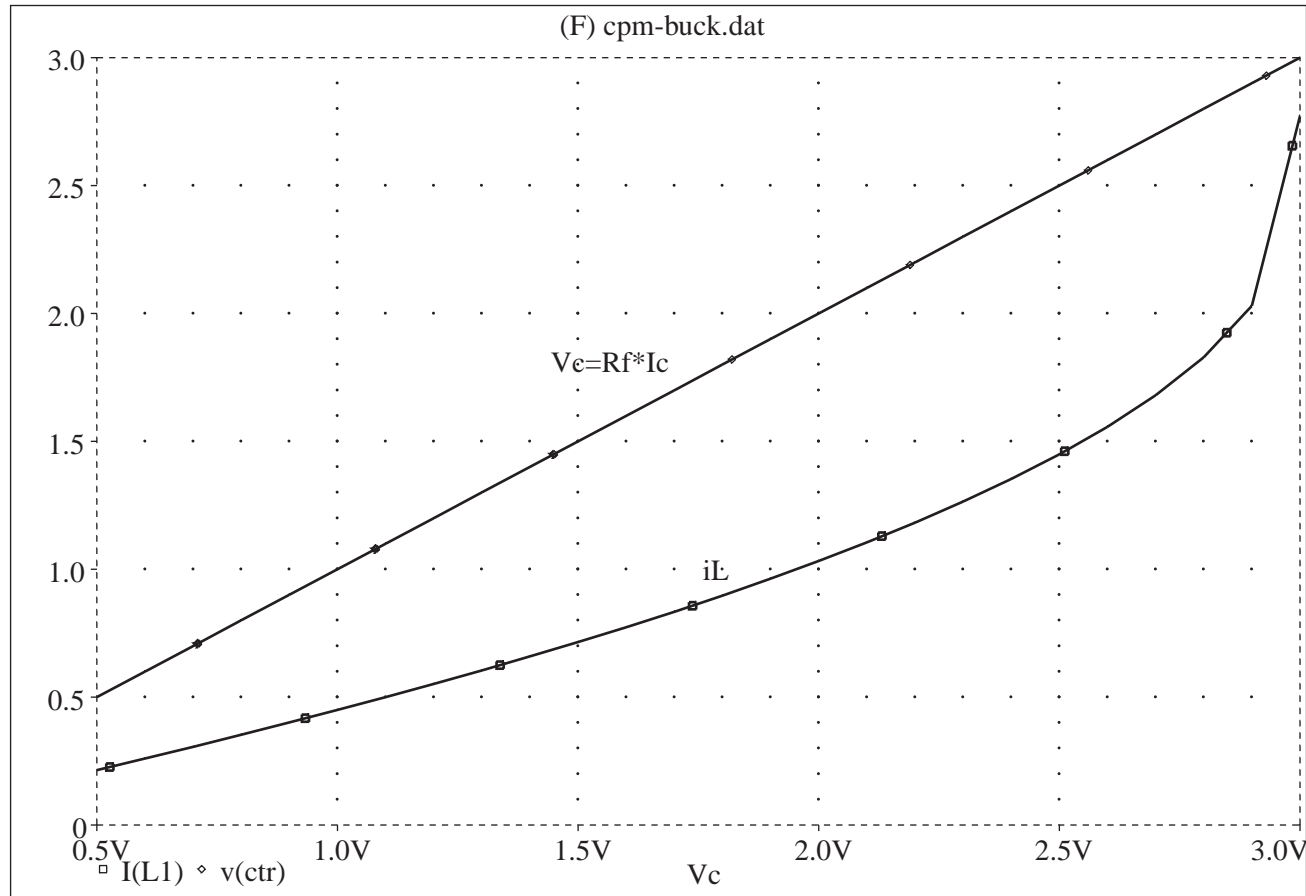

Average inductor current  $i_L$  as a function of the control input  $V_c$


# Buck Converter with Current-Mode Control

## Frequency Responses in CCM

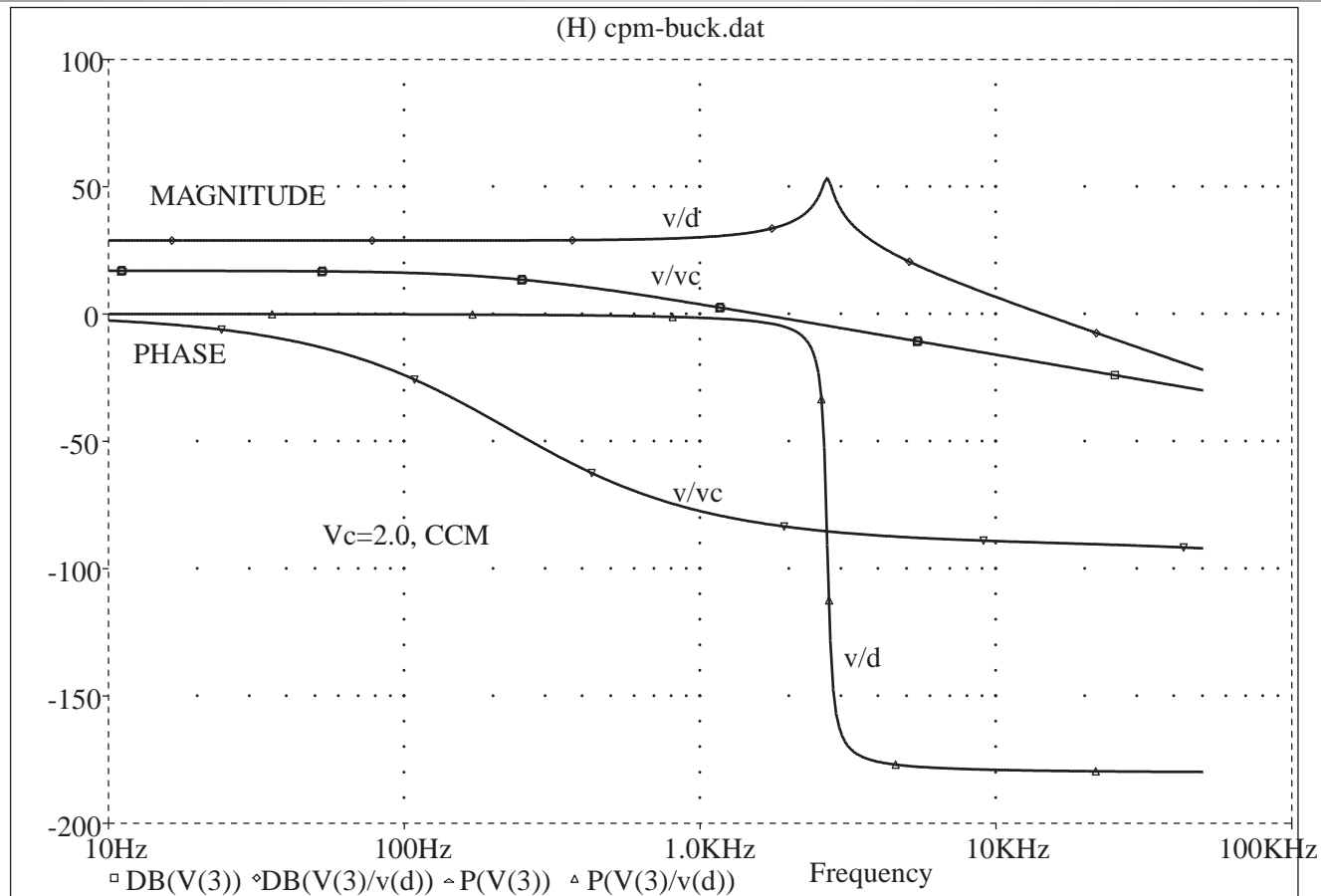

Control-to-output frequency responses for duty-ratio control ( $v/d$ ) and current-mode control ( $v/v_c$ ). The converter operates in CCM.

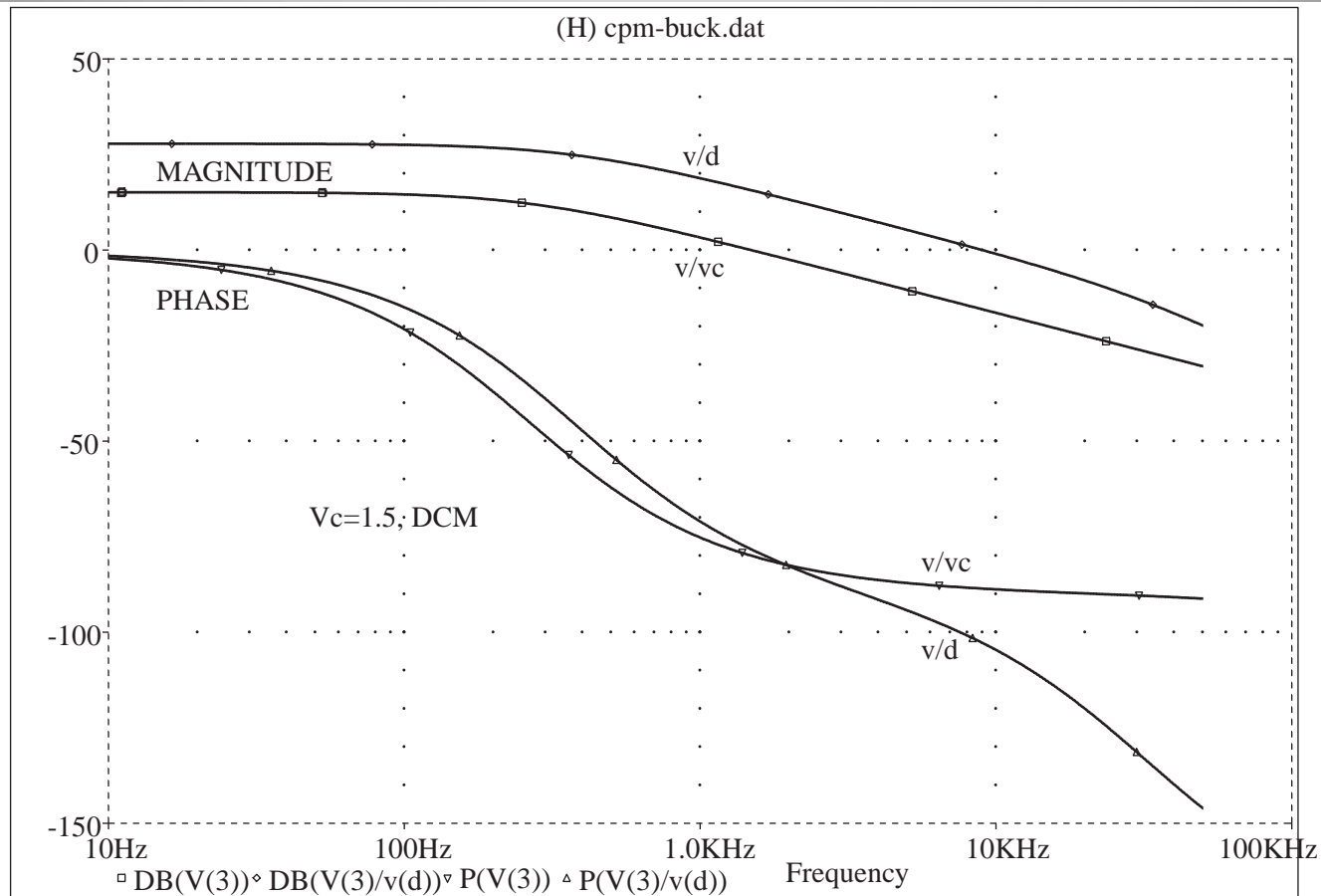
# Buck Converter with Current-Mode Control Frequency Responses in DCM



Control-to-output frequency responses for duty-ratio control ( $v/d$ ) and current-mode control ( $v/v_c$ ). The converter operates in DCM.

# Buck Converter with Current-Mode Control

## Audio-susceptibility Analysis

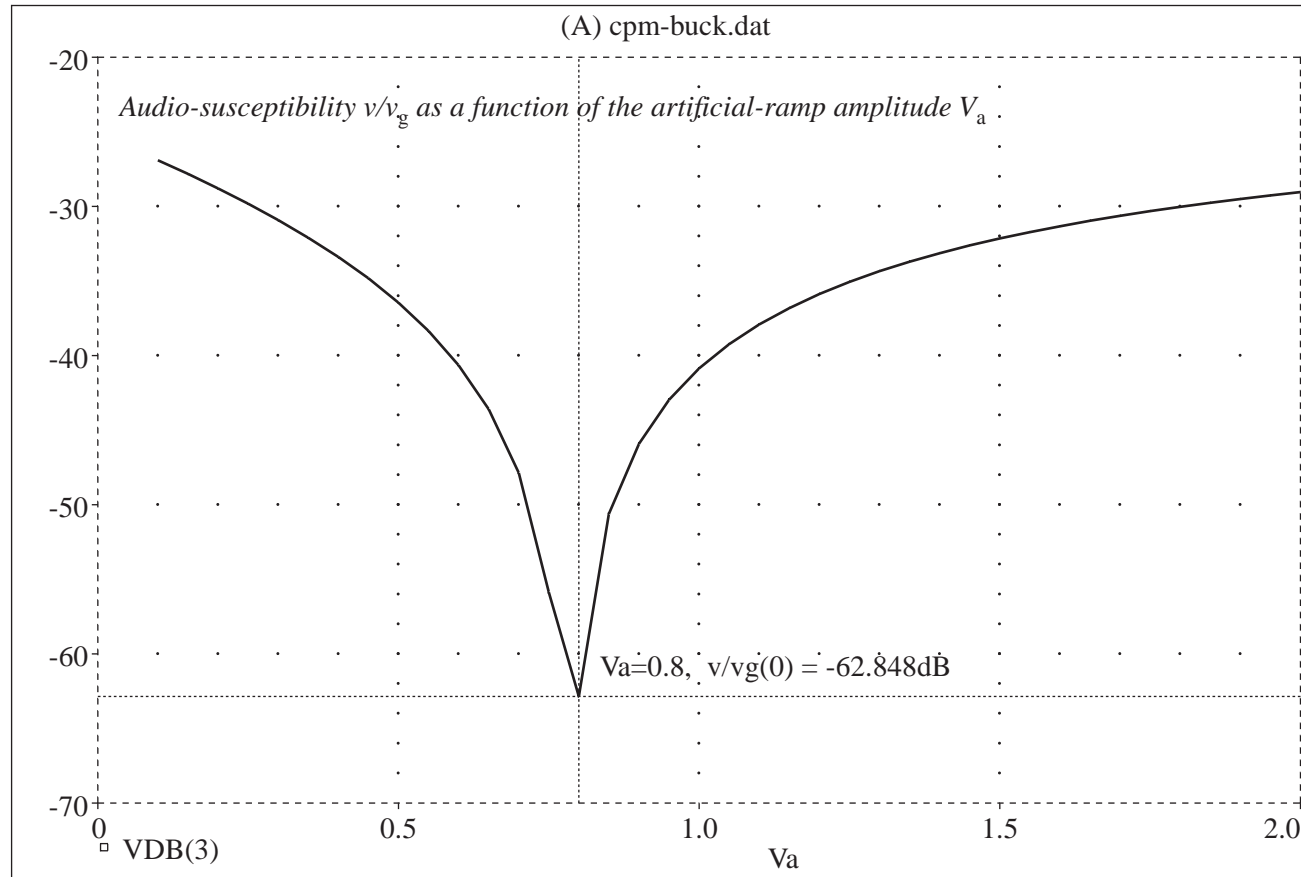

Parametric sweep used to determine amplitude of the artificial ramp  $V_a$  to minimize input-to-output response (audio-susceptibility)  $v/v_g$ .

## 5. Averaged modeling of single-phase low-harmonic rectifiers

---

- **Ideal rectifier**
- **Averaged model obtained by averaging over switching period**
- **Averaged model obtained by averaging over line period**
- **Application examples:**
  - Power factor corrector based on boost converter operating in DCM
  - Power factor corrector based on SEPIC with nonlinear-carrier control

# Properties of the Ideal Rectifier


---

It is desired that the rectifier present a resistive load to the ac power system. This leads to

- unity power factor
- ac line current has same waveshape as voltage

$$i_{ac}(t) = \frac{v_{ac}(t)}{R_e}$$

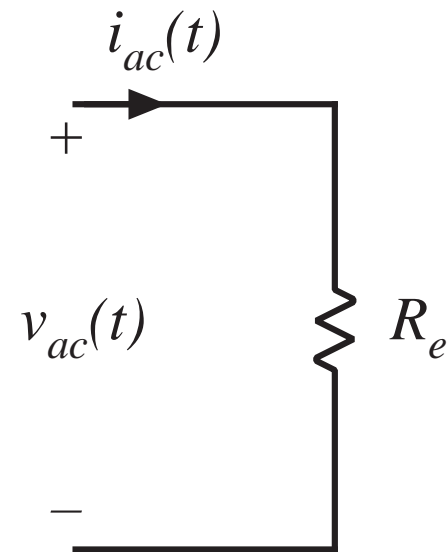$R_e$  is called the *emulated resistance*




# Control of power throughput

---


$$P_{av} = \frac{V_{ac,rms}^2}{R_e(v_{control})}$$

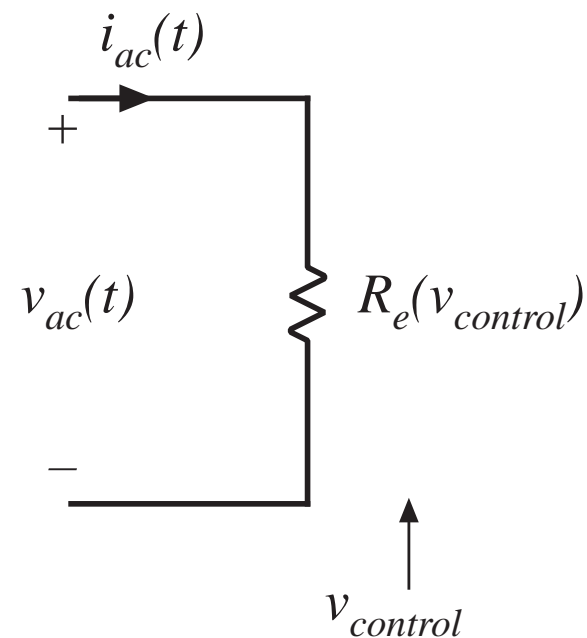Power apparently “consumed” by  $R_e$  is actually transferred to rectifier dc output port. To control the amount of output power, it must be possible to adjust the value of  $R_e$ .


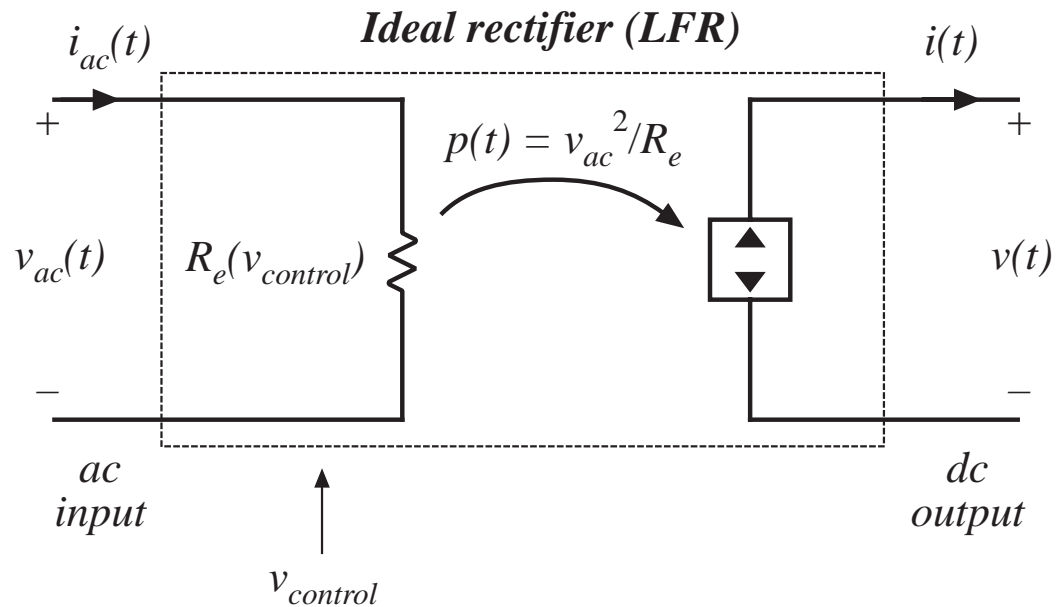
# Output port model

The ideal rectifier is lossless and contains no internal energy storage. Hence, the instantaneous input power equals the instantaneous output power. Since the instantaneous power is independent of the dc load characteristics, the output port obeys a power source characteristic.



$$p(t) = \frac{v_{ac}^2(t)}{R_e(v_{control}(t))} \quad v(t)i(t) = p(t) = \frac{v_{ac}^2(t)}{R_e}$$

# Equations of the ideal rectifier / LFR

---

Defining equations of the ideal rectifier:

$$i_{ac}(t) = \frac{v_{ac}(t)}{R_e(v_{control})}$$

$$v(t)i(t) = p(t)$$

$$p(t) = \frac{v_{ac}^2(t)}{R_e(v_{control}(t))}$$


When connected to a resistive load of value  $R$ , the input and output rms voltages and currents are related as follows:

$$\frac{V_{rms}}{V_{ac,rms}} = \sqrt{\frac{R}{R_e}}$$

$$\frac{I_{ac,rms}}{I_{rms}} = \sqrt{\frac{R}{R_e}}$$

A switch network that is capable of satisfying the above (averaged) equations can be employed in low-harmonic rectifier applications
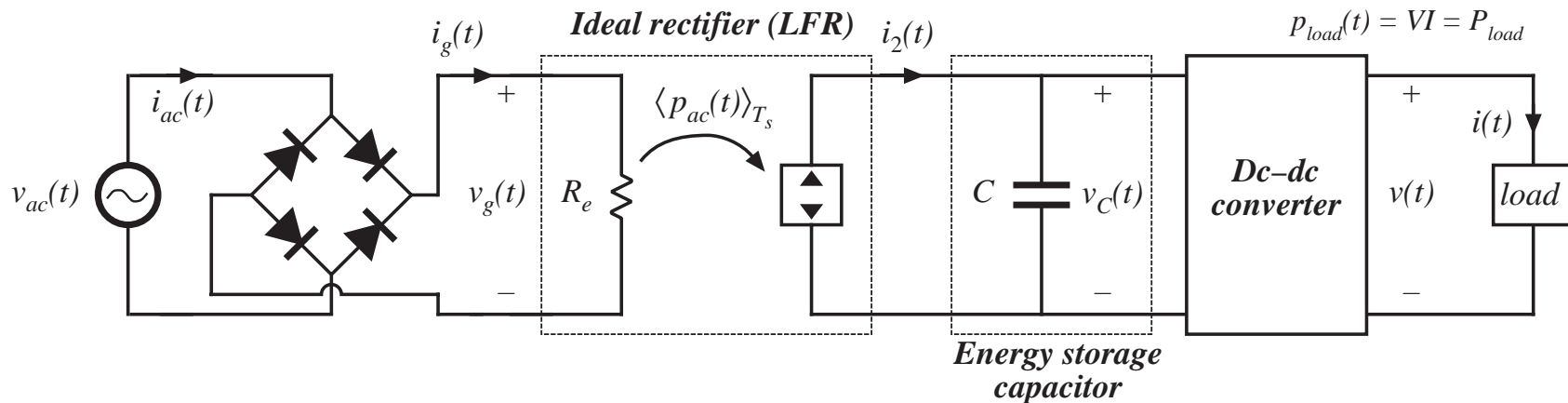
# Single-phase system with internal energy storage



Energy storage capacitor voltage  $v_C(t)$  must be independent of input and output voltage waveforms, so that it can vary according to


$$\frac{d\left(\frac{1}{2} C v_C^2(t)\right)}{dt} = p_{ac}(t) - p_{load}(t)$$

This system is capable of

- Wide-bandwidth control of output voltage
- Wide-bandwidth control of input current waveform
- Internal independent energy storage

# Large signal model

averaged over switching period  $T_s$

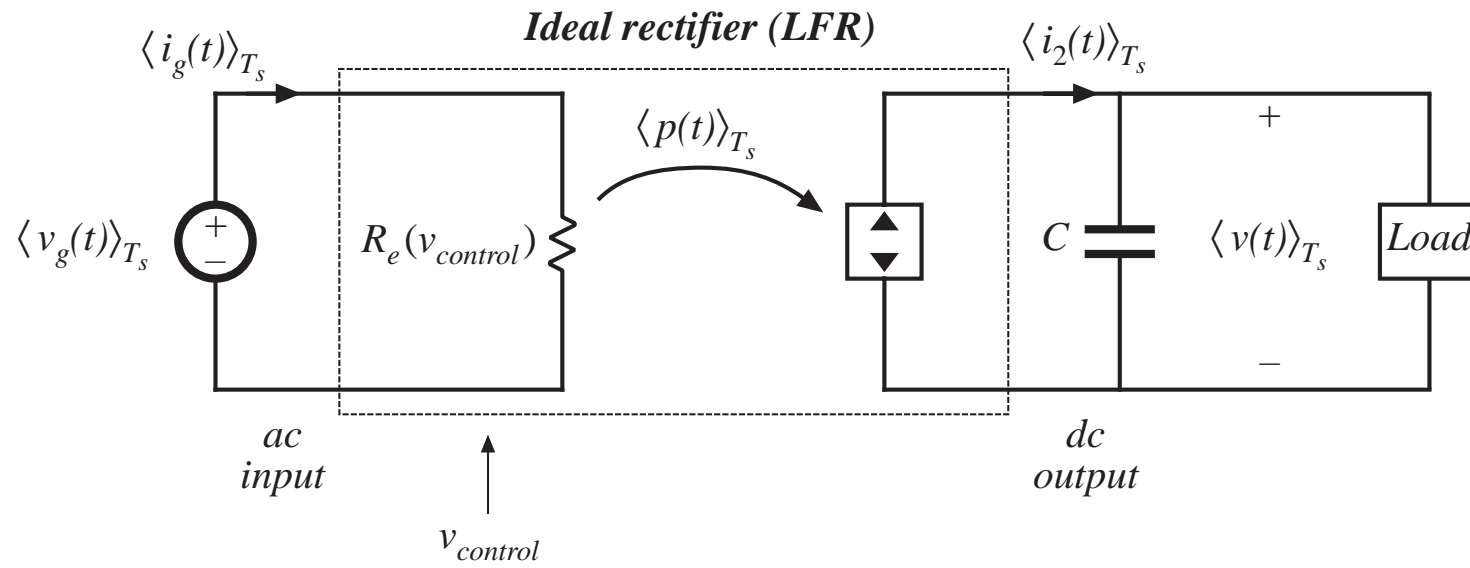

Ideal rectifier model, assuming that inner wide-bandwidth loop operates ideally

High-frequency switching harmonics are removed via averaging

Ac line-frequency harmonics are included in model

Nonlinear and time-varying

# Predictions of large-signal model


If the input voltage is

$$v_g(t) = \sqrt{2} v_{g,rms} |\sin(\omega t)|$$


Then the instantaneous power is:

$$\langle p(t) \rangle_{T_s} = \frac{\langle v_g(t) \rangle_{T_s}^2}{R_e(v_{control}(t))} = \frac{v_{g,rms}^2}{R_e(v_{control}(t))} (1 - \cos(2\omega t))$$

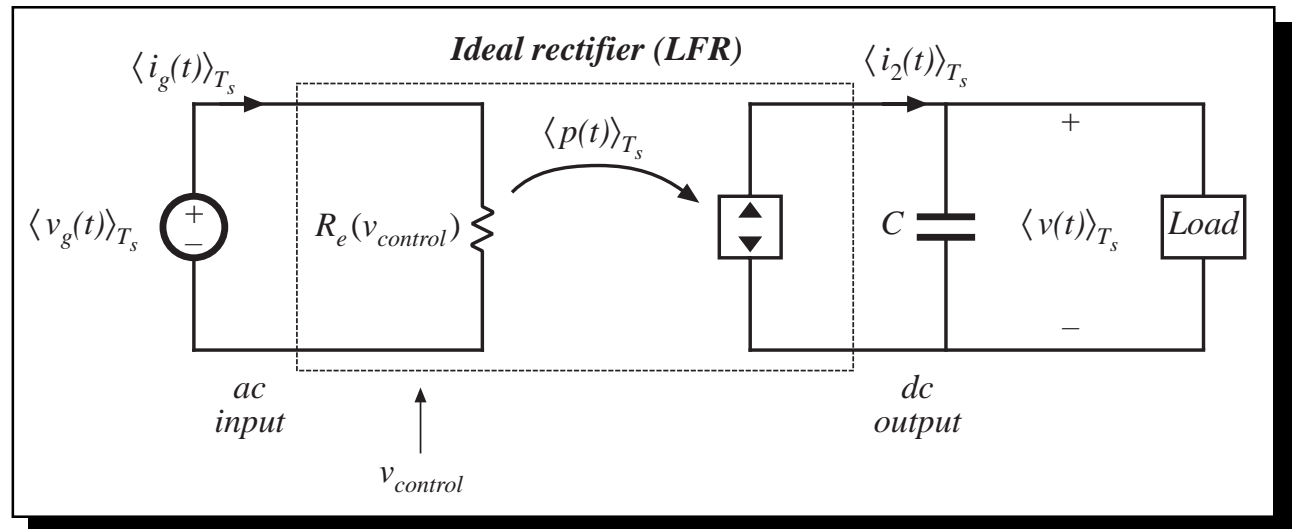which contains a constant term plus a second-harmonic term



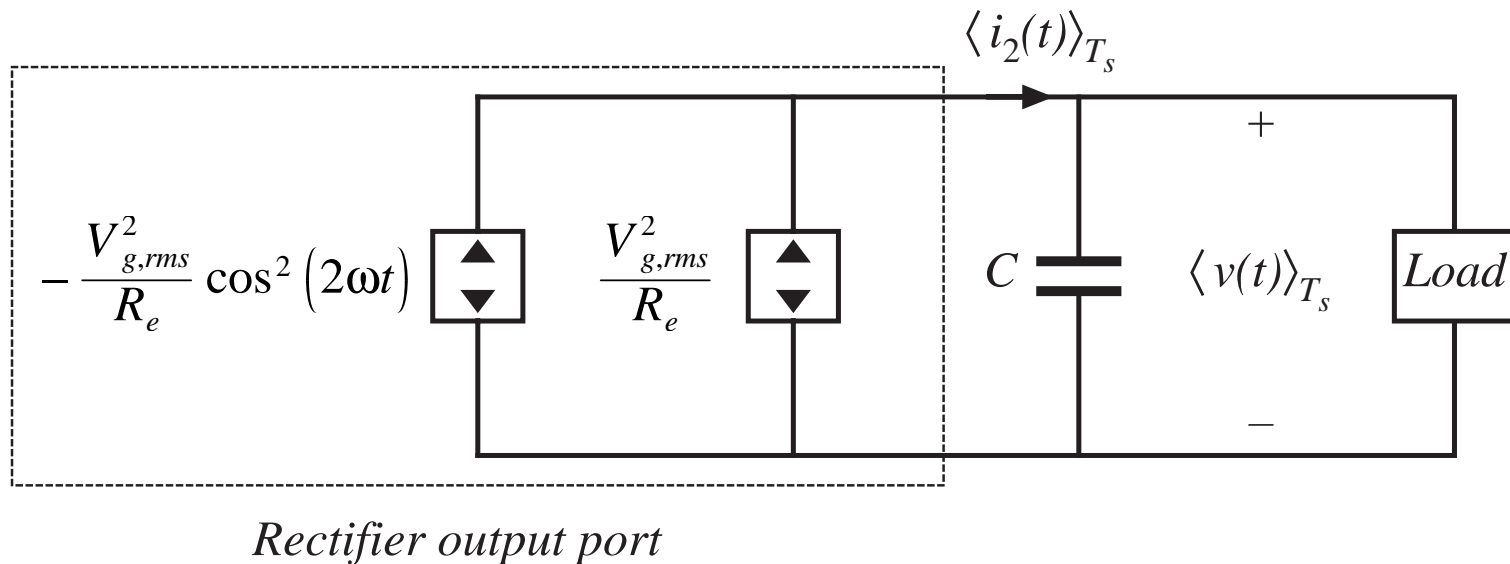
# Separation of power source into its constant and time-varying components



The second-harmonic variation in power leads to second-harmonic variations in the output voltage and current

# Removal of even harmonics via averaging


---

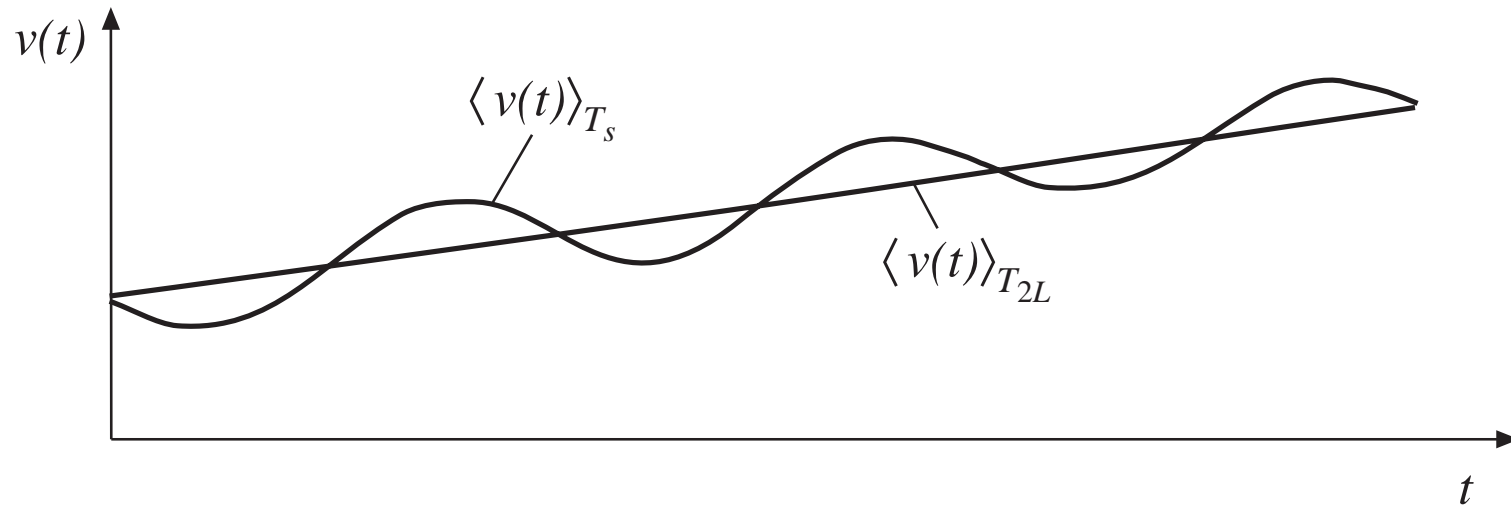

$$T_{2L} = \frac{1}{2} \frac{2\pi}{\omega} = \frac{\pi}{\omega}$$

# Resulting averaged model

---

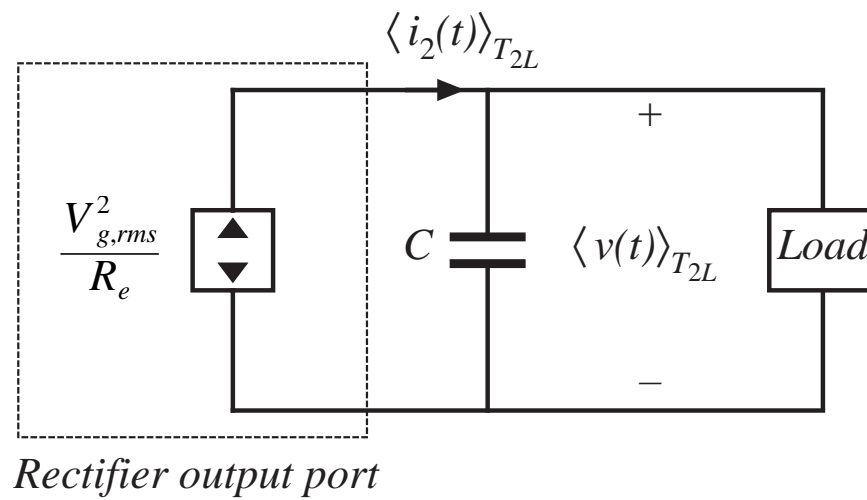

Time invariant model

Power source is nonlinear

# Perturbation and linearization

---

The averaged model predicts that the rectifier output current is

$$\begin{aligned}\langle i_2(t) \rangle_{T_{2L}} &= \frac{\langle p(t) \rangle_{T_{2L}}}{\langle v(t) \rangle_{T_{2L}}} = \frac{v_{g,rms}^2(t)}{R_e(v_{control}(t)) \langle v(t) \rangle_{T_{2L}}} \\ &= f\left(v_{g,rms}(t), \langle v(t) \rangle_{T_{2L}}, v_{control}(t)\right)\end{aligned}$$

Let

$$\langle v(t) \rangle_{T_{2L}} = V + \hat{v}(t)$$

$$\langle i_2(t) \rangle_{T_{2L}} = I_2 + \hat{i}_2(t)$$

$$v_{g,rms} = V_{g,rms} + \hat{v}_{g,rms}(t)$$

$$v_{control}(t) = V_{control} + \hat{v}_{control}(t)$$

with

$$V \gg |\hat{v}(t)|$$

$$I_2 \gg |\hat{i}_2(t)|$$

$$V_{g,rms} \gg |\hat{v}_{g,rms}(t)|$$

$$V_{control} \gg |\hat{v}_{control}(t)|$$

# Linearized result

$$I_2 + \hat{i}_2(t) = g_2 \hat{v}_{g,rms}(t) + j_2 \hat{v}(t) - \frac{\hat{v}_{control}(t)}{r_2}$$


where

$$g_2 = \left. \frac{df(v_{g,rms}, V, V_{control})}{dv_{g,rms}} \right|_{v_{g,rms} = V_{g,rms}} = \frac{2}{R_e(V_{control})} \frac{V_{g,rms}}{V}$$

$$\left( -\frac{1}{r_2} \right) = \left. \frac{df(V_{g,rms}, \langle v \rangle_{T_{2L}}, V_{control})}{d\langle v \rangle_{T_{2L}}} \right|_{\langle v \rangle_{T_{2L}} = V} = -\frac{I_2}{V}$$

$$j_2 = \left. \frac{df(V_{g,rms}, V, v_{control})}{dv_{control}} \right|_{v_{control} = V_{control}} = -\frac{V_{g,rms}^2}{VR_e^2(V_{control})} \left. \frac{dR_e(v_{control})}{dv_{control}} \right|_{v_{control} = V_{control}}$$

# Small-signal equivalent circuit

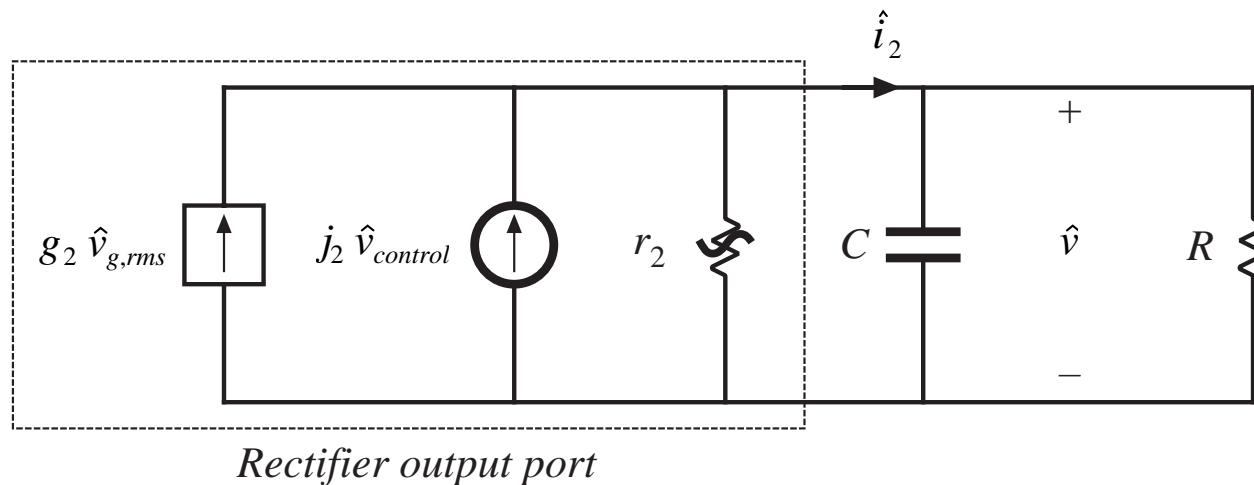


Predicted transfer functions

*Control-to-output* 
$$\frac{\hat{v}(s)}{\hat{v}_{control}(s)} = j_2 R || r_2 \frac{1}{1 + sC R || r_2}$$

*Line-to-output* 
$$\frac{\hat{v}(s)}{\hat{v}_{g,rms}(s)} = g_2 R || r_2 \frac{1}{1 + sC R || r_2}$$

# Constant power load

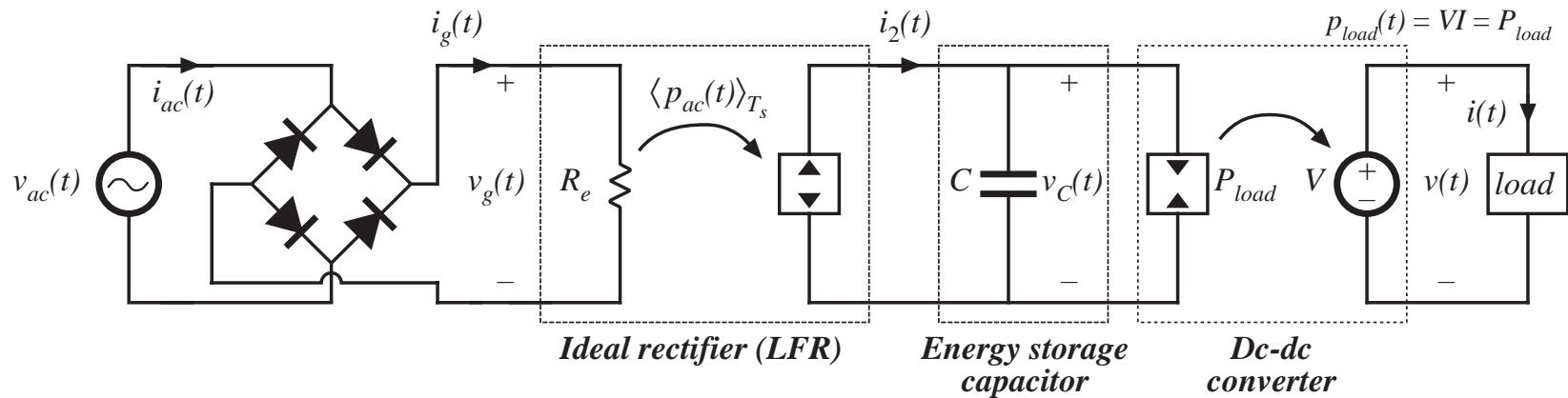

Rectifier and dc-dc converter operate with same average power

Incremental resistance  $R$  of constant power load is negative, and is

$$R = -\frac{V^2}{P_{av}}$$

which is equal in magnitude and opposite in polarity to rectifier incremental output resistance  $r_2$  for all controllers except NLC

# Transfer functions with constant power load

---

When  $r_2 = -R$ , the parallel combination  $r_2 \parallel R$  becomes equal to zero. The small-signal transfer functions then reduce to

$$\frac{\hat{v}(s)}{\hat{v}_{control}(s)} = \frac{j_2}{sC}$$

$$\frac{\hat{v}(s)}{\hat{v}_{g,rms}(s)} = \frac{g_2}{sC}$$

# Application Example: Power-Factor Corrector Based on Boost Converter Operating in DCM

---


## **Objectives:**

- Example of how large-signal averaged-switch model can be used for analysis and simulation of a power-factor corrector
- Show examples of averaged pulse-width modulator model, and implementation of closed-loop control
- Use transient simulation to study start-up transient response of the PFC and harmonic distortion of the AC line current in steady state

## **Specifications:**

- Input: 120Vrms, 50Hz. Output: 300VDC, 100W
- Switching frequency: 100kHz

# DCM Boost PFC

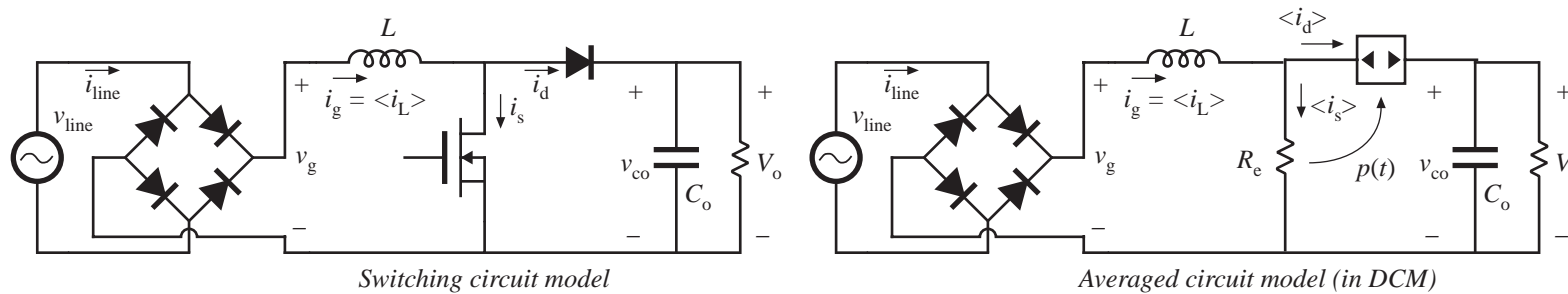

Boost converter operates in DCM at constant duty ratio, constant frequency


$$i_g = \langle i_s \rangle_{T_s} + \langle i_d \rangle_{T_s} = \frac{v_g}{R_e} + \frac{P}{V - v_g} = \frac{v_g}{R_e} + \frac{v_g^2}{R_e(V - v_g)}$$

$$i_g = \frac{v_g}{R_e} \left( \frac{1}{1 - \frac{v_g}{V}} \right) \quad R_e = \frac{2L}{D^2 T_s}$$

Line current distortion due to this term

# DCM Boost PFC


Averaged model of the boost rectifier

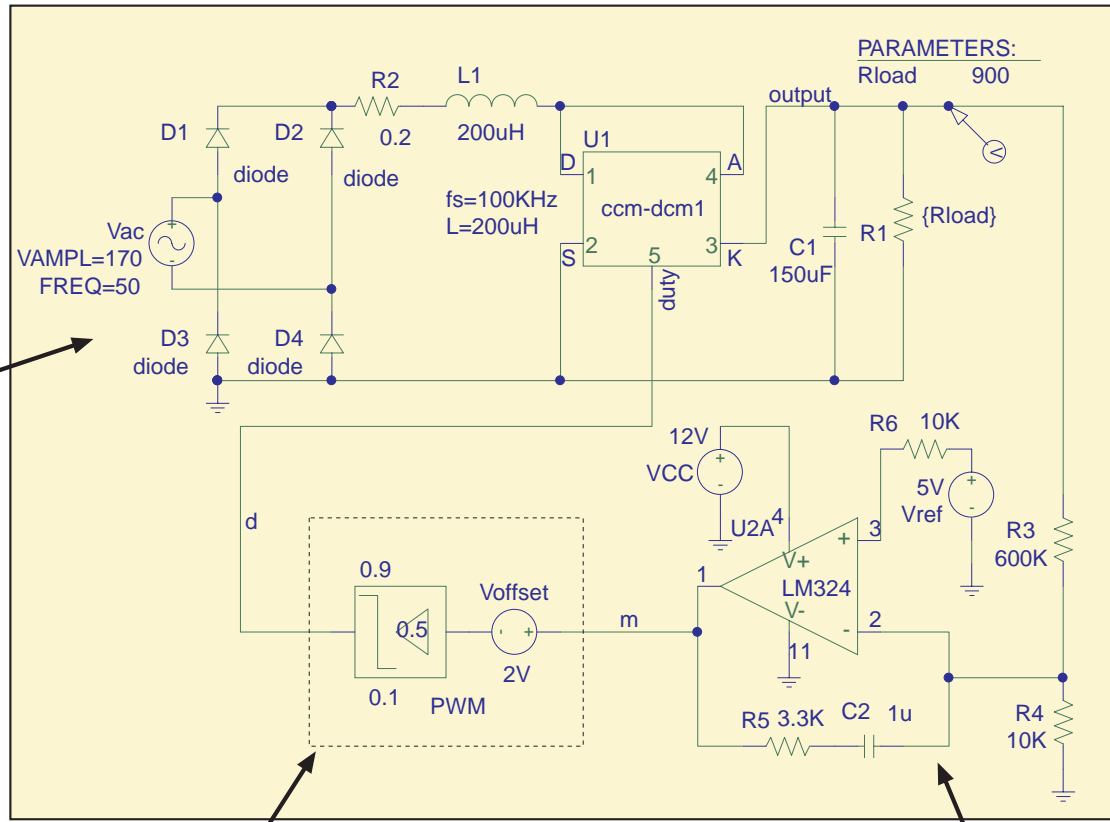

Averaged PWM model:  $d = v_m / V_M = 0.5 v_m$ ,  
 $D_{\min} = 0.1$ ,  $D_{\max} = 0.9$  limits


Closed-loop output voltage control

# DCM Boost PFC: Start-Up Transient

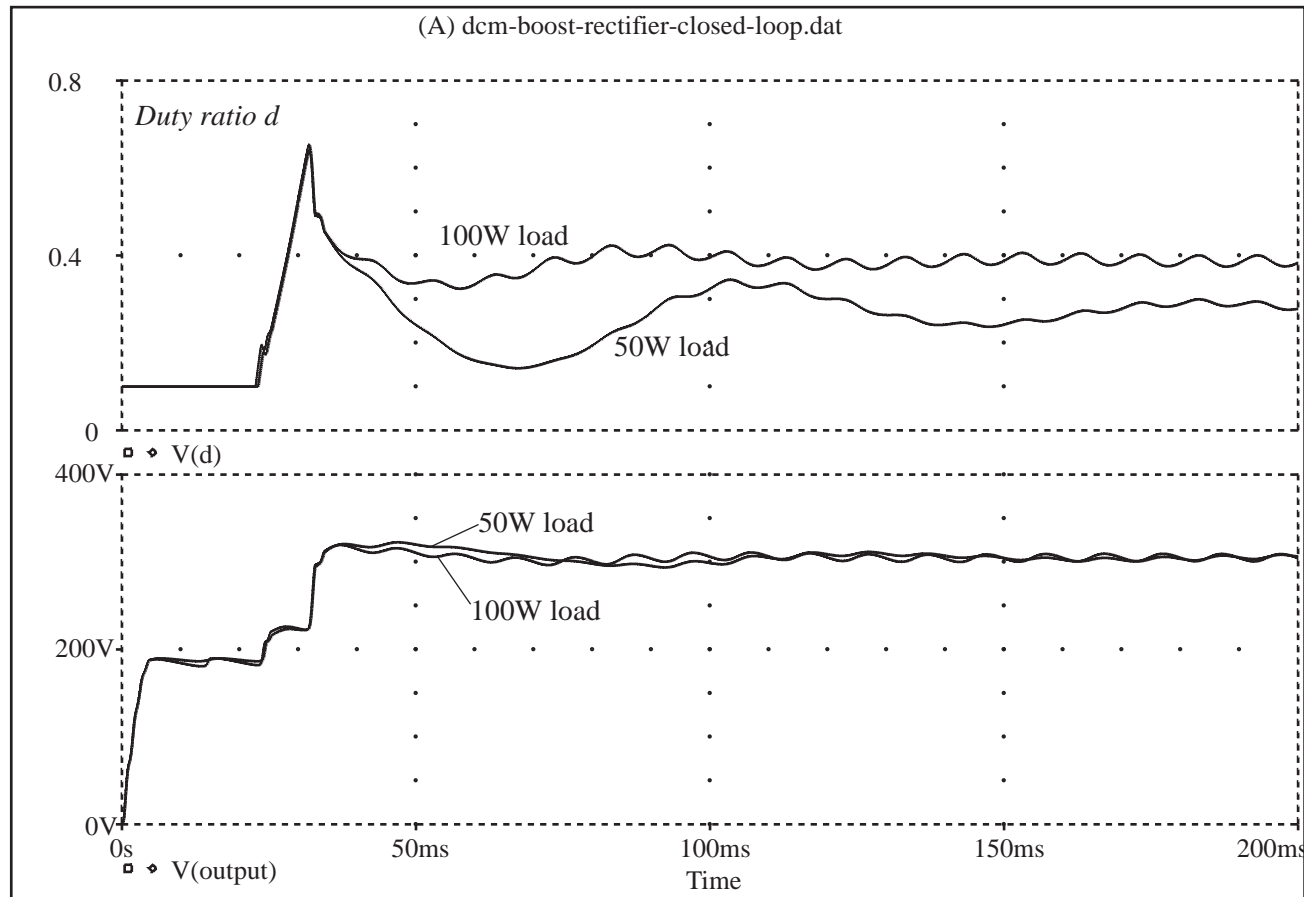


Start-up transient response for full load and 50% load
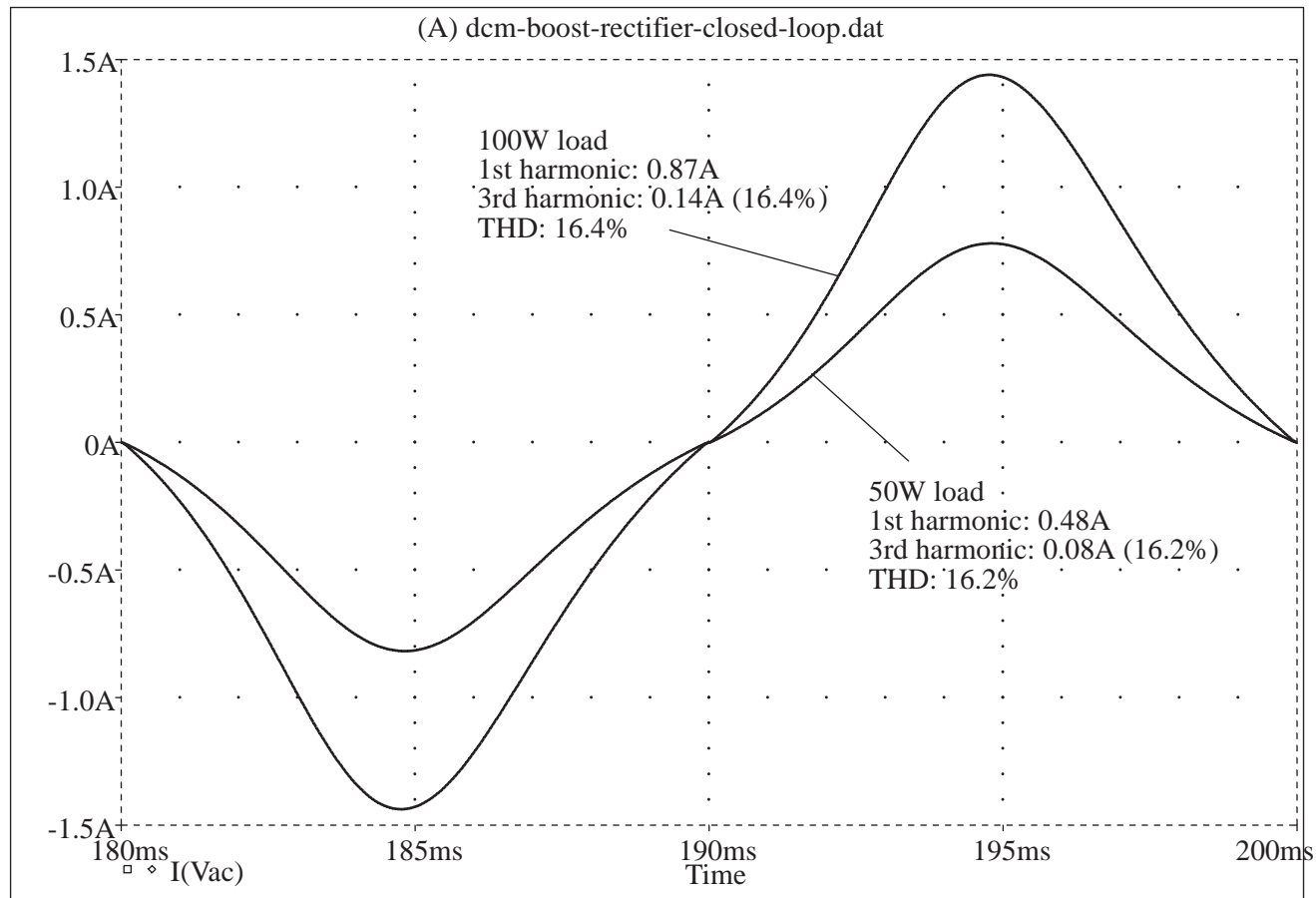
# DCM Boost PFC: AC Line Current Waveforms




AC line current waveforms at full load and 50% load
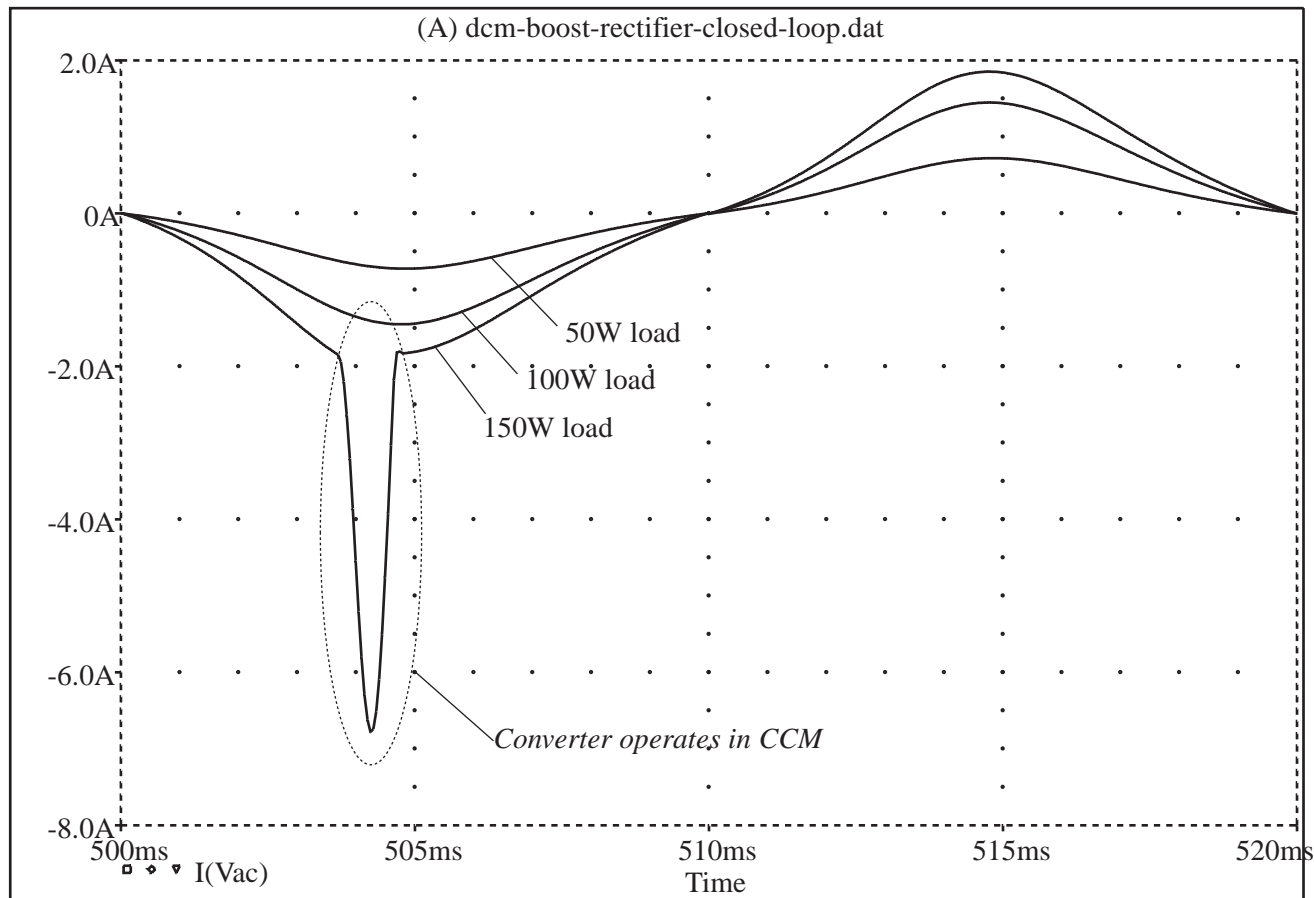
# DCM Boost PFC: AC Line Current Distortion in CCM



AC line current waveforms at full load (100W),  
50% load, and 150% load
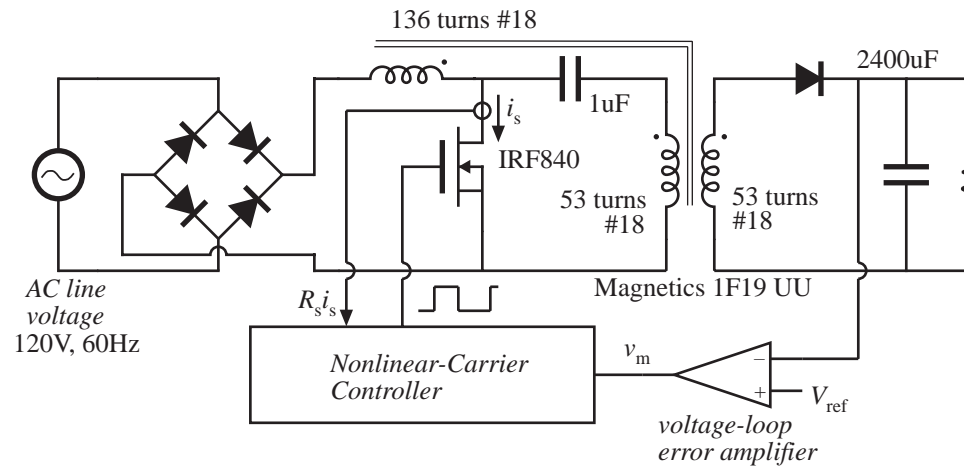
# Application Example: Sepic PFC with NLC Control



- Active current shaping using Nonlinear Carrier Control method
- Sepic converter has integrated magnetics designed for zero switching ripple in the AC line current
- Specifications:
  - Input: 90-120Vrms, 60Hz. Output: 48VDC, 200W
  - Switching frequency: 90kHz


# Application Example: Sepic PFC with NLC Control

---

## **Objectives:**

- Show application of the CCM/DCM averaged-switch model in power-factor correctors with active current shaping and closed-loop output voltage control
- Show average model implementation of a nonlinear pulse-width modulator (NLC controller)
- Compare average model predictions to experimental results:
  - AC line current waveshapes
  - Start-up and load transient responses

# NLC Controller Operation

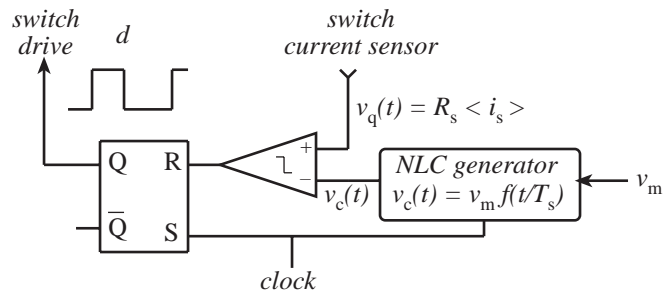


$$f(t/T_s) = v_m \frac{T_s}{t} \left(1 - \frac{t}{T_s}\right) \rightarrow R_s \langle i_s \rangle_{T_s} = v_m \frac{1-d}{d}$$

$$\frac{1-d}{d} = \frac{v_g}{V}$$

$$i_g = \langle i_s \rangle_{T_s}$$

$$i_g = \left( \frac{v_m}{R_s V} \right) v_g$$

→ Ideal current shaping

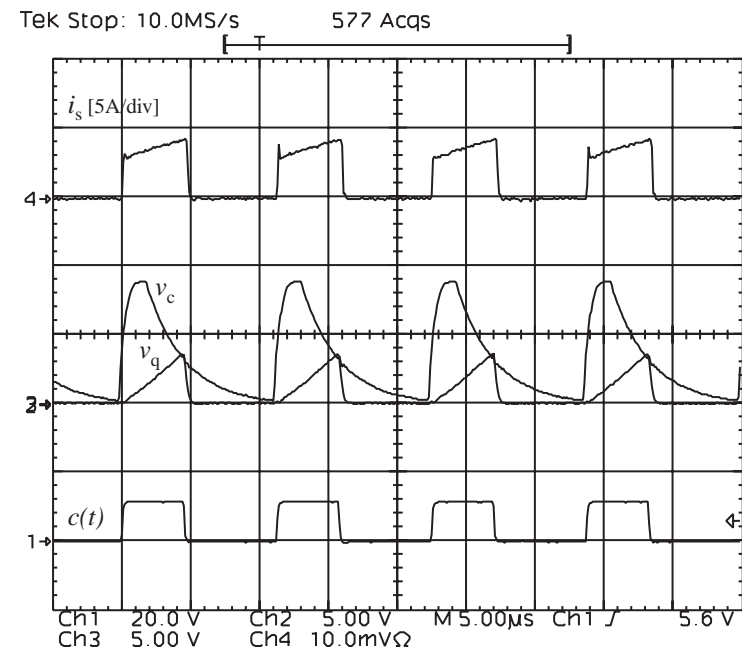


$$d = \frac{v_m}{R_s \langle i_s \rangle_{T_s} + v_m}$$

NLC Controller Model

# Sepic PFC with NLC Control: Simulation Model

Coupled-inductor model

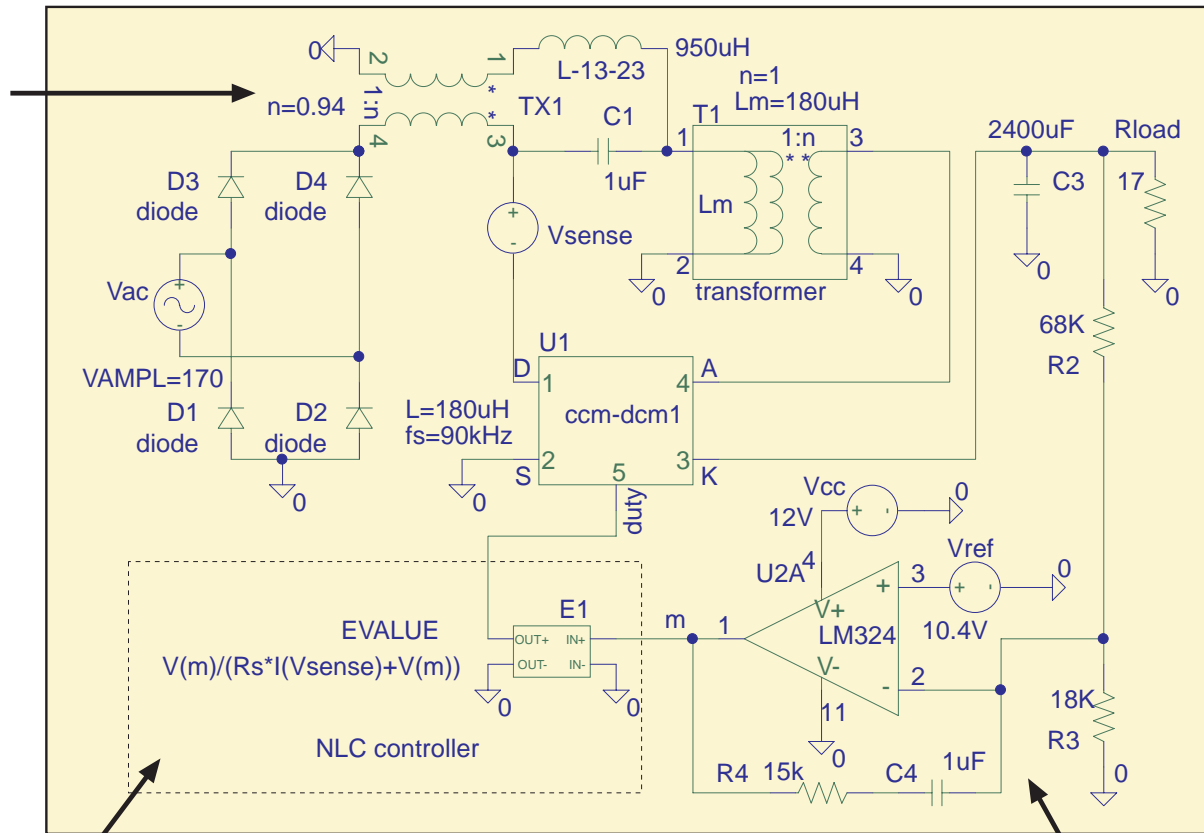


NLC controller model

Closed-loop output voltage control

# Sepic PFC with NLC Control

## Experimental vs. Simulation Results

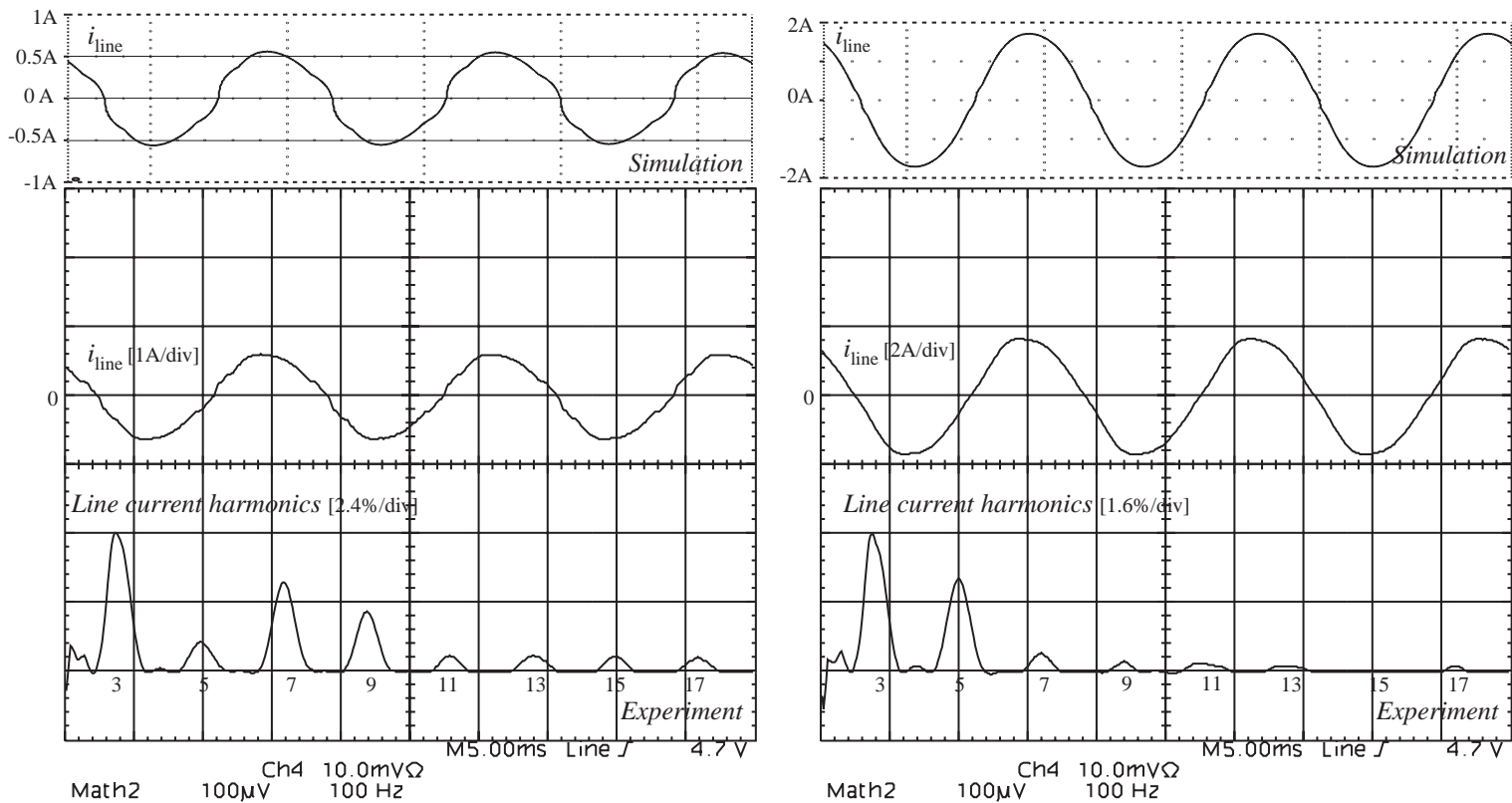


AC line current waveform and spectrum at 50W load (left) and 170W load (right)


# Sepic PFC with NLC Control

## Experimental vs. Simulation Results

Tek Stop: Single Seq 2.50ks/s

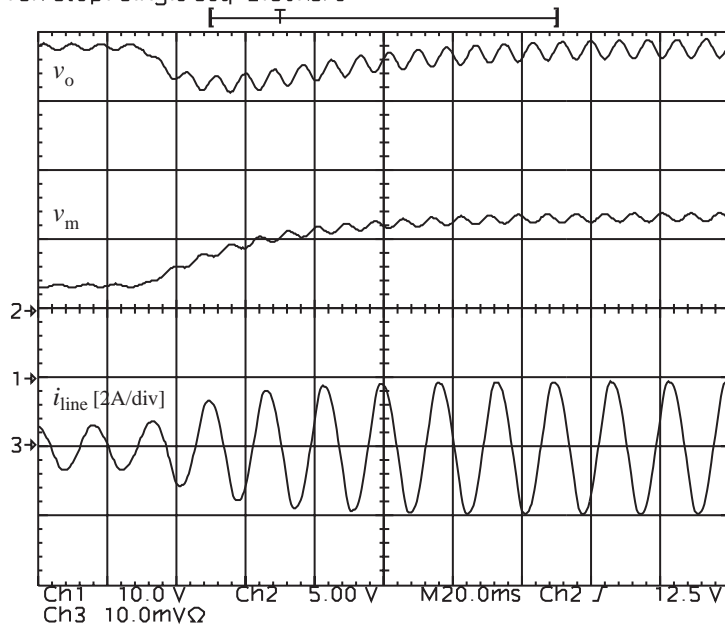

Experiment

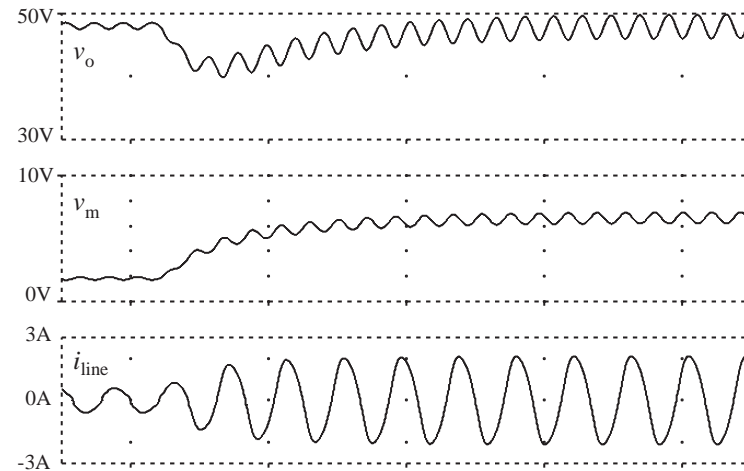


Simulation


50W to 125W load transient in the Sepic PFC

# Sepic PFC with NLC Control

## Experimental vs. Simulation Results

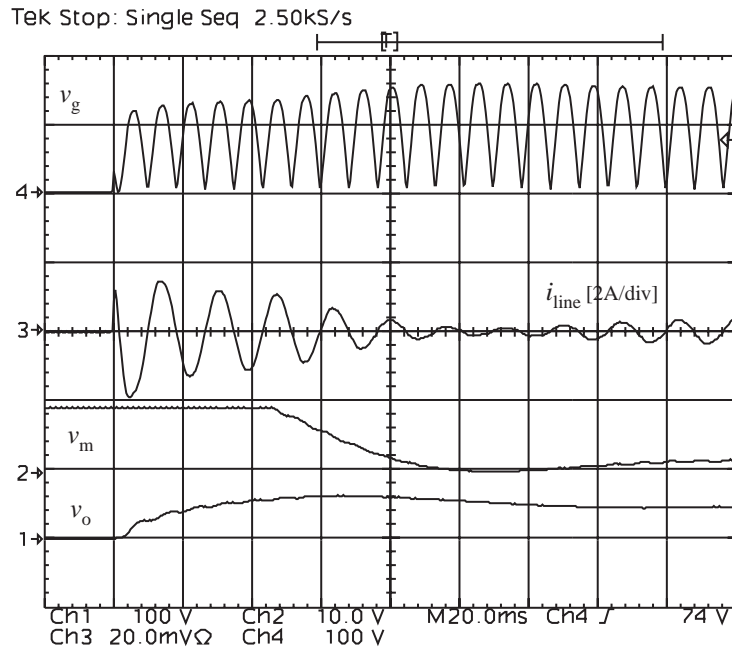

Experiment

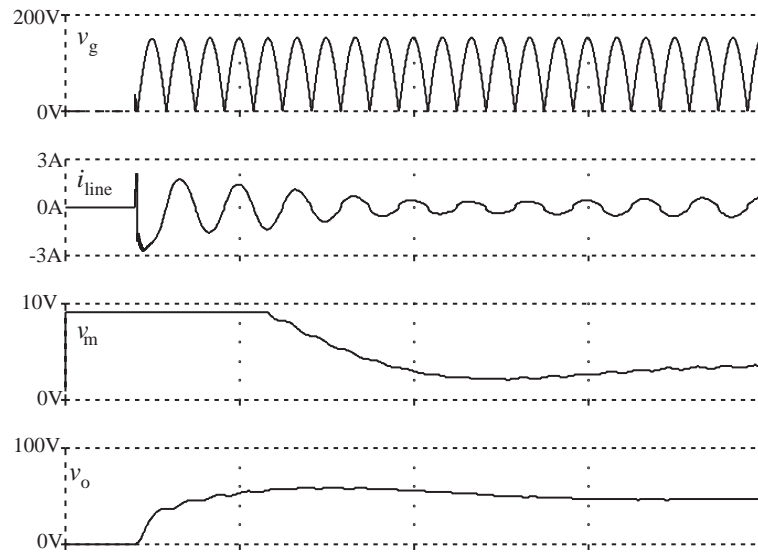

Simulation

Start-up transient in the Sepic PFC at 50W load

## 6. Summary

---

- The averaged switch modeling approach: replace switch network with an equivalent circuit that correctly predicts the low-frequency components of the switch network terminal waveforms
- Seminar addressed:
  - PWM converters in continuous and discontinuous conduction modes
  - PWM converters with current-programmed mode (CPM) control
  - Single-phase low-harmonic rectifiers (power-factor correctors)
- In each case, the large-signal averaged switch model can be used:
  - to develop steady-state and (by linearization) small-signal circuit models suitable for analysis
  - to construct Spice-compatible model implementations suitable for DC, Transient and AC simulations
- A number of PSpice model implementation examples and converter application examples were presented

# 7. Bibliography

---

## **Selected books:**

R.W. Erickson, *Fundamentals of Power Electronics*, Chpman & Hal, 1997.

Web page: <http://ece-www.colorado.edu/~pwrelect/book/bookdir.html>

J.G.Kassakian, M.F.Schlecht, G.C.Verghese, *Principles of Power Electronics*, Addison-Wesley, 1991.

A.Kislovski, R.Redl, N.Sokal, *Dynamic Analysis of Switched-Mode DC/DC Converters*, New York: Van Nostrand Reinhold, 1994.

P.T. Krein, *Elements of Power Electronics*, Oxford University Press, 1998.

Daniel M. Mitchel, *DC-DC Switching Regulator Analysis*, New York: McGraw-Hill, 1988.

N.Mohan, T.Undeland, W.Robbins, *Power Electronics: Converters, Applications and Design*, Second Edition, John Wiley & Sons, 1995.

S.M. Sandler, *SMPS Simulation with Spice 3*, McGraw Hill, 199.

# Bibliography (continued)

---

## **Selected papers on averaged modeling of switching power converters**

R. M. Bass, J. Sun, "Averaging under large-signal conditions," IEEE PESC 1998, pp. 630-632.

R.Erickson, M.Madigan, S.Singer, "Design of a simple high power factor rectifier based on the flyback converter," IEEE APEC, 1990, pp.792-801.

P. Krein, et al, "On the Use of Averaging for the Analysis of Power Electronic Systems," IEEE Transactions on Power Electronics, Vol. 5, No. 2, pp 182-190, April 1990.

K.Mahabir, G.Verghese, J.Thottuvelil, A.Heyman, "Linear averaged and sampled data models for large signal control of high power factor AC-DC converters," IEEE PESC, 1990, pp. 372-381.

D.Maksimovic, S.Cuk, "A unified analysis of PWM converters in discontinuous modes," IEEE Trans. on Power Electronics, Vol.6, No.3, July 1991.

D.Maksimovic, Y.Jang and R.Erickson, "Nonlinear-carrier control for high power factor boost rectifiers," IEEE Transactions on Power Electronics, Vol.11, No.4, July 1996, pp.578-584.

R.D.Middlebrook and Slobodan Cuk, "A general unified approach to modeling switching-converter power stages, International Journal of Electronics, Vol.42, No.6, pp.521-550, June 1977.

R.D.Middlebrook, "Topics in multiple-loop regulators and current-mode programming," IEEE PESC, 1985, pp. 716-732.

# Bibliography (continued)

---

## **Selected papers on averaged modeling of switching power converter (continued)**

R.D.Middlebrook, "Modeling current programmed buck and boost regulators," IEEE Trans. On Power Electronics, Vol.4, No.1, January 1989, pp.36-52.

S.R.Sanders, G.C.Verghese, "Synthesis of averaged circuit models for switched power converters," IEEE Transactions on Circuits and Systems, Vol.38, No.8, pp.905-915, August 1991.

S.Singer, R.W. Erickson, "Power source element and its properties," IEE Proceedings - Circuits Devices Systems, Vol.141, Np.3, pp.220-226, June 1994.

J.Sun, D.M.Mitchel, M.Greuel, P.T.Krain, R.M.Bass, "Averaged modeling of PWM converters in discontinuous conduction mode: a reexamination," IEEE PESC 1998, pp.615-622.

J.Sun, D.M.Mitchel, M.Greuel, P.T.Krain, R.M.Bass, "Averaged models for PWM converters in discontinuous conduction mode," HFPC 1998.

J.Sun, R.M.Bass, "Modeling and practical design issues for average current control," IEEE APEC 1999.

R. Tymerski and V. Vorperian, "Generation, classification and analysis of switched-mode DC-to-Dcconverters by the use of converter cells," INTELEC 1986, pp.181-195.

E. Van Dijk, H.J.N.Spruijt, D.M.O'Sullivan, J.B.Klaassens, "PWM switch modeling of DC/DC converters," IEEE Transactions on Power Electronics, Vol.10, No.6, November 1995, pp. 659-665.

# Bibliography (continued)

---

## **Selected papers on averaged modeling of switching power converter (continued)**

G. Verghese, C. Bruzos, K. Mahabir, "Averaged and sampled-data models for current mode control: a reexamination," IEEE PESC, 1989, pp.484-491.

V.Vorperian, R.Tymerski, F.C.Lee, "Equivalent circuit models for resonant and PWM switches," IEEE Transactions on Power Electronics, Vol.4, No.2, pp.205-214.

V.Vorperian, "Simplified analysis of PWM converters using the model of the PWM switch: Parts I and II," IEEE Transactions on Aerospace and Electronic Systems, Vol.AES-26, pp.490-505, May 1990.

G.W.Wester and R.D.Middlebrook, "Low-frequency characterization of switched Dc-Dc converters," IEEE Transactions on Aerospace and Electronic Systems, Vol.AES-9, pp.376-385, May 1973.

R.~Zane, D.~Maksimovic, ``Nonlinear-carrier control for high-power-factor rectifiers based on flyback, Cuk or Sepic converters," Proc. IEEE APEC, March 3-7, 1996, San Jose, CA, pp.814-820.

# Bibliography (continued)

---

## **Selected papers on averaged model implementation for computer simulation**

V. Bello, "Computer Aided Analysis of Switching Regulators Using SPICE2," IEEE PESC, 1980 Record, pp 3-11.

V. Bello, "Using The SPICE2 CAD Package for Easy Simulation of Switching Regulators in Both Continuous and Discontinuous Conduction Modes," Powercon 8, April, 1981, pp H3-1-14.

V. Bello, "Using the SPICE2 CAD Package to Simulate and Design the Current Mode Converter," Powercon 11, April 1984.

Y. Amran, F. Huliehel, S. Ben-Yaakov, "A unified SPICE compatible average model of PWM converters," IEEE Transactions on Power Electronics, Vol. 6, No. 4, pp. 585-594, 1991.

S. Ben-Yaakov, "Average simulation of PWM converters by direct implementation of behavioral relationships," IEEE APEC, pp.510-516, 1993.

S.Ben-Yaakov, D.Adar, "Average models as tools for studying dynamics of switch mode DC-DC converters," IEEE PESC 1994, pp.1369-1376

S. Ben-Yaakov, Z. Gaaton, "Generic SPICE compatible model of current feedback in switch mode converters, Electronics Letters, Vol. 28, No. 14, 2nd July 1992.

V.M.Canalli, J.A.Cobos, J.A.Oliver, J.Uceda, "Behavioral large signal averaged model for DC/DC switching power converters," IEEE PESC 1996.

# Bibliography (continued)

---

## **Selected papers on averaged model implementation for computer simulation**

D. Edry, M. Hadar, O. Mor, S. Ben-Yaakov, "A SPICE compatible model of tapped inductor PWM converter," IEEE APEC 1994, pp.1035-1041.

S. Hageman, "Behavioral Modeling and PSPICE Simulate SMPS Control Loops," PCIM, April 1990, pp 13-24 and May 1990, pp 47-50.

N. Jayaram, D. Maksimovic, "Power factor correctors based on coupled-inductor Sepic and Cuk converters with nonlinear-carrier control," IEEE APEC 1998.

D. Kimhi, S. Ben-Yaakov, "A SPICE model for current mode PWM converters operating under continuous inductor current conditions," IEEE Transactions on Power Electronics, Vol.6, No.2, pp.281-286, 1991.

R. Michelet and W. Roehr, "Evaluating Power Supply Designs with CAE Models" APEC 89, pp 323-334.

D. Monteith and D. Salcedo, "Modeling Feedforward PWM Circuits Using the Nonlinear Function Capabilities of SPICE II," Powercon 10, March 1983.