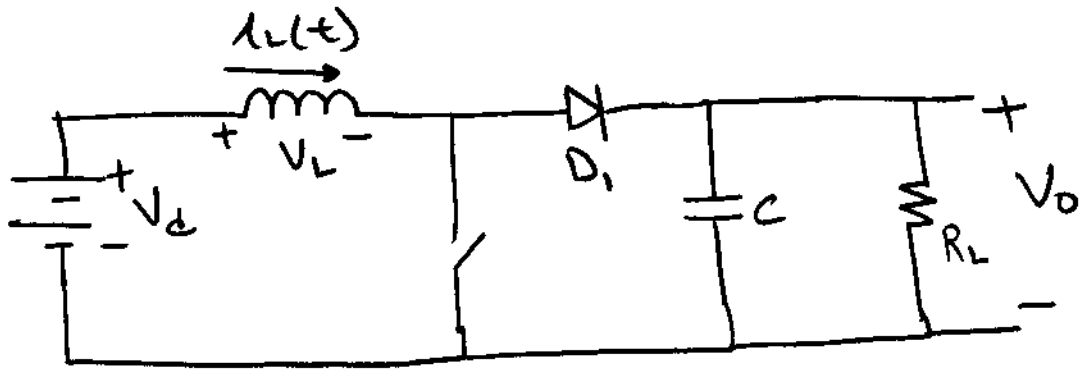



Boost Converter

(Step-Up) converter

$$V_o > V_d$$




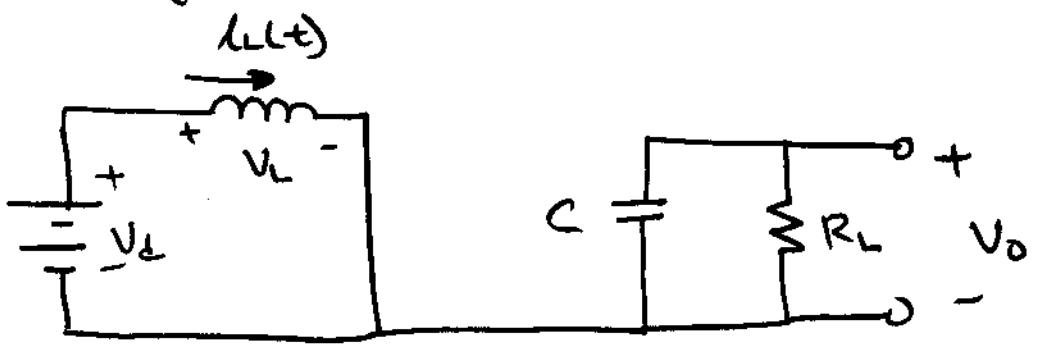During t_{on} : switch closed, $D = \text{off}$




- Inductor charges from V_d
- Capacitor supplies power to Load
- $V_L = V_d$
- Inductor current increases

During t_{off} : Switch open, $D_1 = on$

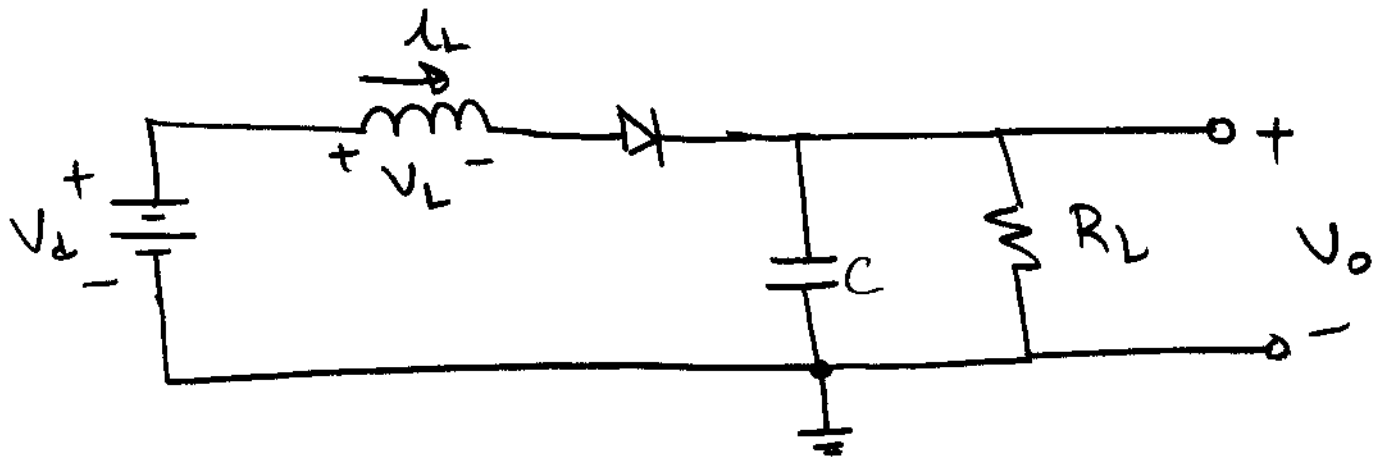

- Assume diode is ideal
- $V_L = V_d - V_o$; Since $V_o > V_d$,
the inductor current will decrease
- Inductor sources power to
C and R_L

Continuous mode

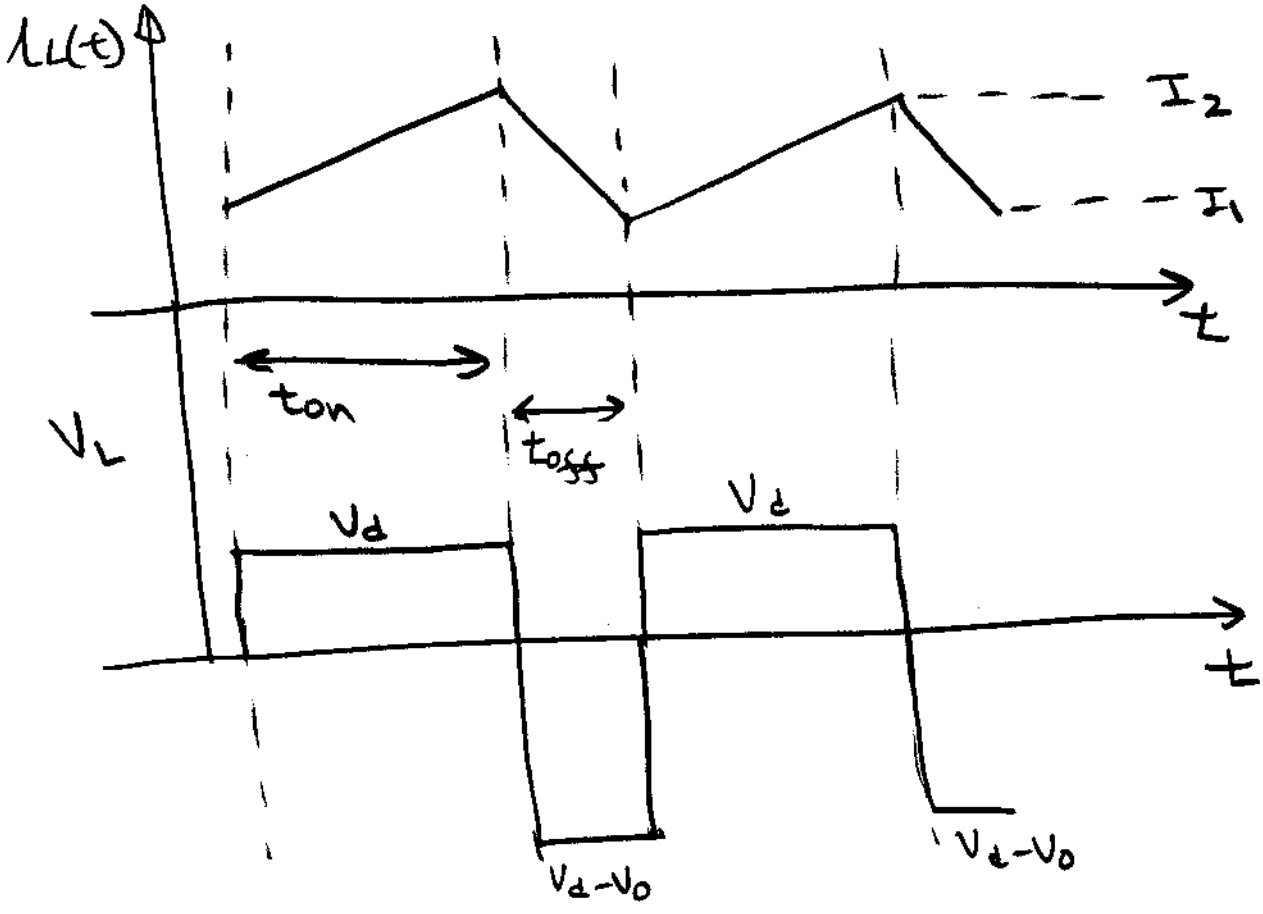

$$T_s = t_{on} + t_{off}$$

Since in steady state, the integral of $V_L = 0$ over one cycle

$$\int_{T_s} V_L(t) dt = 0$$

$$\Rightarrow (V_d t_{on}) + (V_d - V_o)(T_s - t_{on}) = 0$$

$$V_d T_s = V_o (T_s - t_{on})$$

$$V_o = V_d \left[\frac{T_s}{T_s + t_{on}} \right] = V_d \left[\frac{1}{1-D} \right] \quad (1)$$

$$\text{where } D = \frac{t_{on}}{T_s}$$

Assuming a lossless circuit

$$\text{Power}_{in} = \text{Power}_{out}$$

$$V_d I_o = V_o I_o \Rightarrow \frac{I_o}{I_o} = \frac{V_d}{V_o}$$

$$\text{OR } \frac{I_o}{I_o} = (1-D)$$

Where I_o = average input current

What does I_o look like?

$$I_o = i(t)$$

$$\text{SO } I_o = \frac{I_1 + I_2}{2} \quad (2) \quad \text{- Avg input current}$$

$$\text{SO } I_o = \frac{I_o}{1-D} \quad \text{--- from before}$$

30

$$\frac{I_1 + I_2}{2} = \frac{I_0}{1-D} \quad (3)$$

Now using $V_L = L \frac{di}{dt}$

$$i_L(t) = \frac{1}{L} \int V_L dt + i.c.$$

$$I_2 = \frac{1}{L} \int_0^{t_{on}} V_d dt + I_1$$

$$I_2 = \frac{V_d t_{on}}{L} + I_1$$

$$(I_2 - I_1) = \frac{V_d t_{on}}{L} \quad (4)$$

$$I_2 - I_1 = \frac{V_d t_{on}}{L}$$

$$\frac{I_1 + I_2}{2} = \frac{I_0}{1-D}$$

$$I_0 = \frac{I_1 + I_2}{2}$$

$$V_o = V_d \left[\frac{1}{1-D} \right]$$

Next: Find the boundary where the inductor current becomes discontinuous

$$\Rightarrow I_1 = 0$$

Solve for I_1

$$I_1 + I_2 = \frac{2I_0}{1-D} \quad (3)$$

$$I_2 - I_1 = \frac{V_d t_{on}}{L}$$

$$2I_1 = \frac{2I_0}{1-D} - \frac{V_d t_{on}}{L}$$

Solve for $I_1 = 0$

$$\frac{2I_0}{1-D} - \frac{V_d t_{on}}{L} = 0$$

$$I_0 = \left(\frac{V_d t_{on}}{2L} \right) (1-D)$$

From equation 1, $1-D = \frac{V_d}{V_0}$

So we need

$$I_0 \geq \left(\frac{V_d t_{on}}{2L} \right) \left(\frac{V_d}{V_0} \right)$$

Summary

Boost Regulator in continuous mode

$$V_o = V_d \left[\frac{1}{1-D} \right]$$

$$D = \frac{t_{on}}{T_s}$$

$$I_o = I_b [1-D]$$

$$t_{on} + t_{off} = T_s$$

$$\left(\frac{I_1 + I_2}{2} \right) = I_b = \frac{I_o}{1-D}$$

$$I_2 - I_1 = \frac{V_d t_{on}}{L}$$

$$I_o \geq \left(\frac{V_d t_{on}}{2L} \right) \left(\frac{V_d}{V_o} \right) \quad ; \quad \text{For continuous mode}$$


In continuous mode operation, the Boost Regulator has a right half plane zero.

This makes the boost Regulator difficult to stabilize in continuous mode.


Capacitor Rms Ripple Current


For the continuous Boost Converter

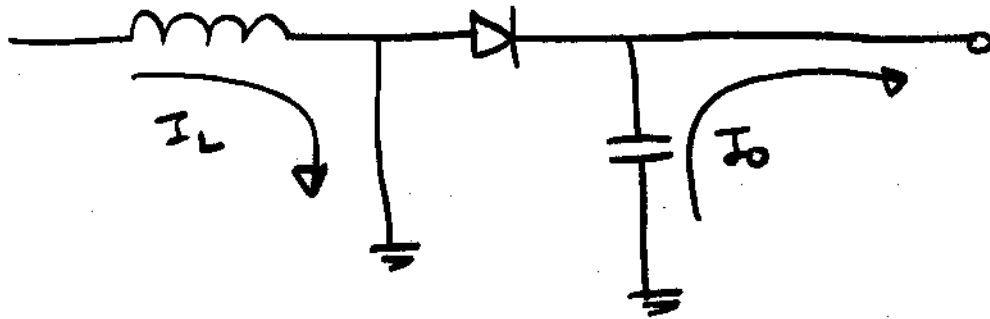-During T_{on} , The switch is on and the capacitor must supply current I_o to the load



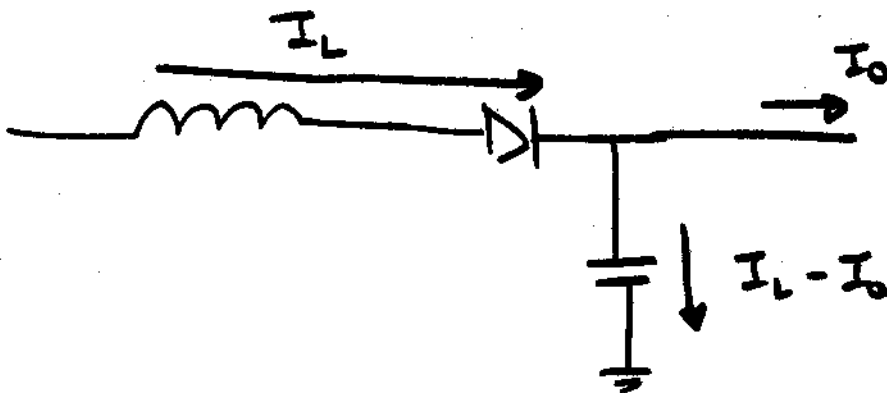-During T_{off} , The switch is off. The inductor provides I_o to the output and also charges the capacitor




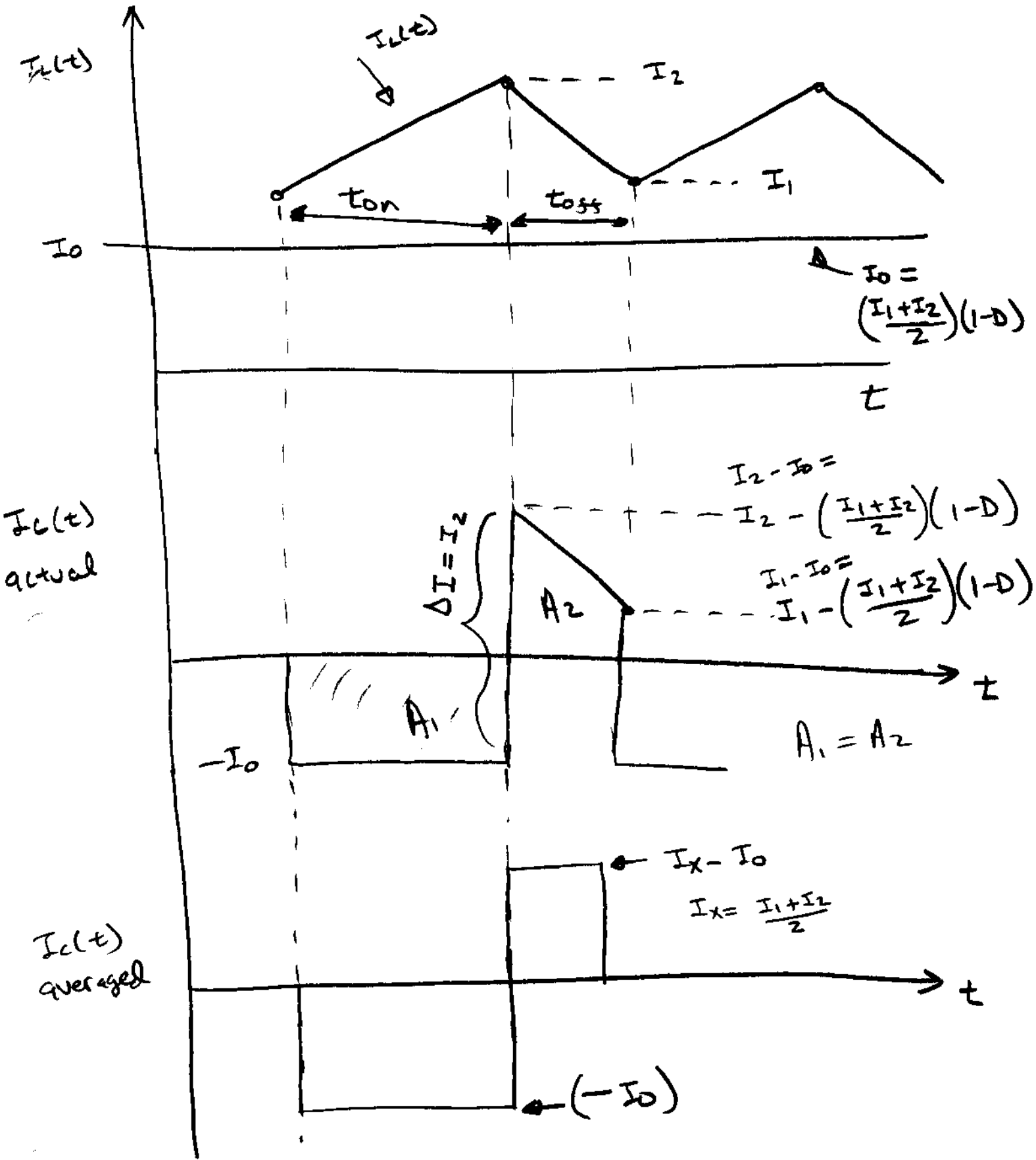

$$I_{RMS} = \sqrt{\frac{1}{T_s} \left[\int_0^{t_{on}} (-I_o)^2 dt + \int_{t_{on}}^{T_s} (I_x - I_o)^2 dt \right]}$$

Ripple Voltage due to ESR = $\Delta I R_{ESR}$

$$V_{RR} = I_2 R_{ESR}$$

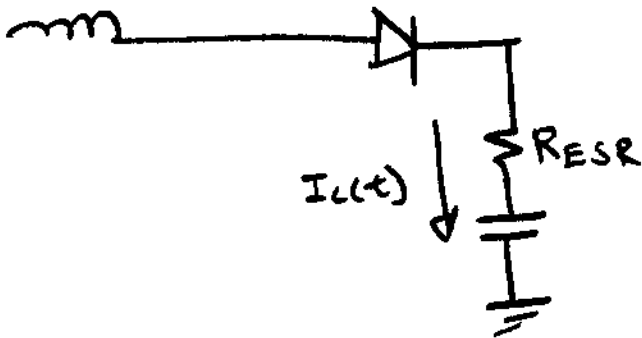

Ripple due to change in capacitor voltage

$$q = CV$$

$$\Delta V = \frac{\Delta q}{C} = \frac{I_o t_{on}}{C} \quad \leftarrow \text{put charge into } C$$

EE 456

Boost Regulator Design - Continuous Mode Operation

$$\mu\text{s} = 10^{-6} \cdot \text{sec}$$

Specify Input Voltage $V_D := 5 \cdot \text{volt}$

Specify Output Voltage $V_o := 50 \cdot \text{volt}$

Specify Switching Frequency $F_S := 20 \cdot \text{kHz}$

$$T_S := \frac{1}{F_S} \quad T_S = 50 \cdot \mu\text{s}$$

Specify the Assumed Efficiency $\text{Eff} := 90 \%$

Specify the Max output Current

The output Power is $P_{\text{out}} := \frac{10 \cdot \text{watt}}{\text{Eff}}$

The output current is $I_o := \frac{P_{\text{out}}}{V_o} \quad I_o = 0.222 \cdot \text{amp}$

Find T_{on} and T_{off}

$$T_{\text{off}} := 1 \cdot \mu\text{s} \quad T_{\text{on}} := 1 \cdot \mu\text{s}$$

Given

$$\frac{T_{\text{on}}}{T_S} = \frac{V_o - V_D}{V_o}$$

$$T_{\text{on}} + T_{\text{off}} = T_S$$

$$\begin{bmatrix} T_{\text{on}} \\ T_{\text{off}} \end{bmatrix} := \text{Find}(T_{\text{on}}, T_{\text{off}})$$

$$T_{\text{on}} = 45 \cdot \mu\text{s}$$

$$T_{\text{off}} = 5 \cdot \mu\text{s}$$

$$D := \frac{T_{\text{on}}}{T_S}$$

$$D = 90\%$$

Find the range of Inductors that will operate in continuous mode

Specify the minimum current we want the supply to operate in the continuous mode

$$I_{\min} := \frac{I_o}{10}$$

$$L := \frac{V_D \cdot T_{\text{on}}}{2 \cdot I_{\min}} \cdot \frac{V_D}{V_o}$$

For Continuous Mode, We need L greater than $L = 506.25 \mu\text{H}$

Choose the Inductor $L := 1 \cdot \text{mH}$

Find the Min and max inductor currents

$$I_1 := 1 \cdot \text{amp} \quad I_2 := 1 \cdot \text{amp}$$

Given

$$\frac{I_1 + I_2}{2} = \frac{I_o}{1 - D}$$

$$I_1 - I_2 = V_D \cdot \frac{T_{\text{on}}}{L}$$

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} := \text{Find}(I_1, I_2) \quad I_1 = 2.335 \cdot \text{amp} \quad I_2 = 2.11 \cdot \text{amp}$$

Choose the filter capacitor using Ripple voltage due to ESR and capacitor change in charge.

Specify the ripple voltage

$$V_{CR} := 20 \cdot \text{mV}$$

$$ESR := \frac{V_{CR}}{I_1} \quad ESR = 8.566 \cdot 10^{-3} \cdot \Omega$$

For all electrolytic caps, assume that $ESR \cdot C = 80 \mu\text{s}$

$$C_{ESR} := \frac{80 \cdot \mu\text{s}}{ESR} \quad C_{ESR} = 9.339 \cdot 10^3 \cdot \mu\text{F}$$

Choose the capacitor using the ripple voltage due to the change in charge

$$C_q := \frac{I_o \cdot T_{on}}{V_{CR}} \quad C_q = 500 \cdot \mu\text{F}$$

Choose Choose a standard cap value greater than both calculations

$$C := 10000 \cdot \mu\text{F}$$

Calculate the Capacitor RMS Ripple Current

$$I_x := \frac{I_1 + I_2}{2} \quad I_x = 2.222 \cdot \text{amp}$$

$$I_{\text{rms}} := \sqrt{\frac{1}{T_S} \left[\int_{0 \cdot \text{sec}}^{T_{on}} I_o^2 dt + \int_{T_{on}}^{T_S} (I_o - I_x)^2 dt \right]}$$

$$I_{\text{rms}} = 0.667 \cdot \text{amp}$$

Summary

$$L = 1 \cdot 10^3 \cdot \mu\text{H}$$

$$I_2 = 2.11 \cdot \text{amp}$$

$$I_1 = 2.335 \cdot \text{amp}$$

$$\frac{I_1 + I_2}{2} = 2.222 \cdot \text{amp}$$

$$T_{\text{on}} = 45 \cdot \mu\text{s}$$

$$T_{\text{off}} = 5 \cdot \mu\text{s}$$

$$V_D = 5 \cdot \text{volt}$$

$$V_o = 50 \cdot \text{volt}$$

$$I_o = 0.222 \cdot \text{amp}$$

$$C = 1 \cdot 10^4 \cdot \mu\text{F}$$



$$V_{\text{CR}} = 20 \cdot \text{mV}$$

$$I_{\text{rms}} = 0.667 \cdot \text{amp}$$

$$\text{Cap Voltage} = V_o = 50 \cdot \text{volt}$$


Boost Regulator

Discontinuous mode

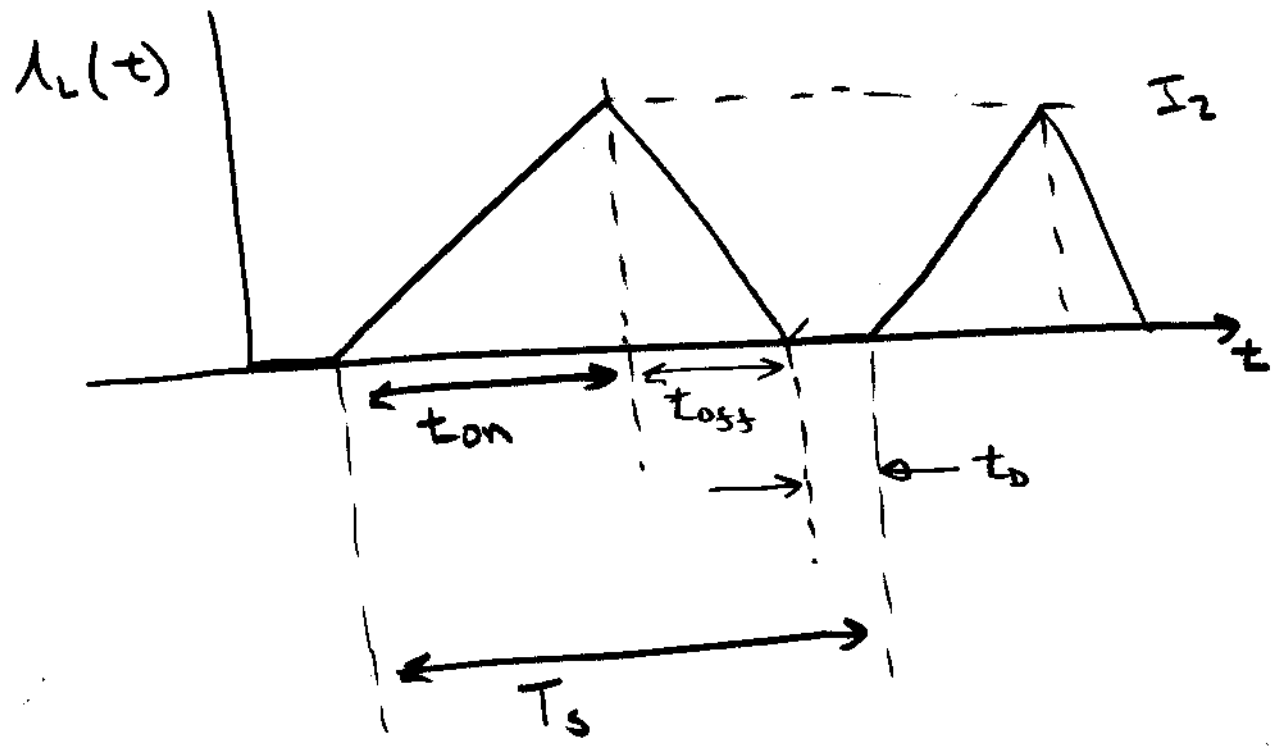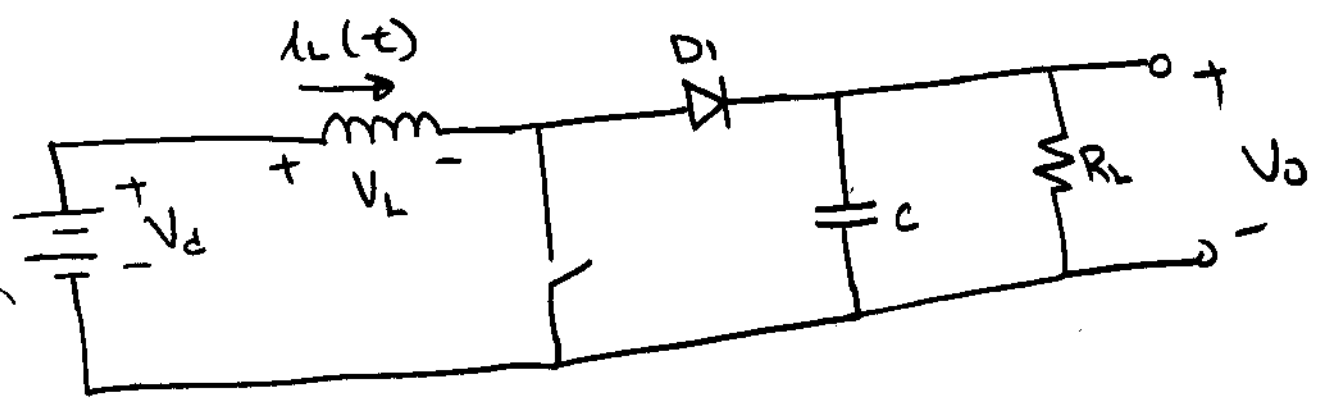

$t_0 = \text{dead Time}$

during t_{on} we have

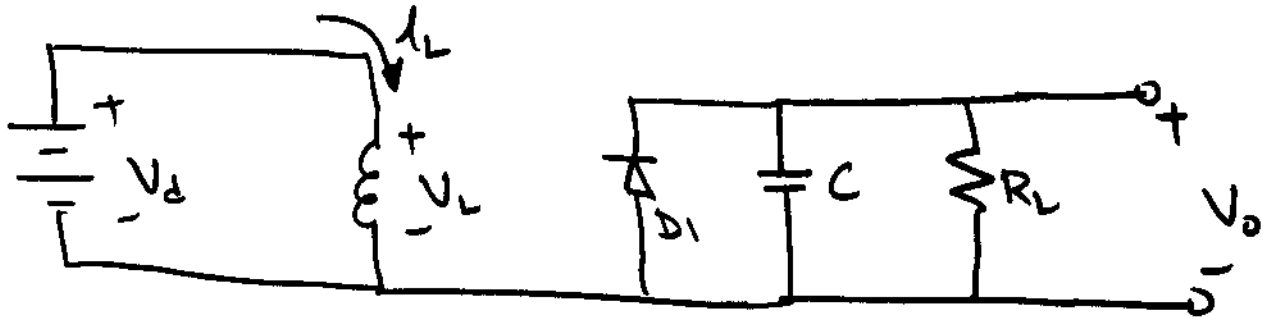

C supplies power to R_L

$D_1 = \text{off}$

$V_L = V_d$


for the inductor: $V_L = L \frac{dI_L(t)}{dt}$

$$I_L(t) = \frac{1}{L} \int_0^{t_{on}} V_L(t) dt$$

OR

$$I_2 = \frac{V_d t_{on}}{L} \quad (1)$$

During t_{off} we have

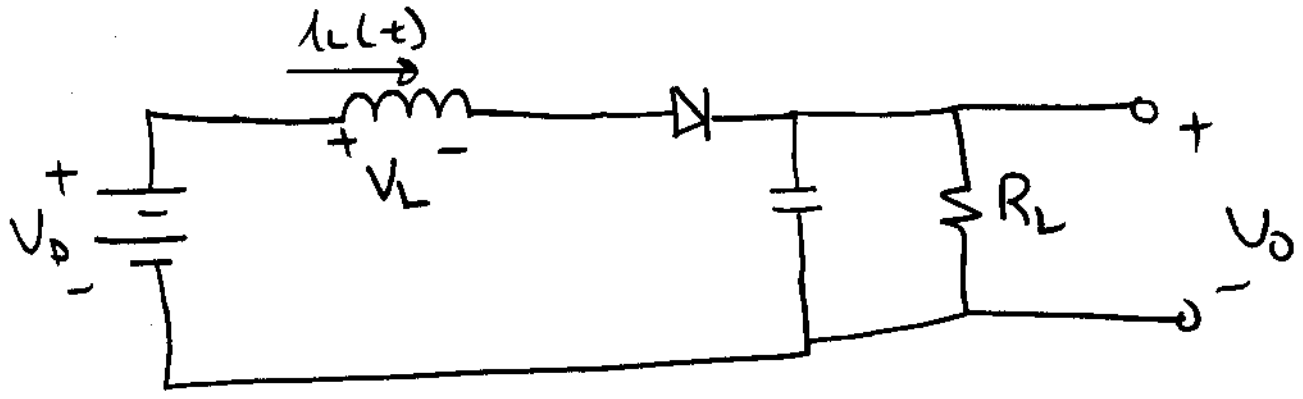

- Diode is ideal
- $D_1 = ON$
- $V_L = V_d - V_o$; $V_L < 0 \Rightarrow i_L(t) \downarrow$

For the inductor: $V_L = L \frac{di_L(t)}{dt}$

$$i_L(t) = \frac{1}{L} \int V_L(t) dt + I_a$$

OR

$$0 = \frac{1}{L} \int_{t_{on}}^{t_{on}+t_{off}} (V_d - V_o) dt + I_a$$

OR $I_a = \frac{V_o - V_d}{L} t_{off}$ (2)

To ensure discontinuous mode
 choose $t_d = 0.2 T_s$

$$\Rightarrow \boxed{t_{on} + t_{off} \leq 0.8 T_s} \quad (3)$$

Power balance: Avg power delivered
 by source

$$P_D = V_d \langle i_L \rangle$$

During $t_{on} + t_{off}$ $\langle \hat{i}_L \rangle = \frac{I_2}{2}$
 so over T_s

$$\langle i_L \rangle = \langle \hat{i}_L \rangle \frac{(t_{on} + t_{off})}{T_s}$$

$$= \frac{I_2}{2} \left[\frac{t_{on} + t_{off}}{T_s} \right]$$

OR

$$P_D = \frac{V_d I_2}{2} \left[\frac{t_{on} + t_{off}}{T_s} \right]$$

and from equation ①, $I_2 = \frac{V_d t_{on}}{L}$

$$P_D = \frac{V_d^2 t_{on}}{2LT_s} [t_{on} + t_{off}]$$

Output power $P_o = V_o I_o$

so $P_o = P_D$


$$V_o = \frac{V_d^2 t_{on}}{2LT_s I_o} [t_{on} + t_{off}] \quad \text{④}$$

Energy balance

- Energy dissipated in Load for Entire cycle

$$E_o = V_o I_o T_s$$

DURING Loss

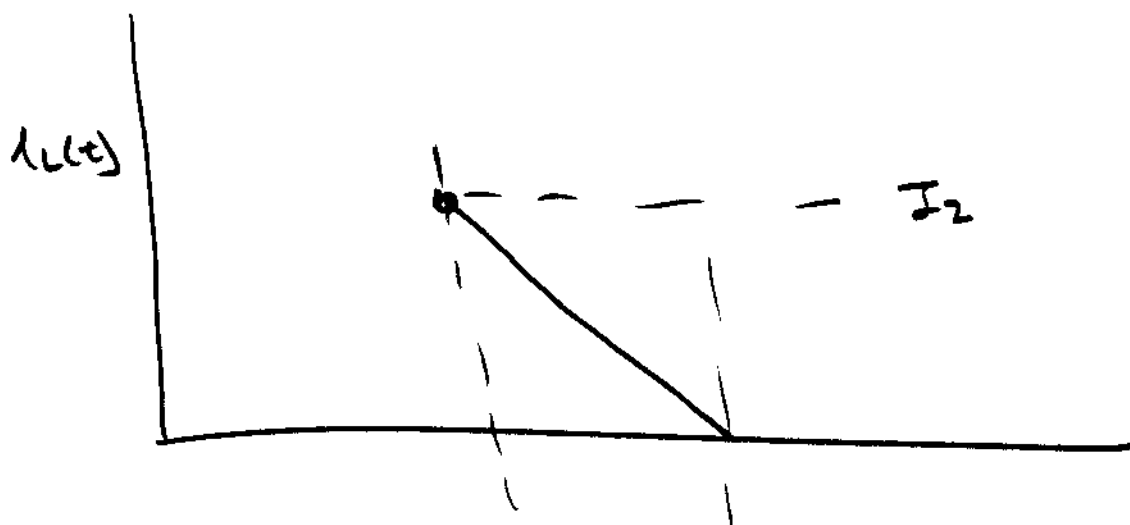

- all energy stored in L is delivered to Load

- Source V_d delivers energy to Load

$$E_L = \frac{1}{2} L I_0^2$$

$$I_0 = \frac{V_d t_{on}}{L}$$

$$\Rightarrow E_L = \frac{1}{2L} V_d^2 t_{on}^2$$

Now Find Energy delivered by the source

$$E_s = V_d \langle I_d \rangle t_{off}$$

$$\langle I_d \rangle = \frac{I_2}{2} = \frac{V_d t_{on}}{2L}$$

so

$$E_s = V_d \langle I_d \rangle t_{off} = \frac{V_d^2 t_{on}}{2L} t_{off}$$

so for energy balance

$$E_L + E_s = E_o$$

$$\frac{1}{2L} V_d^2 t_{on}^2 + \frac{1}{2L} V_d^2 t_{on} t_{off} = V_o I_o T_s$$

OR

$$\frac{1}{2L} V_d^2 t_{on} [t_{on} + t_{off}] = V_o I_o T_s$$

Same as power balance.

Boost Regulator Summary

Discontinuous mode

$$\begin{aligned}
 I_a &= \frac{V_d t_{on}}{L} \\
 I_a &= \left(\frac{V_o - V_d}{L} \right) t_{off}
 \end{aligned}
 \left. \vphantom{\begin{aligned} I_a &= \frac{V_d t_{on}}{L} \\ I_a &= \left(\frac{V_o - V_d}{L} \right) t_{off} \end{aligned}} \right\} \frac{t_{on}}{t_{off}} = \frac{V_o - V_d}{V_d}$$

$$t_{on} + t_{off} \leq 0.8 T_s$$


$$V_o = \frac{V_d^2 t_{on}}{2LT_s I_o} \left[t_{on} + t_{off} \right]$$

$$I_o \leq \left(\frac{V_d t_{on}}{2L} \right) \left(\frac{V_d}{V_o} \right) \quad \text{for discontinuous mode}$$


Boost Converter Discontinuous mode

Capacitor Rms Ripple current

— Inductor Current

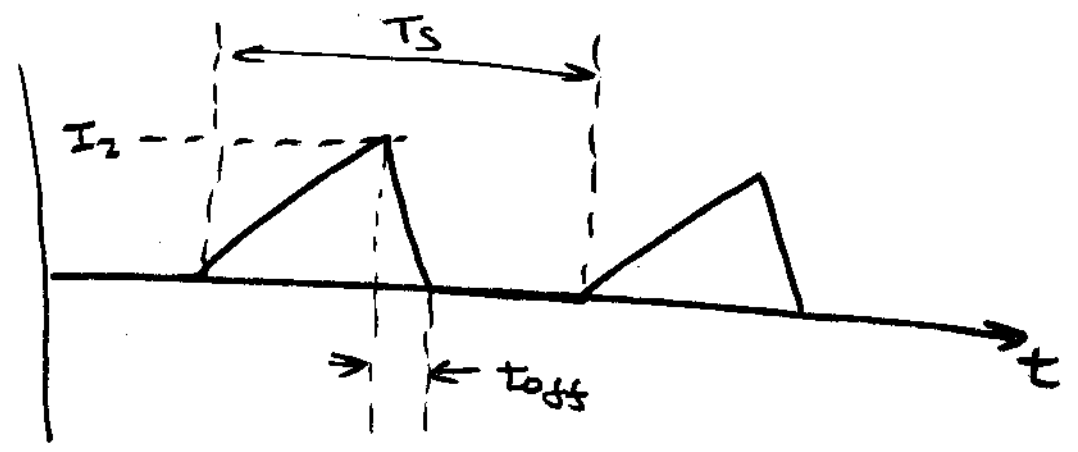

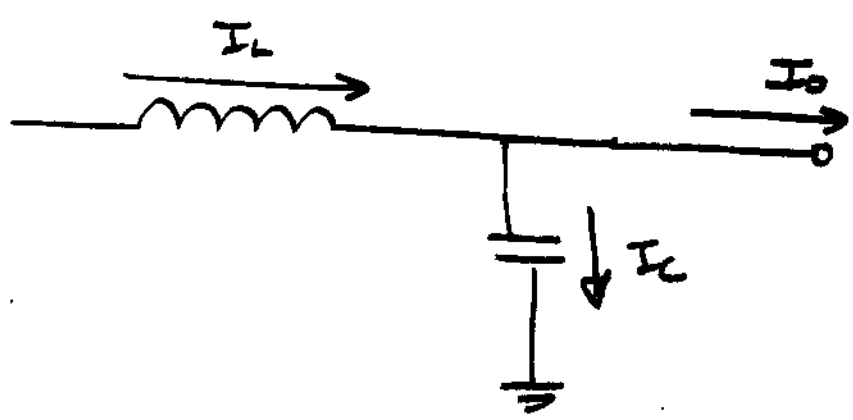- During t_{off} , The inductor supplies I_o and charges the Capacitor




$$I_c = I_L - I_o$$

During t_{off} , the average inductor current is

$$I_x = \frac{I_2}{2}$$

Capacitor current

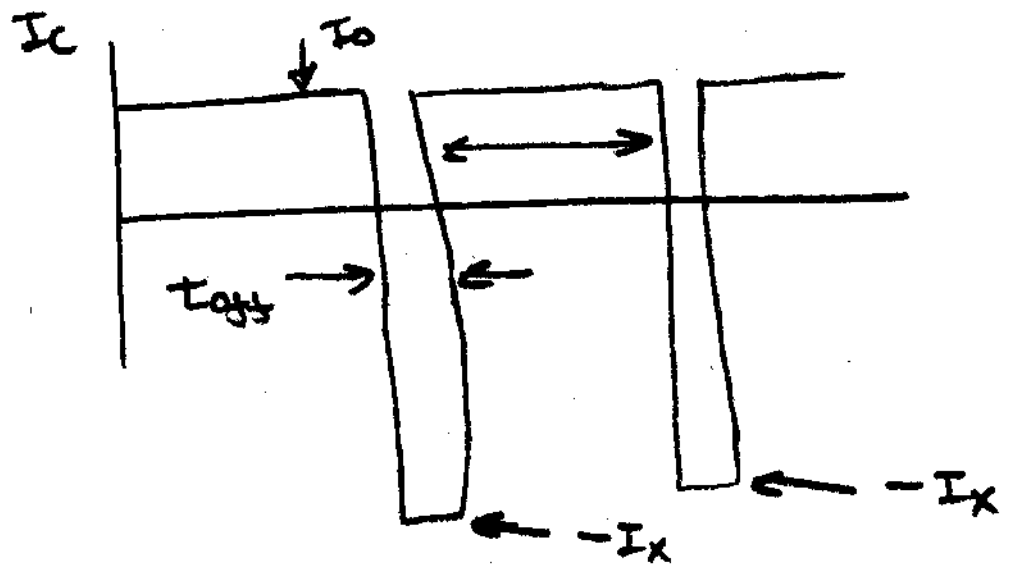

$$I_{RMS} = \sqrt{\frac{1}{T_S} \left[\int_0^{T_S - t_{off}} I_0^2 dt + \int_0^{t_{off}} (-I_x)^2 dt \right]}$$

EE 456

Boost Regulator Design - Discontinuous Mode Operation

Specify Output Voltage $V_o := 50 \cdot \text{volt}$ $\mu\text{S} = 10^{-6} \cdot \text{sec}$

Specify Input Voltage $V_D := 5 \cdot \text{volt}$

Specify Switching Frequency $F_S := 20 \cdot \text{kHz}$

$$T_S := \frac{1}{F_S} \quad T_S = 5 \cdot 10^{-5} \cdot \text{sec}$$

Specify the Max Output Power and Efficiency $P_{\text{out}} := 10 \cdot \text{watt}$ $\text{Eff} := 90 \cdot \%$

Calculated the power for the design

$$P_{\text{design}} := \frac{P_{\text{out}}}{\text{Eff}} \quad P_{\text{design}} = 11.111 \cdot \text{watt}$$

Calculate the output current

$$I_{\text{out}} := \frac{P_{\text{design}}}{V_o} \quad I_{\text{out}} = 0.222 \cdot \text{amp}$$

Find T_{on} and T_{off}

$$T_{\text{off}} := 1 \cdot \text{sec} \quad T_{\text{on}} := 1 \cdot \text{sec}$$

Given

$$\frac{T_{\text{on}}}{T_{\text{off}}} = \frac{V_o - V_D}{V_D}$$

$$T_{\text{on}} + T_{\text{off}} = 0.8 \cdot T_S$$

$$\begin{bmatrix} T_{\text{on}} \\ T_{\text{off}} \end{bmatrix} := \text{find}(T_{\text{on}}, T_{\text{off}})$$

$$T_{\text{on}} = 36 \cdot \mu\text{S}$$

$$T_{\text{off}} = 4 \cdot \mu\text{S}$$

Find the range of Inductors that will operate in discontinuous mode

$$L := \frac{V_D \cdot T_{\text{on}}}{2 \cdot I_{\text{out}}} \cdot \frac{V_D}{V_o}$$

For Discontinuous Mode, We need L less than

$$L = 40.5 \cdot \mu\text{H}$$

Find the inductor Value

$$L := \frac{V_D^2 \cdot T_{\text{on}}}{2 \cdot V_o \cdot T_S \cdot I_{\text{out}}} \cdot (T_{\text{on}} + T_{\text{off}})$$

$$L = 32.4 \cdot \mu\text{H}$$

Choose a standard size inductor

$$L := 30 \cdot \mu\text{H}$$

Find the peak current

$$I_2 := V_D \cdot \frac{T_{\text{on}}}{L} \quad I_2 = 6 \cdot \text{amp}$$

Choose the filter capacitor.

Assume that the major component of the ripple comes from the capacitor ESR

Specify the ripple due to the ESR $V_{\text{RR}} := .05 \cdot \text{volt}$

$$\text{ESR} := \frac{V_{\text{RR}}}{(I_2)} \quad \text{ESR} = 0.00833 \cdot \Omega$$

For all electrolytic caps, assume that $\text{ESR} \cdot C = 80 \mu\text{s}$

$$C := \frac{80 \cdot 10^{-6} \cdot \text{sec}}{\text{ESR}} \quad C = 9.6 \cdot 10^3 \cdot \mu\text{F}$$

Choose the next size std capacitor $C := 10000 \cdot \mu\text{F}$

$$\text{ESR} := \frac{80 \cdot 10^{-6} \cdot \text{sec}}{C}$$

Calculate the new ESR with the chosen capacitor

$$\text{ESR} = 8 \cdot 10^{-3} \cdot \Omega$$

Calculate the Capacitor RMS Ripple Current

$$I_x := \frac{I_2}{2} \quad I_x = 3 \cdot \text{amp}$$

$$I_{\text{rms}} := \sqrt{\frac{1}{T_S} \left[\int_{0 \cdot \text{sec}}^{T_{\text{on}}} I_{\text{out}}^2 dt + \int_{T_{\text{on}}}^{T_S} (I_{\text{out}} - I_x)^2 dt \right]}$$

$$I_{\text{rms}} = 1.482 \cdot \text{amp}$$

Summary



$$L = 30 \cdot \mu\text{H} \quad I_2 = 6 \cdot \text{amp}$$

$$T_{\text{on}} = 36 \cdot \mu\text{S} \quad T_{\text{off}} = 4 \cdot \mu\text{S}$$

$$V_D = 5 \cdot \text{volt} \quad V_o = 50 \cdot \text{volt} \quad I_{\text{out}} = 0.222 \cdot \text{amp}$$

$$C = 1 \cdot 10^4 \cdot \mu\text{F} \quad V_{\text{RR}} = 50 \cdot \text{mV} \quad I_{\text{rms}} = 1.482 \cdot \text{amp}$$

Cap Voltage $V_o = 50 \cdot \text{volt}$

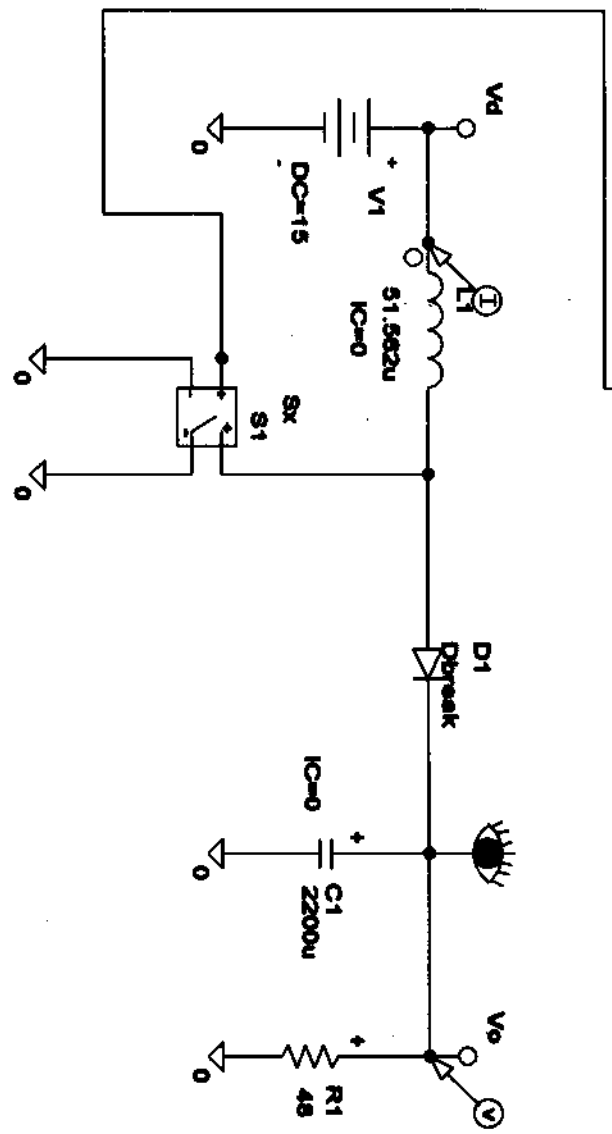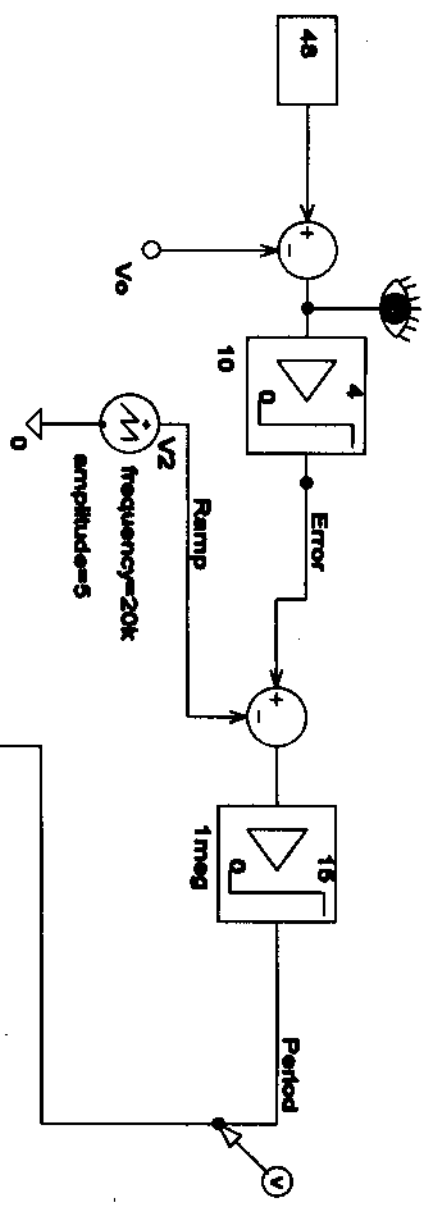


← Should add the
Double-pulse
Suppression CKT

Date/Time run: 09/10/95 22:18:57

* C:\MAD\CLASS\EGR488\SPICE\BOOST\CONT2.SCH

Temperature: 27.0

(A) CONT2.DAT

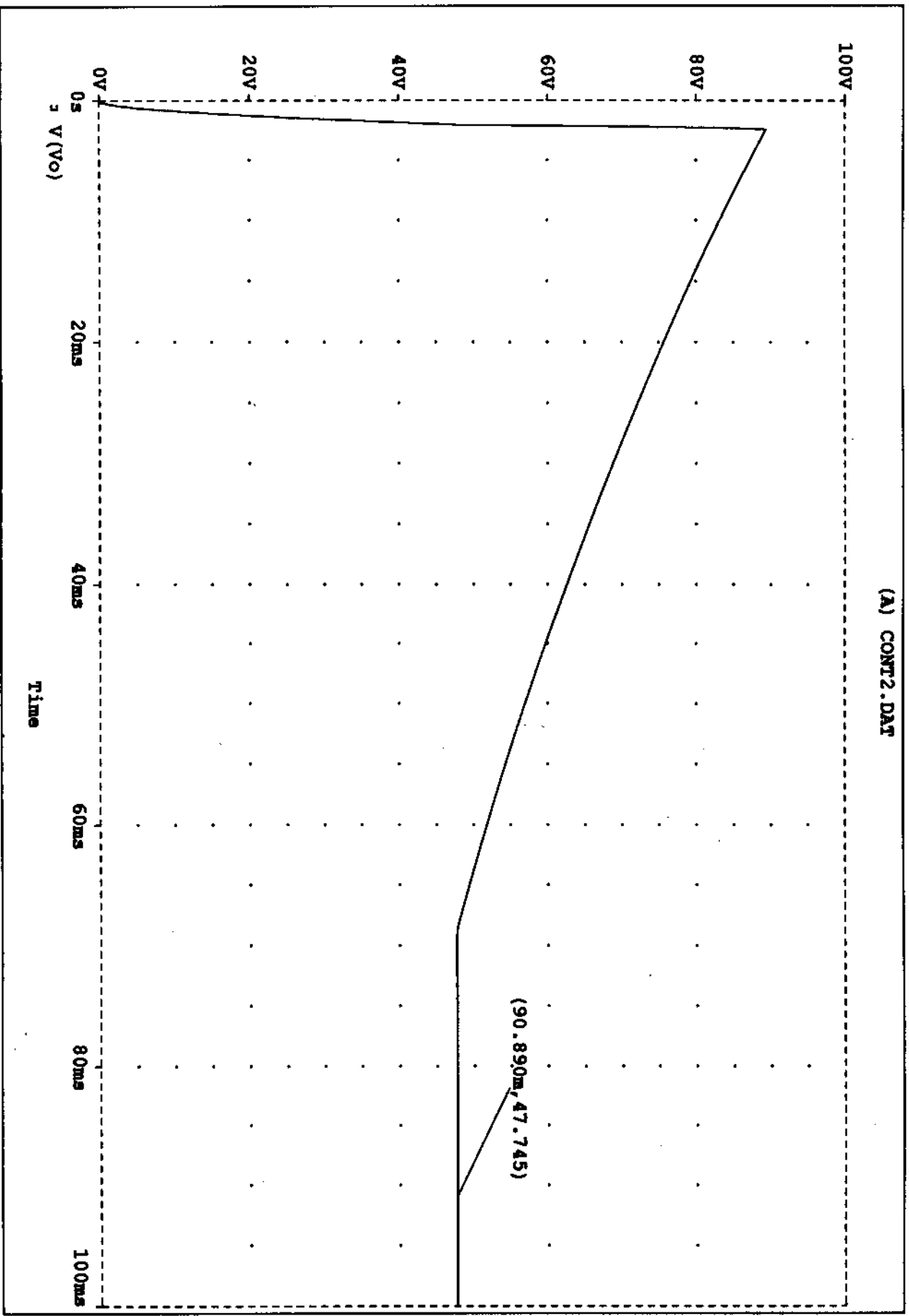

Date: September 10, 1995

Page 2

Time: 22:56:45


123

Date/Time run: 09/10/95 22:18:57

Temperature: 27.0

* C:\NAD\CLASS\EGR488\SPICE\BOOST\CONT2.SCH

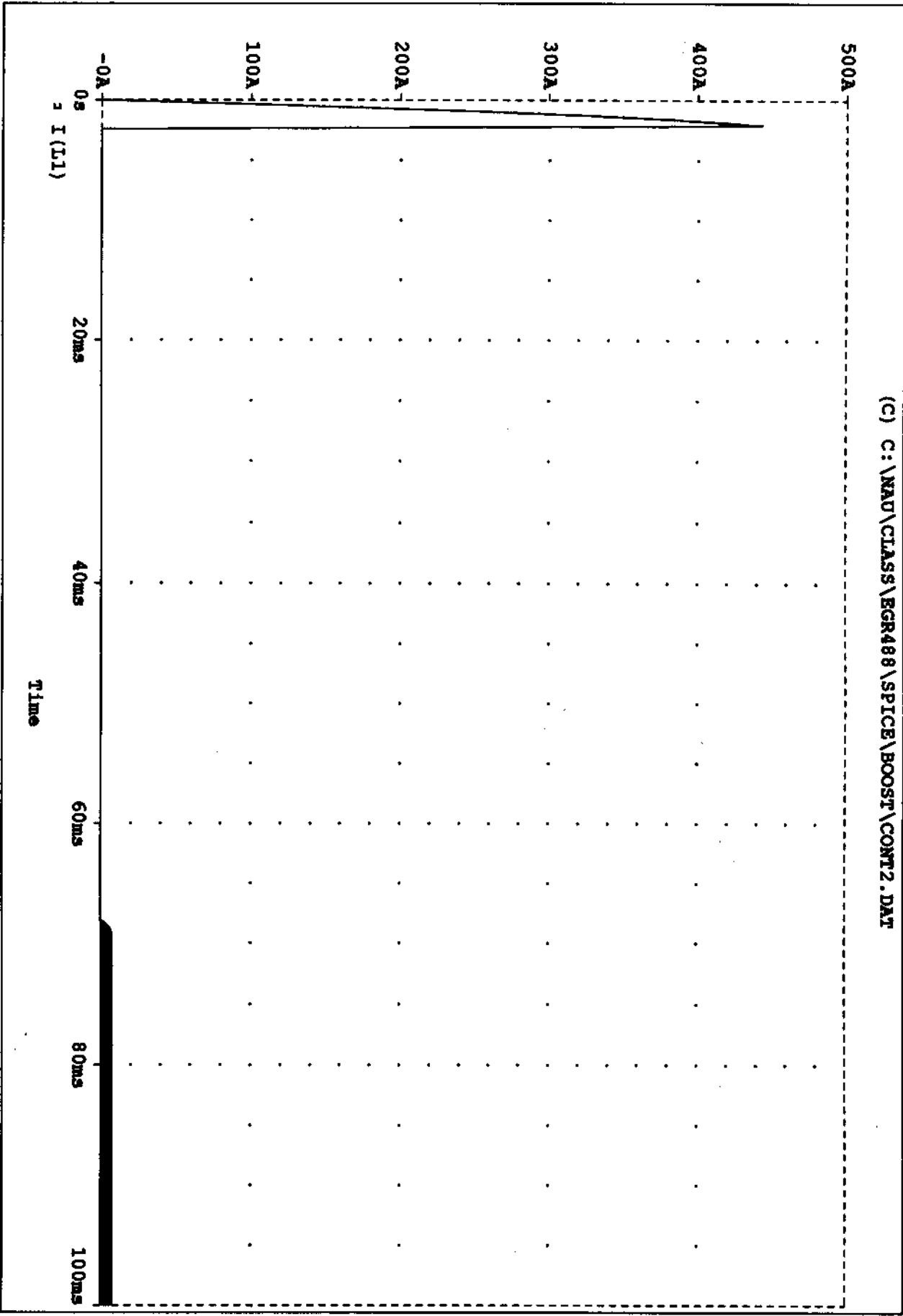(C) C:\NAD\CLASS\EGR488\SPICE\BOOST\CONT2.DAT



Date: September 10, 1995

Page 1


Time: 22:58:46

Date/Time run: 09/10/95 22:18:57

* C:\NAU\CLASS\EGR488\SPICE\BOOST\CONT2.SCH

Temperature: 27.0



(B) CONT2.DAT

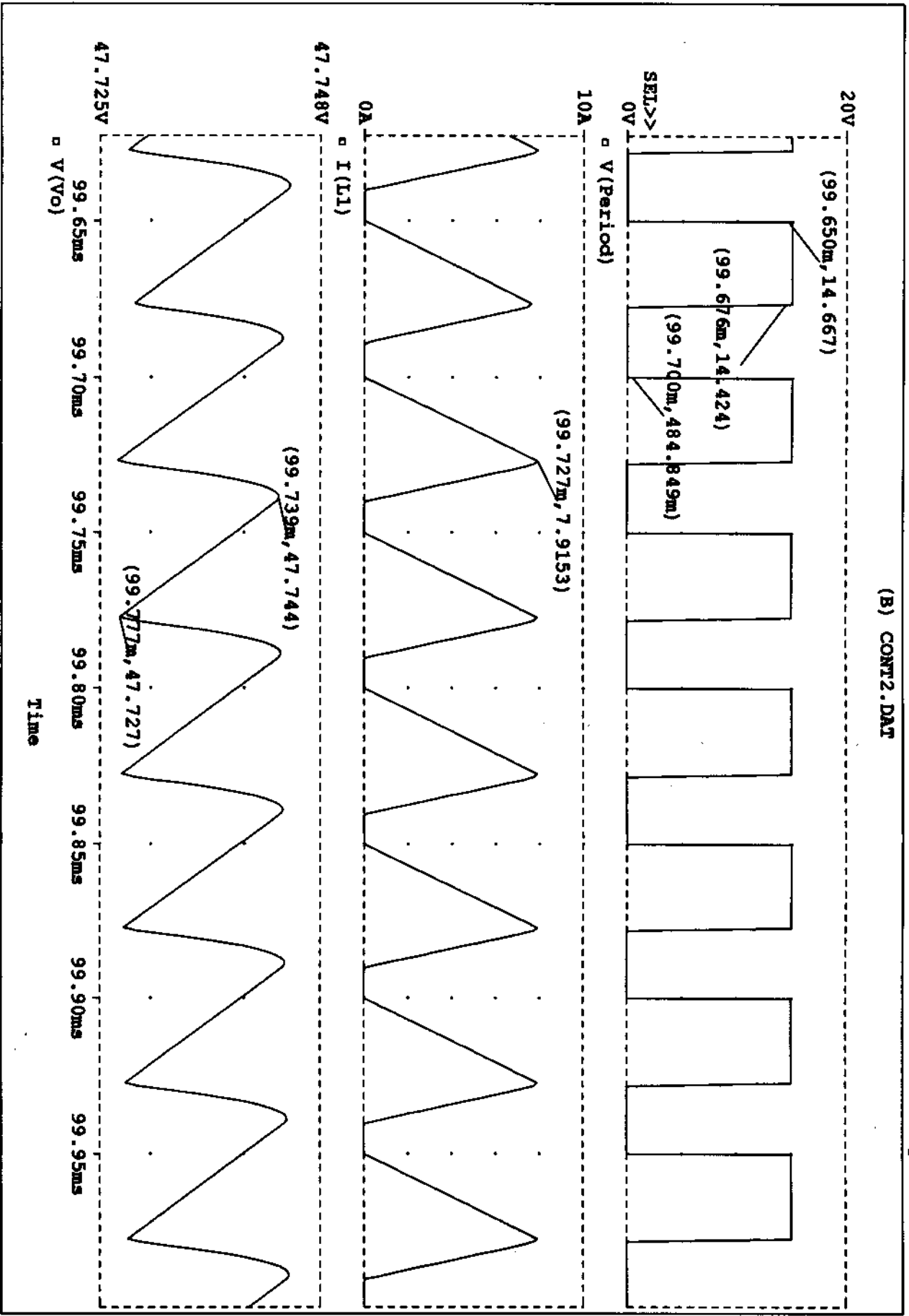

Date: September 10, 1995

Page 1

Time: 22:56:17

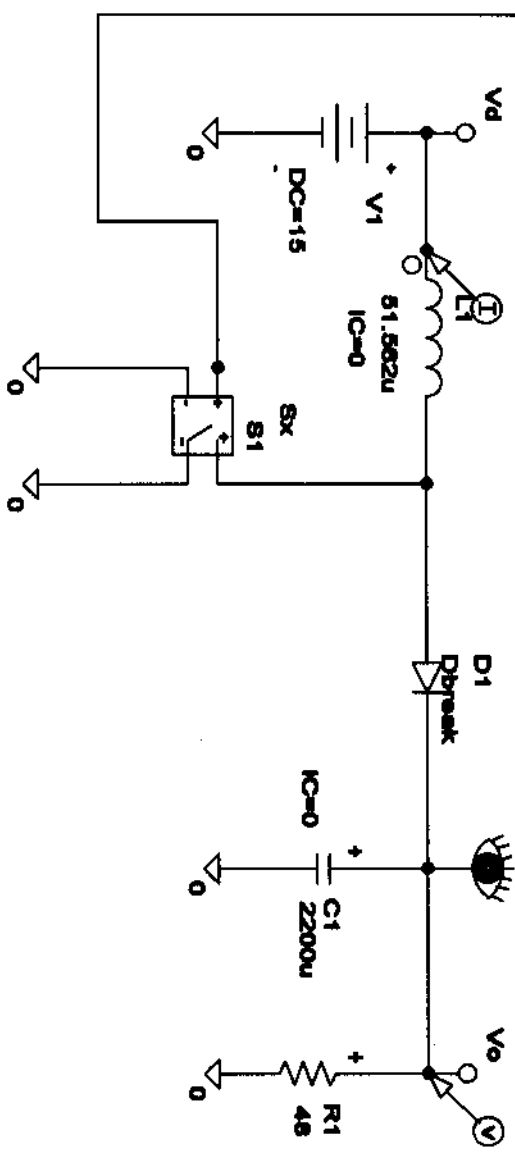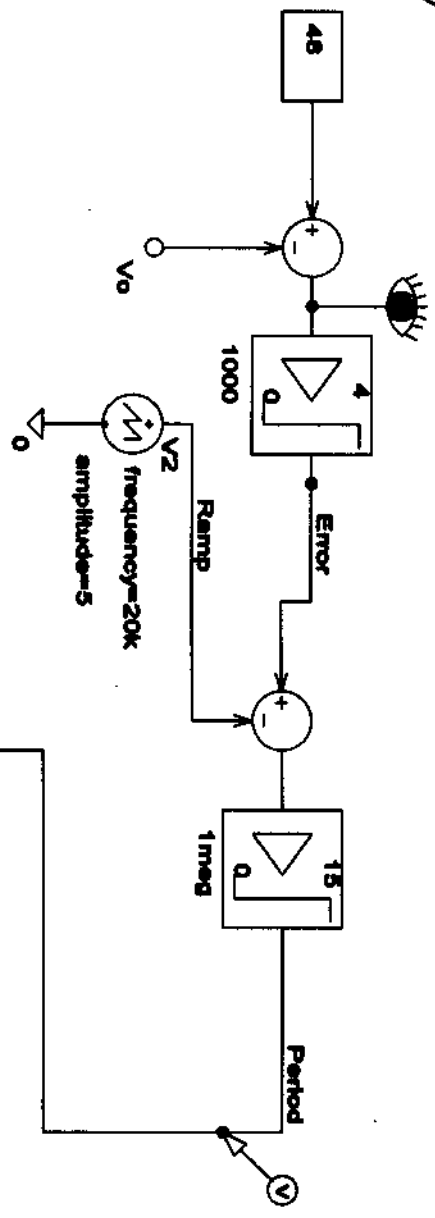


Should add the
Double-pulse
Suppression CKT

Date/Time run: 09/11/95 06:42:24

Temperature: 27.0

* C:\NAD\CLASS\EGR488\SPICE\BOOST\CONT2.SCH

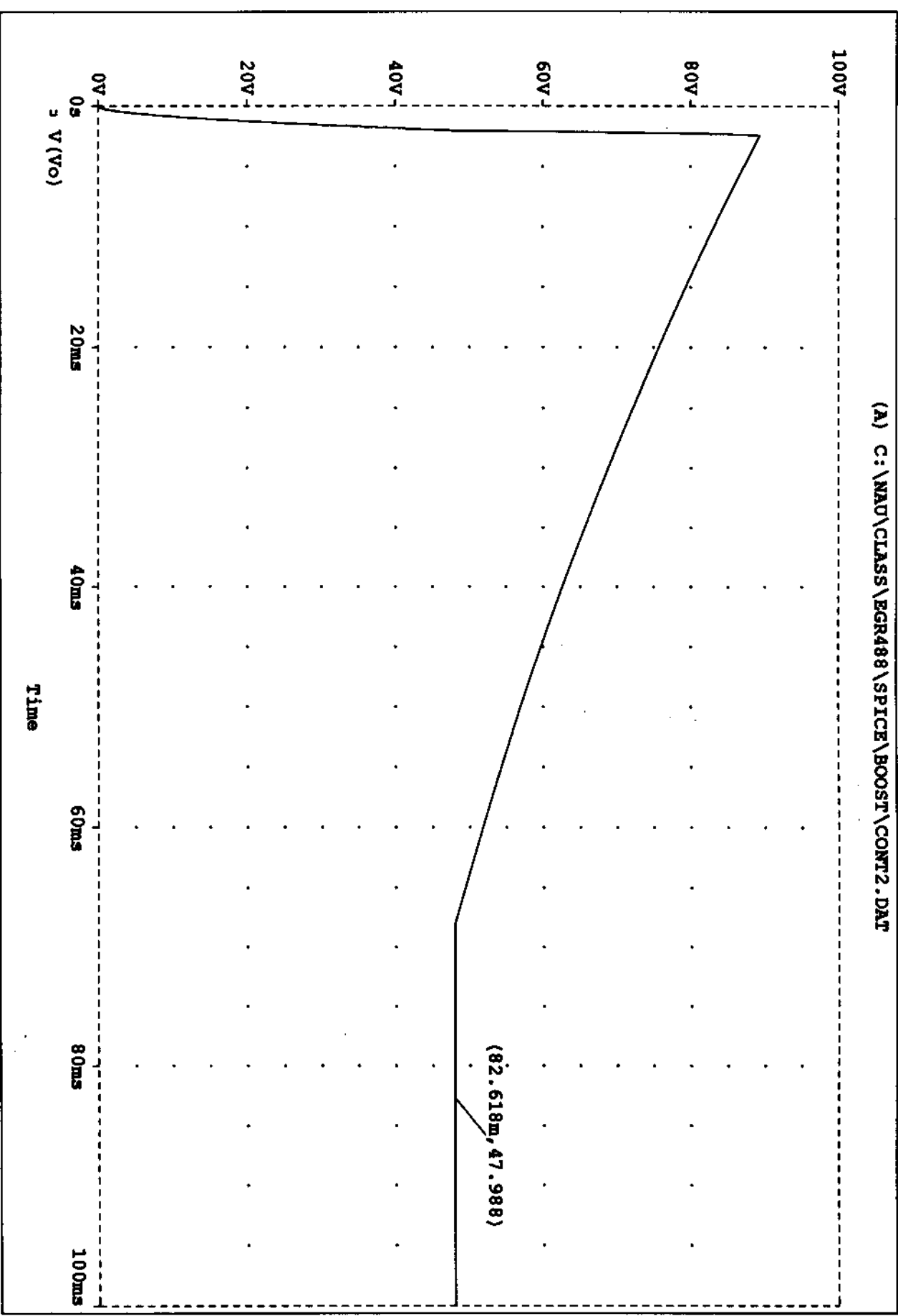(A) C:\NAD\CLASS\EGR488\SPICE\BOOST\CONT2.DAT



Date: September 11, 1995

Page 1

Time: 07:22:47


127

Date/Time run: 09/11/95 06:42:24

Temperature: 27.0

* C:\NAD\CLASS\EGR488\SPICE\BOOST\CONT2.SCH

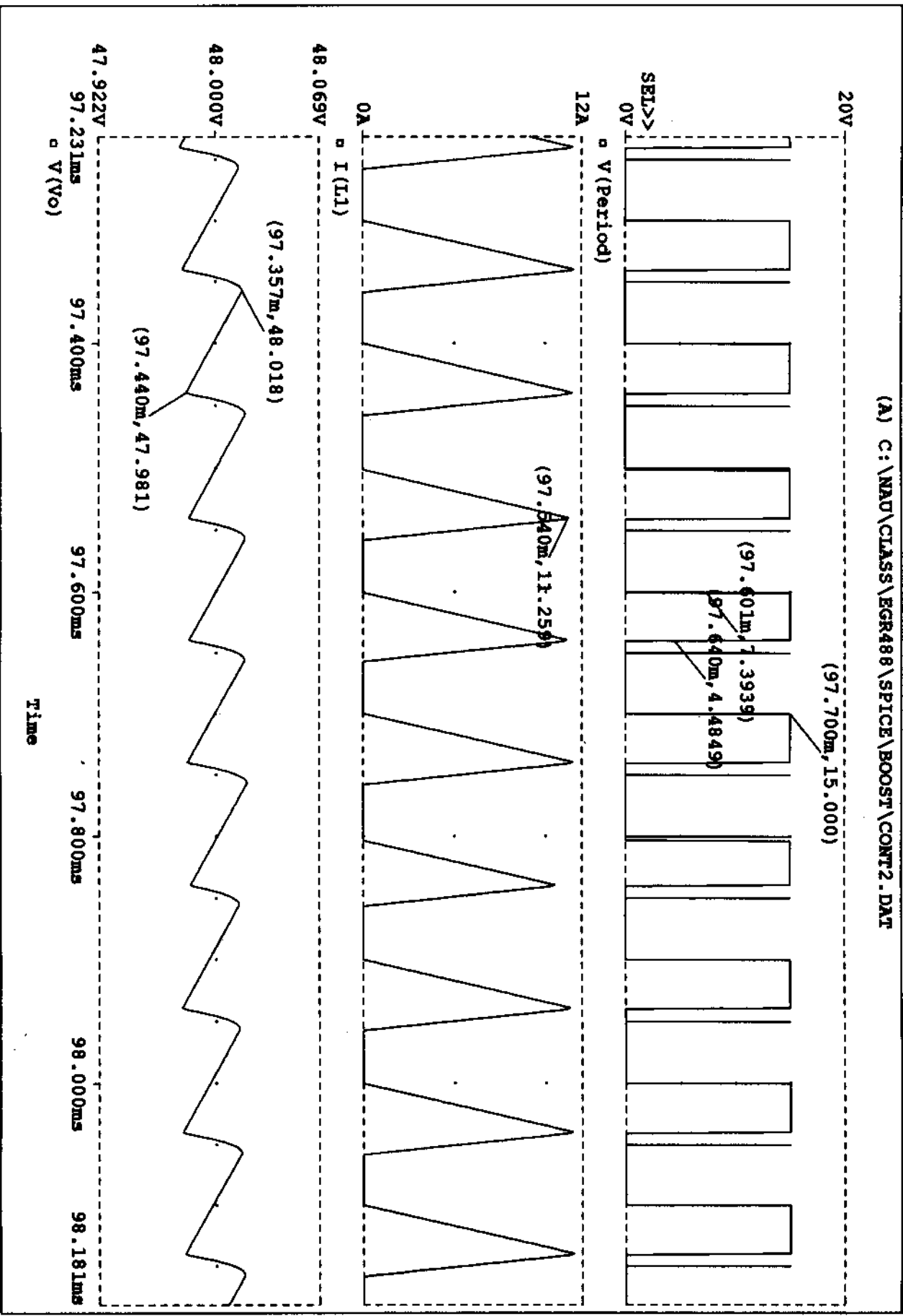(A) C:\NAD\CLASS\EGR488\SPICE\BOOST\CONT2.DAT




Date: September 11, 1995

Page 1

Time: 07:31:38

WORST case Design

Variable V_{in}

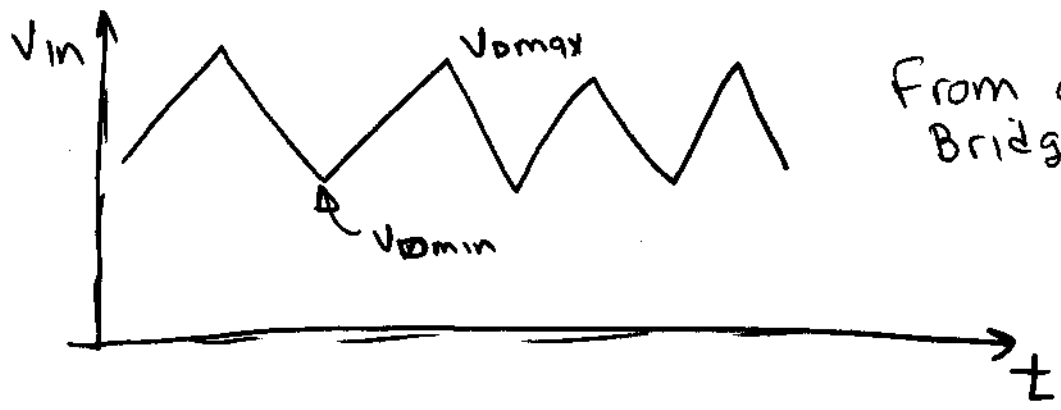

From a Bridge Rect.

$$t_{on} = \frac{I_2 L}{V_d}$$

⇒ The smaller V_d is, The longer it takes to Reach I_2 .

- we are usually concerned with energy transfer $\frac{1}{2} L I_2^2$

- we would like to charge L up to I_2 . The smaller V_d is, the longer t_{on} must be to achieve I_2

⇒ Design with $V_{in\ min}$

$$t_{on-max} = \frac{I_2 L}{V_{dmin}}$$

Variable V_o (Variable Supply)

$$t_{\text{off}} = \frac{I_2 L}{(V_o - V_d)} \quad ; \quad V_o > V_d$$

- During t_{off} we must completely discharge the inductor.

- The smaller $|V_o - V_d|$, the longer t_{off} must be to discharge the inductor

$$t_{\text{off-max}} = \frac{I_2 L}{(V_{\text{omin}} - V_{\text{emax}})}$$

and

$$(t_{\text{on-max}} + t_{\text{off-max}}) = 0.8 T_s$$