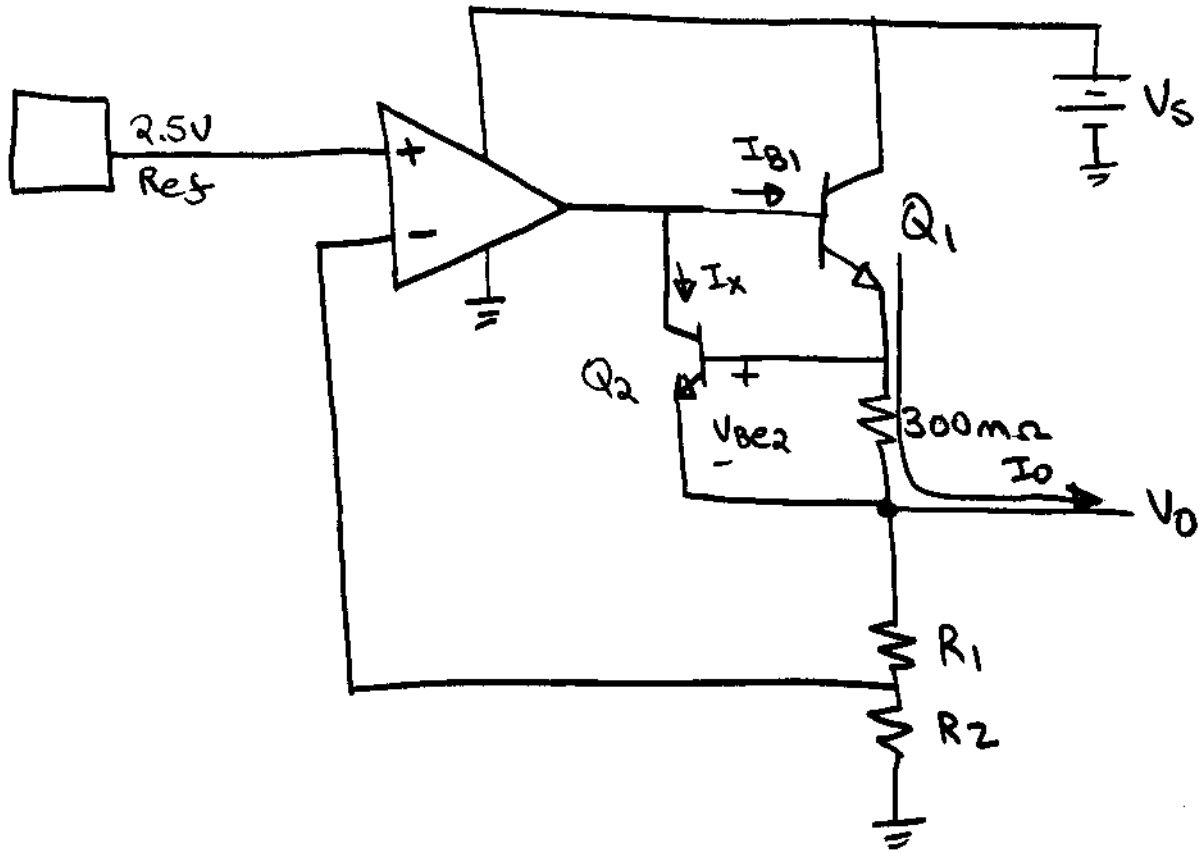


Short circuit protection ?



- when $I_o = 1A$, $V_{be2} \approx 0.3V \Rightarrow I_x = 0$

- when $I_o > 1A$, $V_{be2} > 0.3V$, I_x increases

- as $I_o \uparrow$, $I_x \uparrow$, $I_{B1} \downarrow \Rightarrow I_o \downarrow$

\Rightarrow at some safe value of I_o
The ckt stabilizes & $I_o = \text{const} > 1A$

57B


568

Date/Time run: 08/29/95 21:20:19

* C:\NAU\CLASS\BGR488\SPICE\LIN_REG\OPAMP2.SCH

Temperature: 27.0

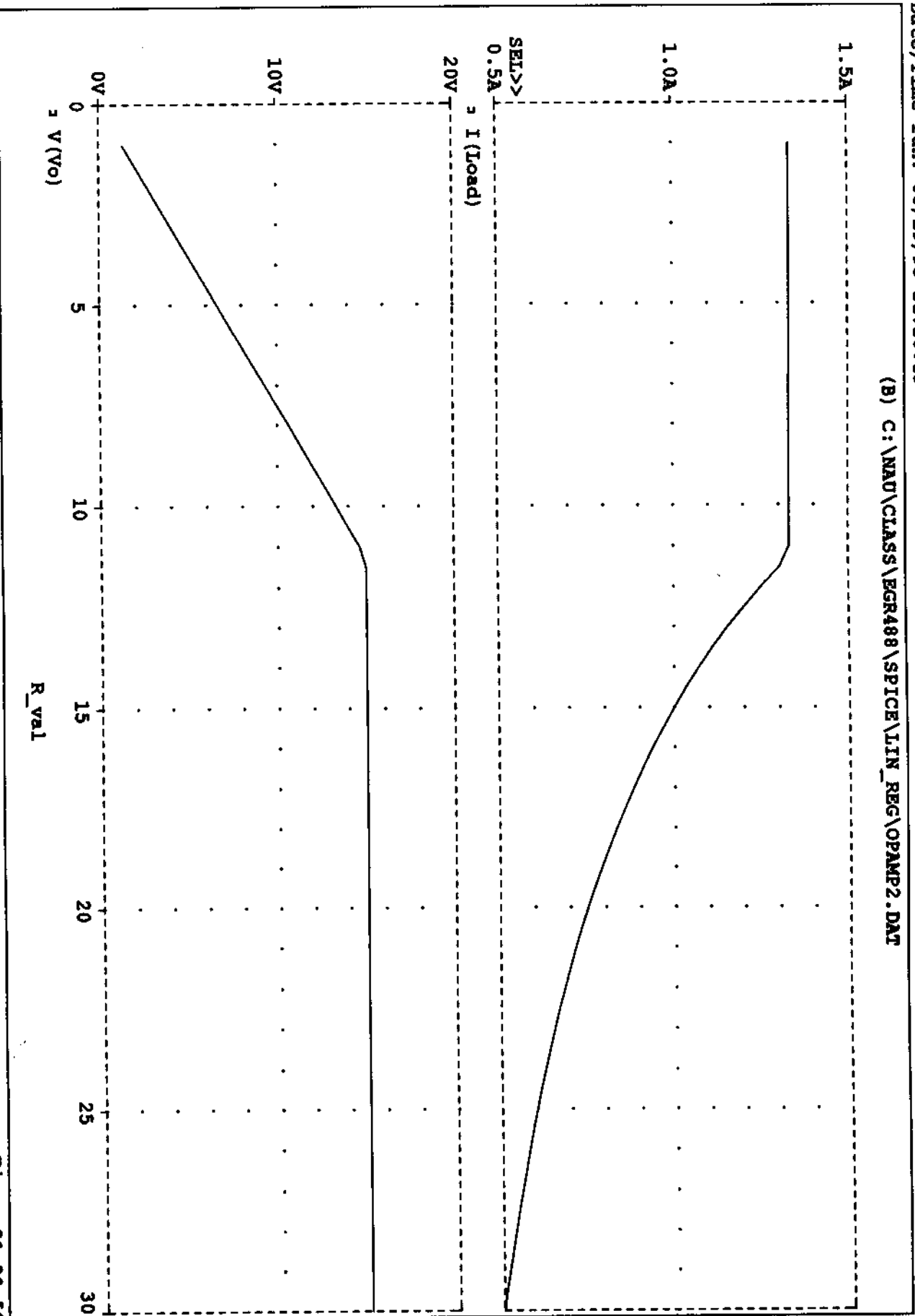(B) C:\NAU\CLASS\BGR488\SPICE\LIN_REG\OPAMP2.DAT




Date: August 29, 1995

Page 1

Time: 21:20:50

561

Frequency Compensation

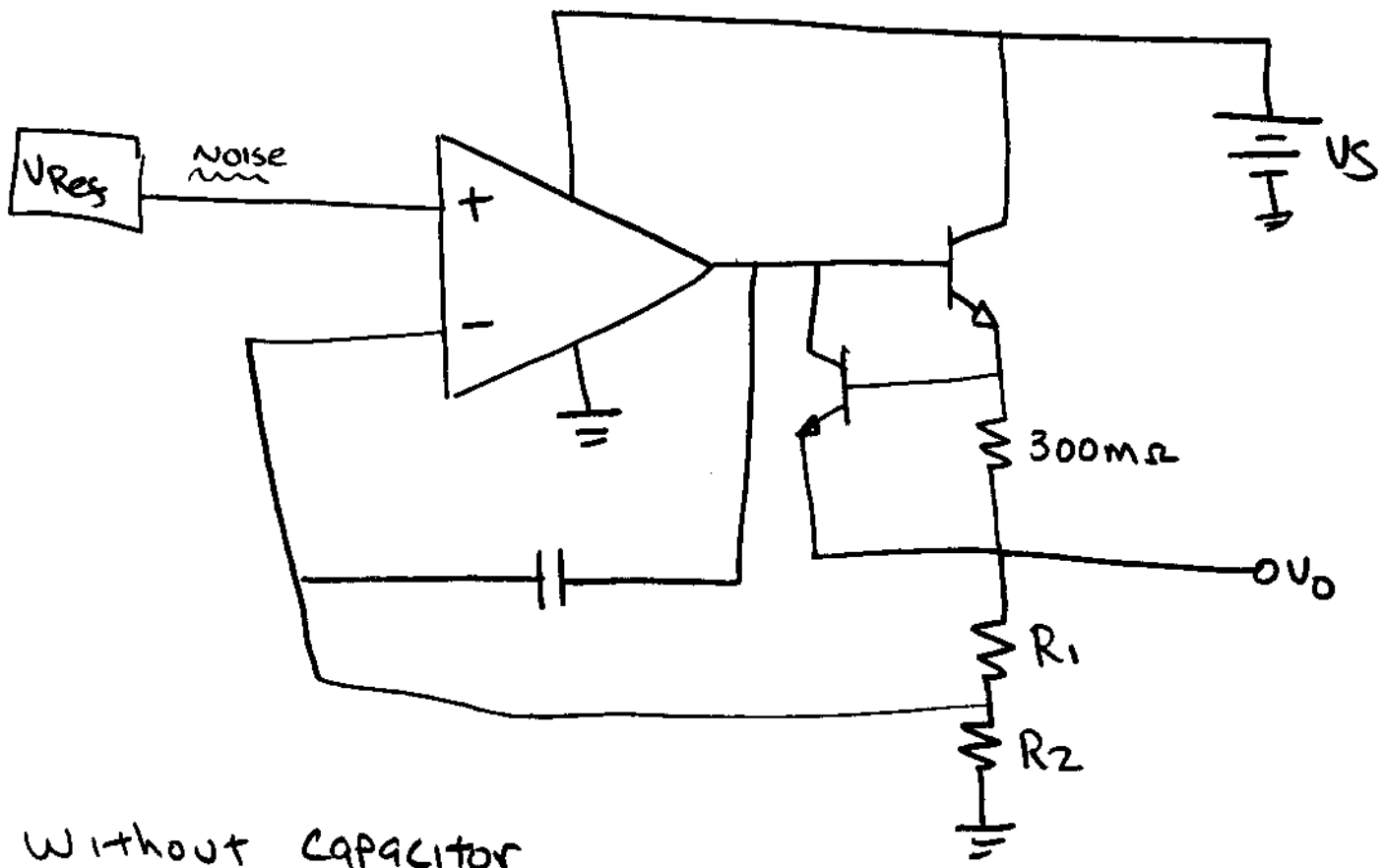



Without capacitor

$$V_o = \left(1 + \frac{R_1}{R_2}\right) (V_{Ref} + \text{Noise}) \quad ; \text{ without capacitor}$$

With capacitor

- Assume cap is short to noise
- Unity gain connection
- noise is not amplified by $1 + \frac{R_1}{R_2}$

DC - DC Step Down Converter (BUCK)

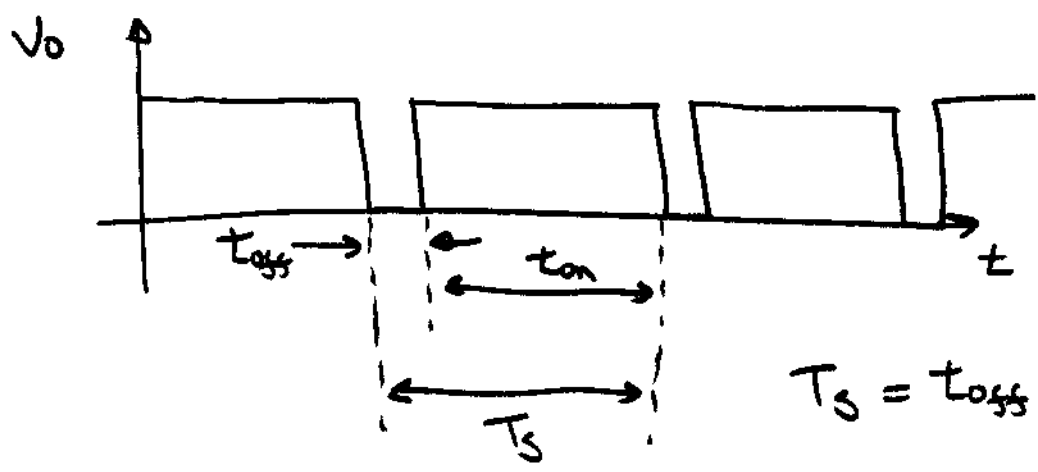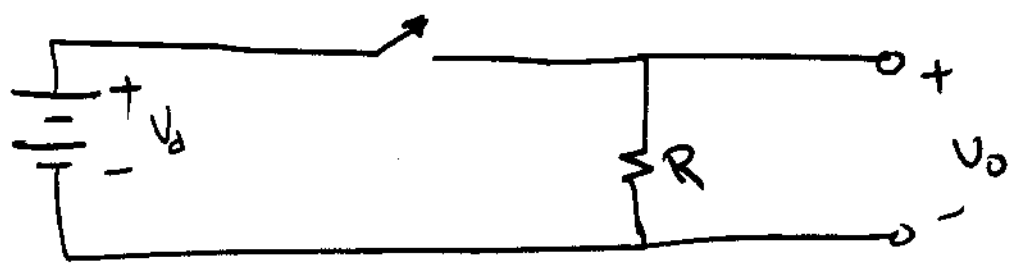

$$T_s = t_{off} + t_{on} = \text{const}$$



$$\langle V_o \rangle = \frac{1}{T_s} \int_{T_s} V_o(t) dt = \frac{1}{T_s} \int_0^{t_{off}} 0 \cdot dt + \frac{1}{T_s} \int_{t_{off}}^{t_{on} + t_{off}} V_d dt$$

$$\langle V_o \rangle = \frac{t_{on}}{T_s} V_d$$

Let $D = \frac{t_{on}}{T_s} = \text{duty Cycle}$


$\Rightarrow \langle V_o \rangle = D V_d \Rightarrow V_o$ only depends on Duty Cycle, NOT Frequency

Control of DC-DC Supply

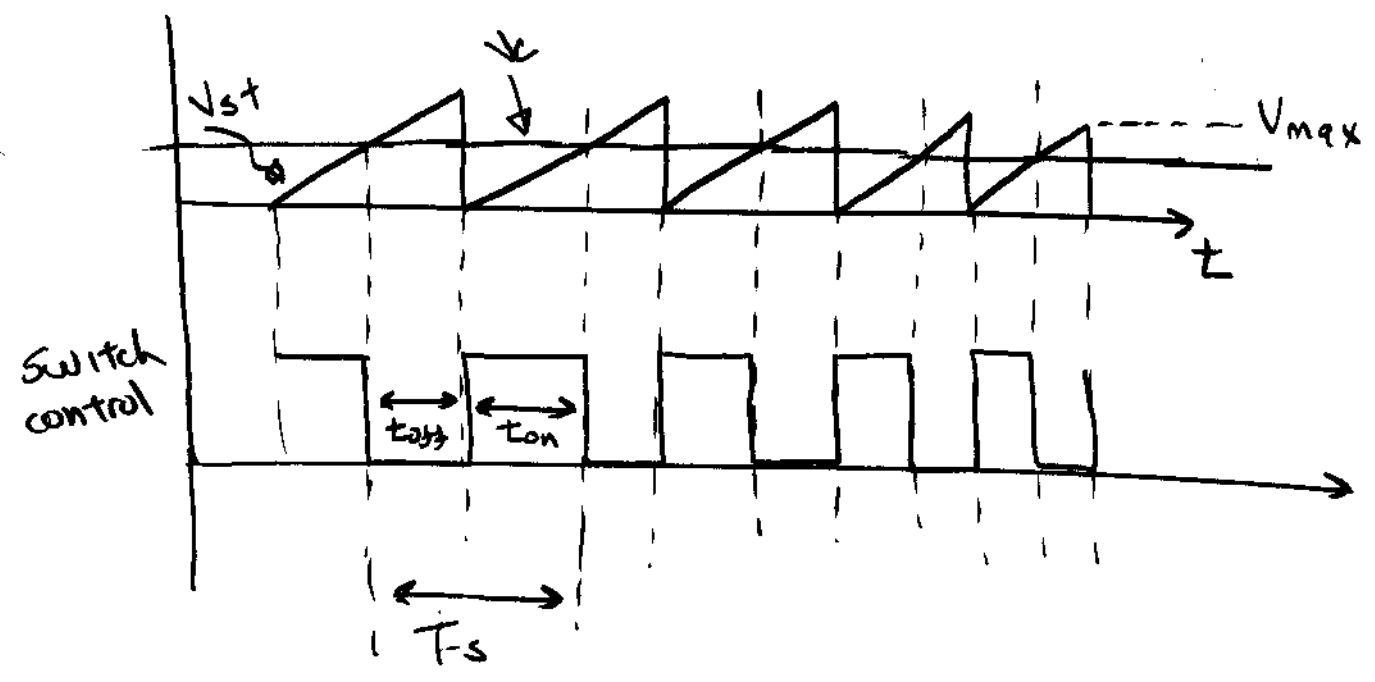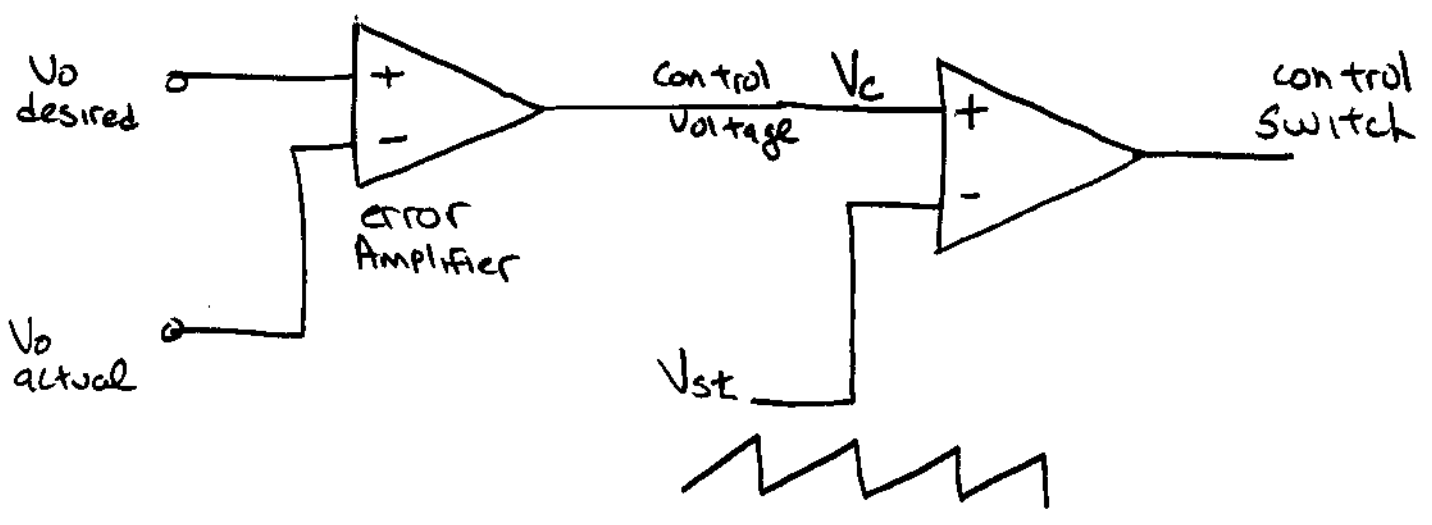

- Switching Frequency $F_s = \frac{1}{T_s}$
- as error increases, t_{on} increases

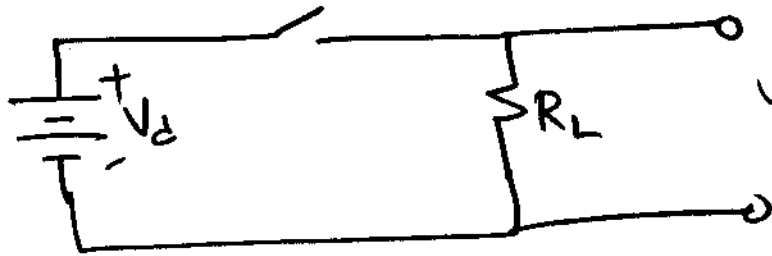
$$D = \frac{t_{on}}{T_s} = \frac{V_c}{V_{max}}$$



$$V_o = \frac{t_{on}}{T_s} V_d = DV_d$$


V_o has lots of ripples:

⇒ add a low pass filter


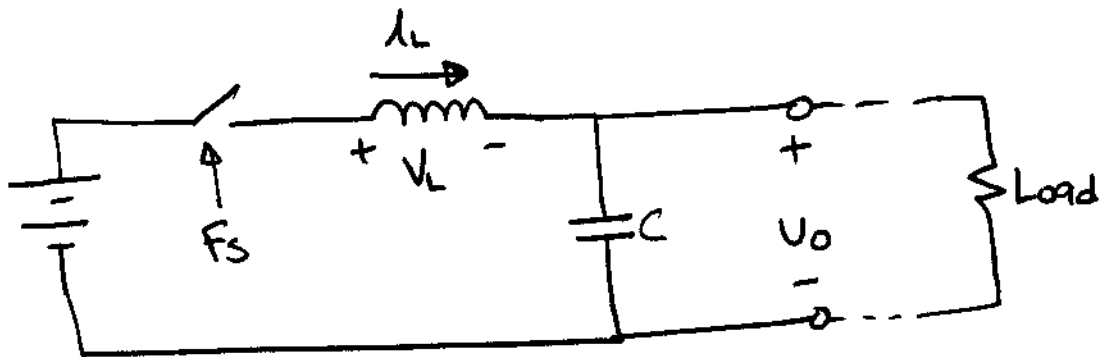


$F_s =$ Switching frequency

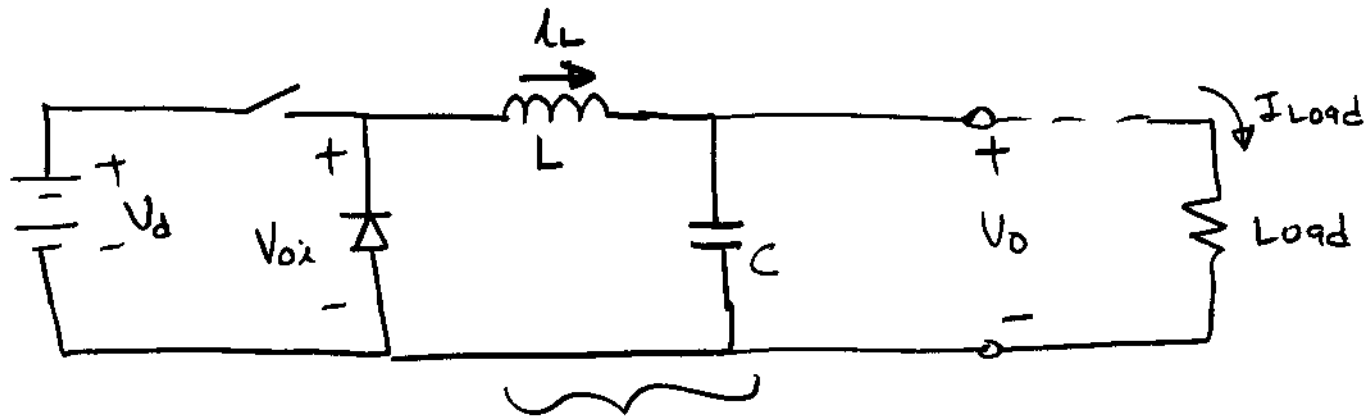- What is the problem with this circuit?
- When switch opens, inductor current can not go to zero instantaneously.




Low pass Filter

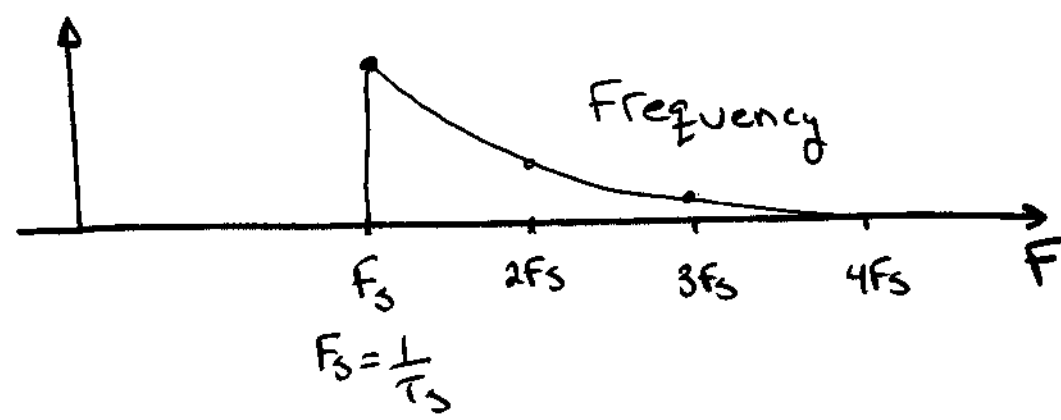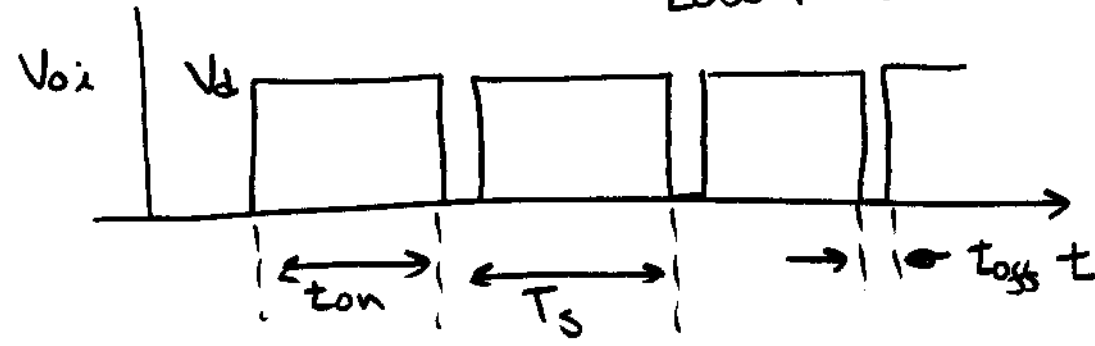

Low Pass Filter

f_c = Filter cutoff frequency

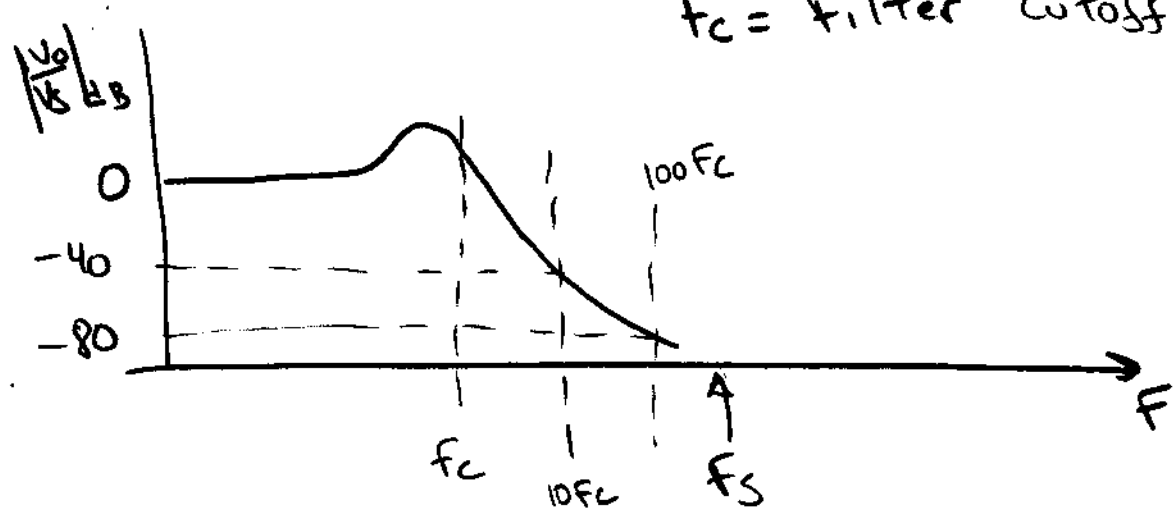

NOTE: $\langle I_L \rangle = \langle I_{Load} \rangle$


\Rightarrow average inductor current = average output I

Continuous - conduction mode

\Rightarrow definition: inductor current never goes to ϕ

$$\Rightarrow I_L(t) > 0$$

When the switch is closed: t_{on}

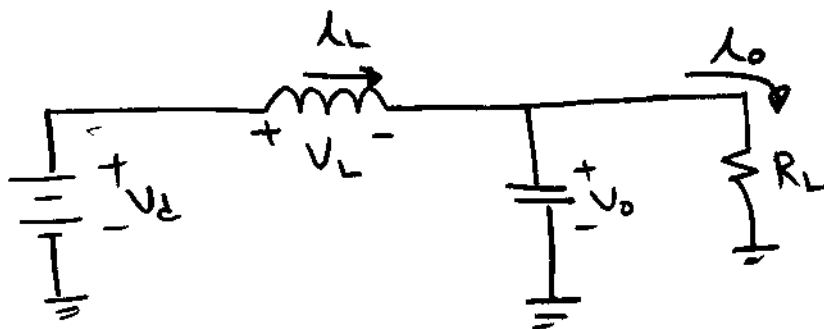


$$V_L = V_d - V_o$$

$$V_L = L \frac{dI_L}{dt} \Rightarrow I_L(t) = \frac{1}{L} \int (V_d - V_o) dt$$

Since $V_d - V_o > 0$, $I_L(t)$ increases
with slope $\frac{V_d - V_o}{L}$

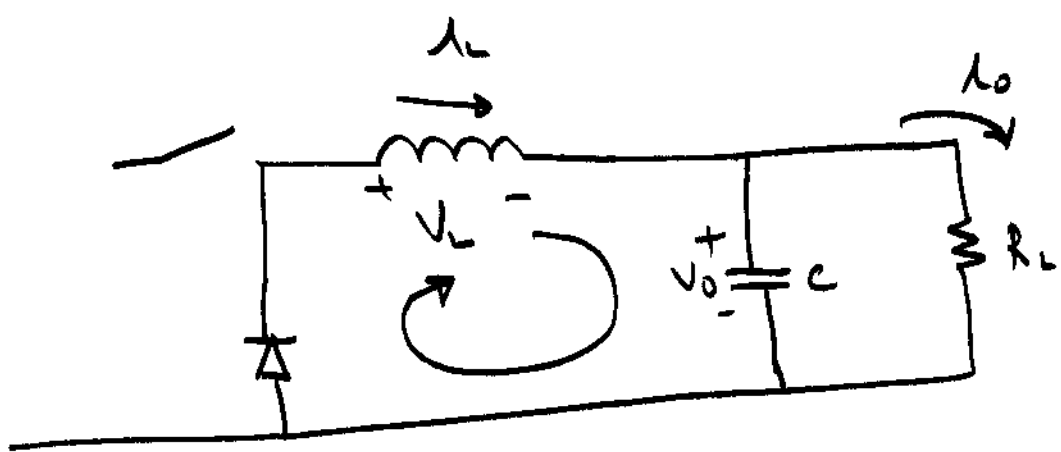- During loss, the switch is off
current must continue to flow:




Assume the diode is ideal

$$\Rightarrow V_L = -V_0$$

$$\Rightarrow V_L = L \frac{dI_L}{dt} \Rightarrow I_L(t) = \frac{1}{L} \int V_L dt$$

$$\text{OR } I_L(t) = \frac{1}{L} \int -V_0 dt$$

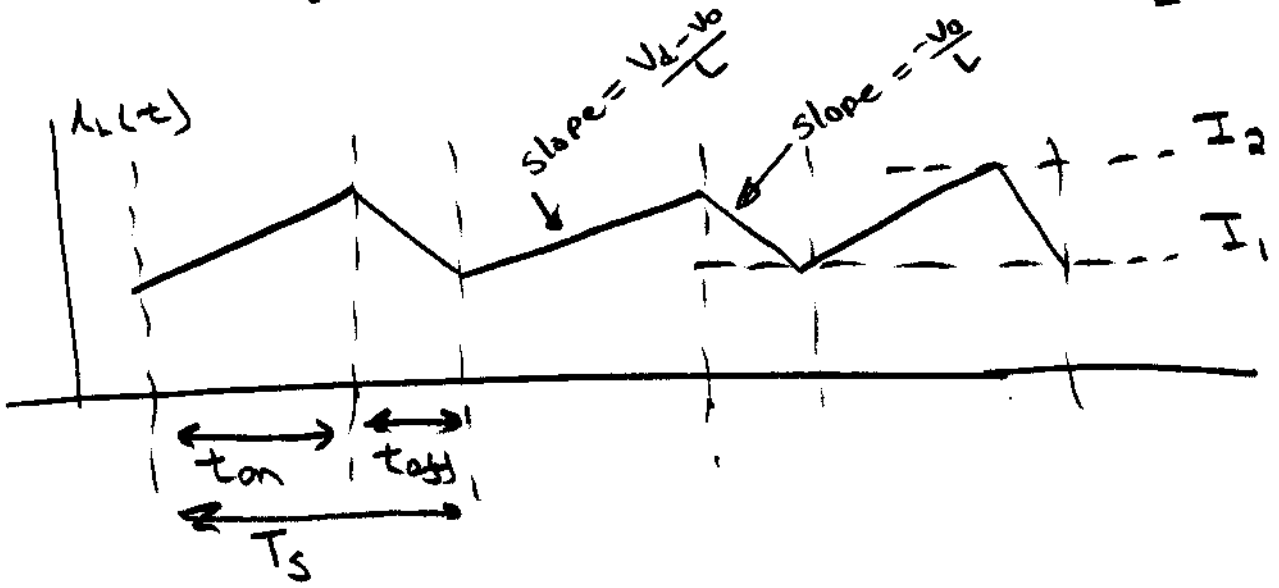$\Rightarrow I_L(t)$ decreases with slope $-\frac{V_0}{L}$



average output current = average $i_L(t)$

$$\langle i_o \rangle = \langle i_L(t) \rangle = \frac{I_2 + I_1}{2} = I_{\text{Load}}$$

In steady state, the average voltage = 0

$$\int_0^T v_L dt = \int_0^{t_{\text{on}}} v_L dt + \int_{t_{\text{on}}}^T v_L dt = 0$$

↑ why?

$$= \int_0^{t_{\text{on}}} (V_d - V_o) dt + \int_{t_{\text{on}}}^T -V_o dt = 0$$

$$= (V_d - V_o)t_{\text{on}} + (-V_o)(T - t_{\text{on}}) = 0$$

$$\Rightarrow V_d t_{\text{on}} - V_o T = 0$$


$$\Rightarrow \boxed{V_o = V_d \frac{t_{\text{on}}}{T}}$$

V_o is directly controlled
by the duty cycle.


- For fixed $V_o, V_D, \frac{t_{on}}{T} = \text{const}$

- as the current varies the ~~period~~ $D = \text{const}$,
 $V_o = \text{const}, V_D = \text{const}$, independent of L

high avg current:

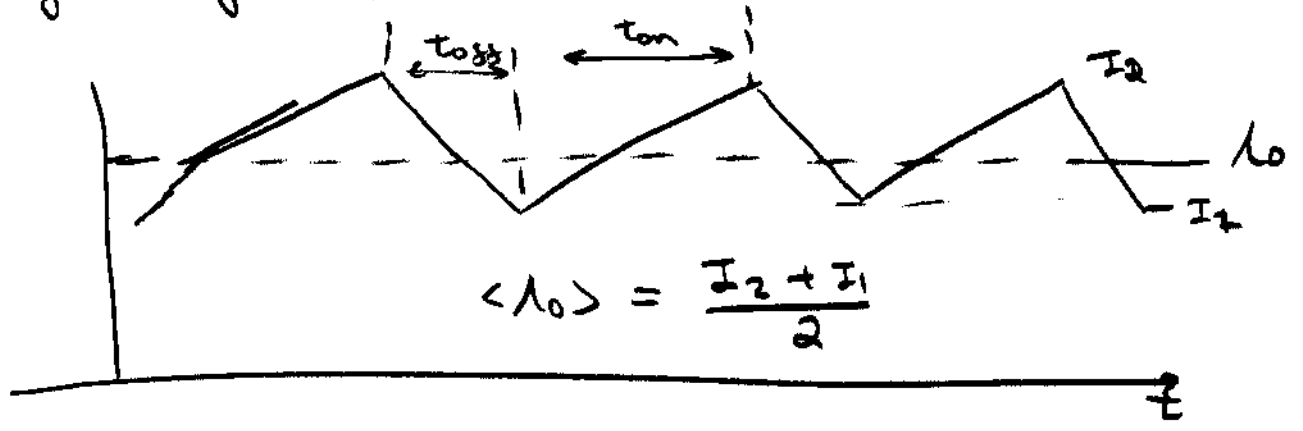

Low Avg current

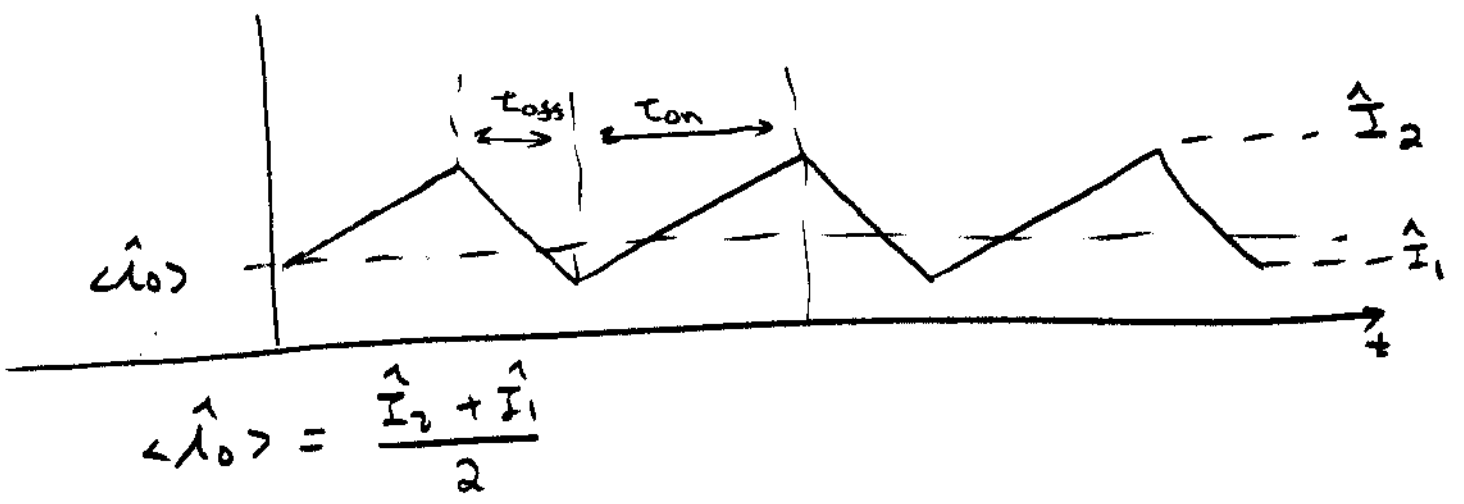


For high or low current $\hat{D} = \bar{D}$
 \Rightarrow Same Duty Cycle

- Since the Duty cycles are the same and Voltages are the same

$$\hat{I}_2 - \hat{I}_1 = I_2 - I_1$$

=> For different average I_0 , ΔI_L is the same.

- How do we find I_1 & I_2

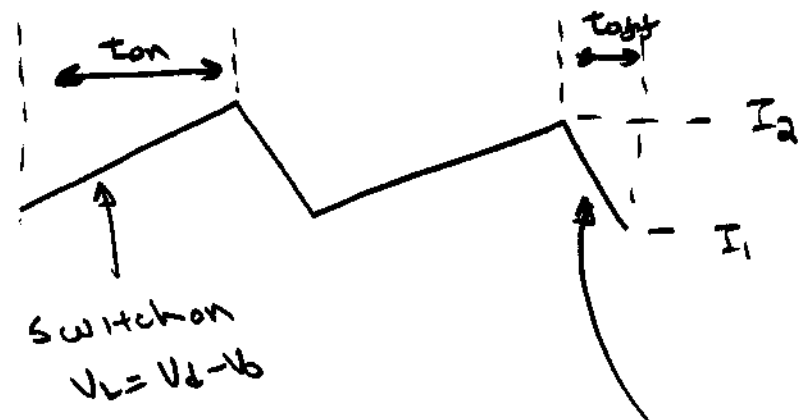

$$i_L(t) = \frac{1}{L} \int_0^{t_{on}} (V_d - V_0) dt + I_1$$

$\underbrace{\hspace{10em}}_{\Delta I_L}$
 ①

$$i_L(t) = \frac{1}{L} \int_{t_{on}}^T (-V_0) dt + I_2$$

$\underbrace{\hspace{10em}}_{\Delta I_L}$

Use equation ①

$$i_L(t) = \frac{1}{L} \int_0^t (V_d - V_o) dt + I_1$$

@ $t = t_{on}$, $i_L(t_{on}) = I_2$

$$I_2 = \frac{1}{L} \int_0^{t_{on}} (V_d - V_o) dt + I_1$$

$$\Rightarrow \boxed{(I_2 - I_1) = \left(\frac{V_d - V_o}{L}\right) t_{on}} \quad \text{①A}$$

Use equation 2

$$i_L(t) = \frac{1}{L} \int_{t_{on}}^T -V_o dt + I_2$$

@ $t = T$, $i_L(t) = I_1$

$$I_1 = \frac{1}{L} \int_{t_{on}}^T -V_o dt + I_2$$

$$I_1 - I_2 = \frac{-V_o}{L} (T - t_{on})$$

in continuous mode $V_o = \frac{t_{on}}{T} V_d$

$$\Rightarrow T = t_{on} \frac{V_d}{V_o}$$

$$I_1 - I_2 = -\frac{V_o}{L} \left(\frac{t_{on} V_d}{V_o} - t_{on} \right)$$

$$I_1 - I_2 = \frac{1}{L} (-t_{on} V_d + t_{on} V_o)$$

$$\Rightarrow I_2 - I_1 = \frac{1}{L} (V_o - V_d) t_{on} \quad - \text{Same as eq 1A on previous page}$$

ALSO

$$\frac{I_2 + I_1}{2} = I_o$$

Avg output current
= Avg inductor
current

In continuous mode

$$\textcircled{1} \quad V_o = \frac{t_{on}}{T} V_d = D V_o$$

$$\textcircled{2} \quad \left\{ \begin{array}{l} I_2 - I_1 = \frac{V_d - V_o}{L} t_{on} \end{array} \right.$$

$$\textcircled{3} \quad \left\{ \begin{array}{l} \frac{I_1 + I_2}{2} = I_o \quad - \text{Avg output current} \end{array} \right.$$

The current is continuous if $I_1 > 0$
 - Find condition when circuit operates in
 Find I_1 ° The continuous mode

$$I_1 - I_2 = \frac{V_o - V_d}{L} t_{on} \quad \textcircled{a}$$

$$I_1 + I_2 = 2 I_o \quad \textcircled{b}$$

Add

$$2 I_1 = \left(\frac{V_o - V_d}{L} t_{on} \right) + 2 I_o$$

Solve for $I_1 = 0$

$$2I_1 = \left(\frac{V_0 - V_D}{L}\right)t_{on} + 2I_0 = 0$$

$$t_{on}\left(\frac{V_0 - V_D}{L}\right) + 2I_0 = 0 \Rightarrow \boxed{I_0 = \left(\frac{V_D - V_0}{2L}\right)t_{on}}$$

So $I_1 > 0$ if $I_0 > \left(\frac{V_D - V_0}{2L}\right)t_{on}$

so for continuous mode

$$V_0 = \frac{t_{on}}{T} V_D = D V_D$$

$$I_2 - I_1 = \frac{V_D - V_0}{L} t_{on}$$

$$\frac{I_1 + I_2}{2} = I_0$$

$$I_0 > \left(\frac{V_D - V_0}{2L}\right)t_{on}$$

as I_0 changes, $D = \text{const}$