
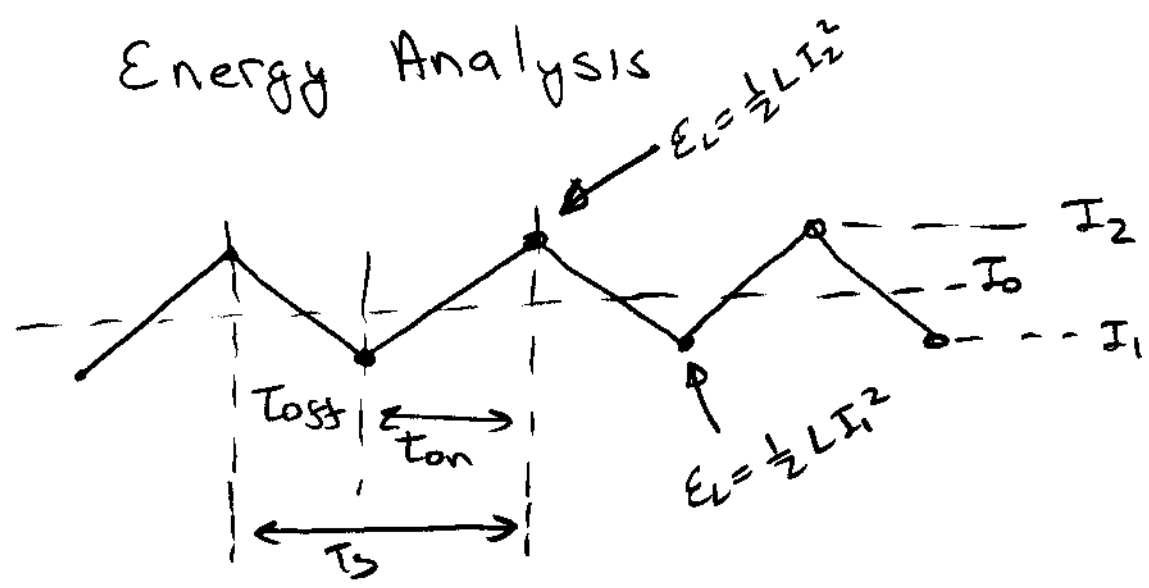


Energy Analysis

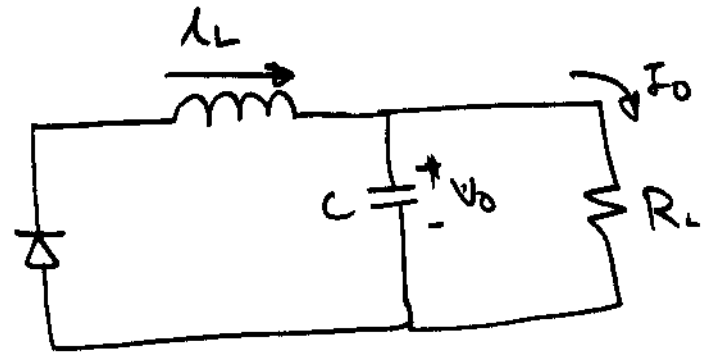

During t_{loss}



- During t_{loss} , $I_2 \rightarrow I_1$

Energy in inductor is delivered to R_L

$$\frac{1}{2} L I_2^2 - \frac{1}{2} L I_1^2 = V_0 I_0 t_{loss}$$

We know that $\frac{I_2 + I_1}{2} = I_0$

$$\frac{1}{2} L (I_2^2 - I_1^2) = \frac{V_o t_{\text{loss}}}{2} (I_1 + I_2)$$

$$\frac{1}{2} L (I_2 + I_1) (I_2 - I_1) = \frac{V_o t_{\text{loss}}}{2} (I_1 + I_2)$$

$$\frac{1}{2} L (I_2 - I_1) = \frac{V_o t_{\text{loss}}}{2} \quad \textcircled{1}$$

and $t_{\text{loss}} = T_s - t_{\text{on}}$

and $V_o = \frac{t_{\text{on}}}{T_s} V_d \Rightarrow T_s = t_{\text{on}} \frac{V_d}{V_o}$

$$\Rightarrow t_{\text{loss}} = t_{\text{on}} \frac{V_d}{V_o} - t_{\text{on}} = t_{\text{on}} \left(\frac{V_d}{V_o} - 1 \right)$$

Sub into $\textcircled{1}$


$$L (I_2 - I_1) = V_o t_{\text{on}} \left(\frac{V_d}{V_o} - 1 \right)$$

OR

$$I_2 - I_1 = \frac{V_d - V_o}{L} t_{\text{on}}$$

Same as before

During t_{on}

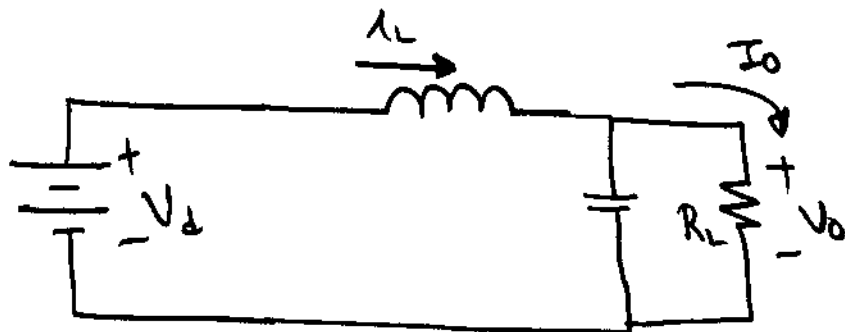

During t_{on} $I_L \rightarrow I_1$ to I_2


Energy dissipated by $R_L = V_o I_o t_{on}$

Energy stored in inductor: $\frac{1}{2} L I_2^2 - \frac{1}{2} L I_1^2$

Both of these energies must be supplied
By V_D

$$E_{V_d} = \int_0^{t_{on}} P_{V_o}(t) dt = \int_0^{t_{on}} V_d I_L(t) dt$$
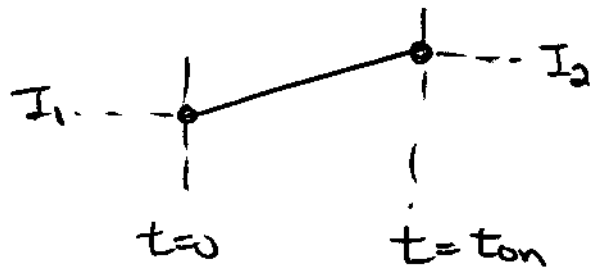
$$I_L(t) = I_1 + \left(\frac{I_2 - I_1}{t_{on}} \right) t$$



$$E_{V_d} = V_d \int_0^{t_{on}} \left(I_1 + \frac{I_2 - I_1}{t_{on}} t \right) dt$$

$$= V_d \left[I_1 t + \frac{(I_2 - I_1)}{t_{on}} \frac{t^2}{2} \right]_0^{t_{on}}$$

$$= V_d \left[I_1 t_{on} + \left(\frac{I_2 - I_1}{2} \right) t_{on} \right] = V_d \left[\frac{I_1 + I_2}{2} t_{on} \right]$$

Next, Energy balance:

Energy Supplied by source = additional Energy
Stored in L + Energy dissipated in R_L

$$V_0 \left[\frac{I_1 + I_2}{2} \right] t_{on} = \frac{1}{2} L [I_2^2 - I_1^2] + V_0 I_0 t_{on}$$

Sub in $I_0 = \frac{I_1 + I_2}{2}$

$$V_0 \left[\frac{I_1 + I_2}{2} \right] t_{on} = \frac{1}{2} L [I_2 + I_1] [I_2 - I_1] + V_0 t_{on} \left[\frac{I_1 + I_2}{2} \right]$$

OR

$$(V_0 - V_0) t_{on} = L (I_2 - I_1)$$

OR

$$I_2 - I_1 = \frac{V_0 - V_0}{L} t_{on}$$

Same as before

Choosing the Capacitor

Method 1


- Design L + C as Low Pass Filter

choose $F_c < \frac{F_s}{100}$

Then $F_c = \frac{1}{2\pi \sqrt{LC}}$

Method 2

Use a Real model of a Capacitor

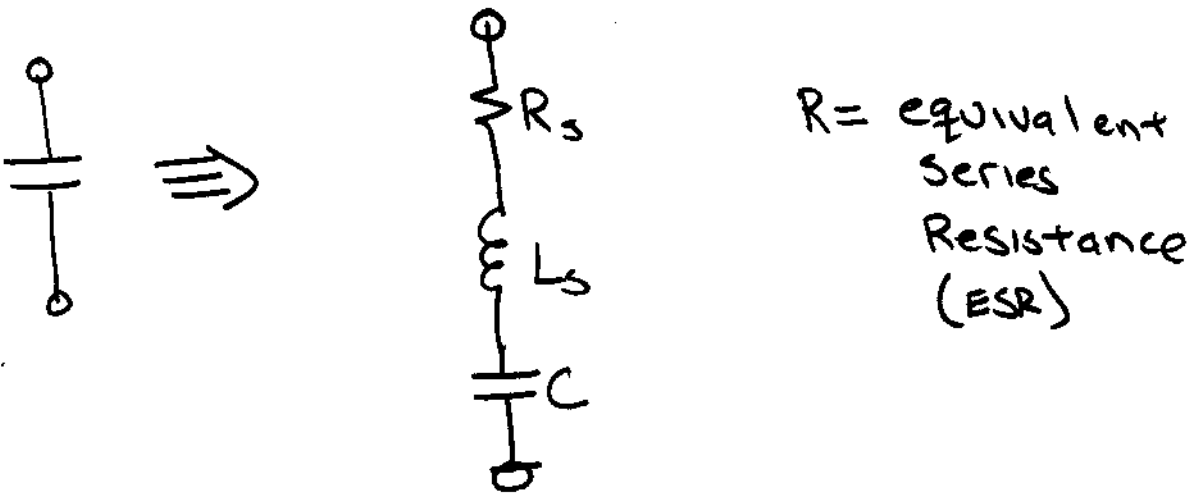

Below 300K - 500 KHz, Ignore L_s



- Two Ripple Components due to C + R_s
- The Two Ripple components are out of phase, but for worst case analysis, we shall Assume they add in phase.


- For Typical Electrolytic $R_s C = \text{const}$

- Typical values for $R_s C$ are in the Range 50 to $80 \times 10^{-6} \mu\text{s}$

Ripple Voltage due to R_s is

$$V_{RR} = (I_2 - I_1) R_s$$

Find the Capacitive Ripple

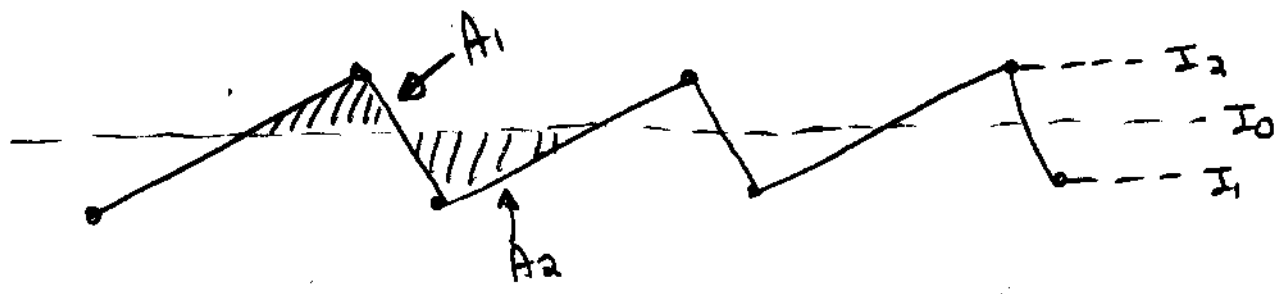

$$I_0 = \text{Load Current} = \frac{I_1 + I_2}{2}$$

During A1 :

- current larger than I_0
- extra current goes into cap.
- Cap Voltage increases

During A2 :

- current smaller than I_0
- Cap supplies current to Load
- Cap Voltage decreases

NOTE : $A_1 = A_2$

During A_1 , The average value of current through L is

$$\frac{I_2 + I_0}{2} = \frac{I_2 + \left(\frac{I_1 + I_2}{2}\right)}{2} = \frac{I_2}{2} + \frac{I_2}{4} + \frac{I_1}{4}$$

$$\langle I_C \rangle = \langle I_L \rangle - I_0$$

$$\begin{aligned} \langle I_C \rangle &= \frac{I_2}{2} + \frac{I_2}{4} + \frac{I_1}{4} - I_0 \\ &= \frac{I_2}{2} + \frac{I_2}{4} + \frac{I_1}{4} - \left(\frac{I_1 + I_2}{2}\right) = \frac{I_2 - I_1}{4} \end{aligned}$$

- The charge deposited into C during A_1

$$q_c = \langle I_C \rangle t = \left(\frac{I_2 - I_1}{4}\right) \frac{T_s}{2}$$

- Capacitor equation

$$q = CV \Rightarrow V = \frac{q}{C}$$

$$\Rightarrow \Delta V = \frac{\Delta q}{C} = \left(\frac{I_2 - I_1}{4}\right) \frac{T_s}{2C}$$

So,

$$V_{RC} = \Delta V_C = \frac{(I_2 - I_1) T_S}{8C}$$

Total Ripple is

$$V_R = V_{RC} + V_{RR}$$

Summary - Buck Regulator
in continuous mode

$$V_o = \frac{t_{on}}{T} V_d = D V_d$$

$$I_2 - I_1 = \frac{V_d - V_o}{L} t_{on}$$

$$\frac{I_1 + I_2}{2} = I_o$$

$$I_o > \left(\frac{V_d - V_o}{2L} \right) t_{on}$$

$$V_{RR} = (I_2 - I_1) R_S$$

$$V_{RC} = \frac{(I_2 - I_1) T_S}{8C}$$

$$R_S C = 50 \text{ to } 80 \mu\text{s}$$

EE 456

Buck Regulator Design - Continuous Mode Operation

Define useful units for Electrical Engineering

$$\mu\text{s} = 10^{-6} \cdot \text{sec}$$

Specify Input Voltage $V_D := 15 \cdot \text{volt}$

Specify Output Voltage $V_o := 5 \cdot \text{volt}$

Specify Switching Frequency $F_S := 20 \cdot \text{kHz}$

$$T_S := \frac{1}{F_S}$$

$$T_S = 50 \cdot \mu\text{s}$$

Find on time assuming continuous mode operation. $t_{\text{on}} := \frac{V_o}{V_D} \cdot T_S$ $t_{\text{on}} = 16.667 \cdot \mu\text{s}$

Specify the Max output Current $I_o := 1 \cdot \text{amp}$

Design the buck regulator so that it operates in the continuous mode for currents down to 10% of the max current.

$$I_{o_min} := 0.1 \cdot I_o$$

$$I_{o_min} = 0.1 \cdot \text{amp}$$

Find L so that the buck regulator operates in continuous mode for the min output current

$$L := \frac{V_D - V_o}{2 \cdot I_{o_min}} \cdot t_{\text{on}}$$

$$L = 833.333 \cdot \mu\text{H}$$

Choose the next size std. inductor $L := 1000 \cdot \mu\text{H}$

With chosen inductor, find min current for continuous operation

$$I_{o_min} := \frac{V_D - V_o}{2 \cdot L} \cdot t_{\text{on}}$$

$$I_{o_min} = 83.333 \cdot \text{mA}$$

For the Max output current, find I1 and I2

$$I_1 := I_o \quad I_2 := I_o$$

Given

$$\frac{I_2 + I_1}{2} = I_o$$

$$I_2 - I_1 = \frac{V_D - V_o}{L} \cdot t_{on}$$

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} := \text{find}(I_1, I_2) \quad I_2 = 1.083 \cdot \text{amp} \quad I_1 = 0.917 \cdot \text{amp}$$

$$I_2 - I_1 = 166.667 \cdot \text{mA}$$

For the Min output current, find I1 and I2

$$I_{1_} := I_{o_min} \quad I_{2_} := I_{o_min}$$

Given

$$\frac{I_{2_} + I_{1_}}{2} = I_{o_min}$$

$$I_{2_} - I_{1_} = \frac{V_D - V_o}{L} \cdot t_{on}$$

$$\begin{bmatrix} I_{1_} \\ I_{2_} \end{bmatrix} := \text{find}(I_{1_}, I_{2_}) \quad I_{2_} = 0.167 \cdot \text{amp} \quad I_{1_} = 0 \cdot \text{amp}$$

$$I_{2_} - I_{1_} = 166.667 \cdot \text{mA}$$

Choose the filter capacitor.

Assume that the major component of the ripple comes from the capacitor ESR

Specify the ripple due to the ESR $V_{RR} := 10 \cdot \text{mV}$

$$\text{ESR} := \frac{V_{RR}}{(I_2 - I_1)} \quad \text{ESR} = 0.06 \cdot \Omega$$

For all electrolytic caps, assume that $\text{ESR} \cdot C = 80 \mu\text{s}$

$$C := \frac{80 \mu\text{s}}{\text{ESR}} \quad C = 1.333 \cdot 10^3 \cdot \mu\text{F}$$

Choose the next size std capacitor $C := 2200 \cdot \mu\text{F}$

Calculate the new ESR with the chosen capacitor

$$\text{ESR} := \frac{80 \cdot \mu\text{s}}{C} \quad \text{ESR} = 0.036 \cdot \Omega$$

Find the ripple due to the capacitor:

$$V_{RC} := \frac{(I_2 - I_1) \cdot T_S}{8 \cdot C} \quad V_{RC} = 0.473 \cdot \text{mV}$$

Find the ripple due to the ESR

$$V_{RR} := (I_2 - I_1) \cdot \text{ESR} \quad V_{RR} = 6.061 \cdot \text{mV}$$

Calculate the RMS ripple current for the capacitor.

Assume a triangular waveform with a 50% duty cycle - Worst case.

$$A := \frac{I_2 - I_1}{2} \quad A = 0.083 \cdot \text{amp}$$

$$I(t) := \frac{A}{\left(\frac{T_S}{4}\right)} \cdot t$$

$$I_{\text{rms}} := \sqrt{\frac{4}{T_S} \left[\int_{0 \cdot \text{sec}}^{\frac{T_S}{4}} I(t)^2 dt \right]}$$

$$I_{\text{rms}} = 0.048 \cdot \text{amp}$$

Summary

Inductor

$L = 1 \cdot \text{mH}$ Peak Current Rating $I_2 = 1.083 \cdot \text{amp}$ Avg Current Rating $I_o = 1 \cdot \text{amp}$

Capacitor

$C = 2.2 \cdot 10^3 \cdot \mu\text{F}$ RMS Ripple Current Rating $I_{\text{rms}} = 0.048 \cdot \text{amp}$

Regulator Specs

Maximim Current $I_o = 1 \cdot \text{amp}$ Period $T_S = 50 \cdot \mu\text{s}$ Switching Frequency $F_S = 20 \cdot \text{kHz}$

Switch on time $t_{\text{on}} = 16.667 \cdot \mu\text{s}$ Output Voltage $V_o = 5 \cdot \text{volt}$ Input Voltage $V_D = 15 \cdot \text{volt}$

Currents $I_2 = 1.083 \cdot \text{amp}$ $I_1 = 0.917 \cdot \text{amp}$ $I_2 - I_1 = 166.667 \cdot \text{mA}$

Attributes Of The Set Signal (V1)


Name	Value
REFDES	V1


period=50u
rise_time=1n
fall_time=1n
Pulse_width=5u
initial_voltage=5
Pulsed_voltage=0
delay_time=0

Include Non-changeable Attributes
 Include System-defined Attributes

Buttons: Save Attr, Change Display, Delete, OK, Cancel

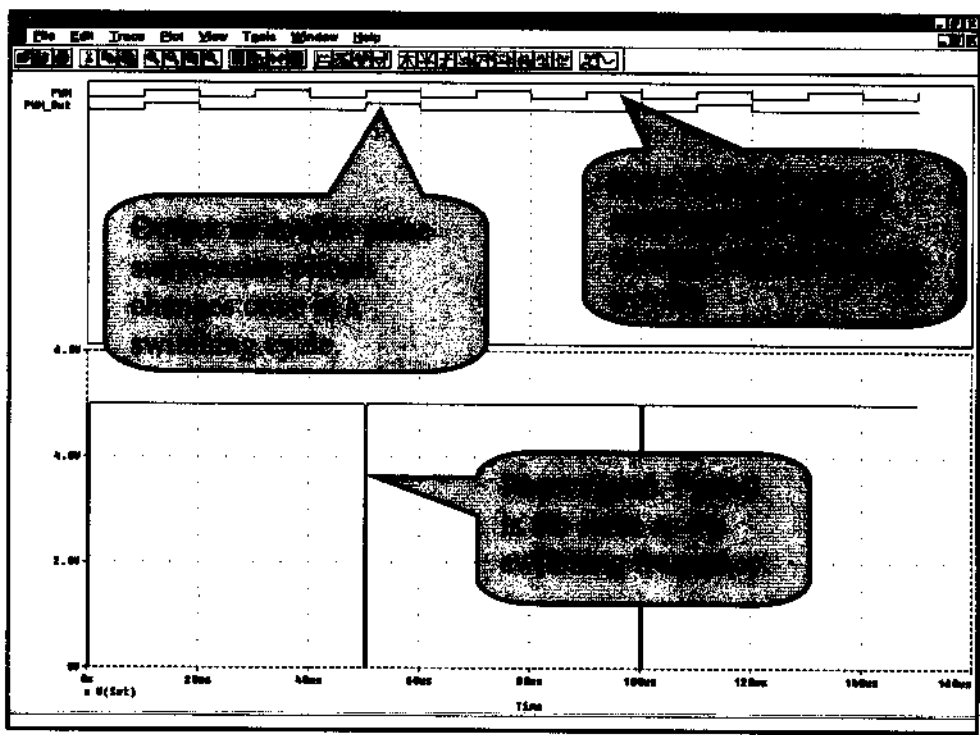Advanced PSpice Workshop – June 7-9, 2000



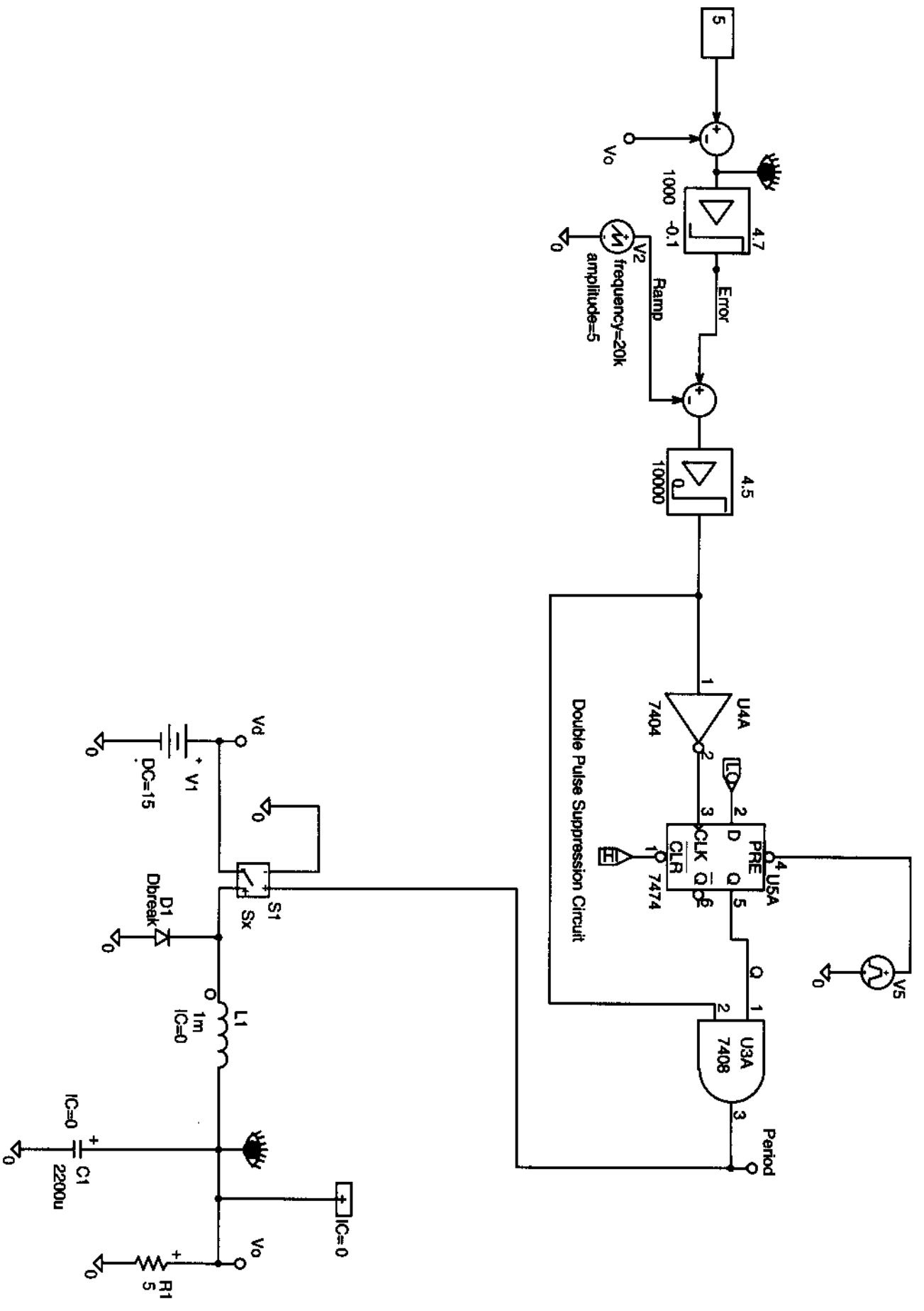


Date/Time run: 06/19/100 09:49:15

* D:\NAU\CLASS\egr456\SPICE\BUCK\CONTR2.SCH

Temperature: 27.0

(B) CONTR2.dat

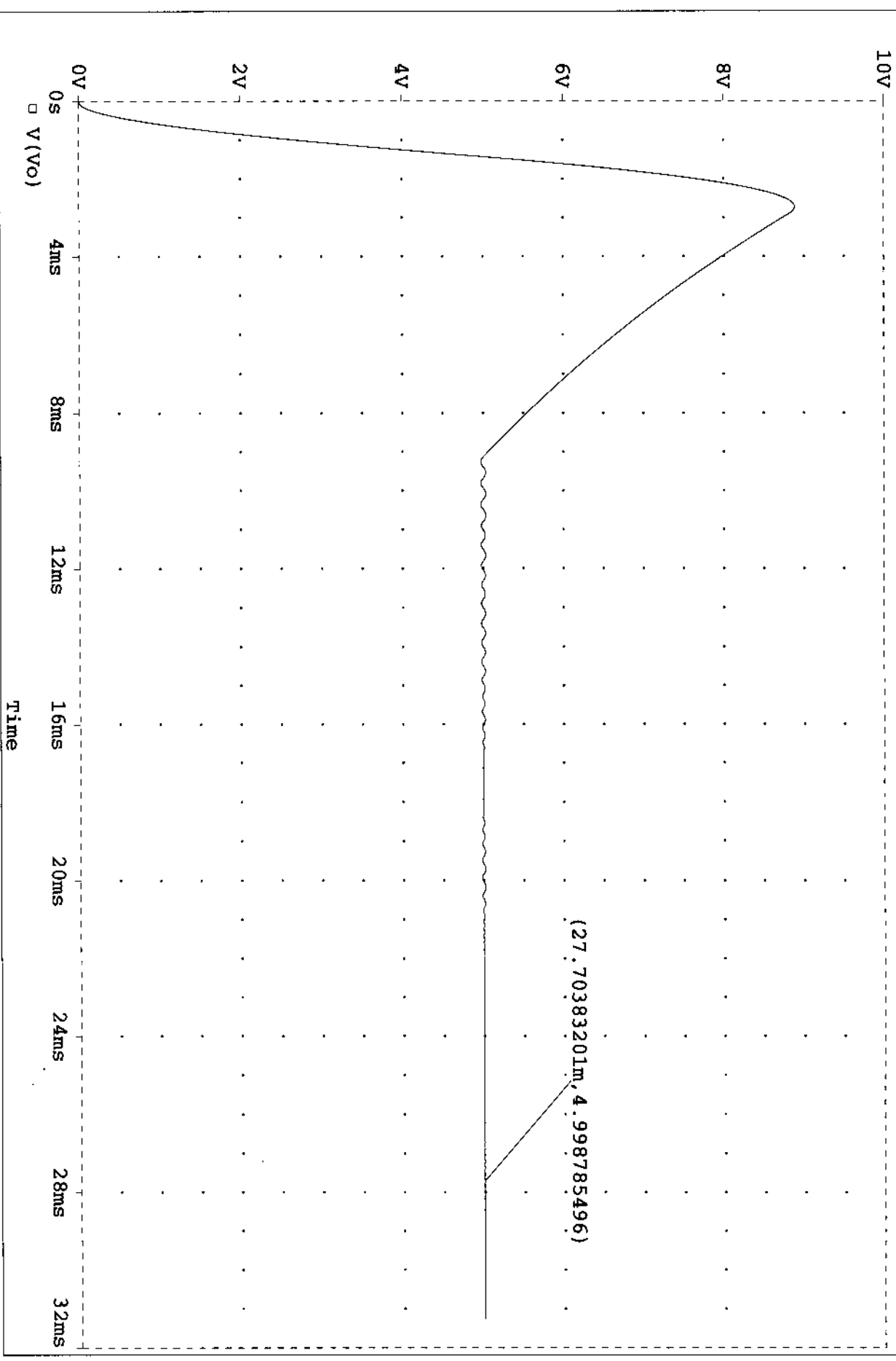

Date: June 19, 2000

Page 1


Time: 09:55:50

Date/Time run: 06/19/100 09:49:15

* D:\NAU\CLASS\egr456\SPICE\BUCK\CONTR2.SCH

Temperature: 27.0

(B) CONTR2.dat

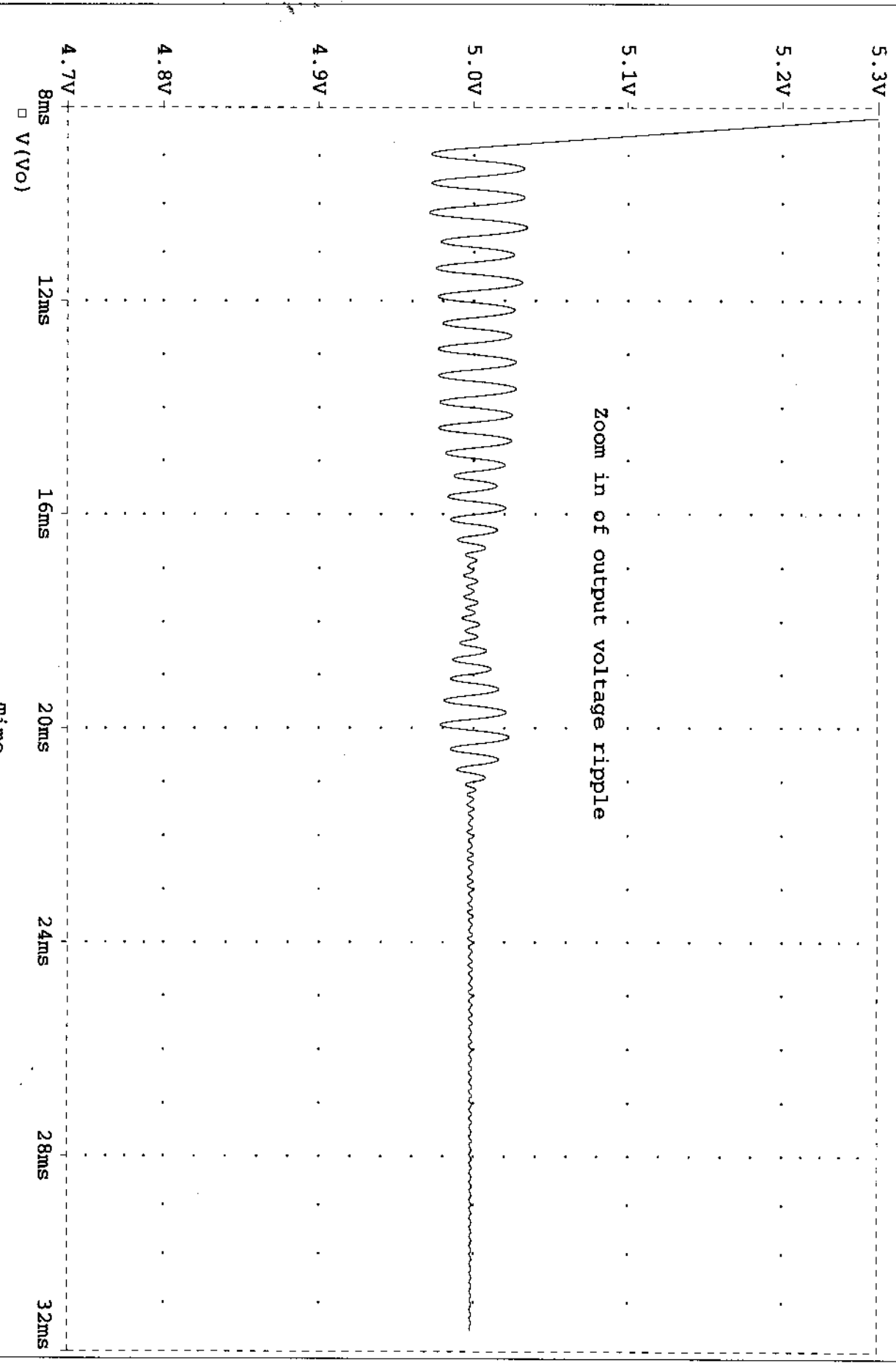


Date: June 19, 2000

Page 1

Time: 09:59:44

(B) CONT2.dat

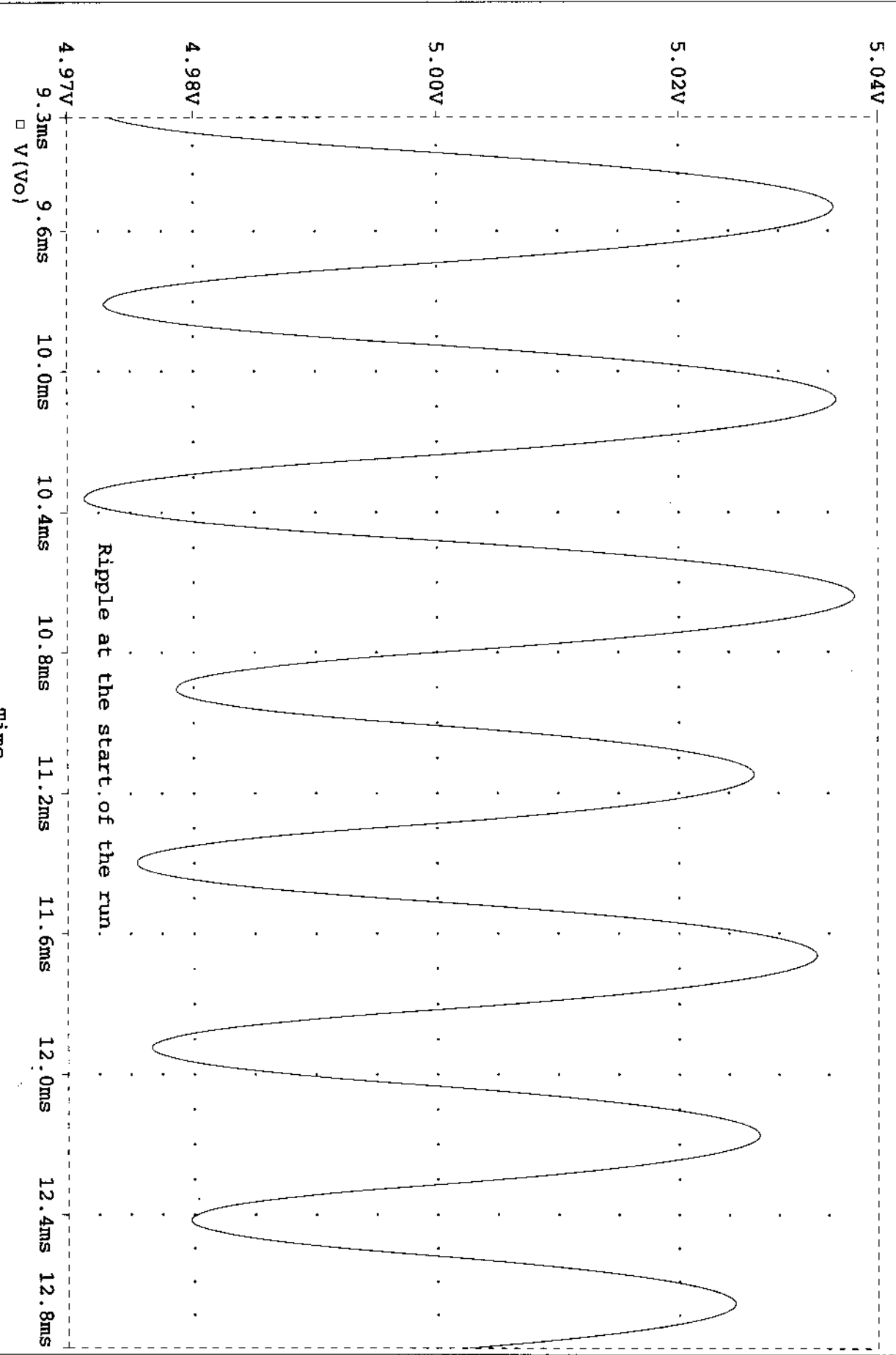

Date/Time run: 06/19/100 09:49:15

* D:\MAU\CLASS\egr456\SPICE\BUCK\CONTR2.SCH

Temperature: 27.0

(B) CONTR2.dat

5.04V

5.02V

Ripple in steady state.

5.00V

4.98V

4.97V

27.8ms
□ V (Vo)

28.5ms

29.0ms

29.5ms

30.0ms

30.5ms

31.0ms

Time

Date: June 19, 2000

Page 1


Time: 10:00:47

Date/Time run: 06/19/100 09:49:15

* D:\NAU\CLASS\egr456\SPICE\BUCK\CONTR2.SCH

Temperature: 27.0

(D) CONTR2.dat


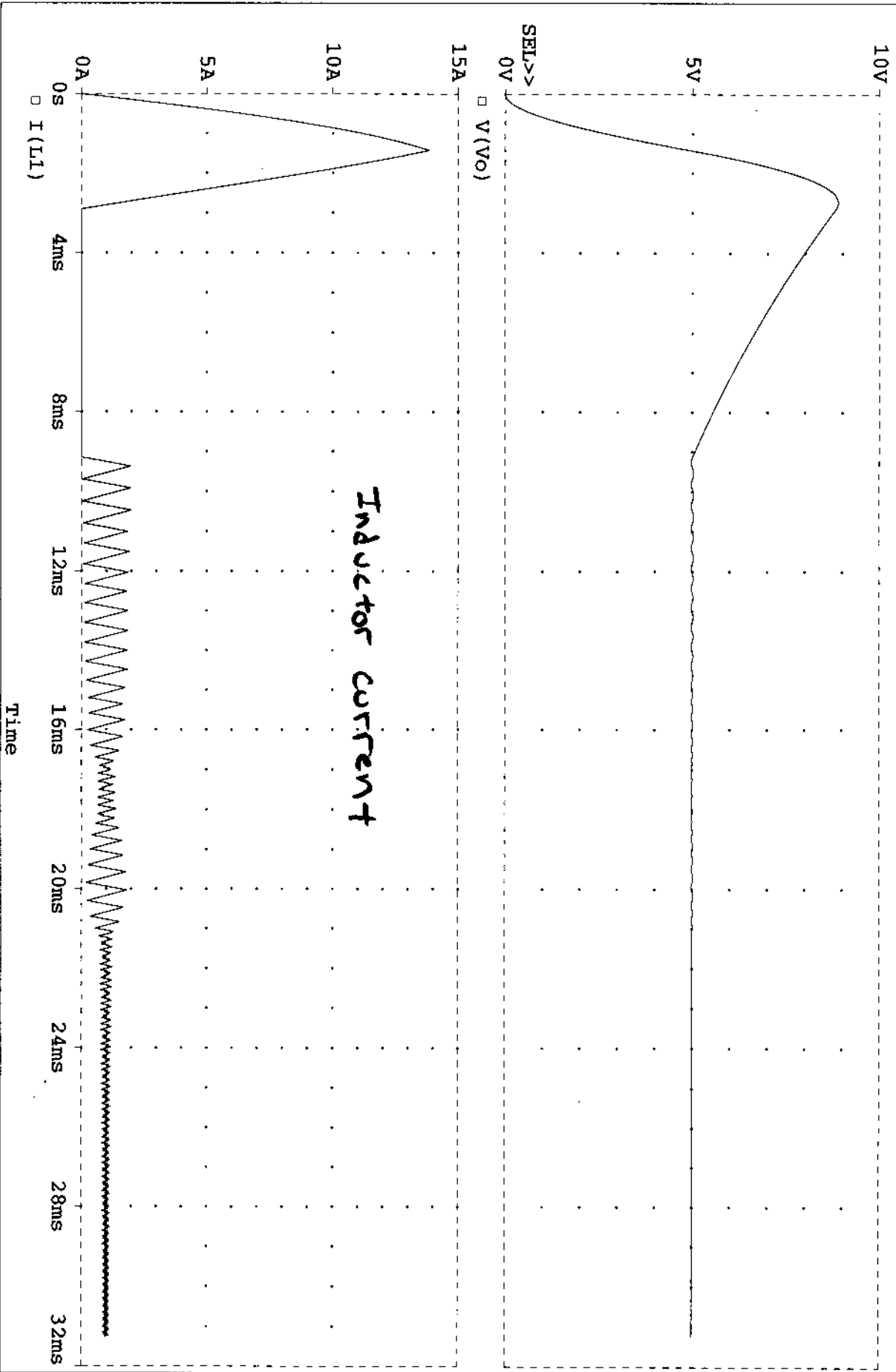


Date: June 19, 2000

Page 1

Time: 10:01:33

(D) CONTR2.dat

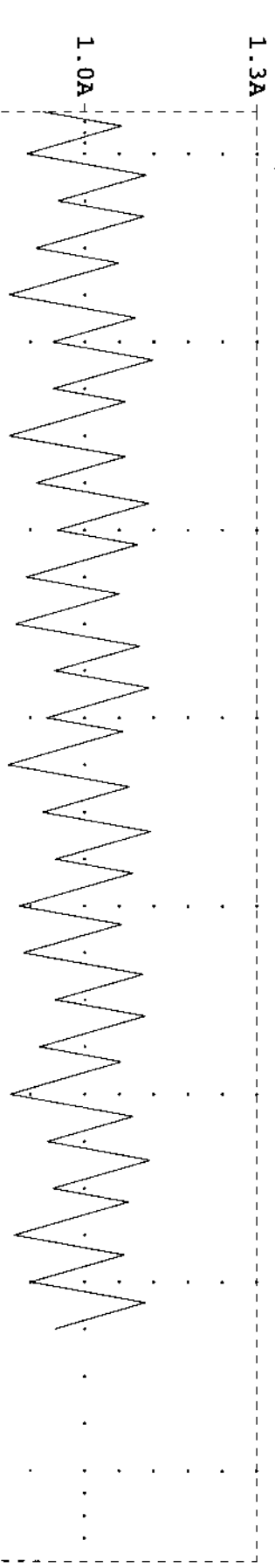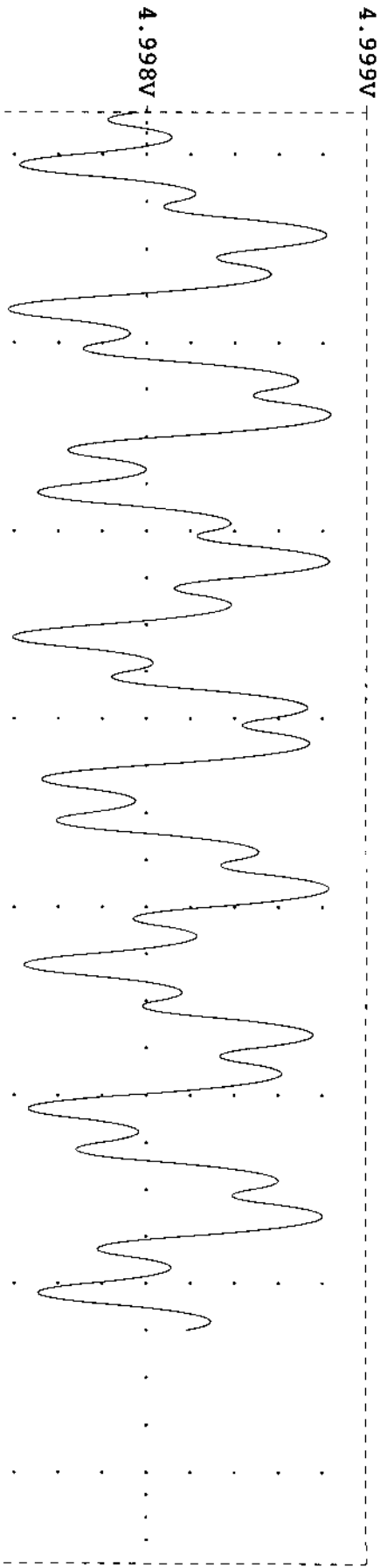


Date/Time run: 06/19/100 09:49:15

* D: \NAU\CLASS\egr456\SPICE\BUCK\CONT2.SCH

Temperature: 27.0


(D) CONT2.dat

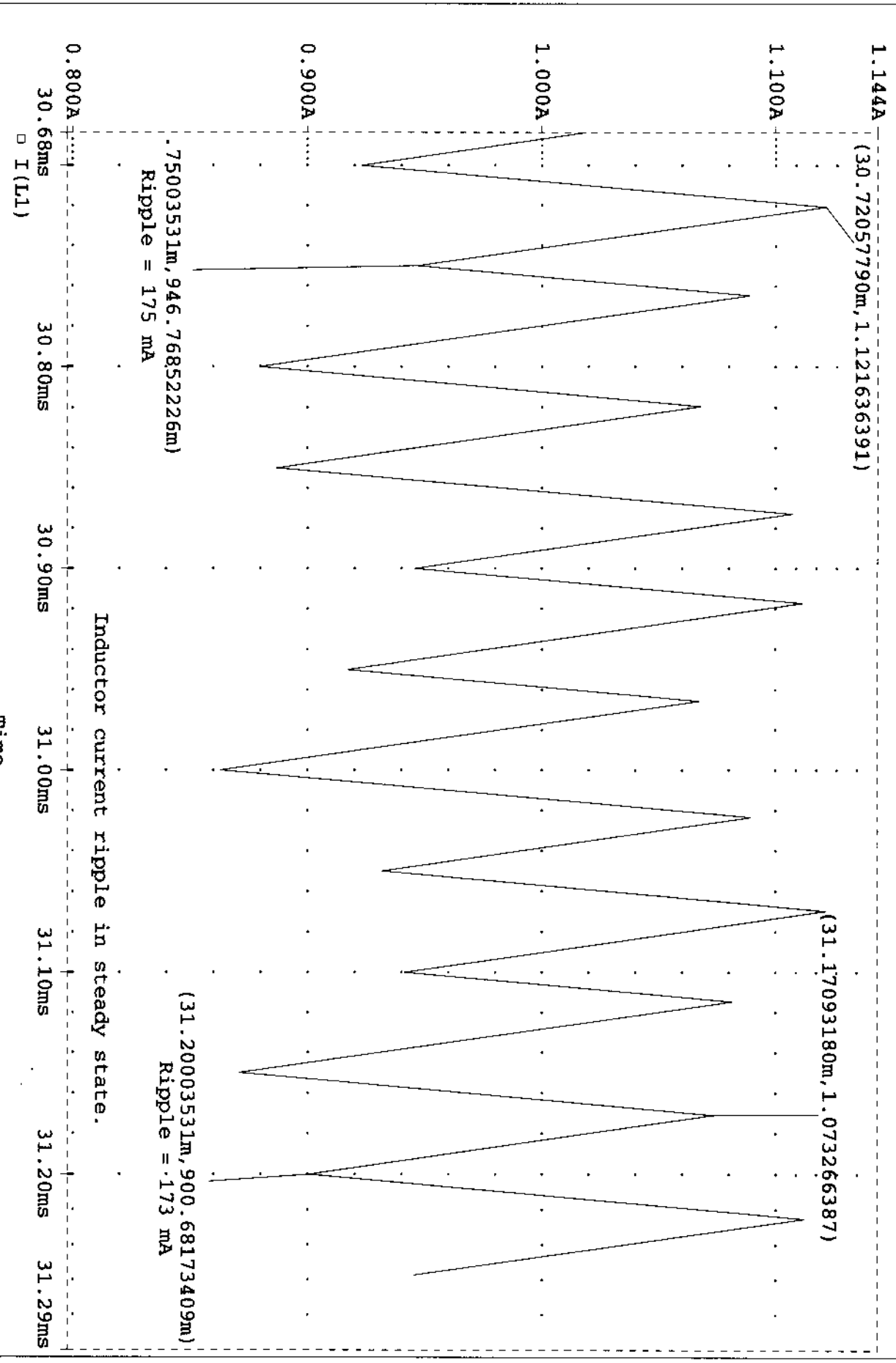


Date: June 19, 2000

Page 1

Time: 10:07:03

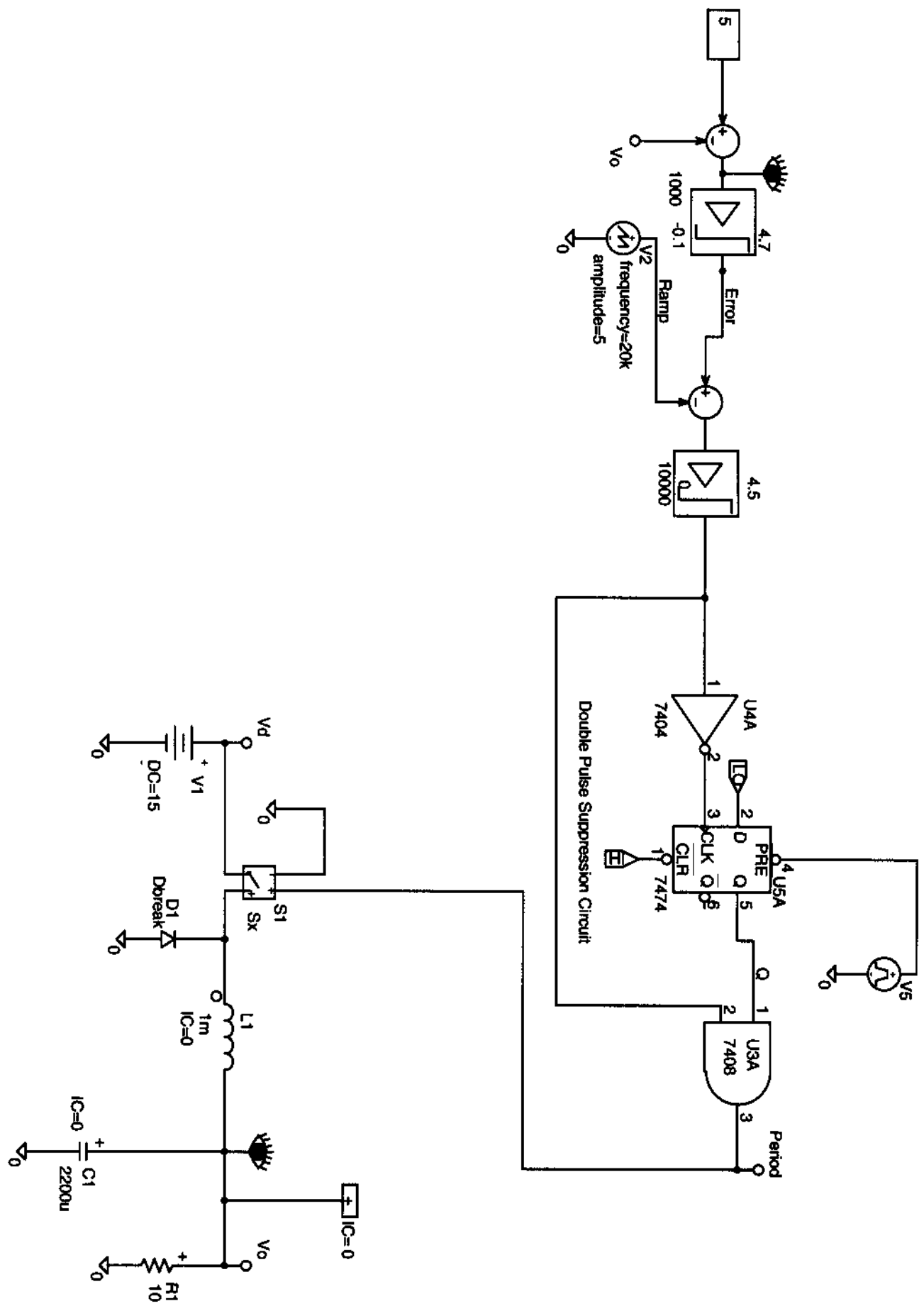

(C) CONT2.dat

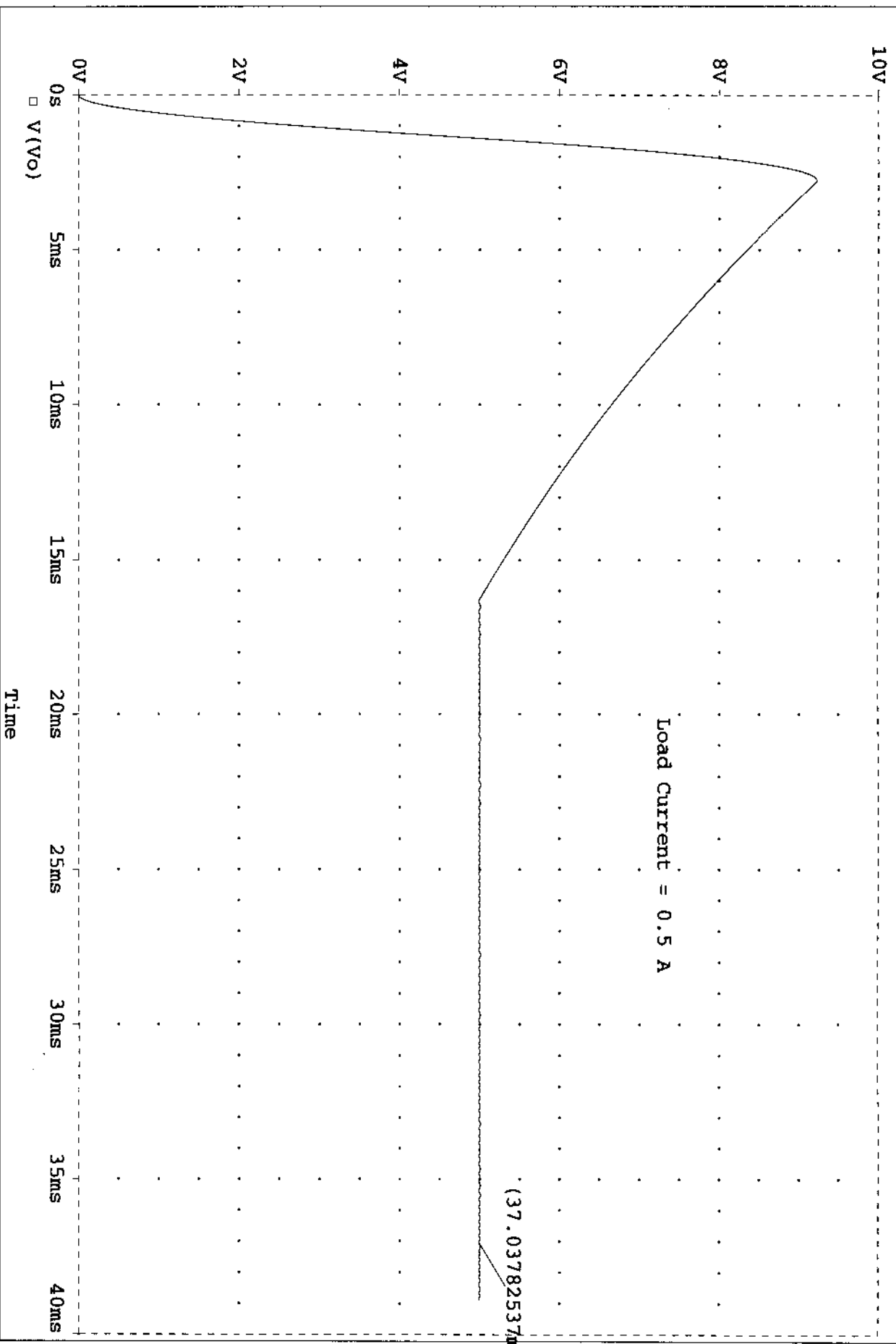


94A

Date/Time run: 06/19/100 10:07:36

* D:\NAU\CLASS\egr456\SPICE\BUCK\CONT2.SCH

Temperature: 27.0

(C) CONT2.dat

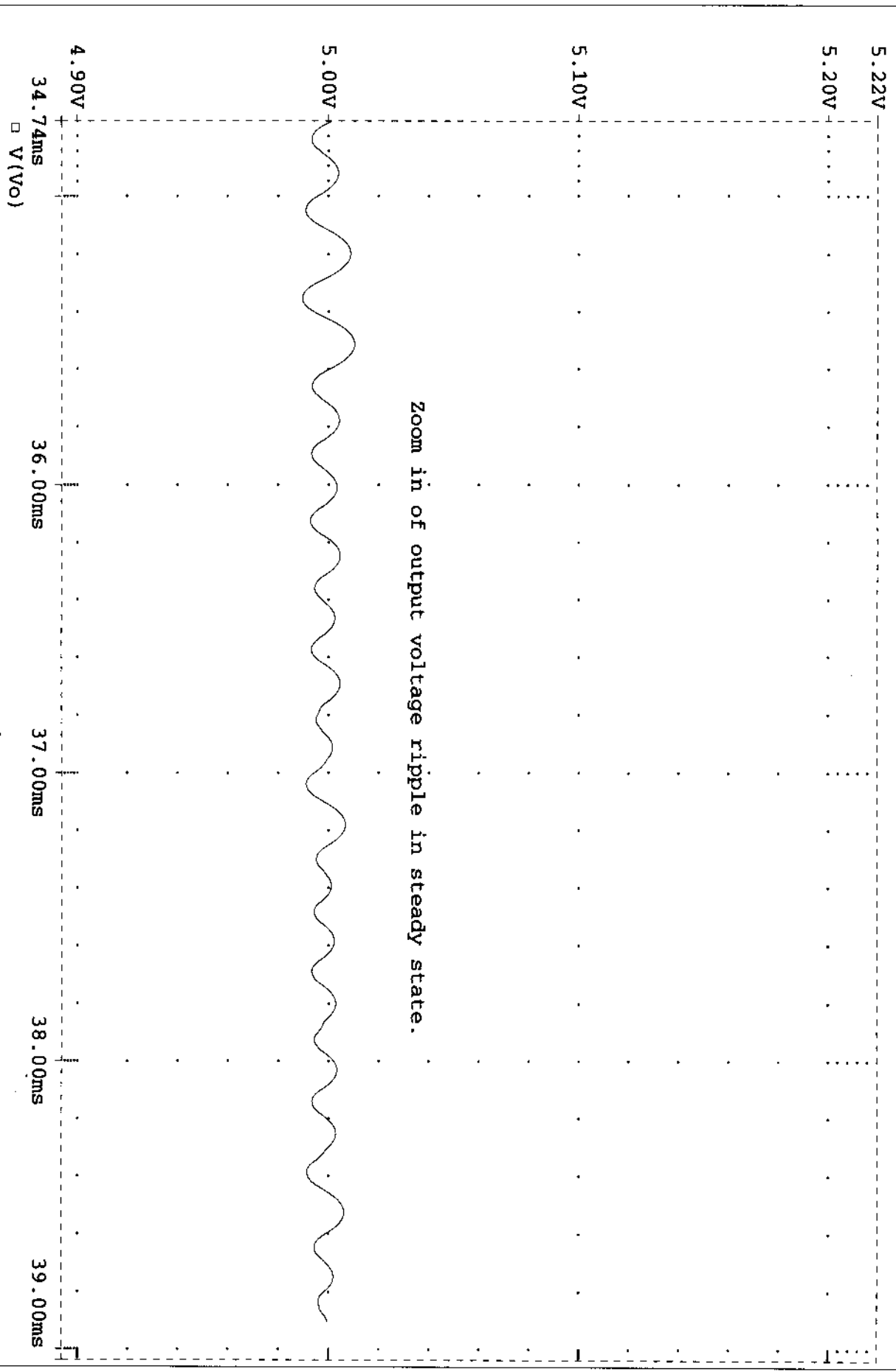

Date: June 19, 2000

Page 1

Time: 10:11:26


948

Date/Time run: 06/19/100 10:07:36

* D:\NAU\CLASS\egr456\SPICE\BUCK\CONTR2.SCH

Temperature: 27.0

(E) CONTR2.dat

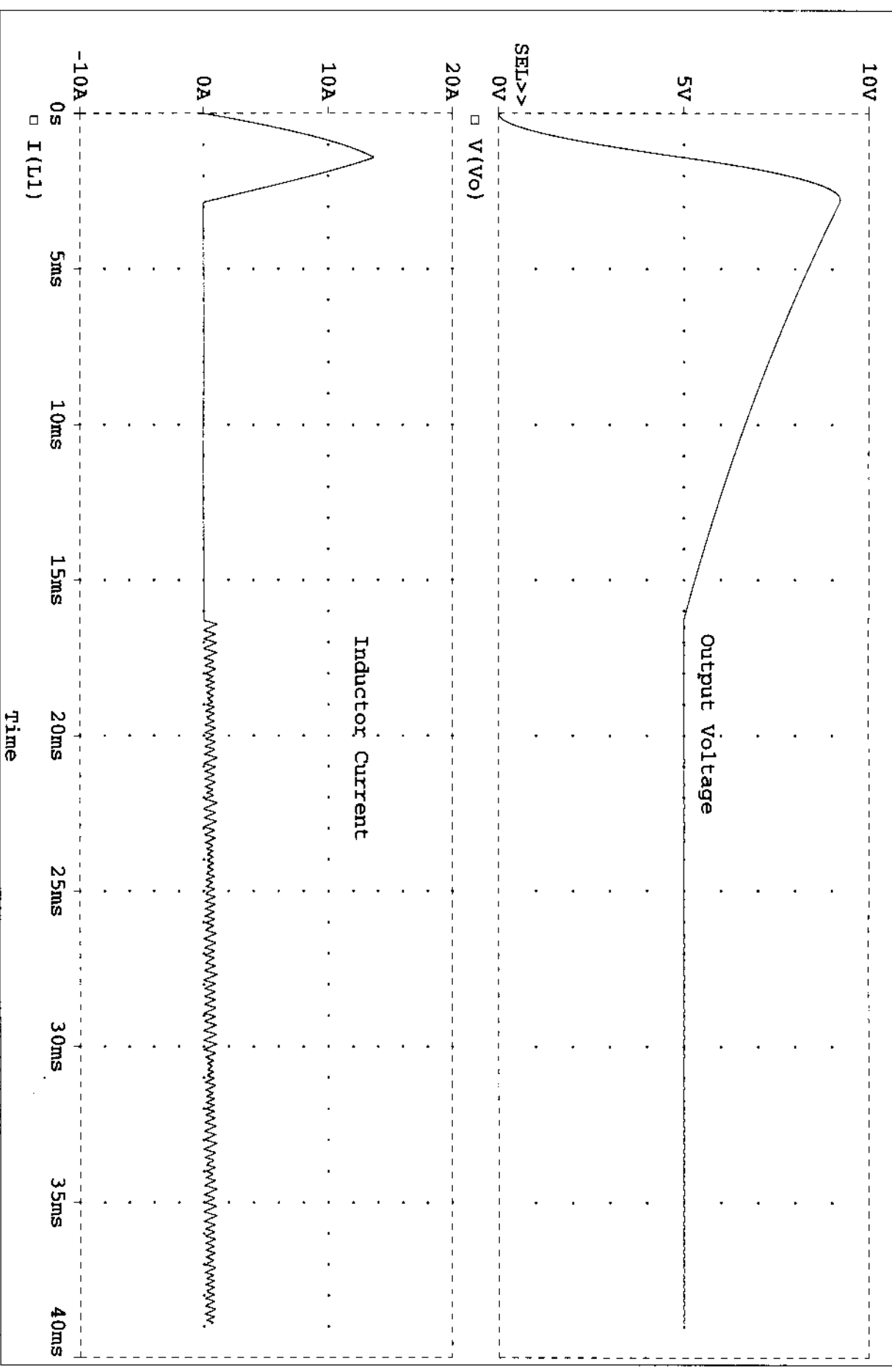

Date: June 19, 2000

Page 1

Time: 10:12:15


94C

Date/Time run: 06/19/100 10:07:36

* D:\NAU\CLASS\egr456\SPICE\BUCK\CONT2.SCH

Temperature: 27.0

(E) CONT2.dat

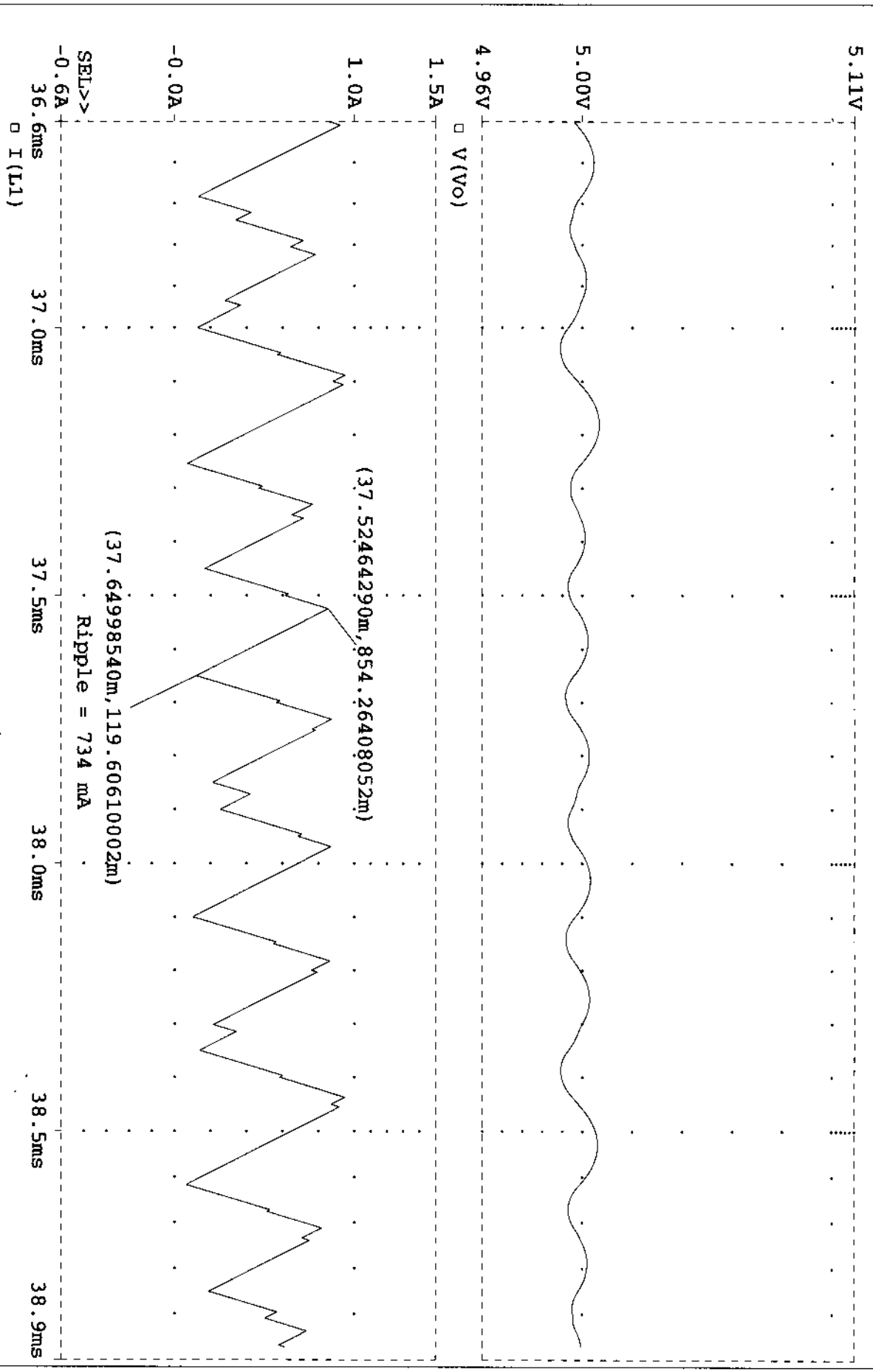

Date: June 19, 2000

Page 1


Time: 10:13:39

94D

Date/Time run: 06/19/100 10:07:36 * D:\NAU\CLASS\egr456\SPICE\BUCK\CONT2.SCH

Temperature: 27.0

(E) CONT2.dat

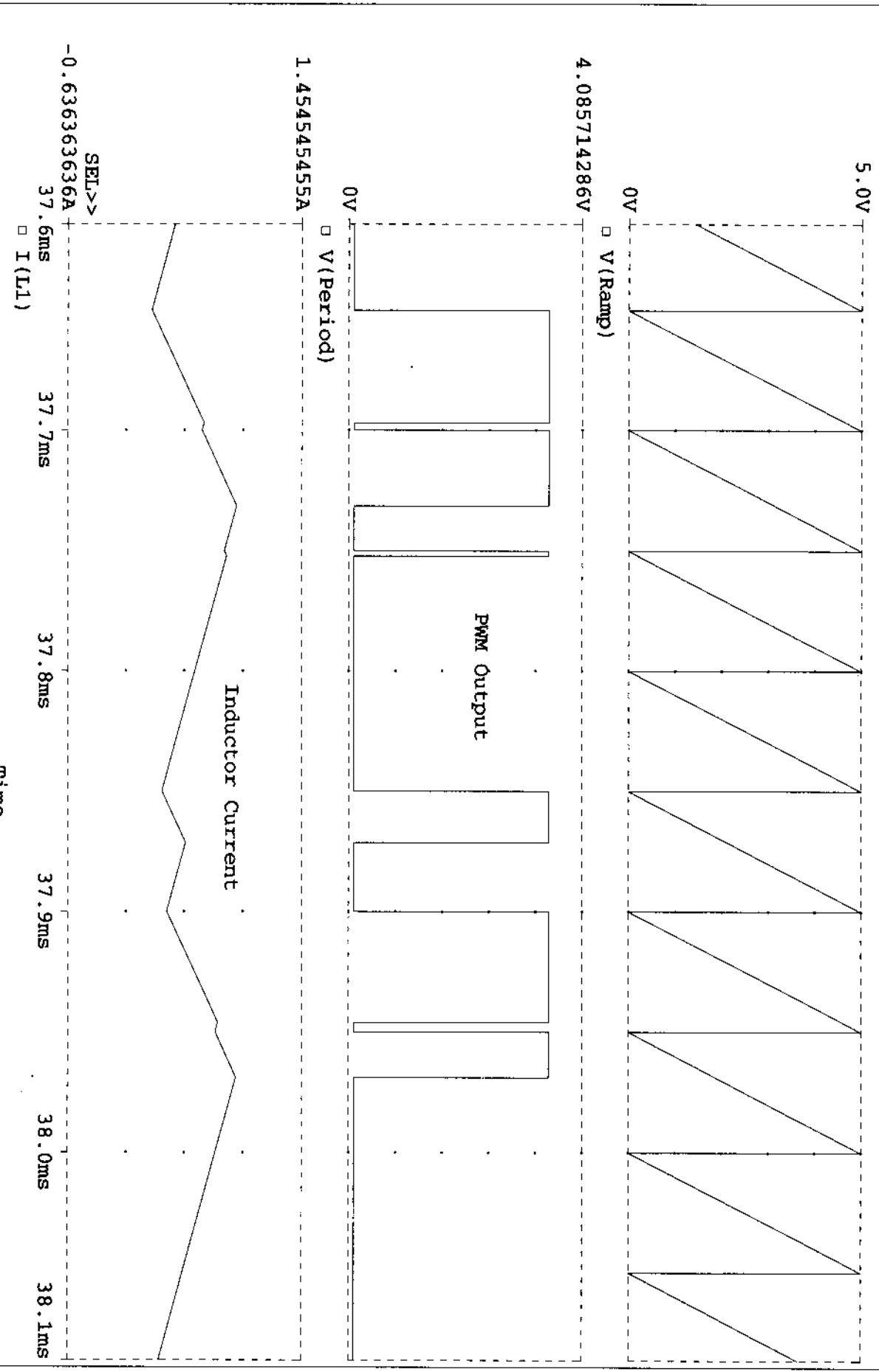

Date: June 19, 2000


Page 1

Time: 10:15:19


Buck Regulator - Discontinuous mode

as $I_o \downarrow, I_1 \rightarrow 0$

Inductor current is zero sometimes

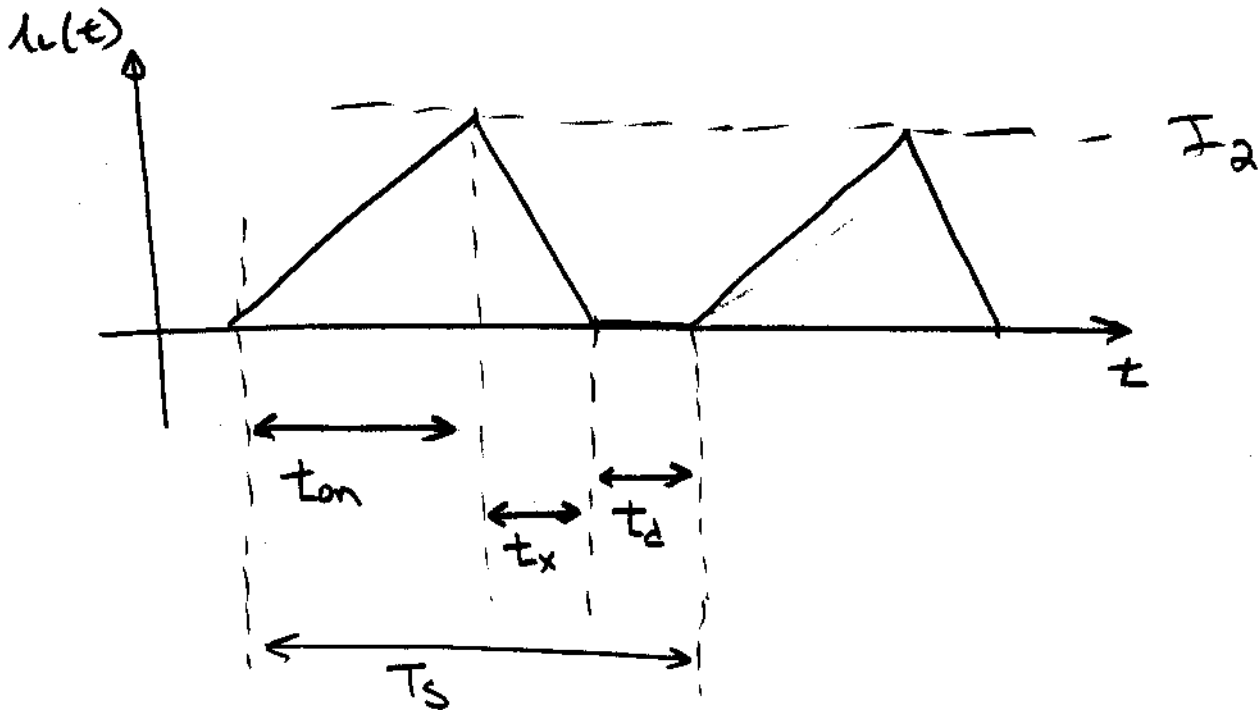

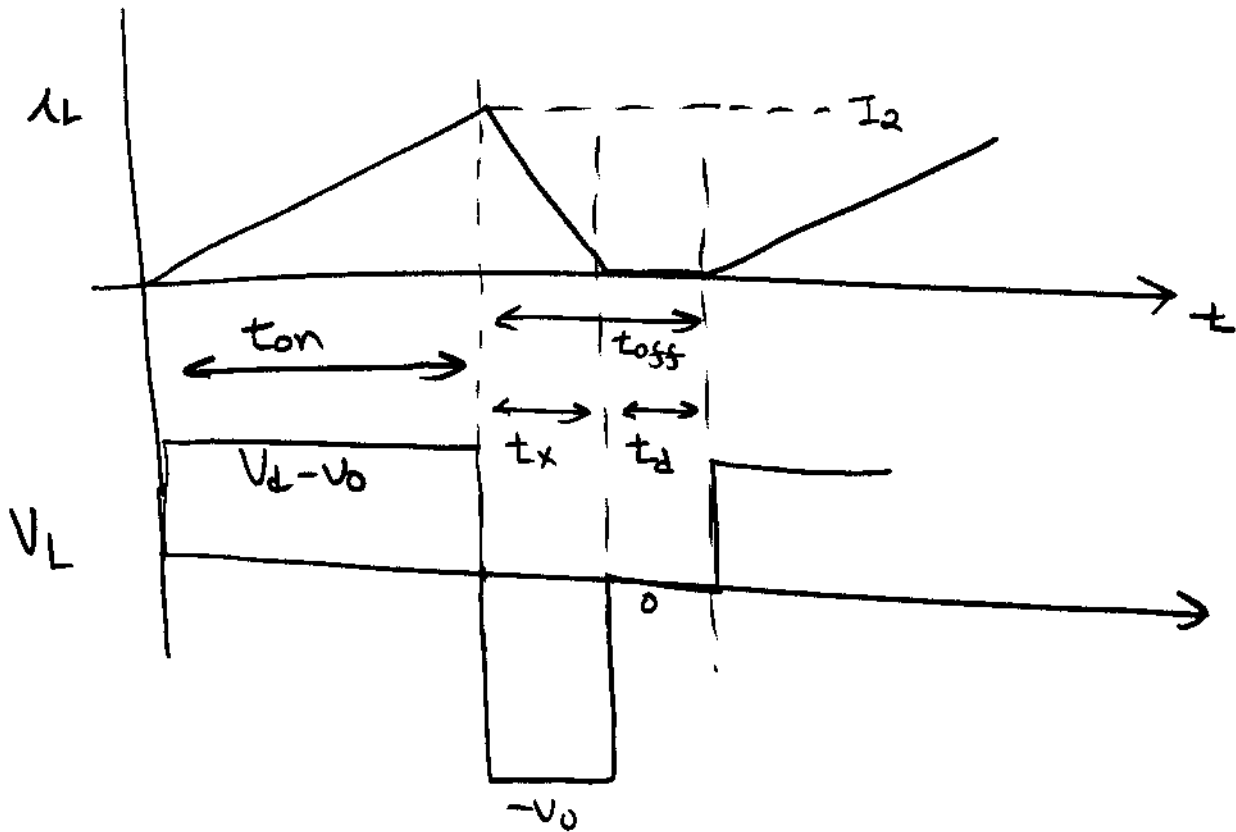In discontinuous mode, All energy stored in the inductor is dumped to output



for Average inductor current to be const,

$$\int_{T_s} V_L(t) dt = 0 \text{ for one period}$$

so

$$(V_d - V_o) t_{on} + (-V_o) t_x + 0 t_d = 0$$

$$V_o = V_d \left[\frac{t_{on}}{t_{on} + t_x} \right] \quad (1)$$

For an inductor

$$V_L = L \frac{di_L(t)}{dt} \Rightarrow i_L(t) = \frac{1}{L} \int V_L dt$$

For t_{on}

$$I_a = \frac{1}{L} (V_d - V_o) t_{on} \quad (2)$$

For t_x

$$I_a = \frac{1}{L} (V_o) t_x \quad (3)$$

Find average current

during t_{on} and t_x

$$\langle \hat{i}_L \rangle = I_a / 2 \quad \text{- avg inductor current}$$

during T_s

$$\langle i_L \rangle = \langle \hat{i}_L \rangle \left(\frac{t_{on} + t_x}{T_s} \right)$$

so

$$\langle i_L \rangle = \frac{I_a}{2} \left(\frac{t_{on} + t_x}{T_s} \right) = I_o \quad (4)$$

Solve equation (4) for $t_{on} + t_x$

$$t_{on} + t_x = \frac{2 I_o T_s}{I_a}$$

Sub into (1)

$$V_o = V_d \left[\frac{t_{on}}{\frac{2 I_o T_s}{I_a}} \right]$$

OR

$$V_o = V_d \left[\frac{t_{on} I_a}{2 I_o T_s} \right] \quad (5)$$

Now eliminate I_a with eq. (2)

$$V_o = V_d \left[\frac{t_{on} (V_d - V_o) t_{on}}{2 I_o T_s L} \right]$$

So

$$V_o \left[1 + \frac{V_o t_{on}^2}{2 I_o T_s L} \right] = \frac{t_{on}^2 V_o^2}{2 I_o T_s L}$$

$$V_o = \frac{t_{on}^2 V_o^2}{2 I_o T_s L + V_o t_{on}^2}$$

$$I_o \leq \left(\frac{V_o - V_o}{2L} \right) t_{on}$$

OR

$$\frac{V_o}{V_o} = \frac{D^2 V_o}{\frac{2 I_o L}{T_s} + D^2 V_o}$$

in Dis continuous mode - To keep V_o const with changing I_o , can change D .

$$D = \frac{t_{on}}{T_s}$$