

EE 456

Buck-Boost Regulator Design Continuous Mode Operation

Specify Input Voltage $V_D := 15 \cdot \text{volt}$

Specify Output Voltage $V_o := -20 \cdot \text{volt}$

Specify Switching Frequency $F_S := 20 \cdot \text{kHz}$

$\mu\text{s} = 10^{-6} \cdot \text{sec}$

$$T_S := \frac{1}{F_S}$$

$$T_S = 50 \cdot \mu\text{s}$$

Specify the Assumed Efficiency

Eff := 90 %

Specify the Max output Current

The output Power is

$$P_{\text{out}} := \frac{50 \cdot \text{watt}}{\text{Eff}}$$

The output current is

$$I_o := \left| \frac{P_{\text{out}}}{V_o} \right|$$

$$I_o = 2.778 \cdot \text{amp}$$

Find Ton and Toff

$T_{\text{off}} := 1 \cdot \mu\text{s}$

$T_{\text{on}} := 1 \cdot \mu\text{s}$

Given

$$-V_o = V_D \cdot \left(\frac{T_{\text{on}}}{T_S - T_{\text{on}}} \right)$$

$$T_{\text{on}} := \text{find}(T_{\text{on}})$$

$$T_{\text{on}} = 28.571 \cdot \mu\text{s}$$

Find the range of Inductors that will operate in discontinuous mode

Specify the minimum current we want the supply to operate in the continuous mode

$$I_{\min} := \frac{I_o}{10}$$

$$D := \frac{T_{\text{on}}}{T_S}$$

$$L := \frac{V_D \cdot T_{\text{on}}}{2 \cdot I_{\min}} \cdot (1 - D)$$

For Continuous Mode, We need L greater than $L = 330.612 \cdot \mu\text{H}$

Choose the Inductor $L := 560 \cdot \mu\text{H}$ Coilcraft PCV-2-564-08

Find the Min and max inductor currents

$$I_1 := 1 \cdot \text{amp} \quad I_2 := 1 \cdot \text{amp}$$

Given

$$\frac{I_1 + I_2}{2} = \frac{I_o}{1 - D}$$

$$I_1 - I_2 = V_D \cdot \frac{T_{\text{on}}}{L}$$

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} := \text{Find}(I_1, I_2) \quad I_1 = 6.864 \cdot \text{amp} \quad I_2 = 6.099 \cdot \text{amp}$$

Now choose the capacitor

$$\text{Energy dissipated per cycle} \quad E_o := |V_o| \cdot I_o \cdot T_S \quad E_o = 2.778 \cdot 10^{-3} \cdot \text{joule}$$

$$\text{Specify the ripple desired.} \quad V_{\text{CR}} := 60 \cdot \text{mV}$$

$$\text{Initial Guess} \quad C := 1000 \cdot \mu\text{F}$$

Given

$$\frac{1}{2} \cdot C \cdot (|V_o| + V_{\text{CR}})^2 - \frac{1}{2} \cdot C \cdot (|V_o|)^2 = E_o$$

$$C := \text{find}(C)$$

$$C = 2.311 \cdot 10^3 \cdot \mu\text{F}$$

Choose the next standard value $C := 10000 \cdot \mu\text{F}$

Calculate the ripple with the chosen capacitor.

Given

$$\frac{1}{2} \cdot C \cdot (|V_o| + V_{CR})^2 - \frac{1}{2} \cdot C \cdot (|V_o|)^2 = E_o$$

$$V_{CR} := \text{find}(V_{CR}) \quad V_{CR} = 13.884 \cdot \text{mV}$$

Choose the filter capacitor using the capacitor ESR.

Assume that the major component of the ripple comes from the capacitor ESR

Specify the ripple due to the ESR $V_{CR} := 60 \cdot \text{mV}$

$$\text{ESR} := \frac{V_{CR}}{I_1} \quad \text{ESR} = 8.741 \cdot 10^{-3} \cdot \Omega$$

For all electrolytic caps, assume that $\text{ESR} \cdot C = 80 \text{ms}$

$$C := \frac{80 \cdot \mu\text{s}}{\text{ESR}} \quad C = 9152.17939 \cdot \mu\text{F}$$

Choose the next size std capacitor $C := 10000 \cdot \mu\text{F}$

Calculate the Capacitor RMS Ripple Current

$$I_x := \frac{I_1 + I_2}{2} \quad I_x = 6.481 \cdot \text{amp}$$

Use came cap as boost converter.

$$I_{\text{rms}} := \sqrt{\frac{1}{T_S} \cdot \left[\int_{0 \cdot \text{sec}}^{T_{\text{on}}} I_o^2 dt + \int_{T_{\text{on}}}^{T_S} (I_o - I_x)^2 dt \right]}$$

$$I_{\text{rms}} = 3.208 \cdot \text{amp}$$

Summary

$$L = 560 \cdot \mu\text{H}$$

$$I_2 = 6.099 \cdot \text{amp}$$

$$T_{\text{on}} = 28.571 \cdot \mu\text{s}$$

$$T_{\text{off}} = 1 \cdot \mu\text{s}$$

$$V_D = 15 \cdot \text{volt}$$

$$V_o = -20 \cdot \text{volt}$$

$$I_o = 2.778 \cdot \text{amp}$$

$$C = 1 \cdot 10^4 \cdot \mu\text{F}$$

$$V_{\text{CR}} = 60 \cdot \text{mV}$$

Average Inductor Current

$$\frac{I_1 + I_2}{2} = 6.481 \cdot \text{amp}$$

EE 456

Buck-Boost Regulator Design Continuous Mode Operation

Specify Input Voltage $V_D := 12 \cdot \text{volt}$

Specify Output Voltage $V_o := -20 \cdot \text{volt}$

Specify Switching Frequency $F_S := 20 \cdot \text{kHz}$

$\mu\text{s} = 10^{-6} \cdot \text{sec}$

$$T_S := \frac{1}{F_S}$$

$$T_S = 50 \cdot \mu\text{s}$$

Specify the Assumed Efficiency

Eff := 90 %

Specify the Max output Current

The output Power is

$$P_{\text{out}} := \frac{50 \cdot \text{watt}}{\text{Eff}}$$

The output current is

$$I_o := \left| \frac{P_{\text{out}}}{V_o} \right|$$

$$I_o = 2.778 \cdot \text{amp}$$

Find Ton and Toff

$T_{\text{off}} := 1 \cdot \mu\text{s}$

$T_{\text{on}} := 1 \cdot \mu\text{s}$

Given

$$-V_o = V_D \cdot \left(\frac{T_{\text{on}}}{T_S - T_{\text{on}}} \right)$$

$$T_{\text{on}} := \text{find}(T_{\text{on}})$$

$$T_{\text{on}} = 31.25 \cdot \mu\text{s}$$

Find the range of Inductors that will operate in discontinuous mode

Specify the minimum current we want the supply to operate in the continuous mode

$$I_{\min} := \frac{I_o}{10}$$

$$D := \frac{T_{\text{on}}}{T_S}$$

$$L := \frac{V_D \cdot T_{\text{on}}}{2 \cdot I_{\min}} \cdot (1 - D)$$

For Continuous Mode, We need L greater than $L = 253.125 \cdot \mu\text{H}$

Choose the Inductor $L := 560 \cdot \mu\text{H}$ Coilcraft PCV-2-564-08

Find the Min and max inductor currents

$$I_1 := 1 \cdot \text{amp} \quad I_2 := 1 \cdot \text{amp}$$

Given

$$\frac{I_1 + I_2}{2} = \frac{I_o}{1 - D}$$

$$I_1 - I_2 = V_D \cdot \frac{T_{\text{on}}}{L}$$

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} := \text{Find}(I_1, I_2) \quad I_1 = 7.742 \cdot \text{amp} \quad I_2 = 7.073 \cdot \text{amp}$$

Now choose the capacitor

$$\text{Energy dissipated per cycle} \quad E_o := |V_o| \cdot I_o \cdot T_S \quad E_o = 2.778 \cdot 10^{-3} \cdot \text{joule}$$

$$\text{Specify the ripple desired.} \quad V_{\text{CR}} := 60 \cdot \text{mV}$$

$$\text{Initial Guess} \quad C := 1000 \cdot \mu\text{F}$$

Given

$$\frac{1}{2} \cdot C \cdot (|V_o| + V_{\text{CR}})^2 - \frac{1}{2} \cdot C \cdot (|V_o|)^2 = E_o$$

$$C := \text{find}(C)$$

$$C = 2.311 \cdot 10^3 \cdot \mu\text{F}$$

Choose the next standard value $C := 10000 \cdot \mu\text{F}$

Calculate the ripple with the chosen capacitor.

Given

$$\frac{1}{2} \cdot C \cdot (|V_o| + V_{CR})^2 - \frac{1}{2} \cdot C \cdot (|V_o|)^2 = E_o$$

$$V_{CR} := \text{find}(V_{CR}) \quad V_{CR} = 13.884 \cdot \text{mV}$$

Choose the filter capacitor using the capacitor ESR.

Assume that the major component of the ripple comes from the capacitor ESR

Specify the ripple due to the ESR $V_{CR} := 60 \cdot \text{mV}$

$$\text{ESR} := \frac{V_{CR}}{I_1} \quad \text{ESR} = 7.75 \cdot 10^{-3} \cdot \Omega$$

For all electrolytic caps, assume that $\text{ESR} \cdot C = 80 \text{ms}$

$$C := \frac{80 \cdot \mu\text{s}}{\text{ESR}} \quad C = 10322.97178 \cdot \mu\text{F}$$

Choose the next size std capacitor $C := 10000 \cdot \mu\text{F}$

Calculate the Capacitor RMS Ripple Current

$$I_x := \frac{I_1 + I_2}{2} \quad I_x = 7.407 \cdot \text{amp}$$

Use came cap as boost converter.

$$I_{\text{rms}} := \sqrt{\frac{1}{T_S} \cdot \left[\int_{0 \cdot \text{sec}}^{T_{\text{on}}} I_o^2 dt + \int_{T_{\text{on}}}^{T_S} (I_o - I_x)^2 dt \right]}$$

$$I_{\text{rms}} = 3.586 \cdot \text{amp}$$

Summary

$$L = 560 \cdot \mu\text{H}$$

$$I_2 = 7.073 \cdot \text{amp}$$

$$T_{\text{on}} = 31.25 \cdot \mu\text{s}$$

$$T_{\text{off}} = 1 \cdot \mu\text{s}$$

$$V_D = 12 \cdot \text{volt}$$

$$V_o = -20 \cdot \text{volt}$$

$$I_o = 2.778 \cdot \text{amp}$$

$$C = 1 \cdot 10^4 \cdot \mu\text{F}$$

$$V_{\text{CR}} = 60 \cdot \text{mV}$$


$$\text{Average Inductor Current} \quad \frac{I_1 + I_2}{2} = 7.407 \cdot \text{amp}$$

Power Chokes – Vertical Mount



The PCV-2 Series uses a ferrite bobbin core to provide the highest possible inductance at the lowest cost. It features 130°C class insulation and comes in a wide range of standard values.

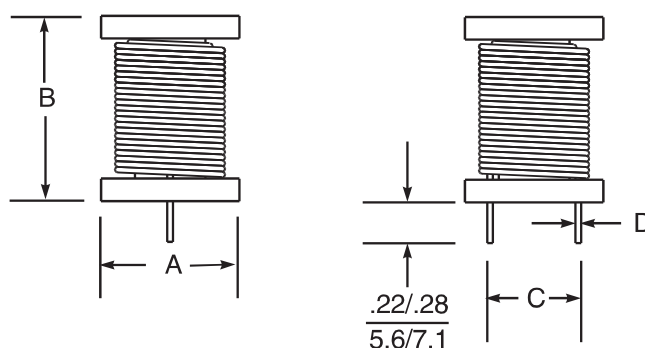Coilcraft **Designer's Kit P205** contains samples of the parts shown in bold as well as values from our PCV-0 Series. To order, contact Coilcraft.



Part Number	Inductance ¹ ±10% (μH)	Current Rating ² (Amps)	DCR Max (Ω)	A Max	B Max	C ±.015/0,38	D ±.004/0,10
PCV-2-103-05	10	5	.015	.61/15,49	.83/21,08	.42/10,67	.042/1,07
PCV-2-103-10	10	10	.010	.61/15,49	.83/21,08	.50/12,70	.054/1,37
PCV-2-223-05	22	5	.020	.61/15,49	.83/21,08	.42/10,67	.042/1,07
PCV-2-223-10	22	10	.015	.86/21,84	.83/21,08	.58/14,73	.054/1,37
PCV-2-473-05	47	5	.035	.70/17,78	.83/21,08	.48/12,19	.038/0,97
PCV-2-473-10	47	10	.020	1.00/25,40	.83/21,08	.70/17,78	.054/1,37
PCV-2-104-03	100	3	.080	.84/21,34	.83/21,08	.58/14,73	.031/0,79
PCV-2-104-05	100	5	.045	.84/21,34	.83/21,08	.70/17,78	.042/1,07
PCV-2-104-10	100	10	.032	1.05/26,67	1.10/27,94	.88/22,35	.054/1,37
PCV-2-184-05	180	5	.092	.80/20,32	.90/22,86	.58/14,73	.035/0,89
PCV-2-184-10	180	10	.048	1.44/36,58	1.10/27,94	1.05/26,67	.054/1,37
PCV-2-224-05	220	5	.075	1.05/26,67	1.10/27,94	.75/19,05	.042/1,07
PCV-2-274-03	270	3	.13	1.00/25,40	.83/21,08	.75/19,05	.035/0,89
PCV-2-274-05	270	5	.080	1.05/26,67	1.05/26,67	.80/20,32	.042/1,07
PCV-2-274-10	270	10	.060	1.50/38,10	1.10/27,94	1.08/27,43	.054/1,37
PCV-2-394-05	390	5	.13	1.10/29,34	.83/21,08	.85/21,59	.038/0,97
PCV-2-564-02	560	2	.27	.80/20,32	.90/22,86	.57/14,48	.028/0,71
PCV-2-564-06	560	6	.17	1.21/30,73	1.10/27,94	.90/22,86	.038/0,97
PCV-2-564-08	560	8	.090	1.50/38,10	1.43/36,32	1.08/27,43	.054/1,37
PCV-2-684-01	680	1	.70	.70/17,78	.83/21,08	.50/12,70	.018/0,46
PCV-2-105-02	1000	2	.37	1.00/25,40	.83/21,08	.72/18,29	.028/0,71

¹ Tested at 15.75 kHz, .1 Vrms, with DC bias applied up to the rated current.

² Parts are designed for 40°C Max temperature rise at the rated current.

Parts in bold type are included in Coilcraft Designer's Kit No. P205.

Coilcraft

Document 136 Revised 6/25/97

1102 Silver Lake Road Cary, Illinois 60013 Phone 847/639-6400 Fax 847/639-1469
E-mail info@coilcraft.com Data by Fax 800/651-6974 Web http://www.coilcraft.com

