

Due Monday, April 25th at 5pm

1. (10 pts) In a buck-boost converter, consider all components to be ideal. Let  $V_{in}$  be 8-40V,  $V_o=15V$  (regulated),  $f_s=20kHz$ , and  $C=470\mu F$ . Calculate  $L_{min}$  that will keep the converter operating in continuous-conduction mode if  $P_o \geq 2W$ .

$$V_{inmin} := 8V \quad V_{inmax} := 40V \quad V_o := 15V \quad f_s := 20kHz \quad C_1 := 470\mu F$$

$$P_{omin} := 2W \quad P_{inmin} := 2W \quad T_s := \frac{1}{f_s} = 50 \cdot \mu s$$

$$I_o := \frac{P_{omin}}{V_o} \quad I_o = 0.133 A$$

Use the equation for Duty Cycle of a buck-boost converter to find the range of D. Note that the minimum duty cycle occurs when the input voltage is a maximum.

$$D_{min} := \frac{V_o}{V_o + V_{inmax}} \quad D_{min} = 0.273 \quad D_{max} := \frac{V_o}{V_o + V_{inmin}} \quad D_{max} = 0.652$$

$$I_{inmin} := \frac{P_{inmin}}{V_{inmax}} \quad I_{inmin} = 0.05 A$$

*Since the average value of the inductor current is the sum of the output current (constant) and the input current, the inductor current will be a minimum when the average input current is a minimum.*

To get the minimum average current through the inductor, that happens when  $I_L$  is at a minimum

$$I_{Lmin} := I_o + I_{inmin} \quad I_{Lmin} = 0.183 A$$

$$\Delta i_L := 2 \cdot I_{Lmin} \quad \Delta i_L = 0.367 A$$

$$L_{min} := \frac{V_{inmax}}{\Delta i_L} \cdot D_{min} \cdot T_s \quad L_{min} = 1.488 \text{ mH}$$

Use this inductor value to check for continuous conduction mode.

$$i_{Lmin} := I_{Lmin} - \frac{1}{2} \cdot \frac{V_{inmax}}{L_{min}} \cdot D_{min} \cdot T_s \quad i_{Lmin} = 0 A \quad \text{This is the boundary condition.}$$

To check the other value of inductance that you could calculate:

$$I_{Lmax} := I_o + \frac{P_{inmin}}{V_{inmin}} \quad I_{Lmax} = 0.383 \text{ A}$$

$$\Delta i_{Lmax} := 2 \cdot I_{Lmax} \quad \Delta i_{Lmax} = 0.767 \text{ A}$$

$$L_{other} := \frac{V_{inmin}}{\Delta i_{Lmax}} \cdot D_{max} \cdot T_s \quad L_{other} = 0.34 \text{ mH}$$

Yes, this is smaller, but will it work over the entire range of duty cycles?

$$i_{Lcheck} := I_{Lmax} - \frac{1}{2} \cdot \frac{V_{inmin}}{L_{other}} \cdot D_{max} \cdot T_s \quad i_{Lcheck} = 0 \text{ A}$$

so this works as expected, but then when you use  $L_{other}$  with the minimum duty cycle condition:

$$i_{Lcheck2} := I_{Lmin} - \frac{1}{2} \cdot \frac{V_{inmax}}{L_{other}} \cdot D_{min} \cdot T_s \quad i_{Lcheck2} = -0.618 \text{ A}$$

Puts the converter into DCM at minimum duty cycle.

$$i_{Lmin} := I_{Lmax} - \frac{1}{2} \cdot \frac{V_{inmin}}{L_{min}} \cdot D_{max} \cdot T_s \quad i_{Lmin} = 0.296 \text{ A}$$

This is the boundary condition.

**2. (12 pts Extra Credit) In a buck-boost converter,  $V_{in}=12V$ ,  $V_o=15V$ ,  $I_o=250mA$ ,  $L=150\mu H$ ,  $C=470\mu F$ , and  $f_s=20kHz$ .**

$$V_{in} := 12V \quad V_o = 15V \quad I_{o2} := 250mA \quad L_2 := 150\mu H \quad C_2 := 470\mu F \quad f_s = 20 \cdot kHz$$

**(a) Calculate  $\Delta V_o$  (peak-peak)**

$$T_s = 50 \cdot \mu s$$

$$D_2 := \frac{V_o}{V_o + V_{in}} \quad D_2 = 0.556$$

First need to find  $I_{oB}$  to see if we're in continuous conduction mode.

$$I_{oB} := \frac{T_s \cdot V_o}{2 \cdot L_2} \cdot (1 - D_2)^2 \quad I_{oB} = 493.8 \cdot mA$$

$I_{o2} < I_{oB}$  so the converter is in discontinuous conduction mode

Now that we know the converter is in discontinuous conduction mode, can solve for the actual duty cycle using the equation from Lecture #39

When the duty cycle is at a minimum,  $I_o$  will be a max

$$I_{oBmax} := \frac{T_s \cdot V_o}{2 \cdot L_2} \quad I_{oBmax} = 2.5 \text{ A}$$

$$D_{dcm} := \frac{V_o}{V_{in}} \cdot \sqrt{\frac{I_{o2}}{I_{oBmax}}} \quad D_{dcm} = 0.395$$

To find the  $\Delta V_o$ , need to look at the current through the diode. There will only be current through the diode when the switch is open ( $t_{off}$ ). This will be the same as the value of the current through the inductor at that time. When the switch changes from ton to toff, the current through inductor will be at its peak at that time.

$$i_{Lpeak} = \Delta i_L = i_{Dmax} \quad i_{Dmax} := \frac{V_{in}}{L_2} \cdot D_{dcm} \cdot T_s \quad i_{Dmax} = 1.581 \text{ A}$$

The current through the inductor will decay at a slope of  $-V_o/L$

$$slp_{neg} := \frac{-V_o}{L_2} \quad slp_{neg} = -100 \cdot \frac{kA}{s}$$

Next, plot this characteristic along with the average output current.


Find the equation of the line of the diode current while the switch is off

$$y = mx + b$$

$$i_{Dmax} = \text{slp}_{neg} \cdot D_{dcm} \cdot T_s + b \quad b := i_{Dmax} - \text{slp}_{neg} \cdot D_{dcm} \cdot T_s \quad b = 3.558 \text{ A}$$

$$\text{find out when } i_D = 0 \quad t_0 := \frac{0 - b}{\text{slp}_{neg}} \quad t_0 = 35.576 \mu\text{s}$$
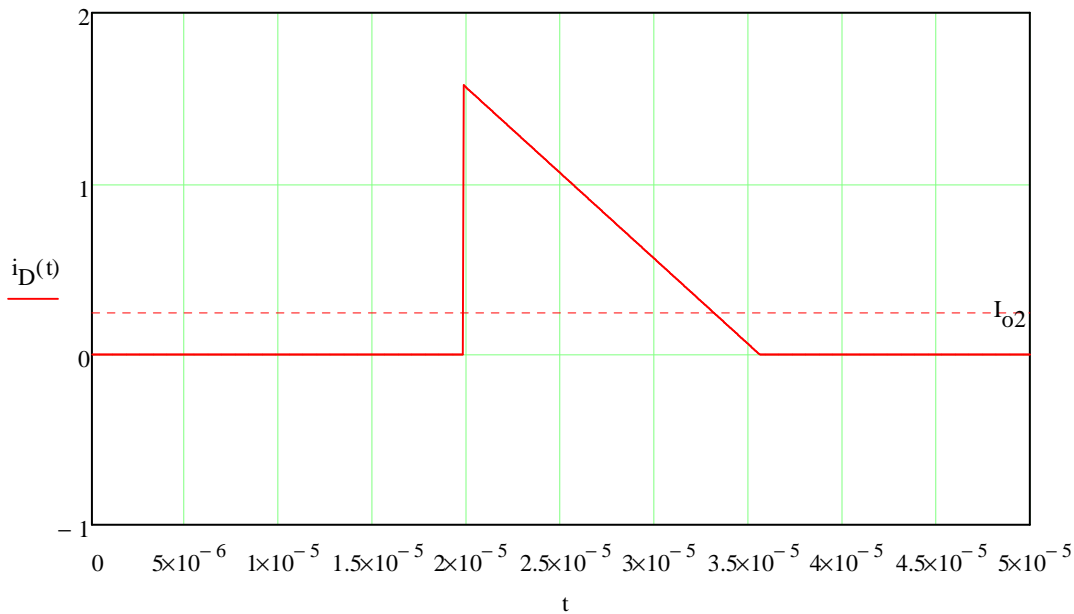
$$i_D(t) := \begin{cases} 0 & \text{if } 0 < D_{dcm} \cdot T_s \\ (\text{slp}_{neg} \cdot t + b) & \text{if } D_{dcm} \cdot T_s \leq t < (t_0) \\ 0 & \text{otherwise} \end{cases}$$



Find out at what time the diode current is equal to the output current

$$t_2 := \frac{I_{o2} - b}{\text{slp}_{neg}} \quad t_2 = 33.076 \mu\text{s} \quad \Delta t := t_0 - t_2 = 2.5 \mu\text{s}$$

$$\Delta Q_2 := I_{o2} \cdot D_{dcm} \cdot T_s + (T_s - t_0) \cdot I_{o2} + \frac{1}{2} \cdot I_{o2} \cdot \Delta t \quad \Delta Q_2 = 8.86 \times 10^{-6} \text{ C}$$

$$\text{As a check: } \Delta Q_{\text{check}} := \frac{1}{2} \cdot (i_{Dmax} - I_{o2}) \cdot (t_2 - D_{dcm} \cdot T_s) \quad \Delta Q_{\text{check}} = 8.86 \times 10^{-6} \text{ C}$$

From here, we can solve for the  $\Delta V_o$

$$\Delta V_o := \frac{\Delta Q_2}{C_2} \quad \Delta V_o = 18.85 \text{ mV}$$

**(b) Calculate the rms value of the ripple current through the diode.**

$$i_{Drms} := \sqrt{\frac{1}{T_s} \int_0^{T_s} i_D(t)^2 dt} \quad i_{Drms} = 0.513 \text{ A}$$

$$i_{D\_ripple\_rms} := \sqrt{i_{Drms}^2 - I_{o2}^2} \quad i_{D\_ripple\_rms} = 0.448 \text{ A}$$

**(c) Derive the expression for  $\Delta V_o$  (peak-peak) in a discontinuous-conduction mode in terms of the circuit parameters.**

*Just take one of your equations for  $\Delta Q$  and simplify it to where it only uses circuit parameter.*

$$\Delta V_{o\_expression} := \frac{I_{o2} \cdot \left[ T_s \cdot \left( 1 - \sqrt{\frac{I_{o2} \cdot 2 \cdot L_2}{T_s \cdot V_o}} \right) + \frac{I_{o2} \cdot L_2}{2 \cdot V_o} \right]}{C_2}$$

As a check:

$$\Delta V_{o\_expression} = 18.85 \text{ mV} \quad \text{Same as above, so expression must be right.}$$

**(d) If  $I_o$  is now equal to  $0.5 \cdot I_{oB}$ , calculate  $\Delta V_o$  (peak-peak)**

$$I_{onew} := \frac{1}{2} \cdot I_{oB} \quad I_{onew} = 246.914 \text{ mA}$$

$$\Delta V_{o\_new} := \frac{I_{onew} \cdot \left[ T_s \cdot \left( 1 - \sqrt{\frac{I_{onew} \cdot 2 \cdot L_2}{T_s \cdot V_o}} \right) + \frac{I_{onew} \cdot L_2}{2 \cdot V_o} \right]}{C_2}$$

$$\Delta V_{o\_new} = 18.66 \text{ mV}$$