

PSpice Applications for Power Electronics

jonathan@onyxtech.co.kr

TEL: 031-908-7577

FAX: 031-908-7579

Mobile: 011-237-3846

Magnetic Core Modeling

- The parameters in the model library([magnetics.lib](#)) were derived from the data sheets for each core.

The Jiles-Atherton magnetics model is described in:



Theory of Ferromagnetic Hysteresis, by D C Jiles and D L Atherton,
Journal of Magnetism and Magnetic Materials, vol 61 (1986) pp 48-60

- Model parameters for ferrite material ([Philips 3C8](#)) were obtained by trial simulations, using the B-H curves from the manufacturer's catalog.

Then, the library was compiled from the data sheets for each core geometry.

Notice that only the geometric values change once a material is characterized.

Magnetic Core Modeling

➤ Notes:

- 1) Using a K device (formerly only for mutual coupling) with a model reference changes the meaning of the L device: **the inductance value becomes the number of turns for the winding.**
- 2) K devices can "get away" with specifying only one inductor, as in the example above, to simulate power inductors.

➤ Demonstration of power inductor B-H curve To view results with Probe (B-H curve):

- 1) **Add Trace for B(K1)**
- 2) **set X-axis variable to H(K1)**

Probe x-axis unit is Oersted

Probe y-axis unit is Gauss

Magnetic Core Modeling

Name	Meaning	Unit	Default
AREA	Mean magnetic cross section	cm ²	0.1
PATH	Mean magnetic path length	cm	1.0
GAP	Effective air-gap length	cm	0
PACK	Pack(stacking)		1.0
MS	Magnetic saturation	A/m	1E+6
ALPHA	Mean field parameter		1E-3
A	Shape parameter		1E+3
C	Domain wall-flexing constant		0.2
K	Domain wall-pinning constant		500

Method I

1. K=0 : Anhyseric Curve Setup
2. B_{max} : B_{max}=MS*0.01257
3. A : Get a Curve
4. K : Create Hysteresis
5. C : Initial Permeability

Method II

1. MS ; B_{max}/0.01257
2. 100A/m=1.25 oersted
3. MS, A, C, K ← B-H Loop
4. Core Size Area Path

Magnetic Core Modeling

```
* 3C81_LSW CORE model
* updated using Model Editor release 9.2.2 on 11/15/01 at 11:16
* The Model Editor is a PSpice product.
.MODEL 3C81_LSW CORE
+ GAP=0
+ MS=384.61E3
+ A=27.747
+ C=.2418
+ K=18.396
+ AREA=2.7900
+ PATH=14.400
*$
```

- Ferroxcube 3C81 Core: www.Ferroxcube.com

Magnetic Core Modeling

Example(Ferroxcube)

3C81 →

H(Oersted)	B(Gauss)
0	1100
0.176	0
3.125	4250
0.625	2560
0.625	3400

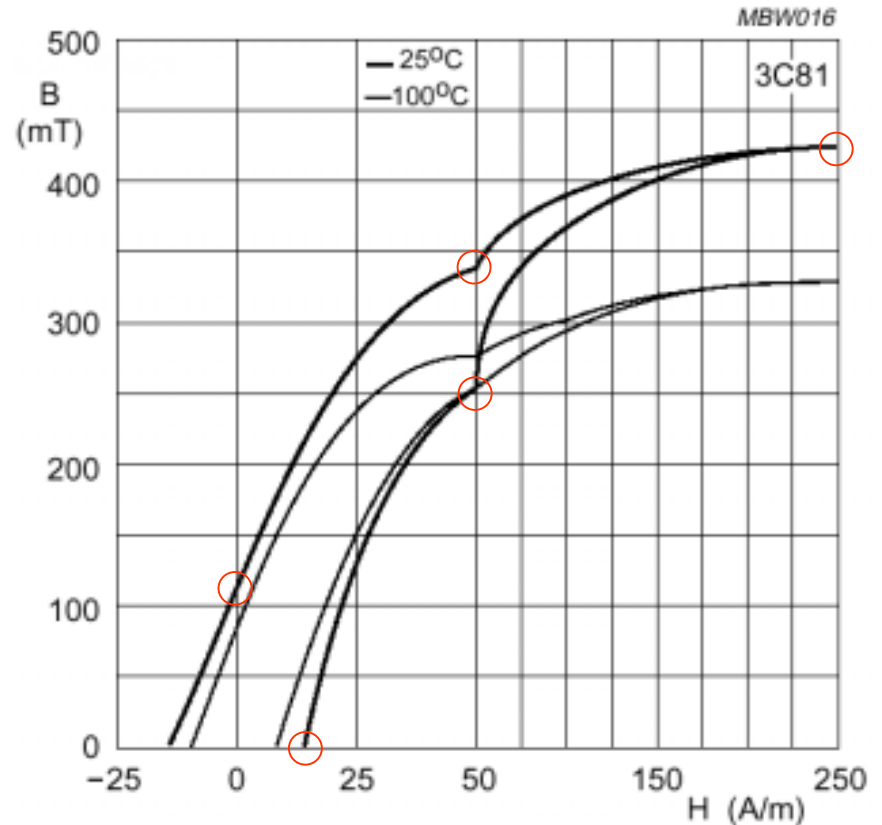


FIG. 1.

Magnetic Core Modeling

Example(Ferroxcube)

H(Oersted)	B(Gauss)
0	1100
0.176	0
3.125	4250
0.625	2560
0.625	3400

Active Parameters	
Initial Perm : 2700	
Name	Value
MS	384610
A	27.747
C	0.2418
K	18.396

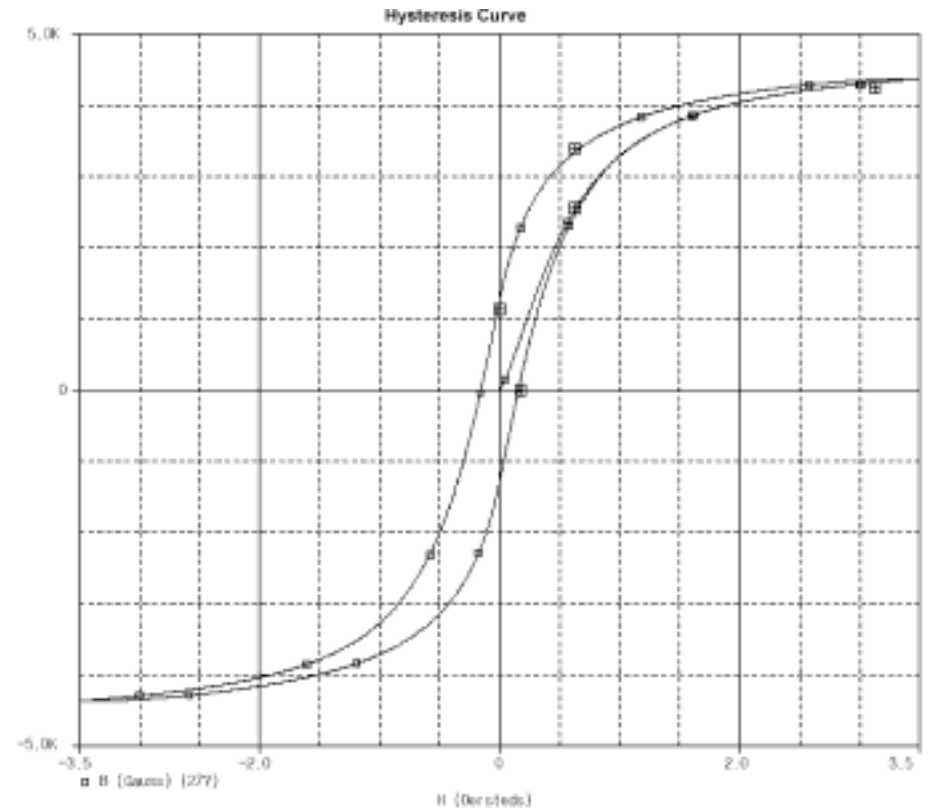


FIG. 2.

Magnetic Core Modeling

B-H Curve
 1. 3C81_LSW
 2. EC70_3C81

IOFF = 0
 IAMPL = 0.5
 FREQ = 10k
 TD = 1usec

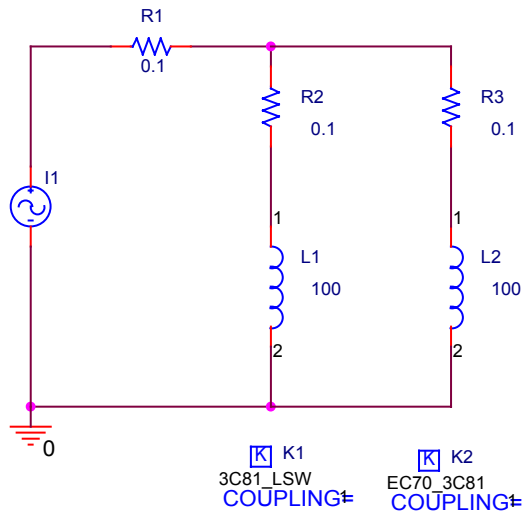


FIG. 3

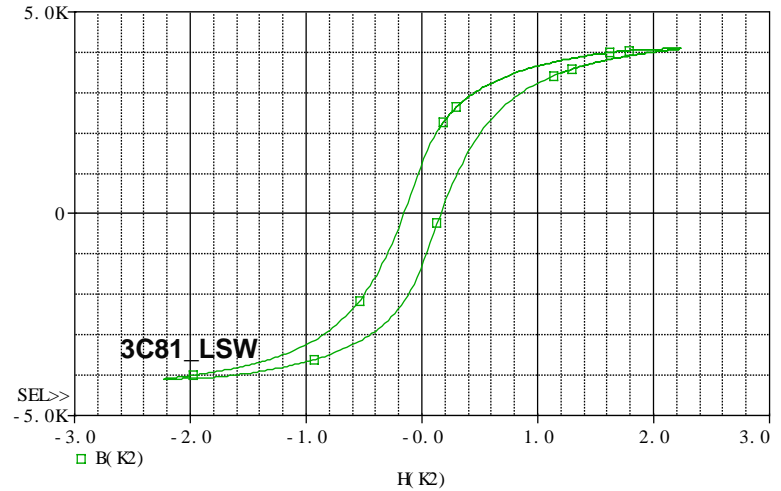


FIG. 4

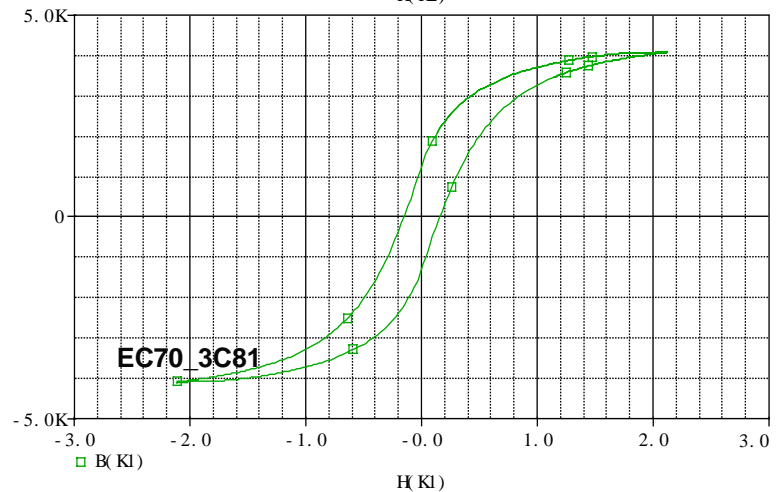


FIG. 5

Magnetic Core Modeling

B-H Curve

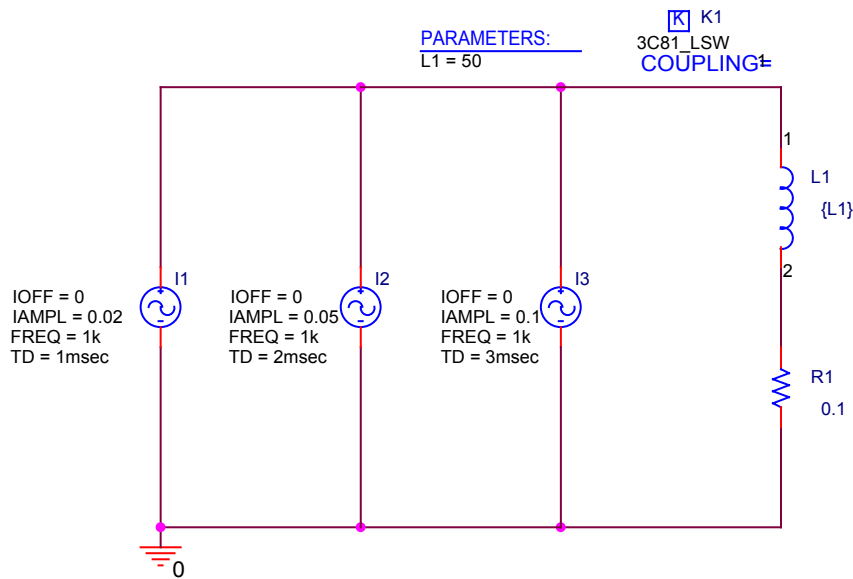


FIG. 6

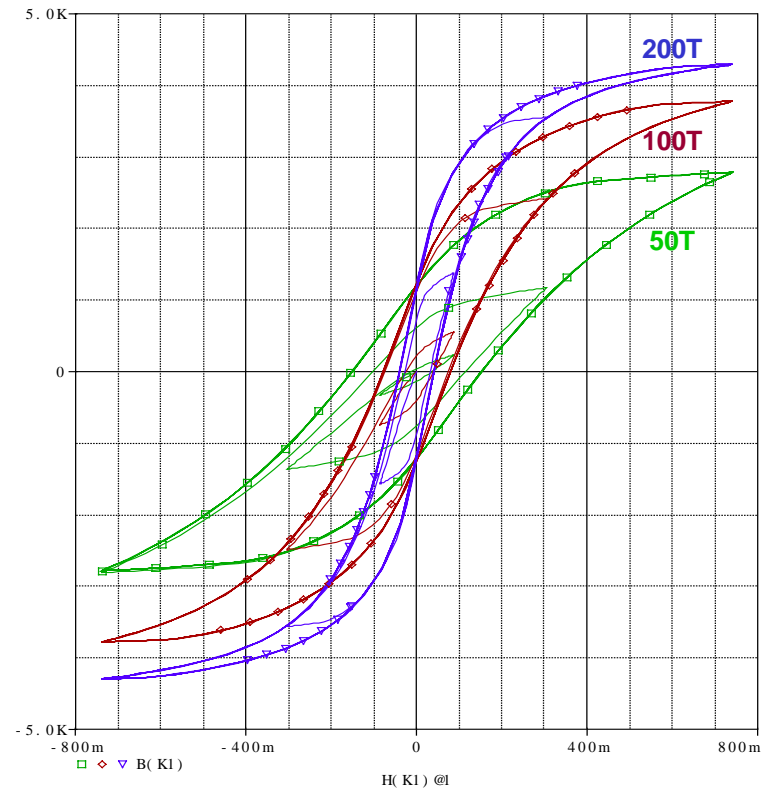


FIG. 7.

Modeling of Transformer

Equivalent Circuit : ABM





1. **K_Linear**
2. **PSpice Template Properties**

What's ABM(Analog Behavioral Modeling)?

Behavioral Modeling is the process of developing a model for a device or system component from the viewpoint of externally observed behavior rather than from a microscopic description

Two important application of Behavioral Modeling in the domain of analog simulation are : **modeling new device types** : and **block-box modeling of complex systems**.

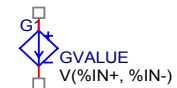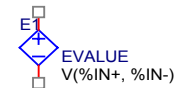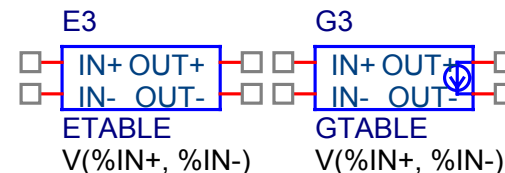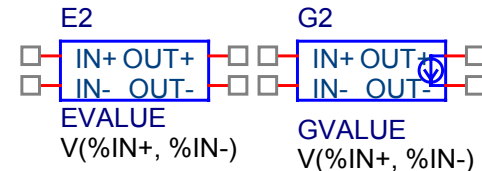Applications → Averaged-PWM Switch, Transformer, PWM IC



Transformer Equivalent Circuit

1. : ABM
2. : R, L C

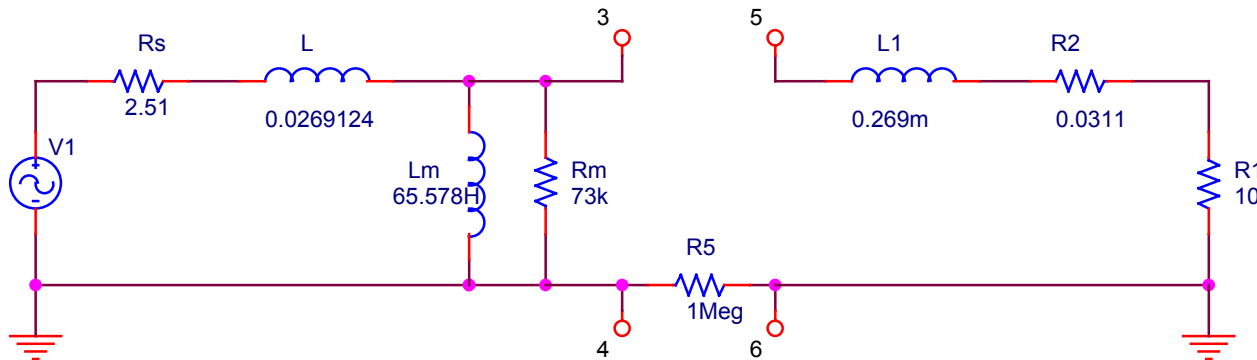


FIG. 8

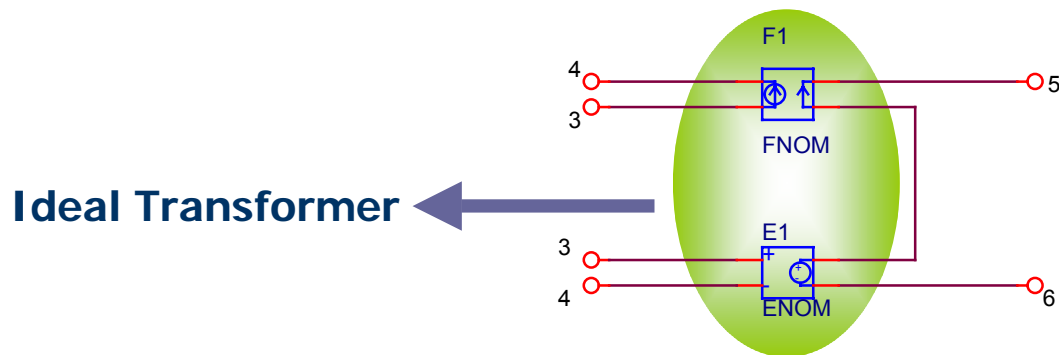


FIG. 9

K_Linear

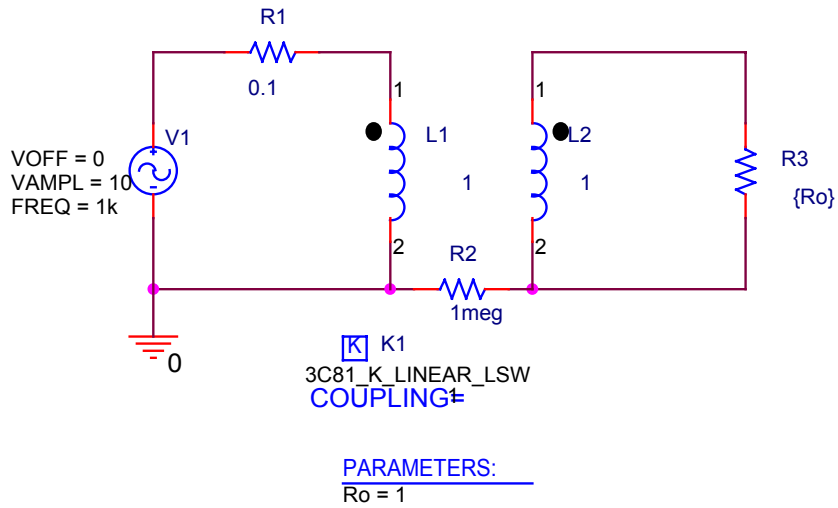


FIG. 10

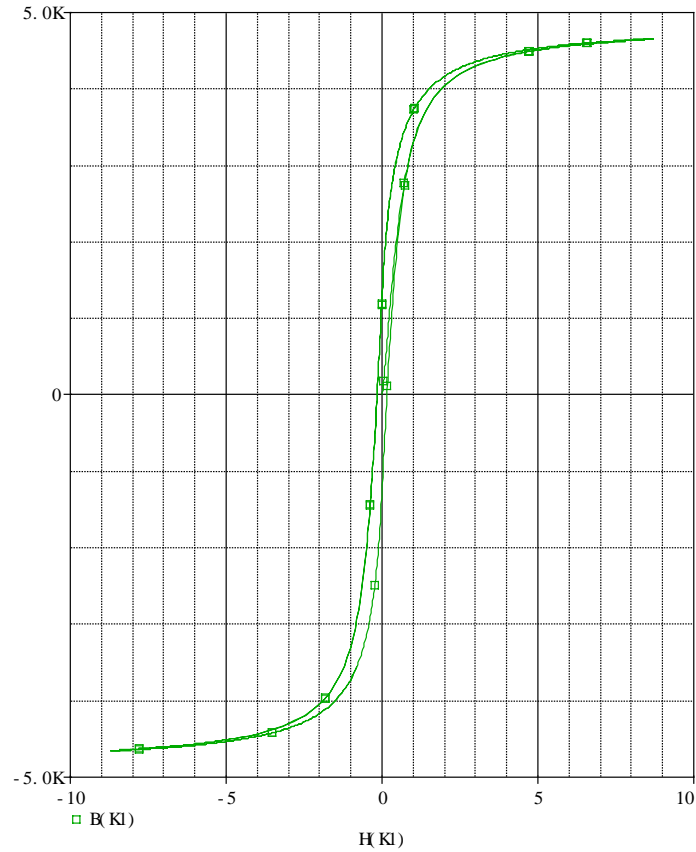


FIG. 11


XFRM_LINEAR or XFRM_NONLINEAR Editing

→ Transformer Template Properties


XFRM_LINEAR


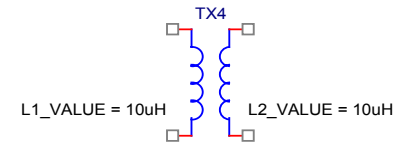
```
K^@REFDES L1^@REFDES L2^@REFDES
@COUPLING\nL1^@REFDES %1 %2
@L1_VALUE\nL2^@REFDES %3 %4 @L2_VALUE
```



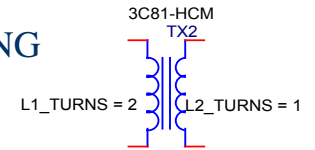
```
K^@REFDES L1^@REFDES L2^@REFDES @COUPLING
@MODEL\nL1^@REFDES %1 %2 @L1_TURNS
\nL2^@REFDES %3 %4 @L2_TURNS
```



XFRM_NONLINEAR


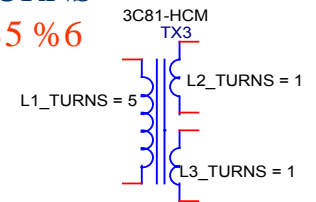
```
K^@REFDES L1^@REFDES L2^@REFDES L3^@REFDES
@COUPLING @MODEL\nL1^@REFDES %1 %2 @L1_TURNS
\nL2^@REFDES %3 %4 @L2_TURNS \nL3^@REFDES %5 %6
@L3_TURNS
```



Waveforms with Nonlinear Transformer

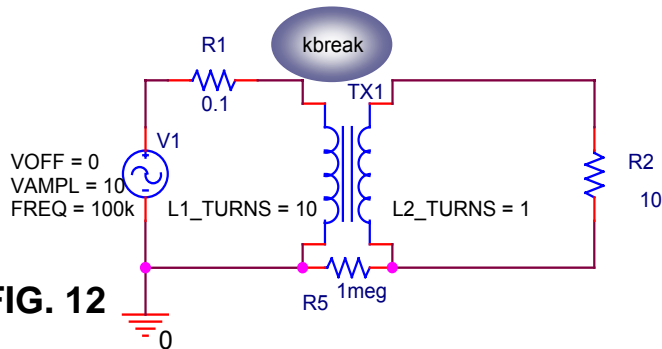


FIG. 12

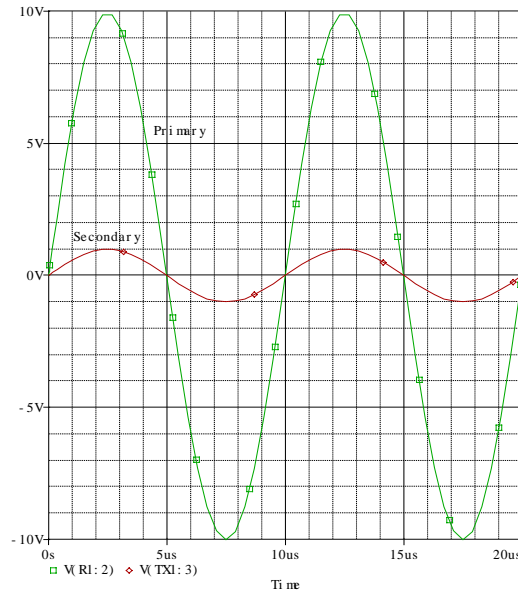


FIG. 13

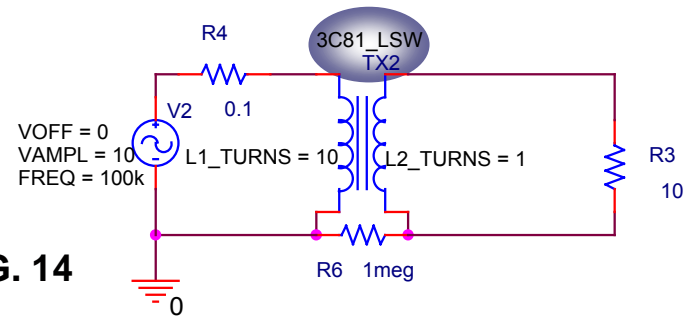


FIG. 14

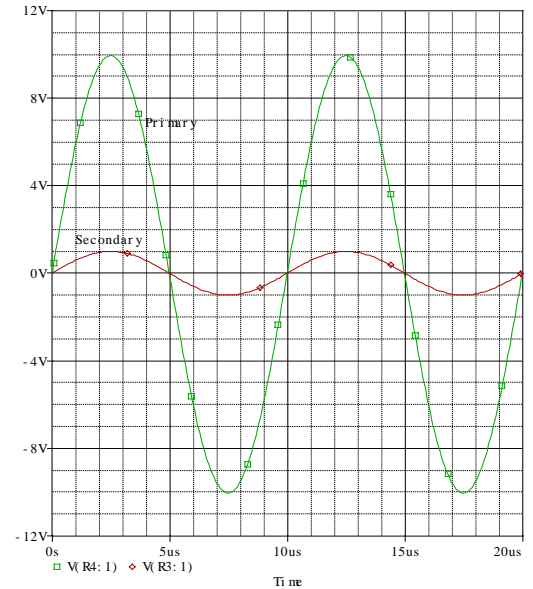


FIG. 15

XFRM_Nonlinear Template

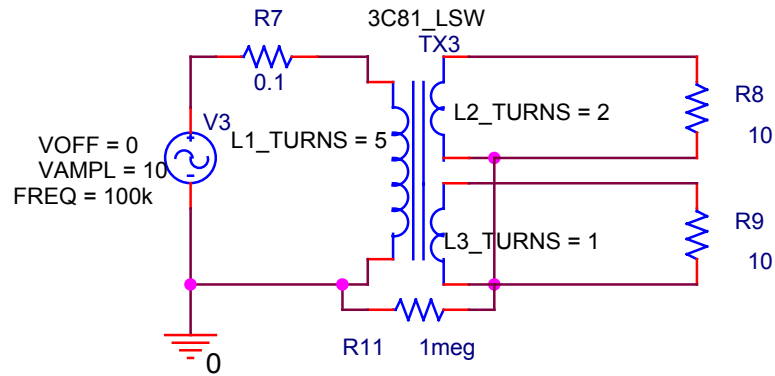


FIG. 16

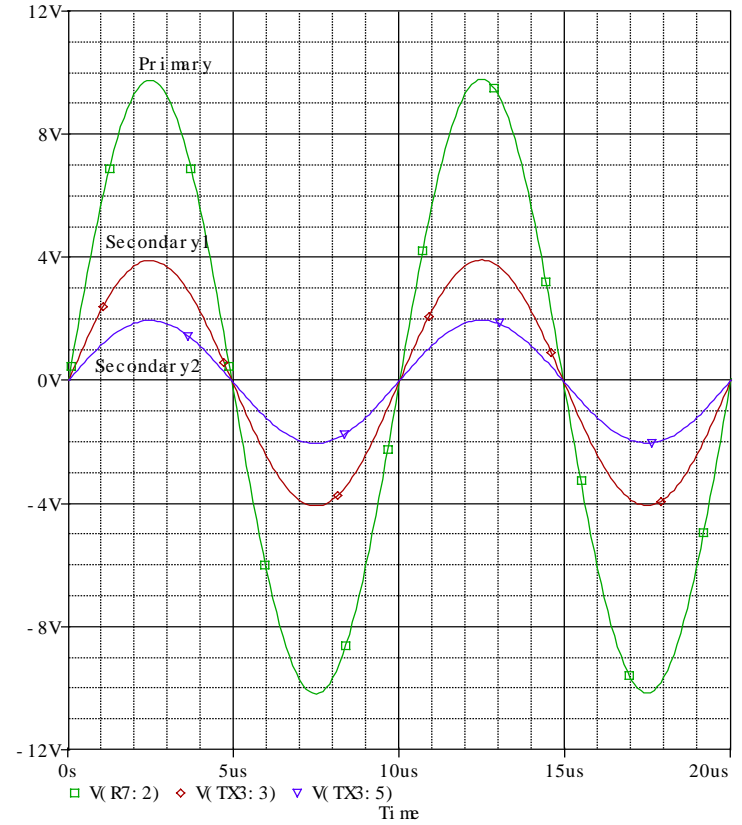


FIG. 17

Switching Mode Power Supply



● Isolation Type

Flyback
Forward
Half Bridge
Full Bridge
Push Pull

● Non-Isolation Type

Buck (Step Down)
Boost (Step Up)
Buck-Boost

Switching Mode Power Supply



Type

● Inductor

Buck (Step Down)

Boost (Step Up)

Buck-Boost

Flyback

Forward

Half Bridge

Full Bridge

Push Pull

● Capacitor

Cuk

Sepic

Zeta

Buck Converter

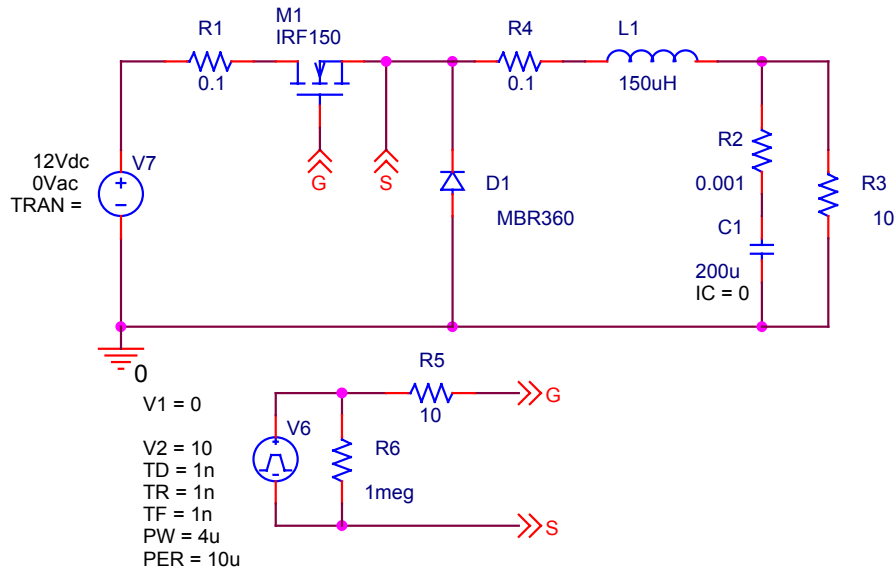


FIG. 18

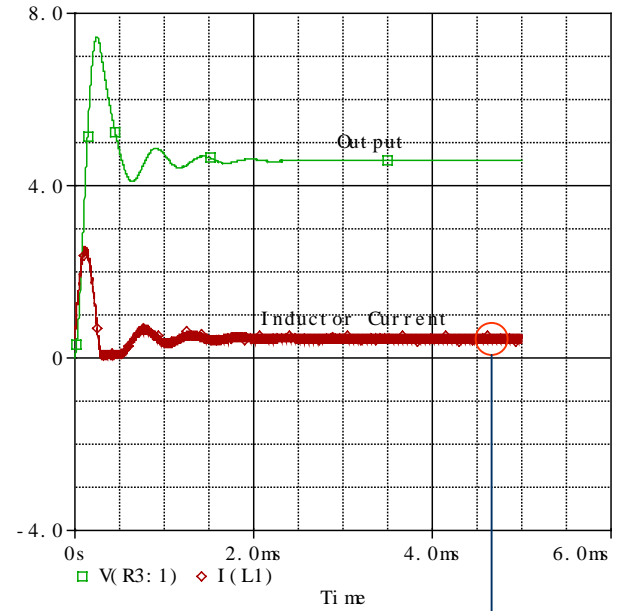


FIG. 19

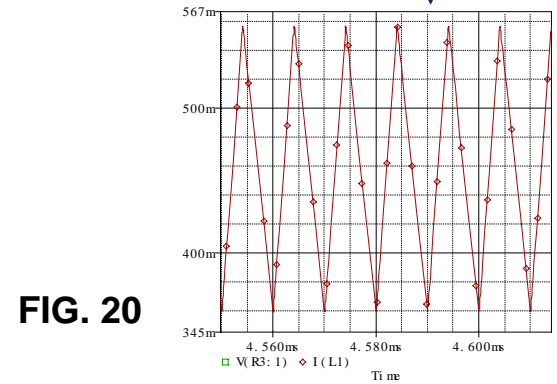


FIG. 20

Design of Buck Converter

Input Voltage : 12V

Output Voltage : 4.8V

Output Current : 0.1 ~ 3A

Frequency : 100kHz

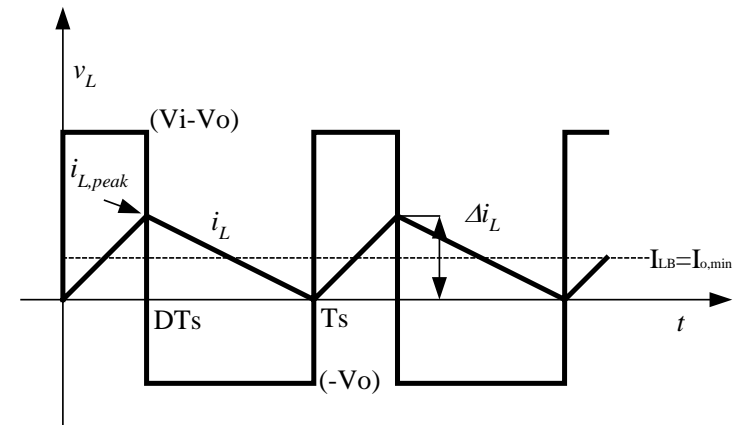


FIG. 21

$$v_L = L \frac{di}{dt} \quad (1)$$

$$(V_i - V_o)DT_s = V_o(1 - D)T_s \quad (2)$$

$$V_o = DV_{in} \quad (3)$$

$$\implies D = 0.4$$

$$\Delta i_L = \frac{V_{in} - V_o}{L} T_{on} = \frac{V_{in} - V_o}{L} DT_s \quad (4)$$

$$I_{LB} = \frac{1}{2} \Delta i_L = \frac{DT_s}{2L} (V_i - V_o) = I_{o,\min} \quad (5)$$

$$L = \frac{V_o(1 - D)T_s}{2I_{o,\min}} \quad (6)$$

$$\Delta v_o = \frac{1}{C} \int i_c dt + i_c R_c \cong i_c R_c = \Delta i_L R_c \quad (7)$$

$$\frac{\Delta v_o}{V_o} = \frac{T_s^2(1 - D)}{8LC} \quad (8)$$

$$C = \frac{T_s^2(1 - D)}{8L} \cdot \frac{V_o}{\Delta v_o} \quad (9)$$

Simulation Waveforms

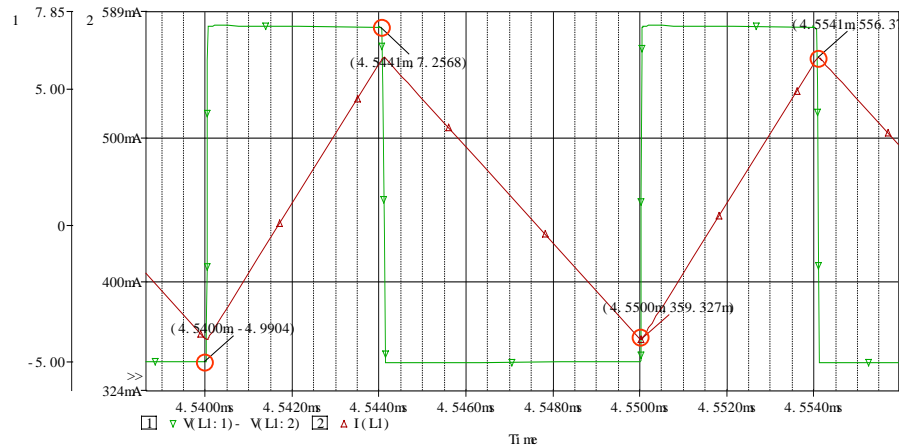


FIG. 22

On time : 4.551ms-4.54ms=4.1us

Off time : 10us-4.1us=5.9us

Δi_L : 556.3mA-359.2mA=197.1mA

($V_i - V_o$) : 7.26

($-V_o$) : 4.99

Inductor Voltage(1)
Inductor Current(2)

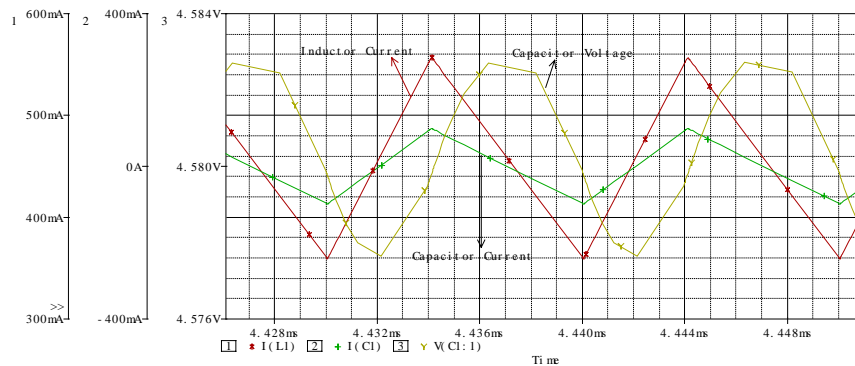


FIG. 23

Inductor Current(1)
Capacitor Current(2)
Capacitor Voltage(3)

Boost Converter

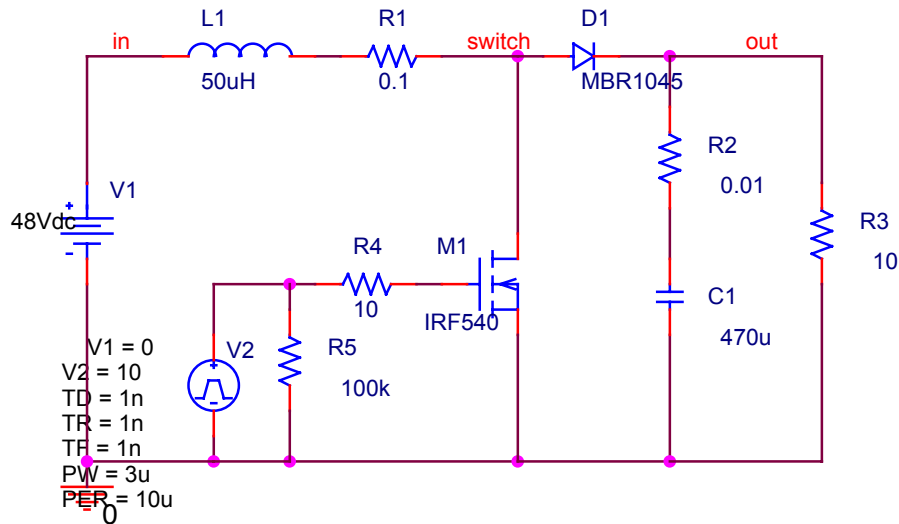


FIG. 24

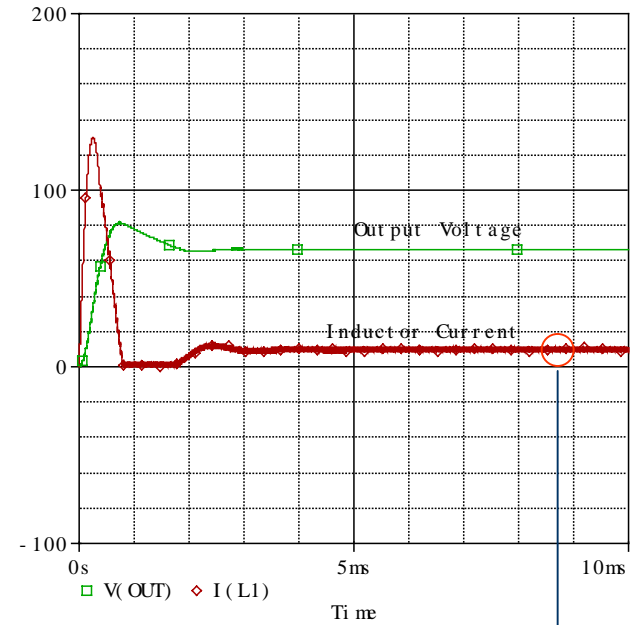


FIG. 25

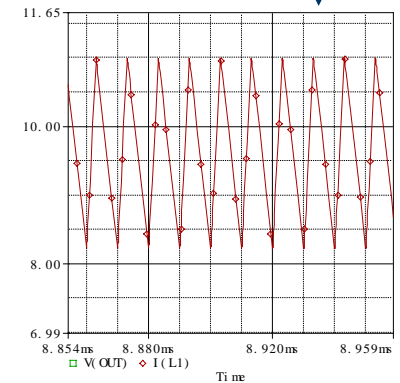


FIG. 26

Design of Boost Converter

Input Voltage : 12V
 Output Voltage : 4.8V
 Output Current : 0.1 ~ 3A
 Frequency : 100kHz

$$v_L = L \frac{di}{dt} \quad (10)$$

$$V_i DT_s = V_o (1-D) T_s \quad (11)$$

$$V_o = \frac{1}{1-D} V_{in} \quad (12)$$

$$\implies D = 0.33$$

$$\Delta i_L = \frac{V_{in} - V_o}{L} T_{on} = \frac{V_{in} - V_o}{L} DT_s \quad (13)$$

$$I_{LB} = \frac{1}{2} \Delta i_L = \frac{DT_s}{2L} V_i \quad (14)$$

$$\begin{aligned}
 I_{OB} &= \int_{DT_s}^{T_s} I_{LB} dt = I_{LB} (1-D) T_s = I_{LB} D' \\
 &= \frac{V_i}{2L} DD' T_s = \frac{V_o}{2L} DD'^2 T_s = I_{o,\min} \quad (15)
 \end{aligned}$$

$$L = \frac{V_o DD'^2 T_s}{2I_{o,\min}} \quad (16)$$

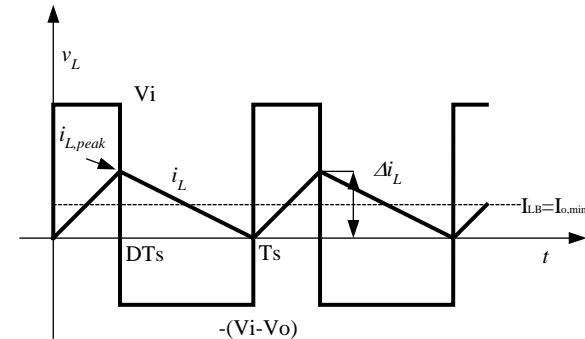


FIG. 27

$$\Delta v_o = \frac{1}{C} \int i_c dt + i_c R_c \cong i_c R_c = \Delta i_L R_c \quad (17)$$

$$\Delta v_o = \frac{\Delta Q}{C} = \frac{I_o DT_s}{C} = \frac{V_o}{R} \cdot \frac{DT_s}{C} \quad (18)$$

$$C = \frac{DT_s}{R} \cdot \frac{V_o}{\Delta v_o} \quad (19)$$

Boost Converter

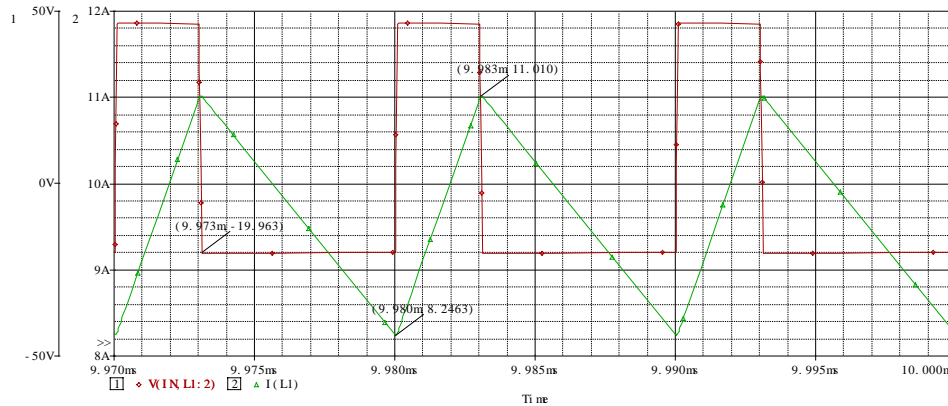



FIG. 28

On time : 4.551ms-4.54ms=4.1us
 Off time : 10us-4.1us=5.9us
 Δi_L : 556.3mA-359.2mA=197.1mA
 $(V_i - V_o)$: 7.26
 $(-V_o)$: 4.99

Inductor Voltage(1)
 Inductor Current(2)

FIG. 29

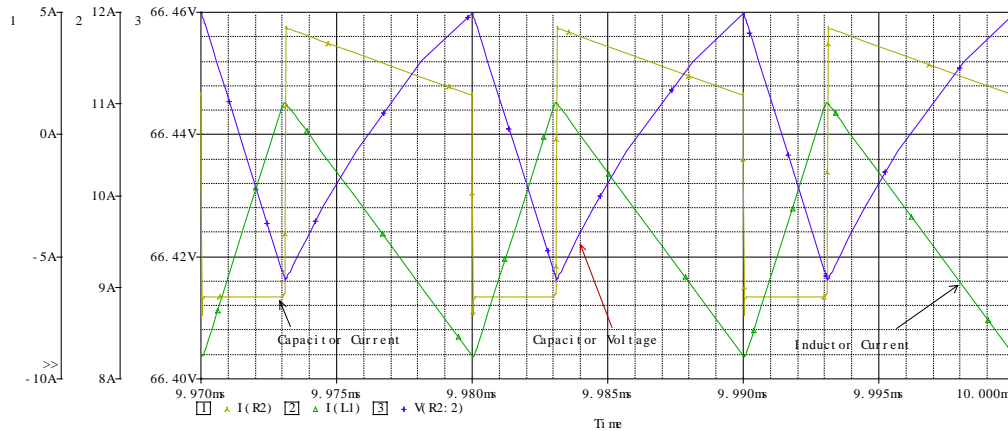Inductor Current(2)
 Capacitor Current(1)
 Capacitor Voltage(3)



Flyback Converter

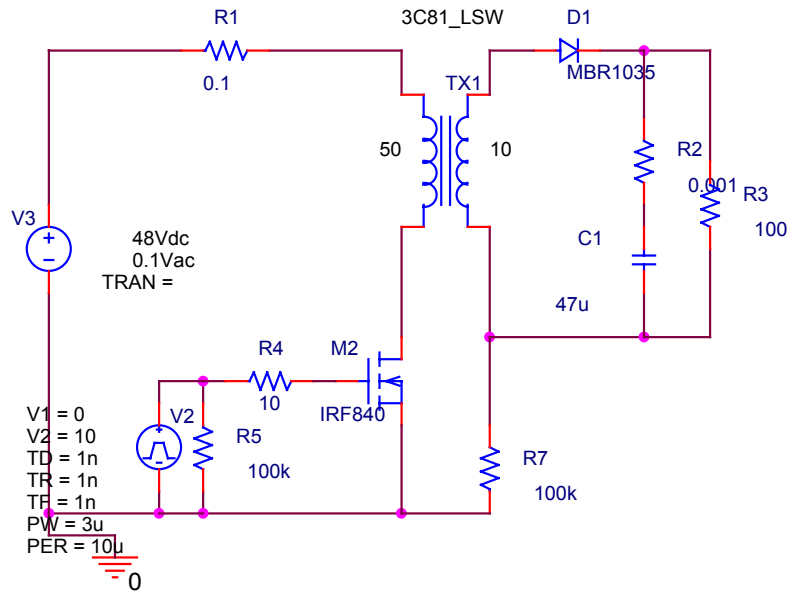


FIG. 30

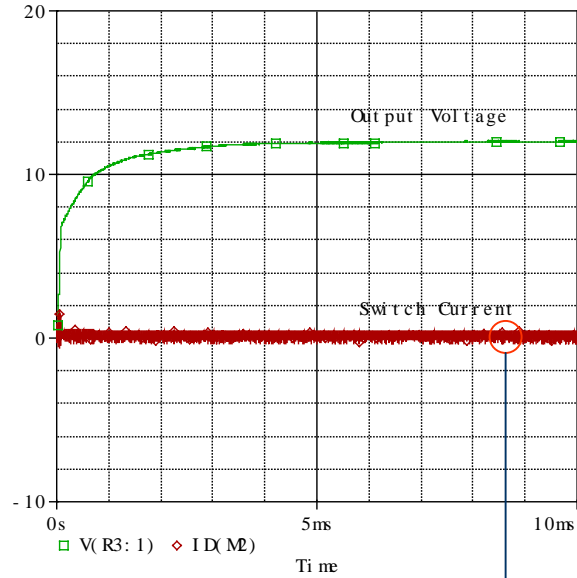


FIG. 31

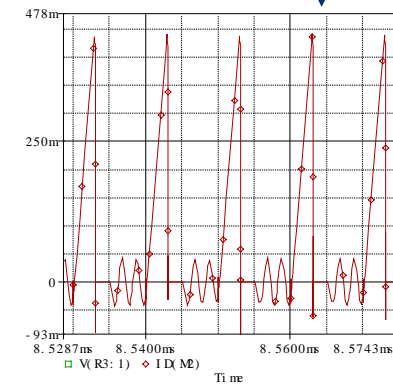


FIG. 32

Forward Converter

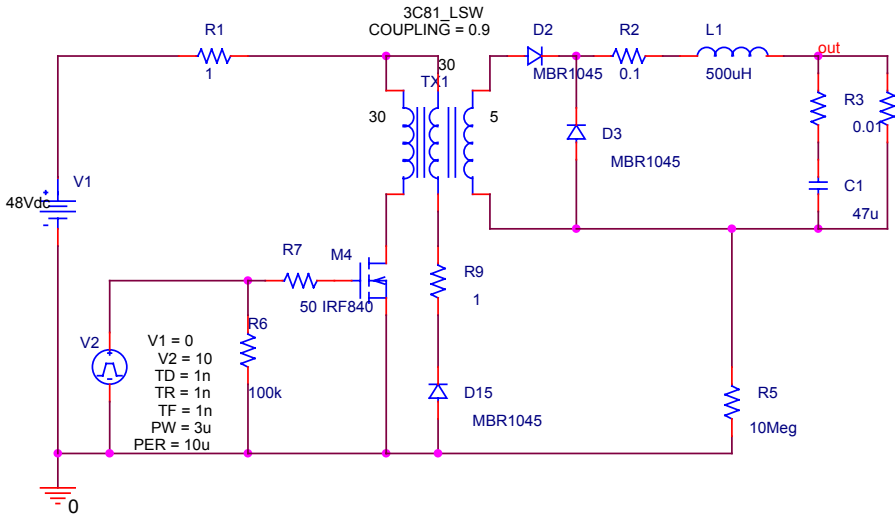


FIG. 33

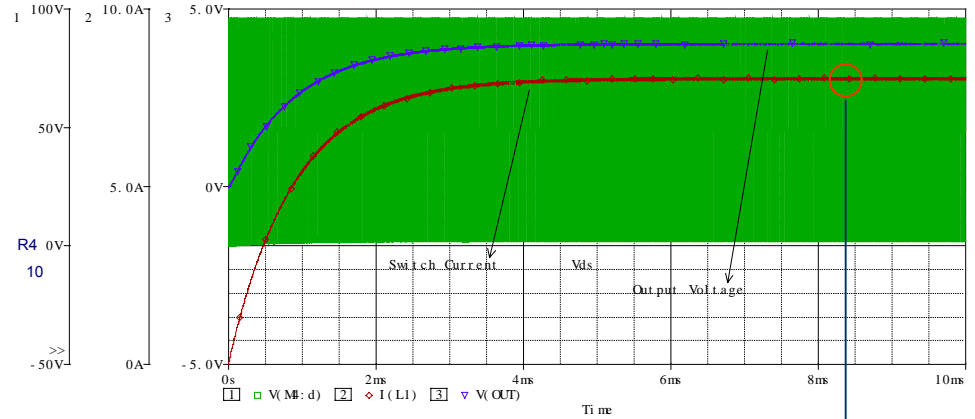


FIG. 34

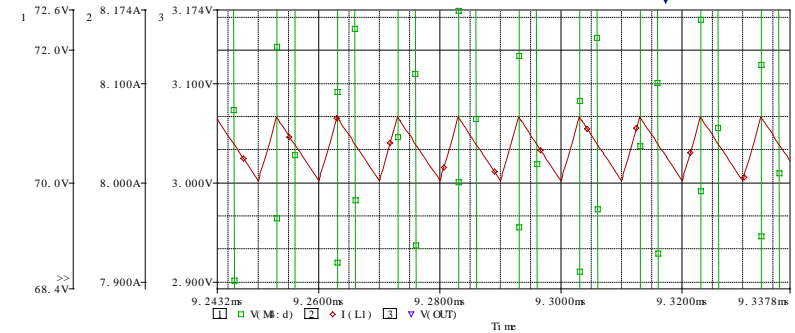


FIG. 35

Buck Converter

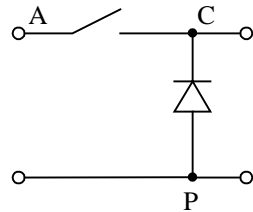


FIG. 36

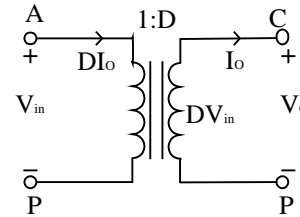


FIG. 37

Averaged PWM-Switch

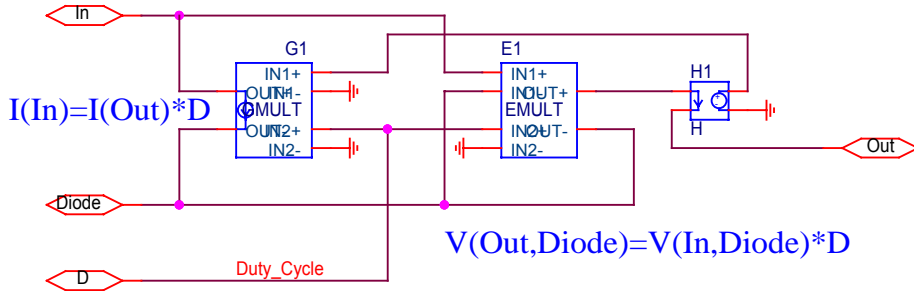


FIG. 38

Averaged PWM Switch

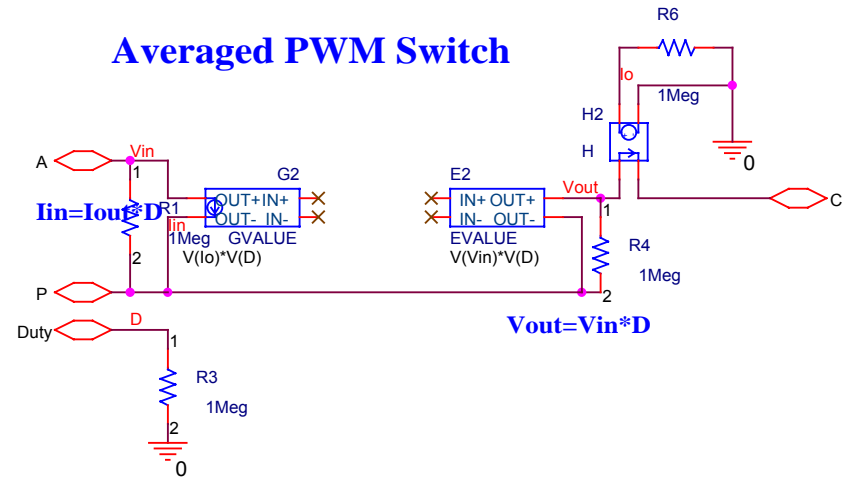


FIG. 39

Boost Converter

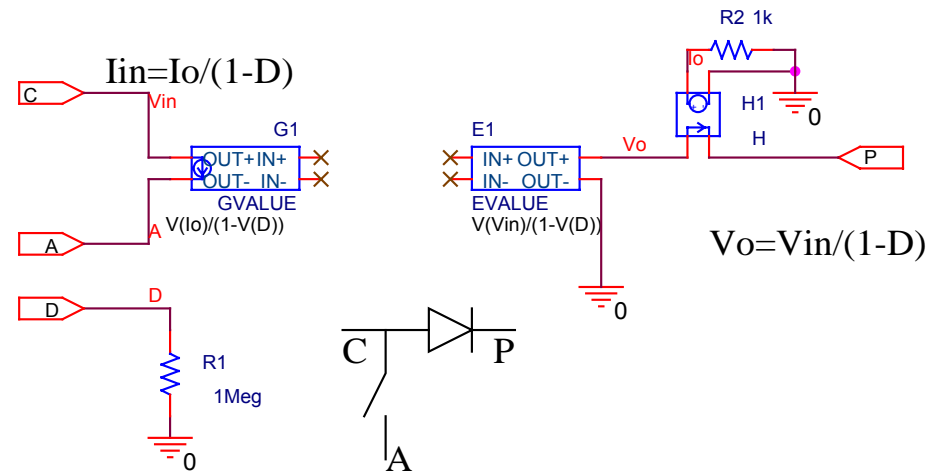


FIG. 40

Average PWM Buck Converter

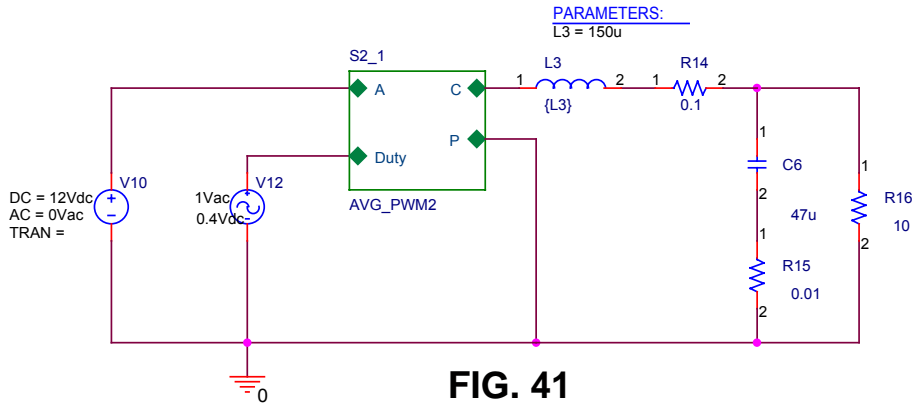


FIG. 41

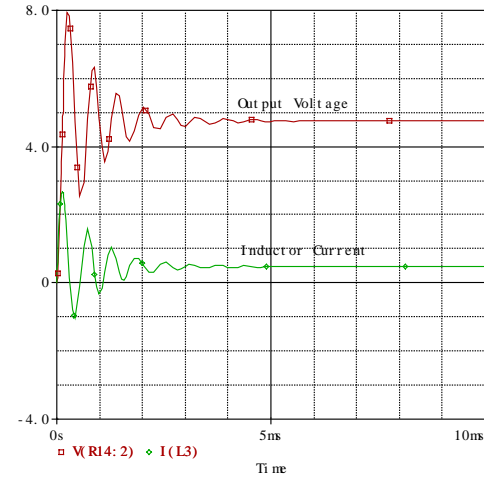


FIG. 42

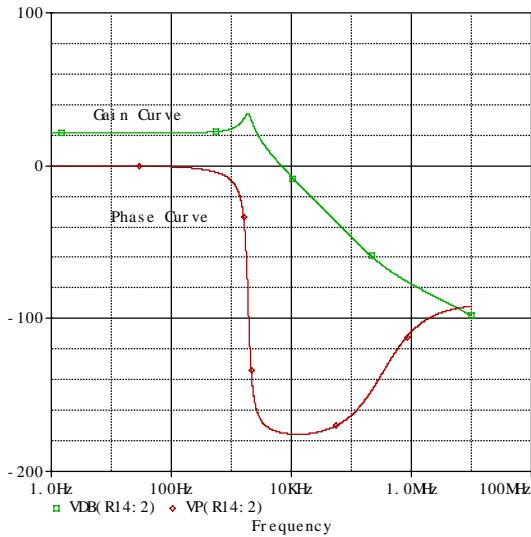


FIG. 43

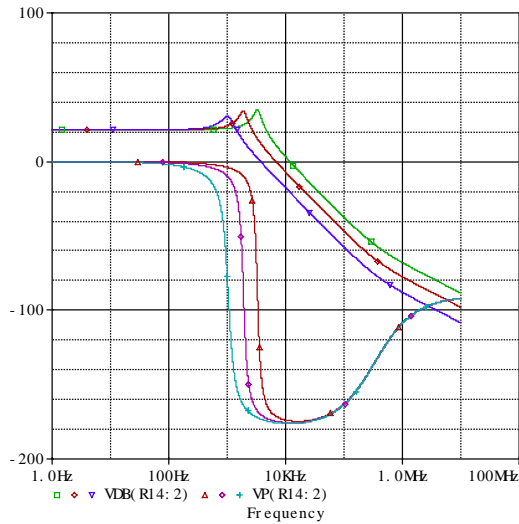


FIG. 44

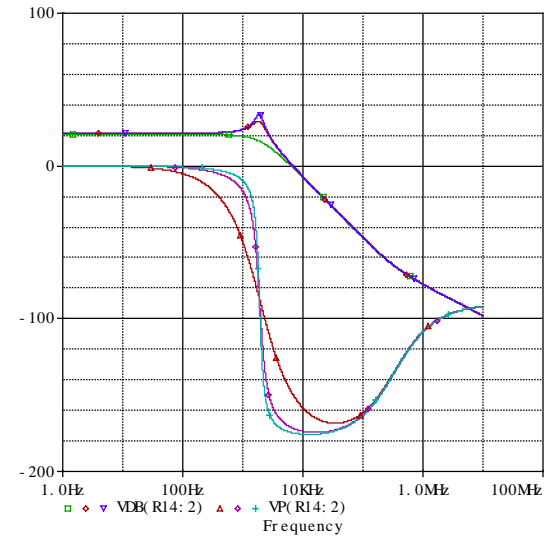


FIG. 45

Average PWM Boost Converter

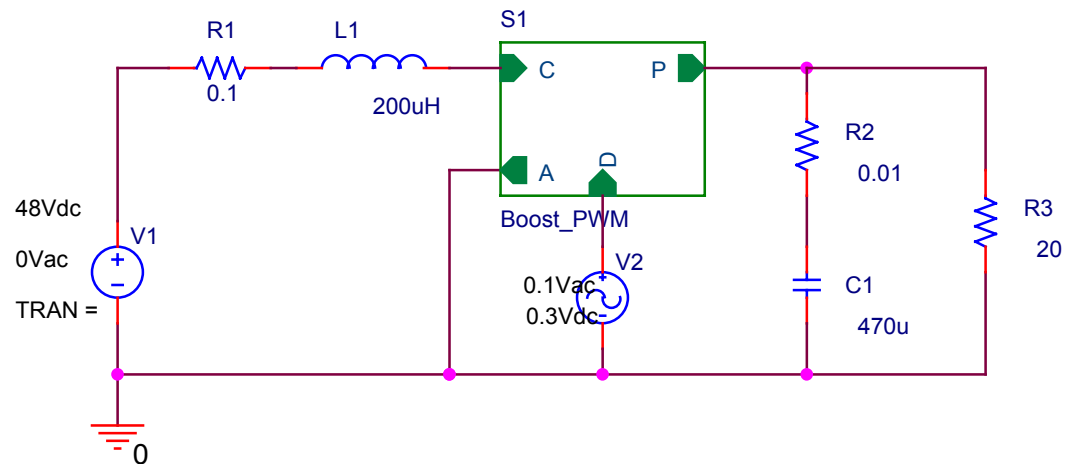


FIG. 46

Compensation

Type I.

$$f_c = \frac{1}{2\pi RC} \quad (20)$$

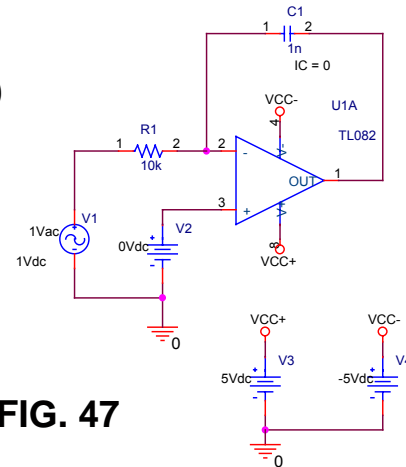


FIG. 47

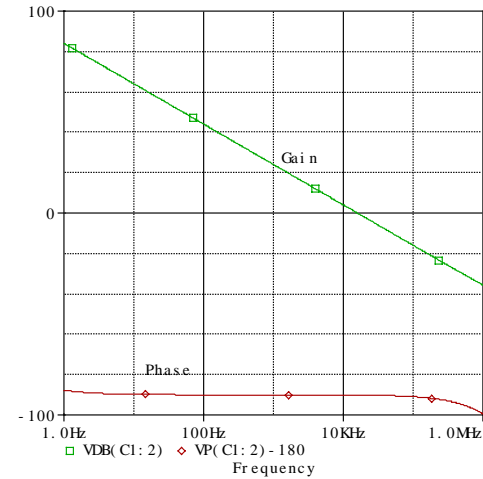


FIG. 49

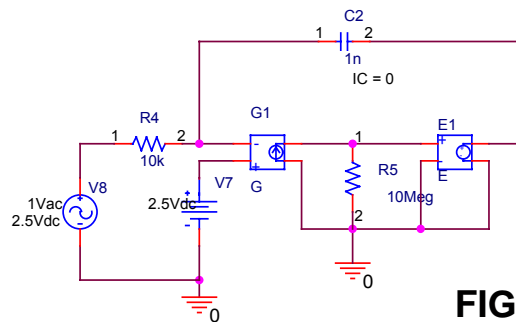


FIG. 48

Type II.

$$\frac{v_c}{v_o} = \frac{(1 + sC_1R_2)}{s(C_1 + C_2)R_1 \left\{ 1 + s \frac{C_1C_2}{(C_1 + C_2)} R_2 \right\}} \quad (21)$$

$$f_Z = \frac{1}{2\pi C_1 R_2} \quad (22)$$

$$f_P = \frac{C_1 + C_2}{2\pi C_1 C_2 R_2} \cong \frac{1}{2\pi C_2 R_2} (\because C_1 \gg C_2) \quad (23)$$

$$A_{V1} = \frac{R_2}{R_1} \quad (24)$$

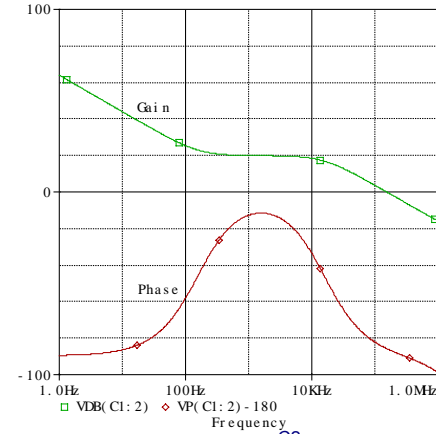


FIG. 50

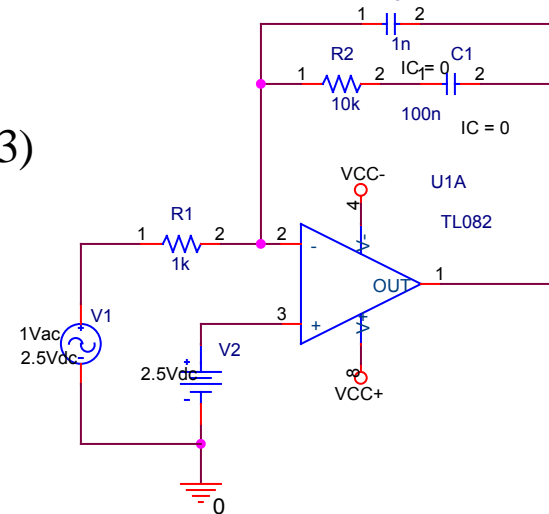


FIG. 51

Type III.

$$\frac{v_c}{v_o} = \frac{(1 + sC_1R_1)(1 + sC_2R_3)}{sC_2R_1(1 + sC_1R_2)} \quad (25)$$

$$f_{Z1} = \frac{1}{2\pi C_1 R_1} \quad (26)$$

$$f_{Z2} = \frac{1}{2\pi C_2 R_3} \quad (27)$$

$$f_P = \frac{1}{2\pi C_1 R_2} \quad (28)$$

$$A_{V1} = \frac{R_3}{R_1 + R_2} \quad (29)$$

$$A_{V2} = \frac{R_3}{R_2} \quad (30)$$

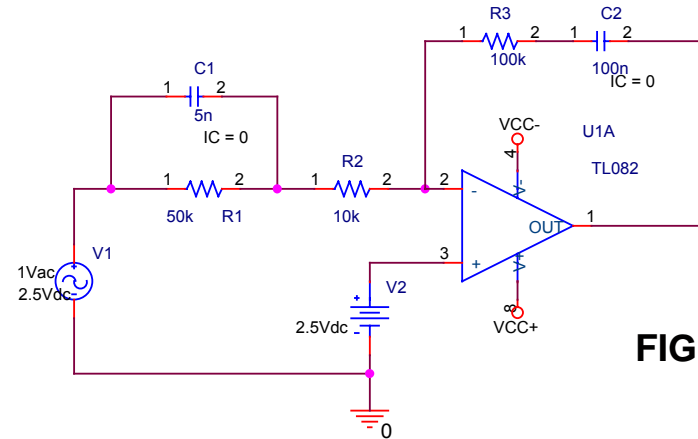


FIG. 52

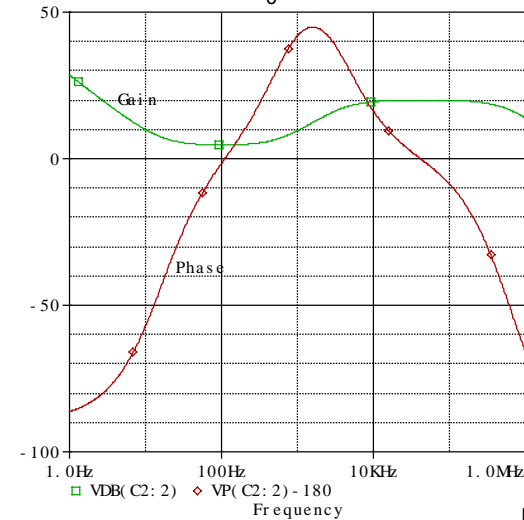


FIG. 53

Type IV.

$$\frac{v_c}{v_o} = \frac{(1 + sC_1R_2)\{1 + sC_3(R_1 + R_3)\}}{s(C_1 + C_2)R_1(1 + sC_3R_3)\left(1 + s\frac{C_1C_2R_2}{C_1 + C_2}\right)} \quad (31)$$

$$f_{Z1} = \frac{1}{2\pi C_1 R_2} \quad (32)$$

$$f_{Z2} = \frac{1}{2\pi C_3 (R_1 + R_3)} \cong \frac{1}{2\pi C_3 R_1} \quad (33)$$

$$f_{P1} = \frac{1}{2\pi C_3 R_3} \quad (34)$$

$$f_{P1} = \frac{C_1 + C_2}{2\pi C_1 C_2 R_2} \cong \frac{1}{2\pi C_2 R_2} (\because C_1 \gg C_2) \quad (35)$$

$$A_{V1} = \frac{R_2}{R_1} \quad (36)$$

(31)

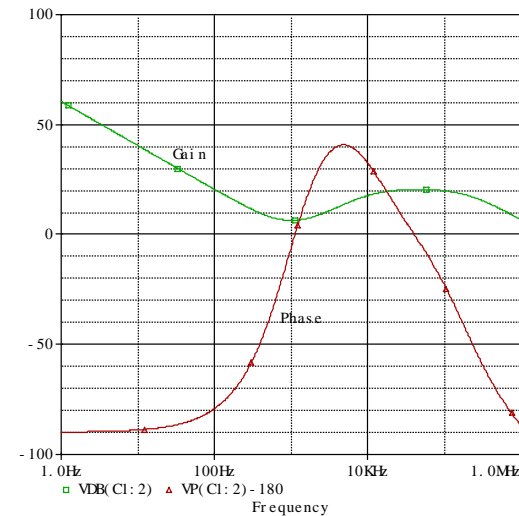


FIG. 54

$$A_{V2} = \frac{R_2(R_1 + R_3)}{R_1 R_3} \cong \frac{R_2}{R_3} \quad (37)$$

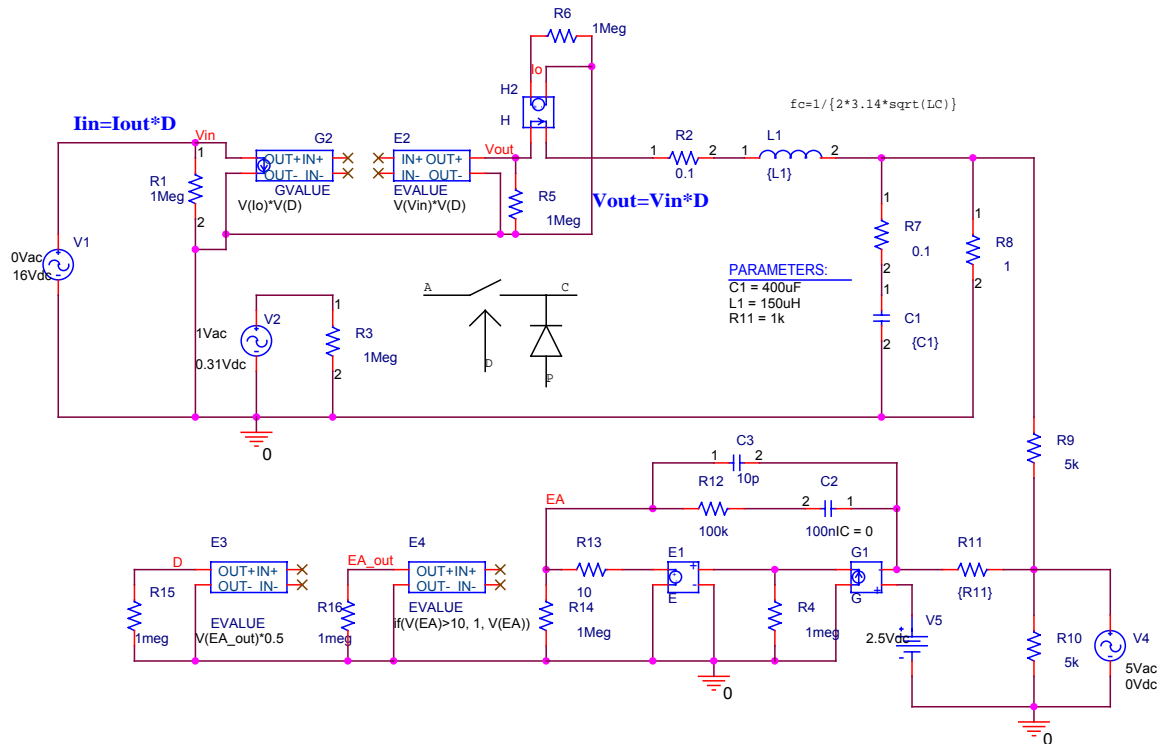


FIG. 55

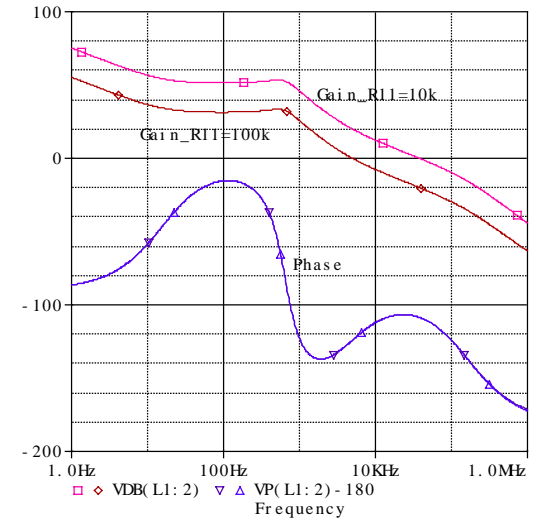


FIG. 56

PF / THD



Power Factor

– What Is It and Why Must It Be Corrected?

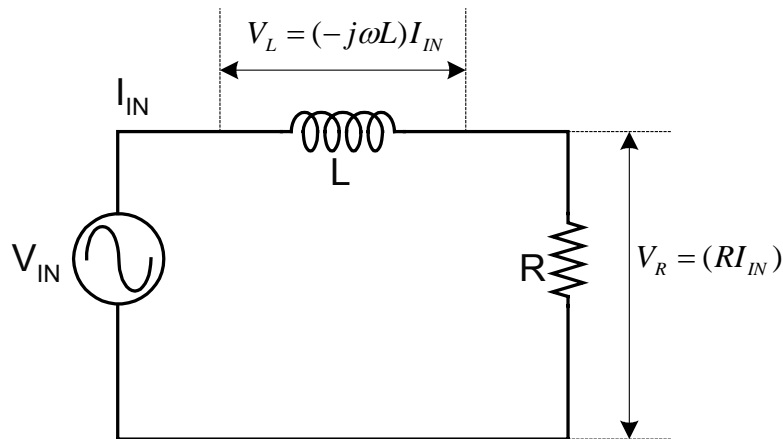


FIG. 57

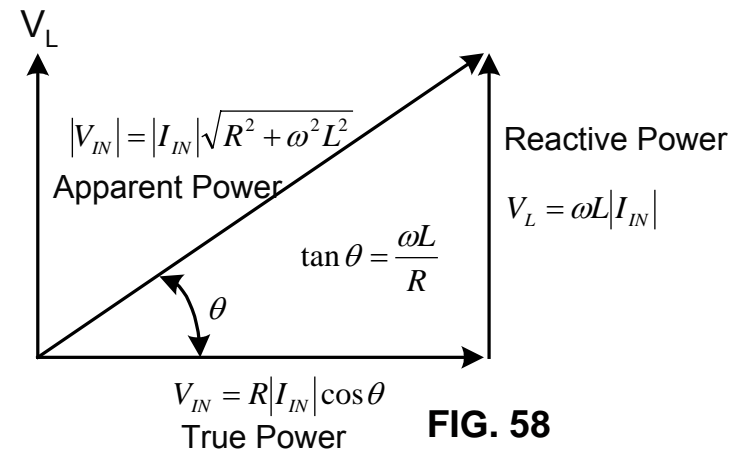


FIG. 58

$$\text{Apparent Power} = V_{IN} I_{IN}$$

$$\text{Actual Power} = V_{IN} I_{IN} \cos \theta$$

PF / THD

$$PF = \frac{\text{Average Power}}{\text{Apparent Power}} = \frac{\text{avg}[v(t) * i(t)]}{V_{rms} * I_{rms}}$$

If $v(t)$ has form of sine wave, power factor can be expressed as following.

$$PF = \frac{V_{rms} * I_{rms(1)} * \cos \theta}{V_{rms} * I_{rms}} = \frac{I_{rms(1)}}{I_{rms}} \cos \theta = K_d * K_\theta$$

$$THD = \frac{I_{rms(DIST)}}{I_{rms(1)}} * 100$$

$$THD = \frac{\sqrt{I^2_{rms} - I^2_{rms(1)}}}{I_{rms(1)}} * 100$$

$$\text{Where, } I_{rms(DIST)} = \sqrt{I^2_{rms} - I^2_{rms(1)}}$$

PF / THD

$$THD = \sqrt{\left(\frac{I_{rms}}{I_{rms(1)}}\right)^2 - 1} * 100$$

$$THD = \sqrt{\frac{1}{K^2 d} - 1} * 100$$

$$Kd = \frac{1}{\sqrt{1 + \left(\frac{THD}{100}\right)^2}}$$

$$PF = \frac{I_{rms(1)}}{I_{rms}} \cos \theta = Kd * K\theta = Kd$$

$$\therefore PF = \frac{1}{\sqrt{1 + \left(\frac{THD}{100}\right)^2}}$$

Relationship Between PF and THD

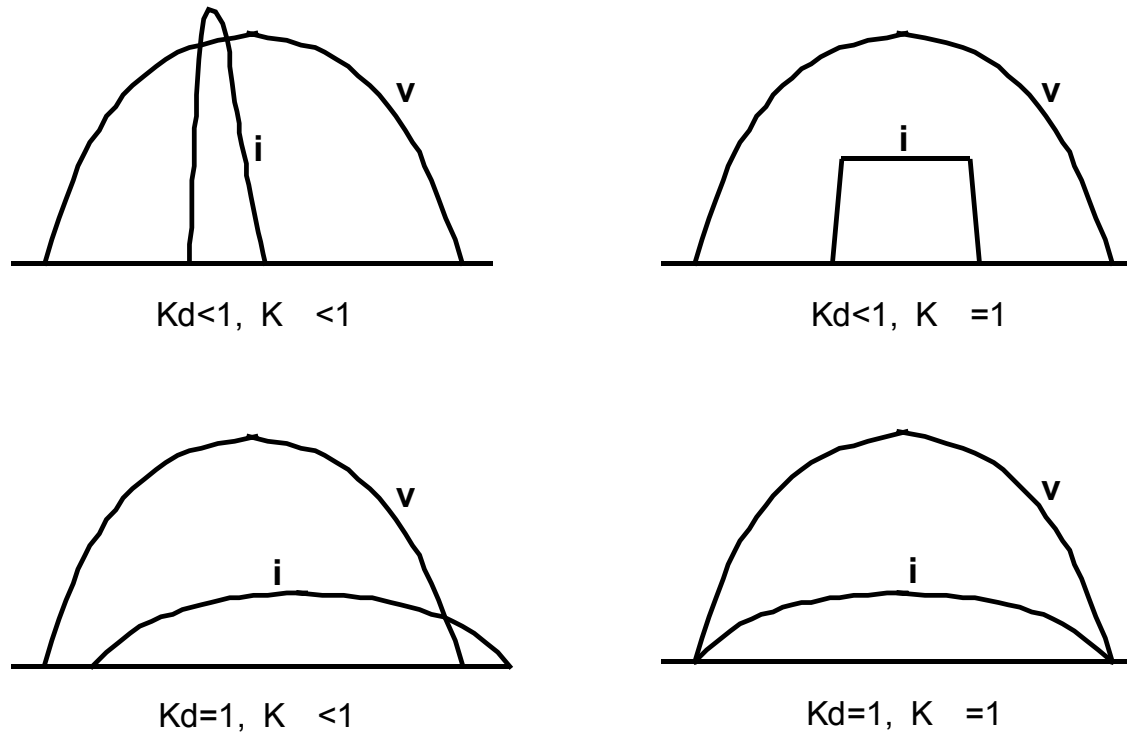


FIG. 59

Equipment Classification


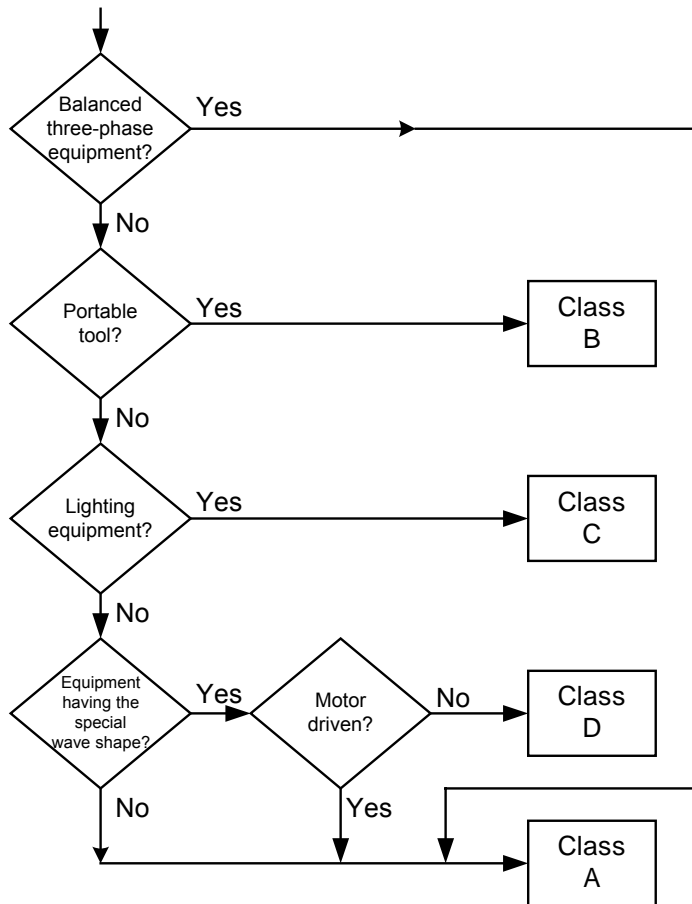


FIG. 60

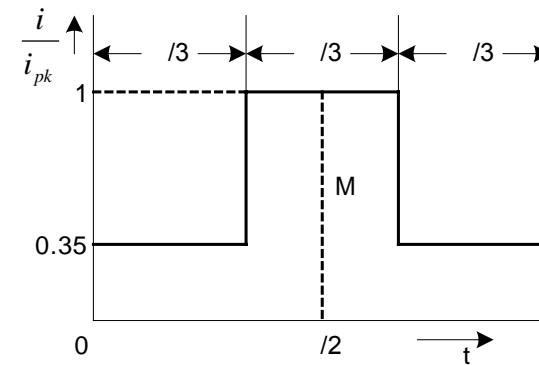

Class D Wave Shape Definition

FIG. 61

IEC 555-2 Absolute Limits

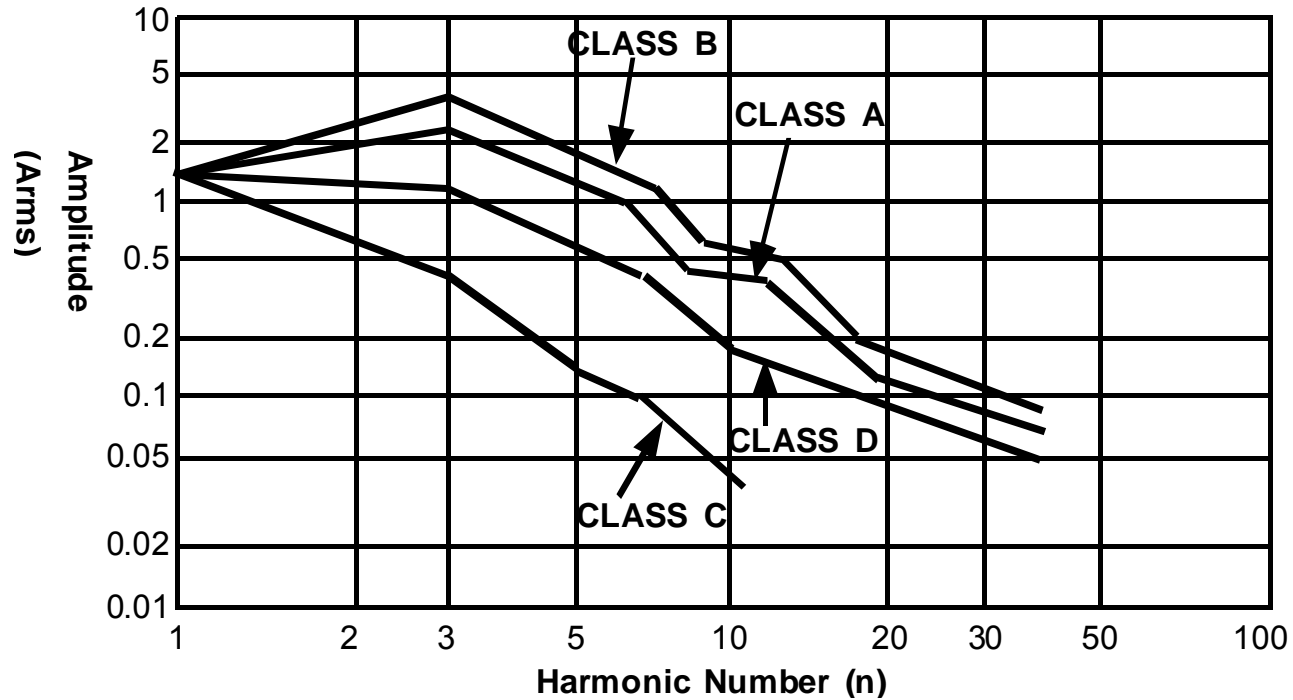


FIG. 62

IEC 555-2 Class D Specification

Harmonic Order	mA/W	Maximum Permissible Harmonic Current
3	3.4	2.30
5	1.9	1.14
7	1.0	0.77
9	0.5	0.40
11	0.35	0.33
13 and on	Linear Extrapolation $3.85/n$	See Limits for Class A Equipment

Notes:

1. Class-D specifications apply to equipment operating from a single-phase 220V ac line with a waveshape such as that exhibited by the input current to a rectifier with a capacitive input filter.
2. Current IEC documentation suggests that the above Class D limits will be applicable from 1st January 1995 to all equipment having an input power from 75W to 600W.

PFC Specification Information

EMiSoft

Summary

- Harmonics+flicker required under 89/336
- Commission has re-listed both EN61000-3-2 and [-3-3] effectively delaying implementation until 1/1/2001
- 4 year transition for the limits for low power [75W>50W] of class D equipment, Start date not defined.
- Do I need to test ?

<http://www.emisoft.co.uk>

Comparison

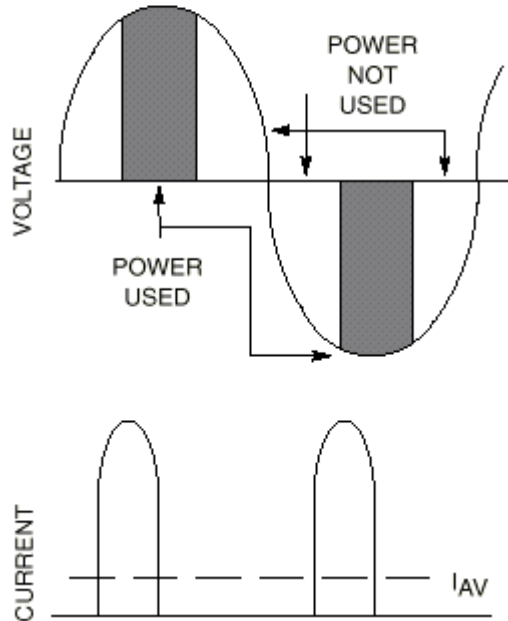
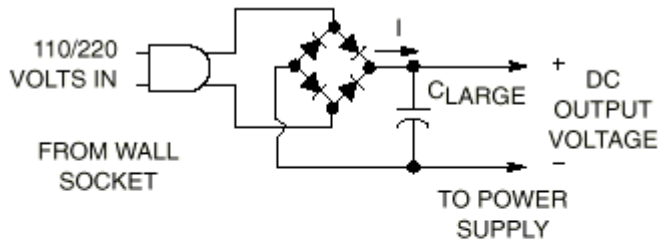


FIG. 63


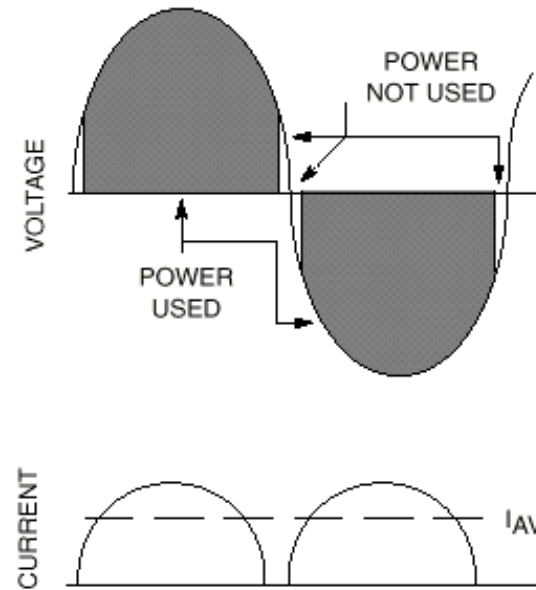
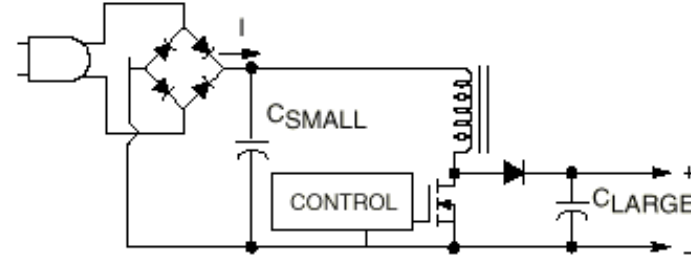


FIG. 64

Single Phase PFC Topologies

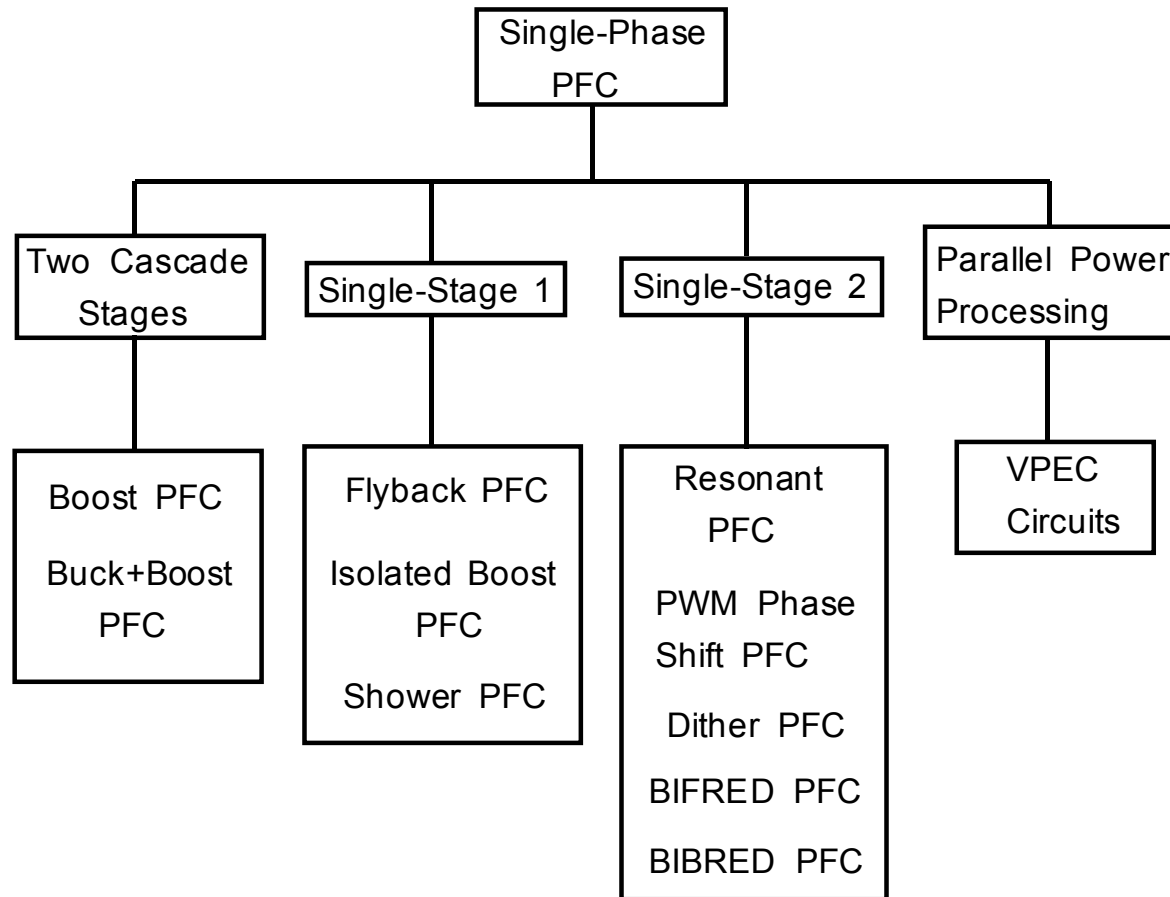

Basic Topology & Control Method

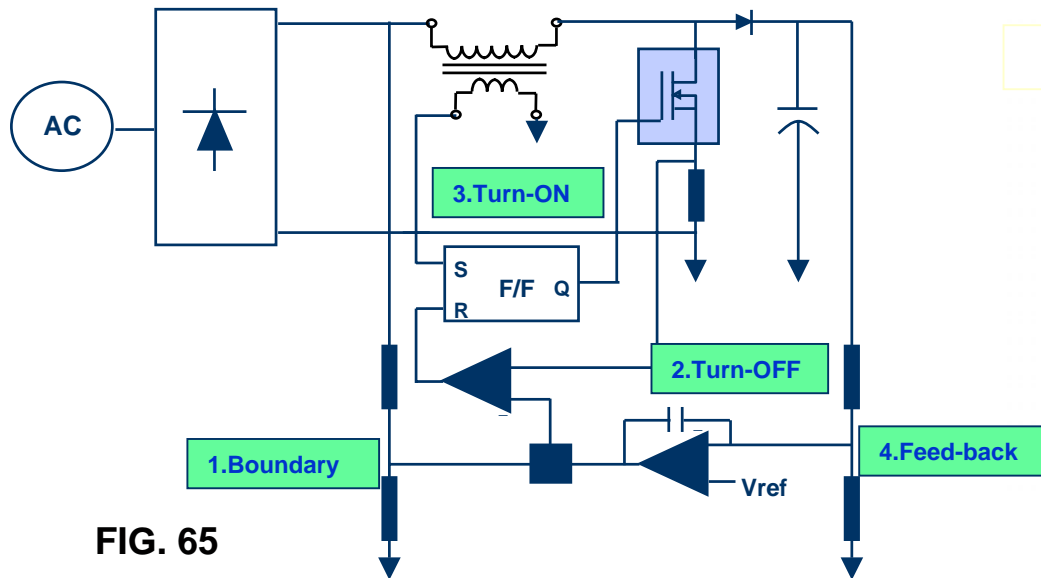


FIG. 65

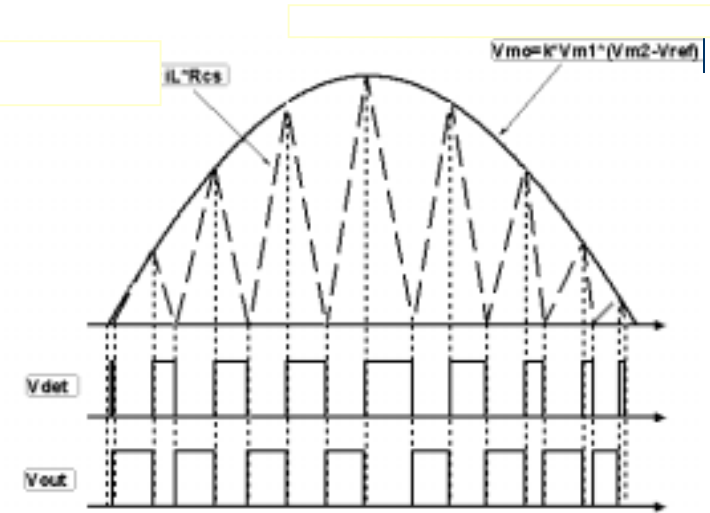


FIG. 66


◆ **Power Factor** : $P.F. = \frac{P}{S} = \frac{P}{V_{rms} I_{rms}} = \frac{V_{1,rms} I_{1,rms}}{V_{1,rms} I_{T,rms}} \cos \theta_1 = \frac{I_{1,rms}}{I_{T,rms}} \cos \theta_1$

◆ **Target** : **Ballast, High Efficiency SMPS**

◆ **Switch turns on when i_L reduces to zero**


◆ **Switch turns off when the switch current exceeds $K \cdot |V_i| \cdot V_c$**

Experimental Results

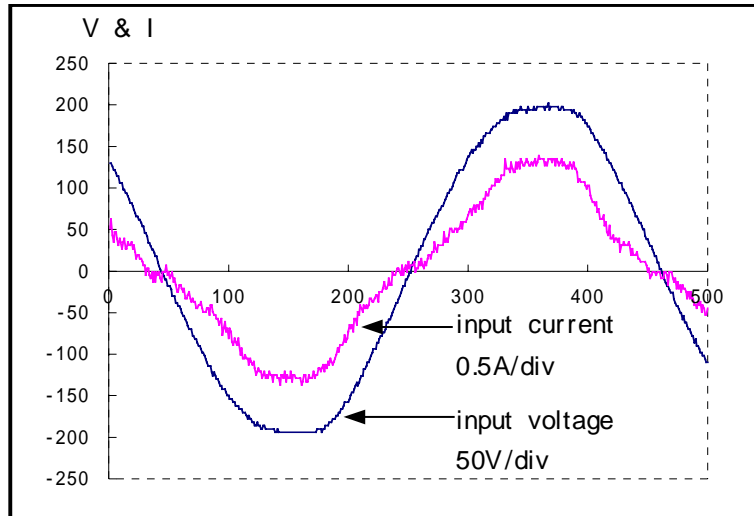

Output Power = 60W


FIG. 67

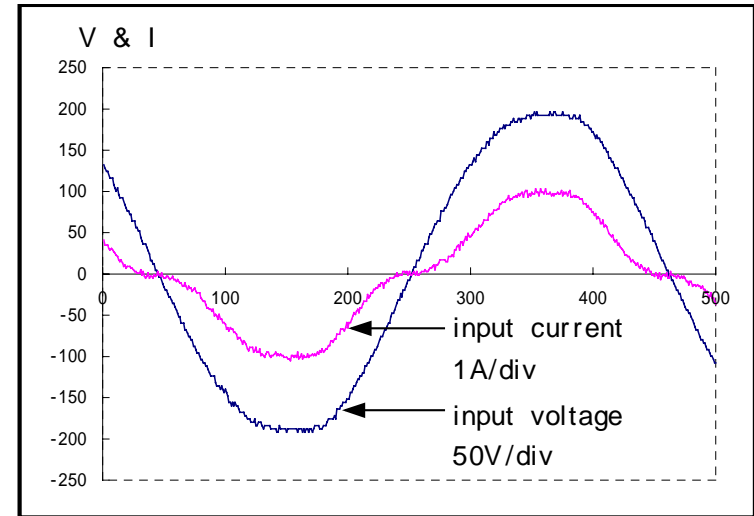

Output Power = 125W


FIG. 68

Experimental Results

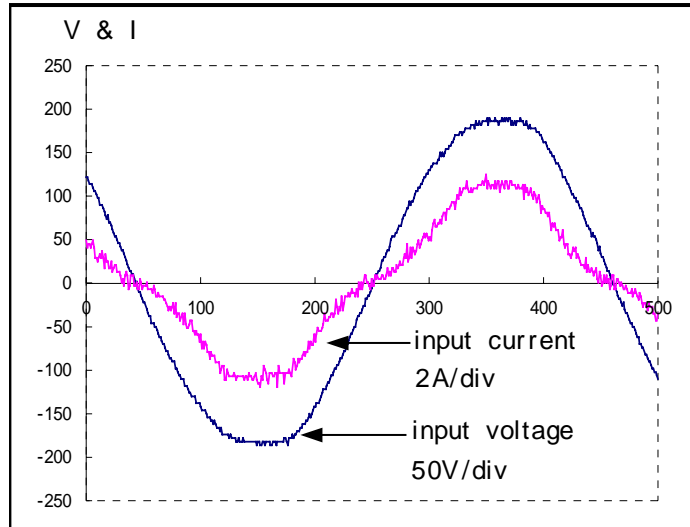

Output Power = 250W


FIG. 69

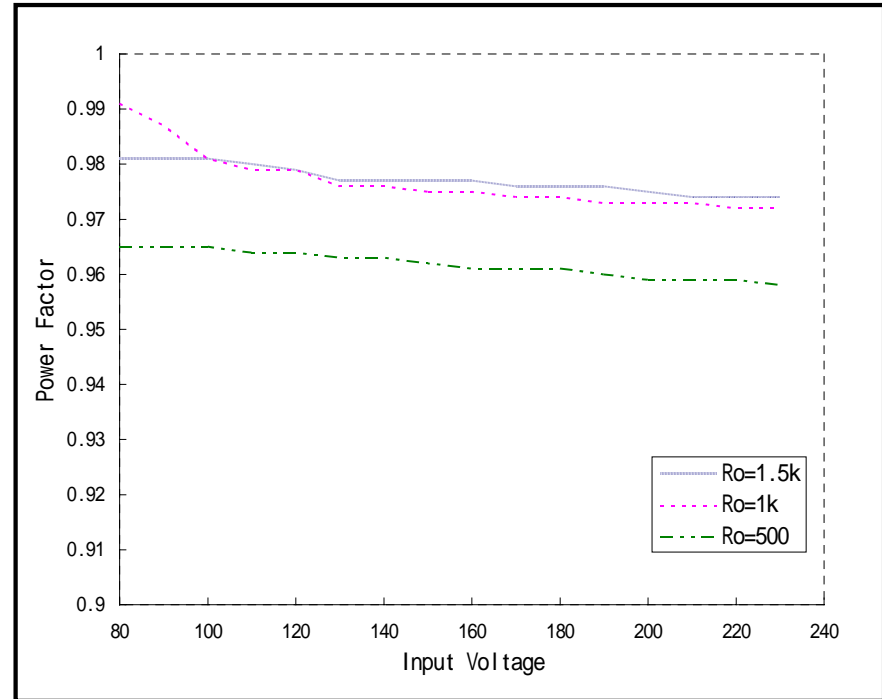

Power Factor Versus the Input Voltage Variation

FIG. 70

Two Stage Topology

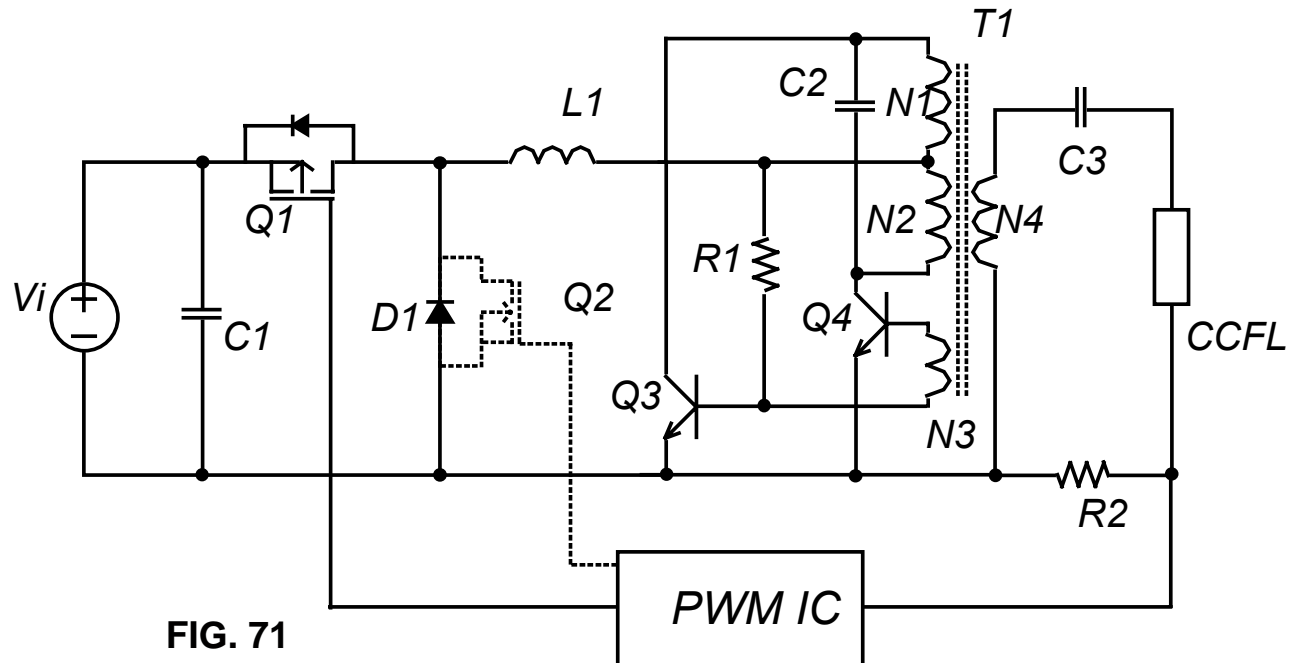

- Buck + Royer Inverter
- Low System Efficiency
- Self Oscillation
- High Cost

Simulation Circuit of Buck + Royer Topology

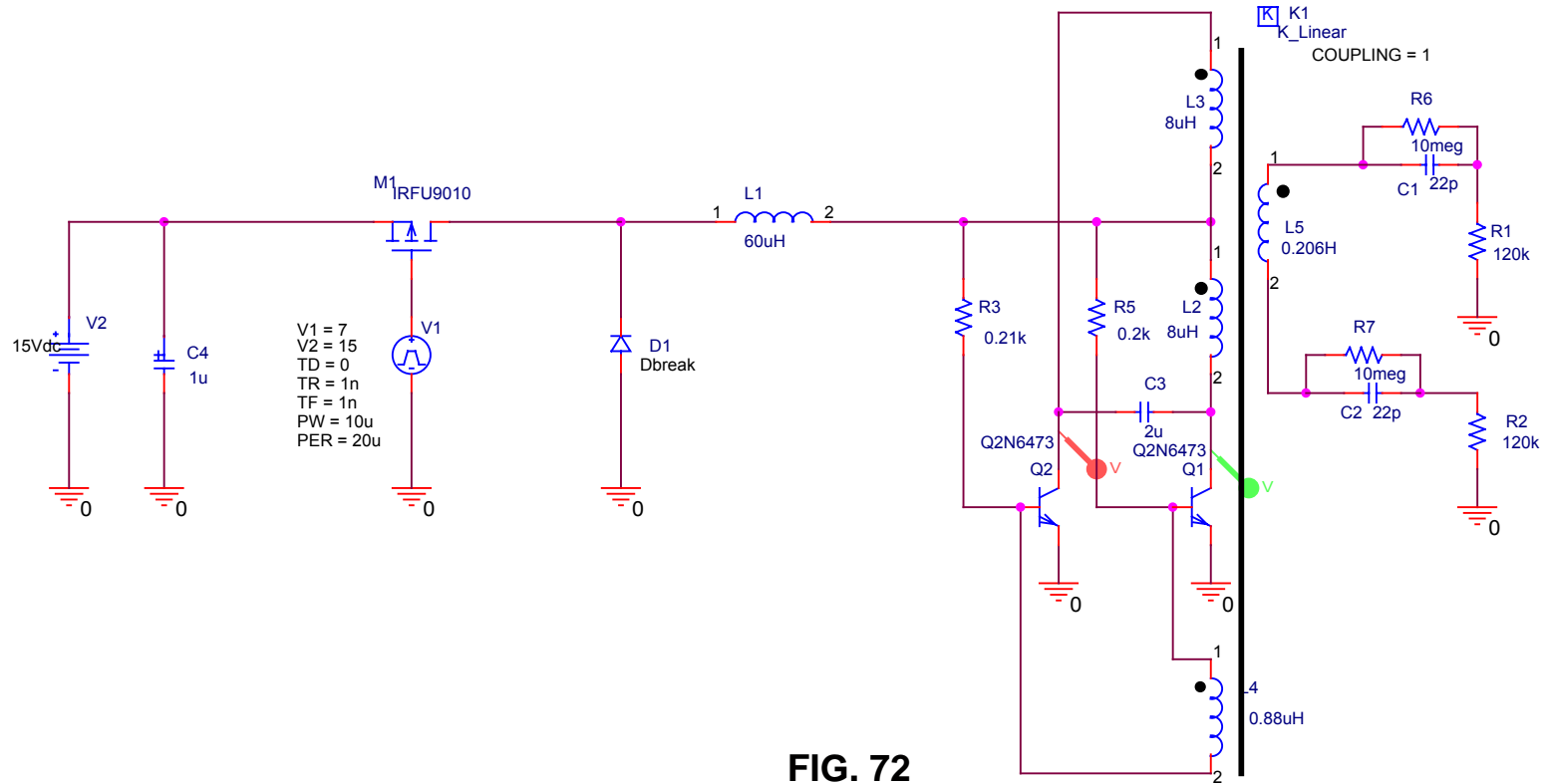


FIG. 72

Simulation Result

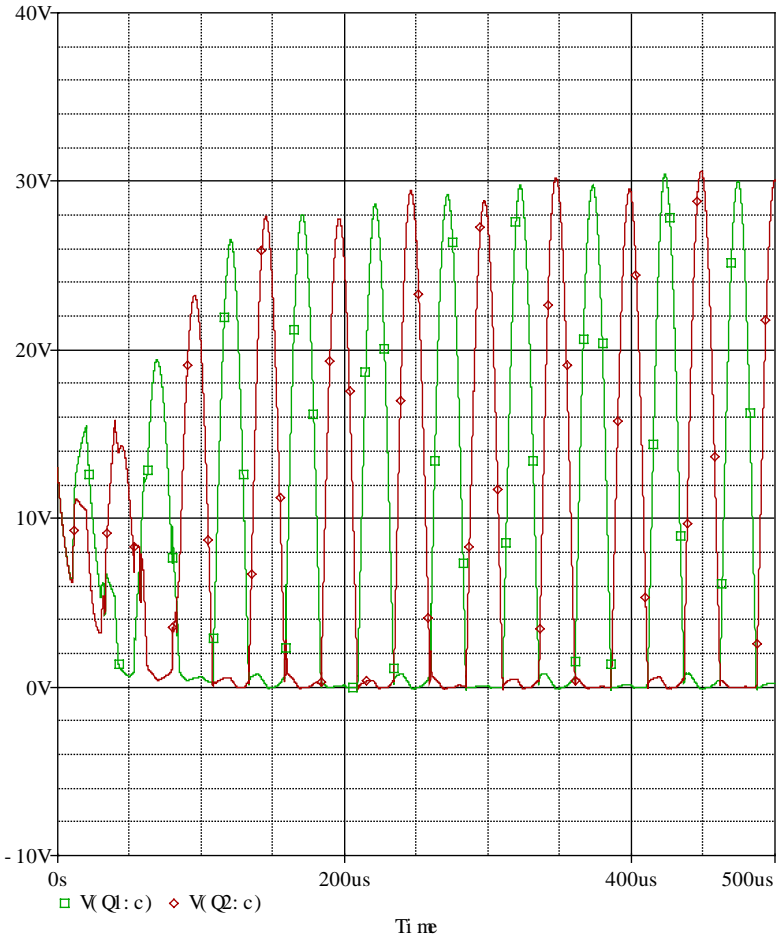


FIG. 73

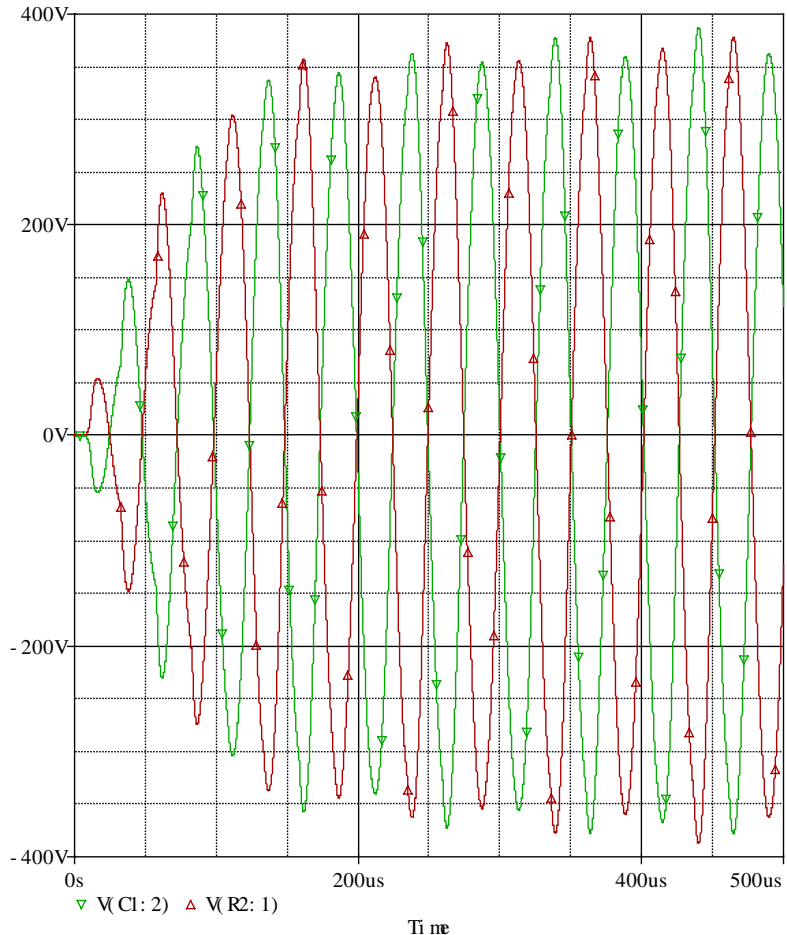


FIG. 74

Single Stage Topology

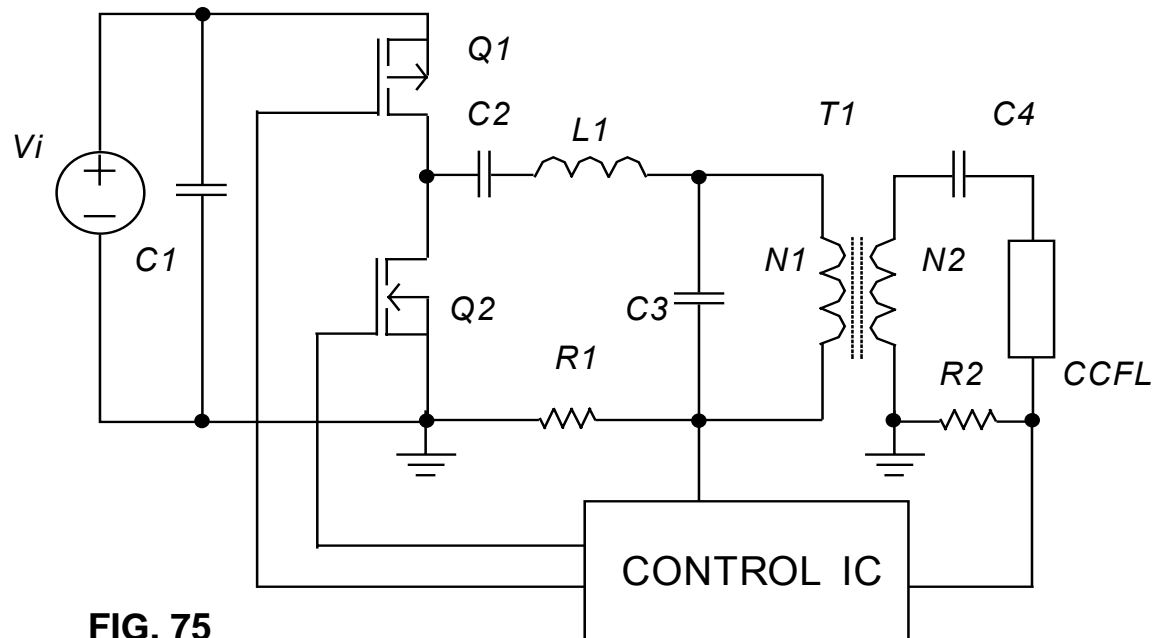


FIG. 75

- Half Bridge Converter
- High System Efficiency
- PWM / PFM Control Method
- Low Cost

Freq. Characteristic of Power Stage

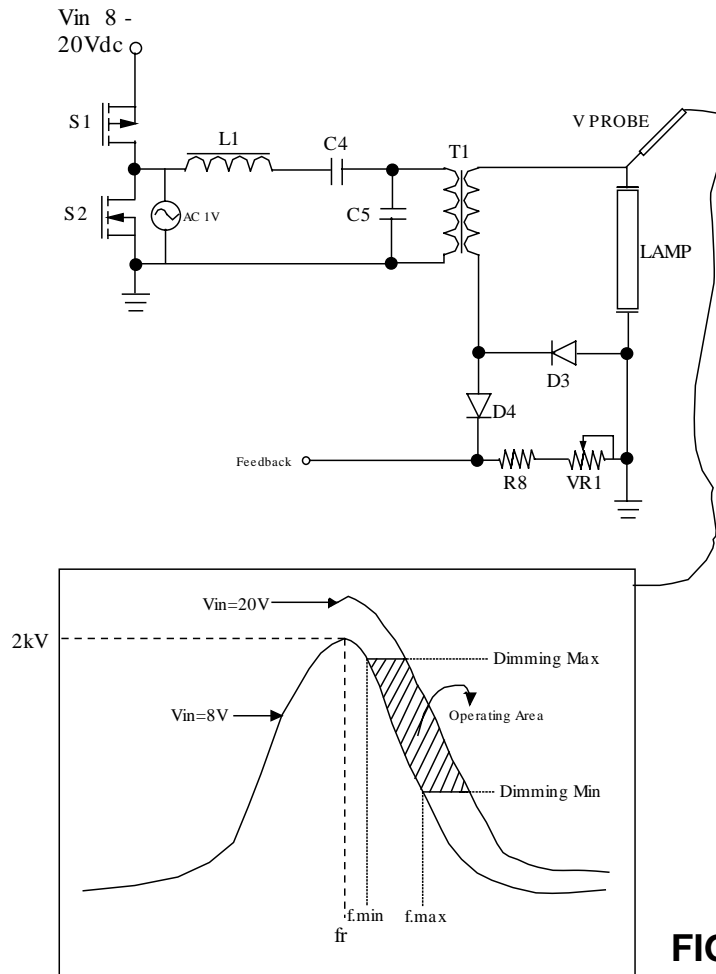


FIG. 76

- Pulse Frequency Modulation
- High Side Gate Drive
- Charge Pump Technique (NMOS)
- High System Efficiency
- Class D Type CCFL Inverter
- Low Cost

Power Stage AC Simulation

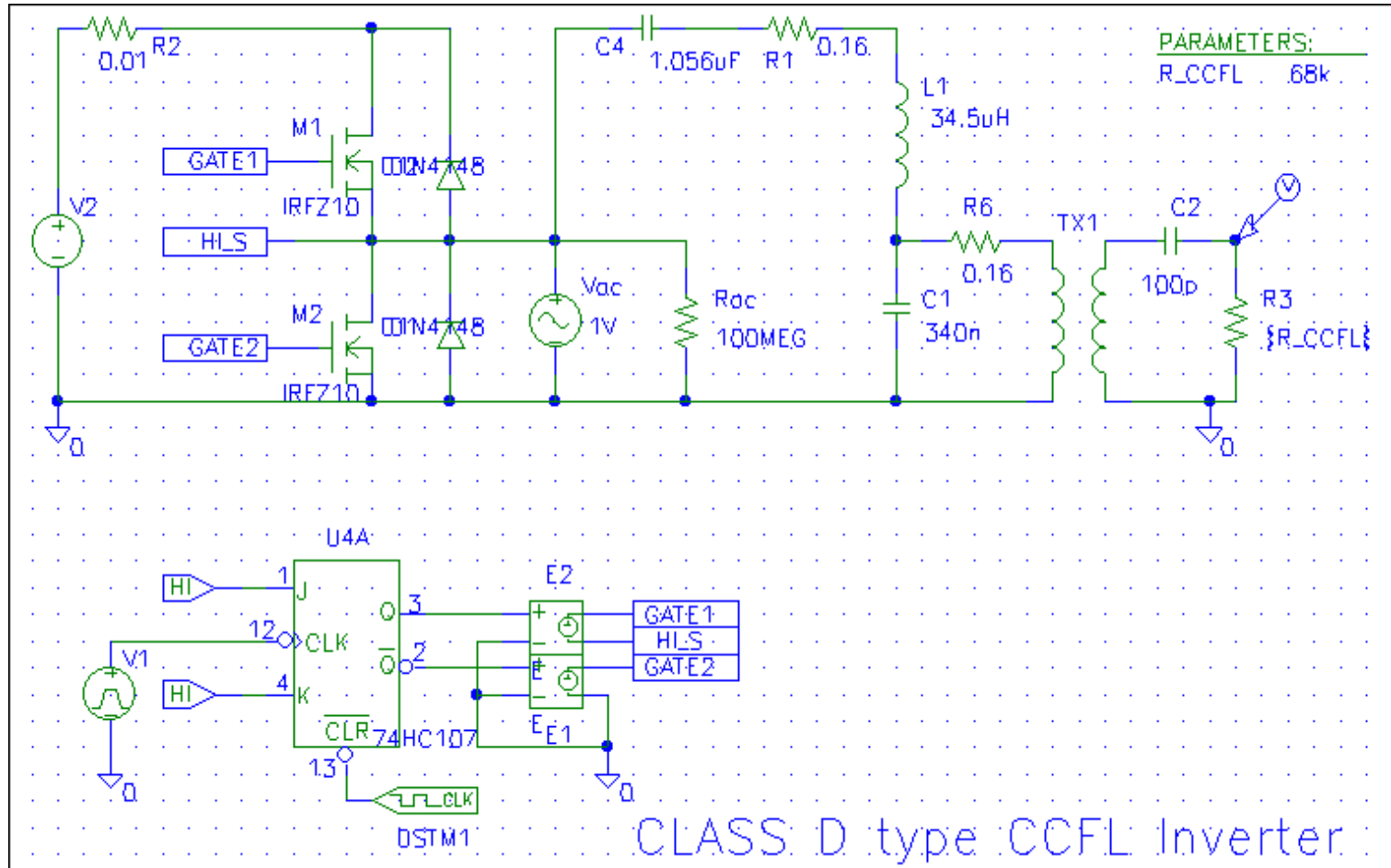


FIG. 77

AC Simulation Result

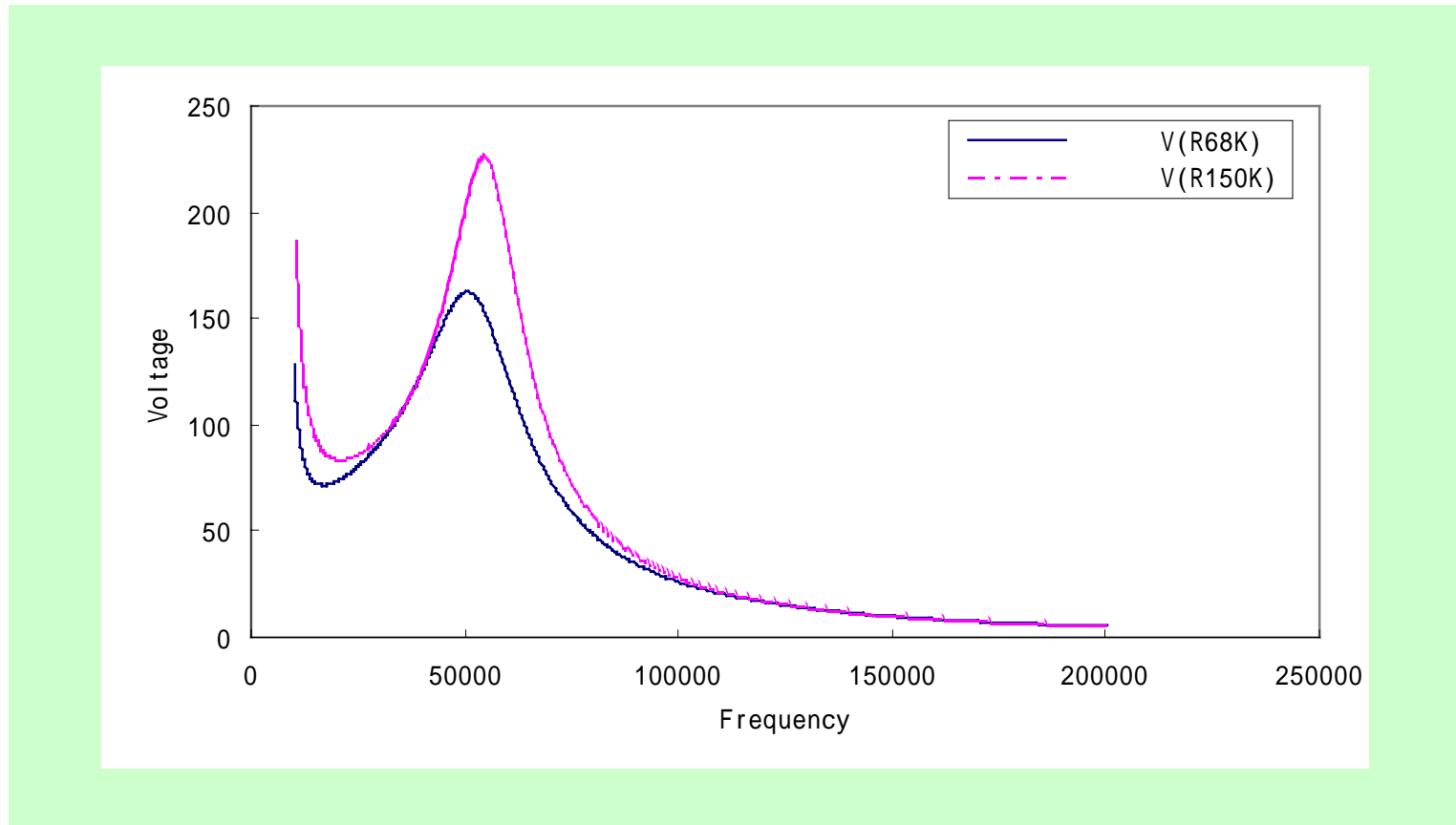


FIG. 78

AC Simulation that Consider Actual Parameters

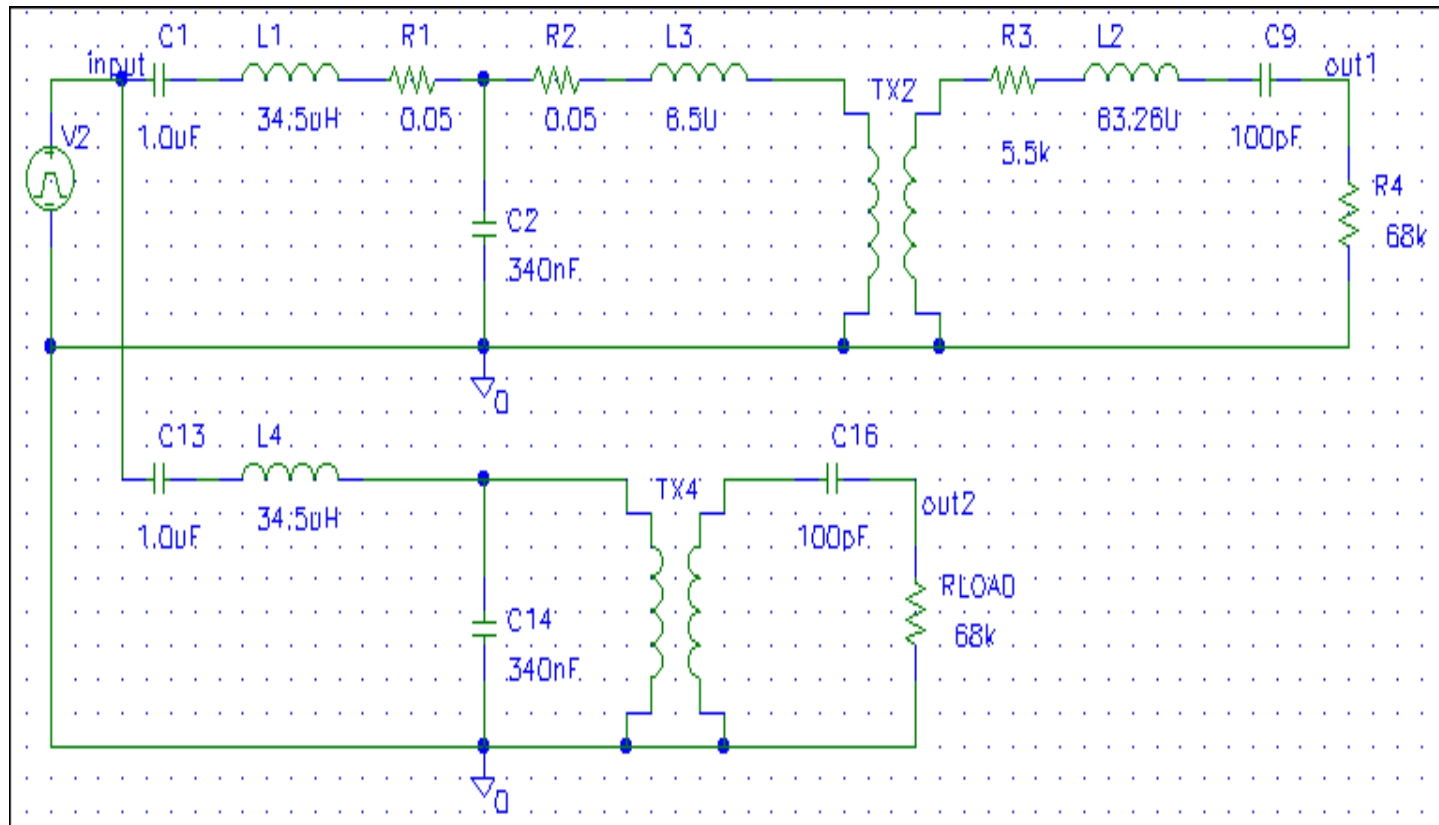


FIG. 79

Simulation Results(Ideal / Actual Case)

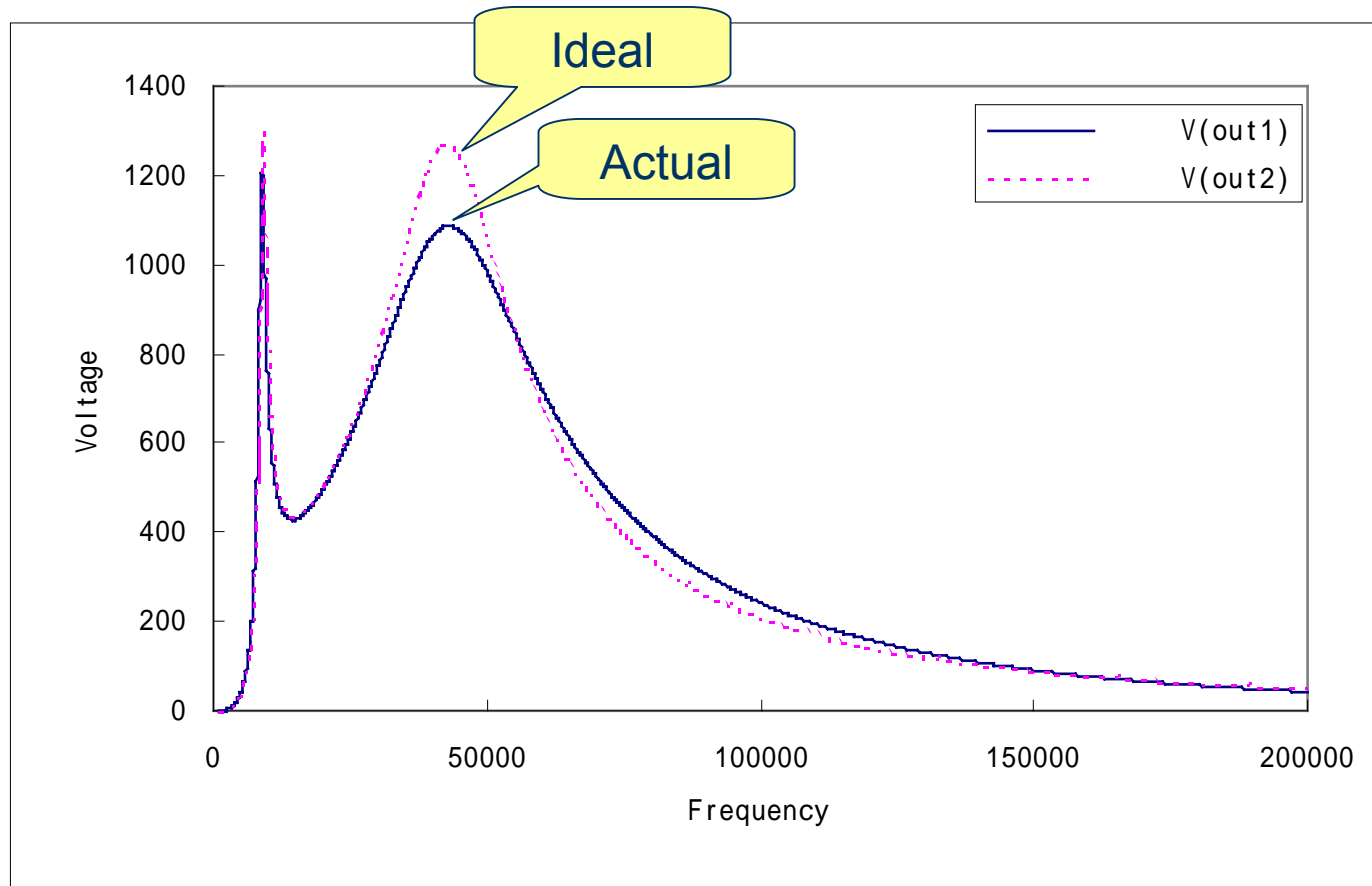


FIG. 80

Power Stage Design Guideline

Program of Design guideline

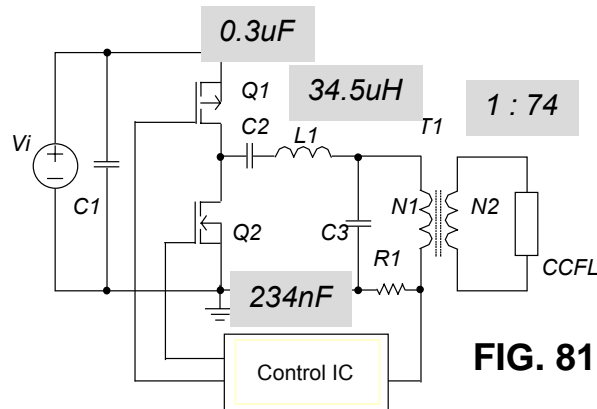


FIG. 81

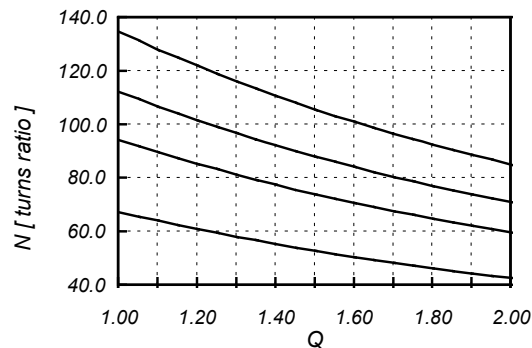


FIG. 82

Parameter	Description	Typical Value	Units
V_{Lrms}	Nominal Lamp Operating Voltage at full brightness	420	V
I_{Lrms}	Nominal Lamp Operating Current at full brightness	5	mA
f_0	Minimum Operating Locked Frequency	53	kHz
L_m	Primary side Magnetizing Inductance	143	μH
C_{out}	Output Ballasting Capacitor	100	μF
V_{in}	Power circuit DC voltage	7	V
C_s	Input DC Decoupling Capacitor	0.8	μH
N	Turns ratio of Transformer	74	none

1. The virtual resistance of the lamp at the operating point	$R_{out} =$	84.0	k Ω
2. The RMS value of the equivalent sinewave source voltage	$V_{rms} =$	3.15	V
3. The input impedance	$R_s =$	4.73	Ω
4. The impedance of the converted secondary capacitance	$X_{cop} =$	48.5	Ω
5. The parallel equivalent load resistance	$R_{op} =$	17.4	Ω
6. The total parallel net capacitance	$X_{ctot} =$	10.6	Ω
7. The net value of the required series inductor	$XL_s =$	11.5	Ω
8. The impedance of the primary side magnetizing inductance	$XL_m =$	47.6	Ω
9. The actual capacitive impedance that must be used	$X_{cp} =$	10.6	Ω
10. The parallel capacitor value	$C_p =$	284	nF
11. The series inductance value	$L_s =$	34.5	μH

Frequency response of output voltage


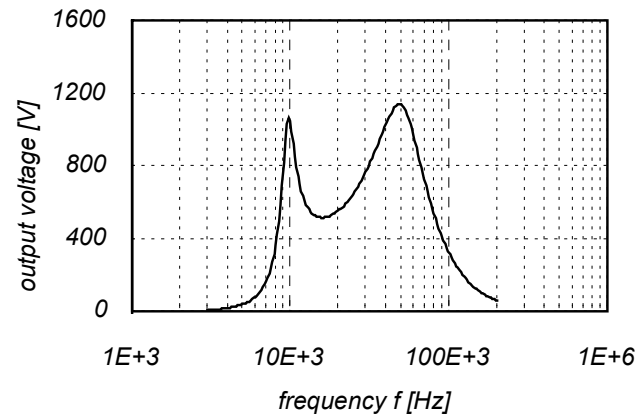


FIG. 83

Mixed Dimming Control Method

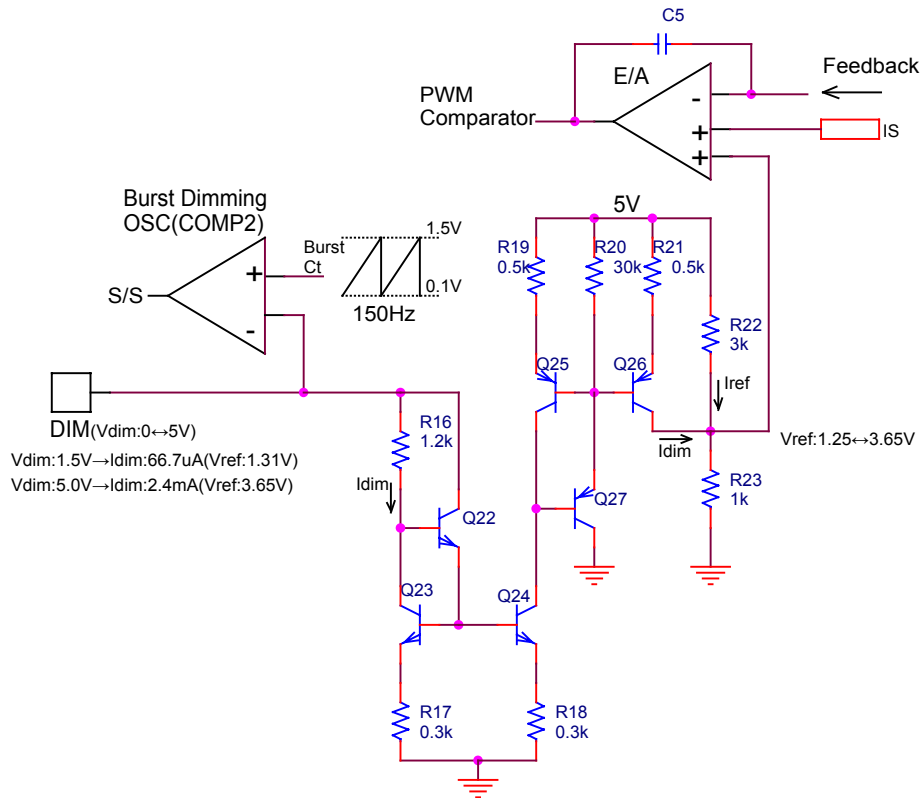

Functional Block Diagram of Mixed Dimming Method

FIG. 84

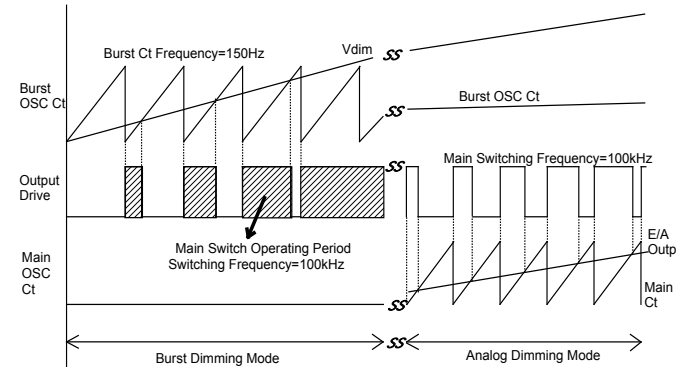


FIG. 85 Timing Waveforms of the Control Circuit


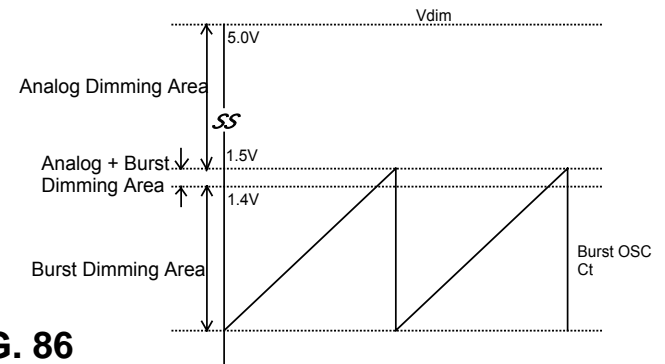


FIG. 86

Operating Area by the Dimming Voltage


Experimental Results

Soft Start

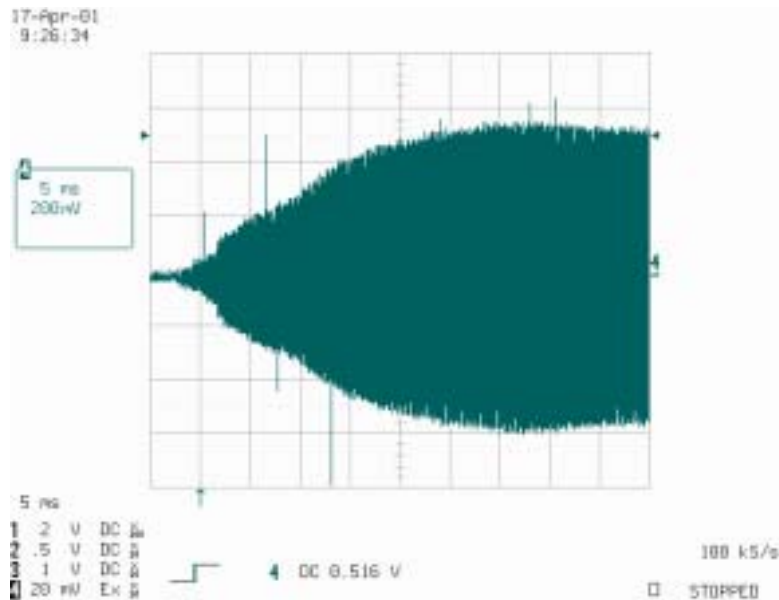

- Lamp Current
- Vin: 8V

FIG. 87

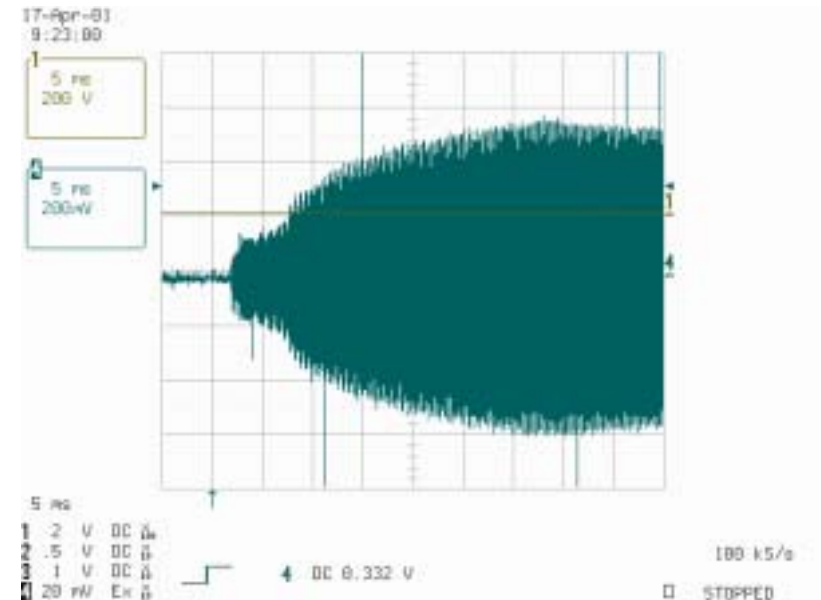

- Lamp Current
- Vin: 20V

FIG. 88

Experimental Results

Burst Dimming Function

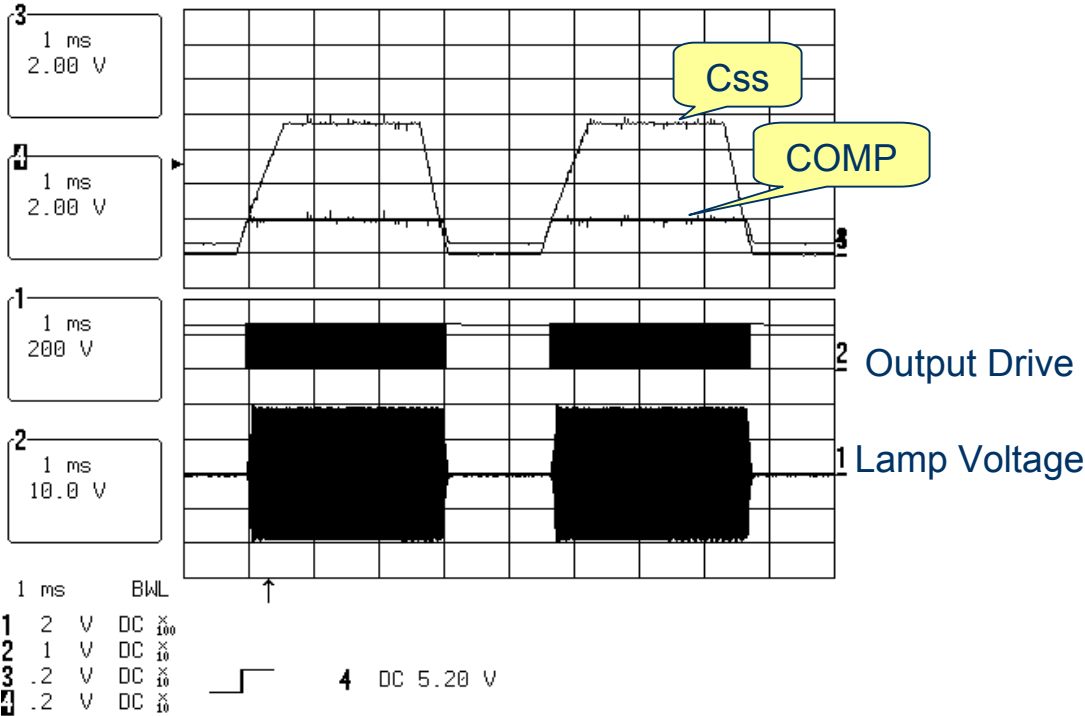


FIG. 89

Experimental Results

Open Lamp Regulation

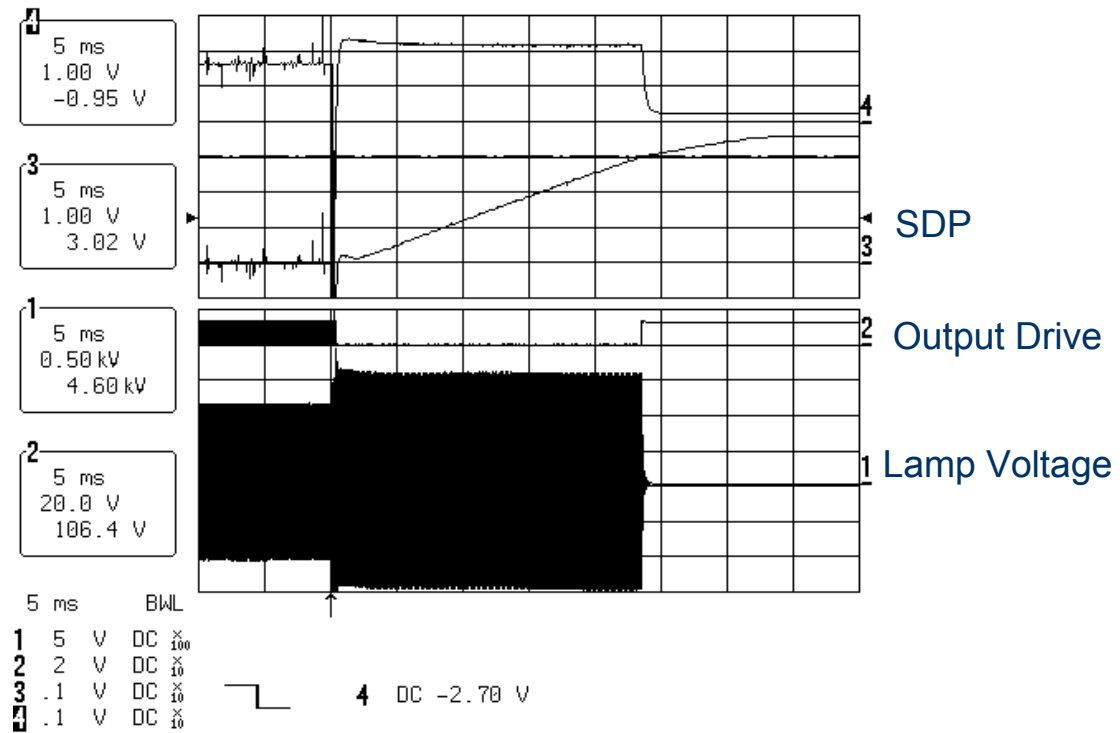


FIG. 90