

# ***ANALOG MODELING WITH VERILOG-A USING CADENCETOOLS***

---

*Eng. Sherief Fathi*

# Hardware Description Language (HDL)

- In electronics, a hardware description language (HDL) is a *specialized computer language* used to *describe the structure and behavior of electronic circuits*.
- Two HDLs used today:


## VHDL and Verilog

Both are industrial standards and are supported by most software tools.


The logo features the text 'VHDL' in a large, blue, 3D-style font at the top. Below it, the word 'OR' is written in a smaller, black, sans-serif font. At the bottom, the word 'Verilog' is written in a large, purple, 3D-style font with a white outline.
 
# Verilog-AMS

- **Combines Verilog, ...**  
Discrete-event / discrete-value simulation
- **Verilog-A, ...**
  - Continuous-time / continuous-value simulation
  - Signal flow modeling
  - Conservative modeling
- **And some extras**
  - Discrete-event / continuous value simulation
  - Automatic interface element insertion



# Mixed-Level Simulation (MLS)

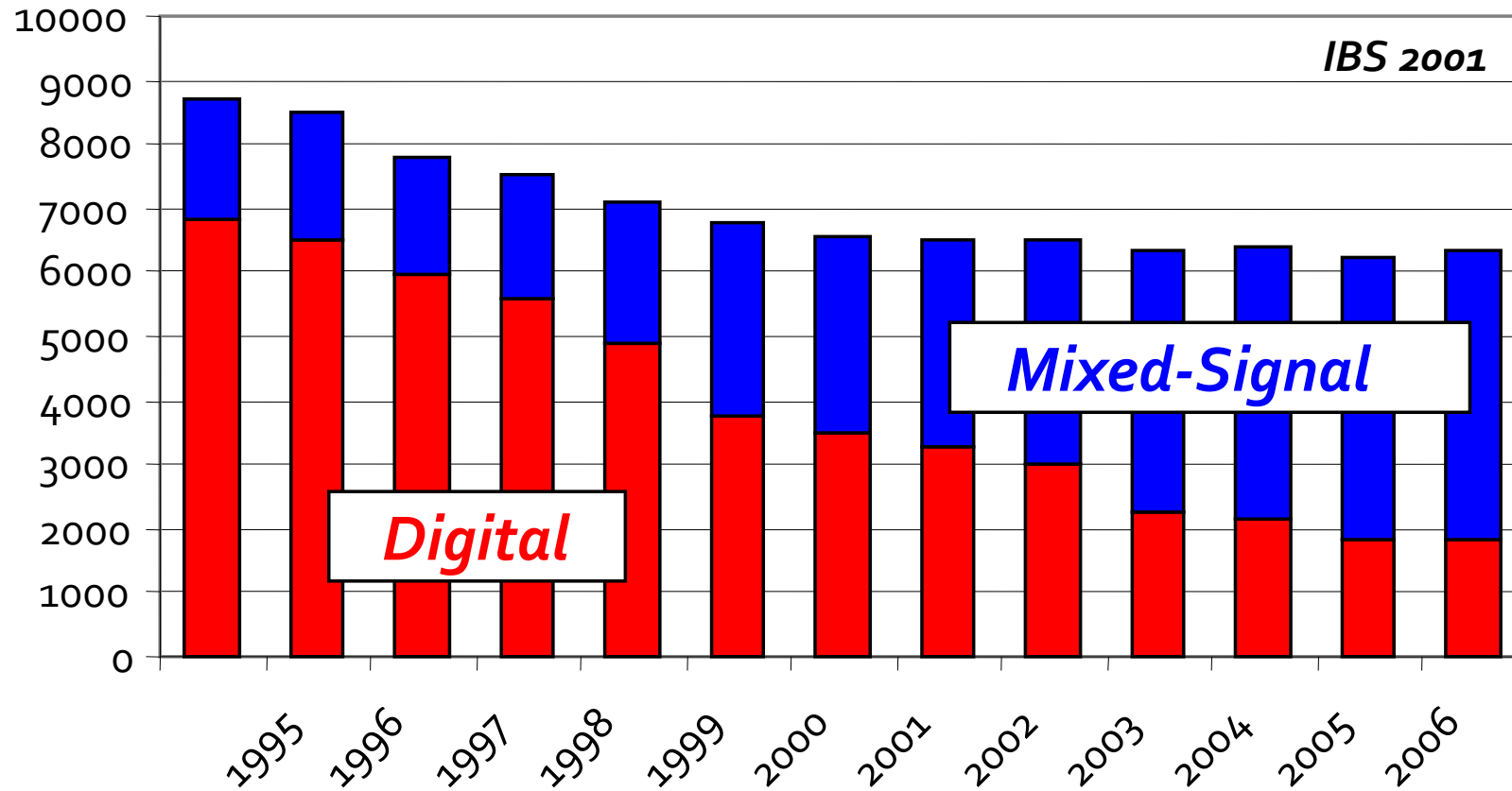

# Verilog-A

- Able to model **analog circuits and systems**
  - **Signal-flow models**


Model relates potentials only

Useful for abstract models
  - **Conservative models**

Model relates potentials and flows

Device modeling and loading at interfaces


# Potentials and Flows

 

*module resistor (a, b);  
electrical a, b;  
parameter r = 1;  
analog  
V(a,b) <+ r\*I(a,b);  
endmodule*
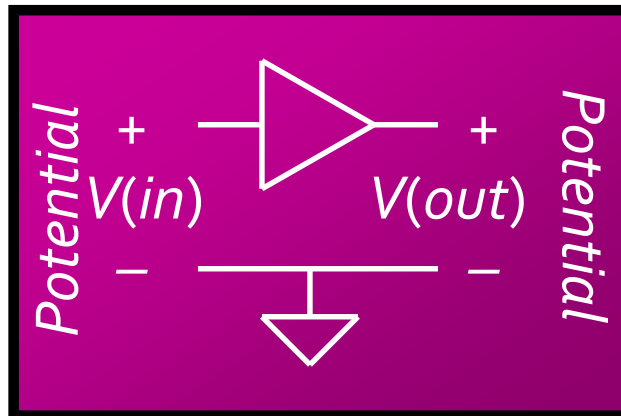
## Resistor

Conservative  
Model  
(potential & flow)



*module amp (out, in);  
output out; input in;  
voltage out, in;  
parameter a = 1;  
analog  
V(out) <+ a\*V(in);  
endmodule*

## Amplifier


Signal-Flow  
Model  
(potential only)

# Declaring Modules

```
module mymod(p,n);
```

```
.....
```

```
endmodule
```

 

# Ports

```
module modName(outPort1, outPort2, inPort, bidirectional);  
    output outPort1;  
    output [3:0] outPort2;  
    input inPort;  
    inout bidirectional;  
    electrical outPort1, [3:0] outport2, inPort, bidirectional;  
    .....  
endmodule
```

# Constants

- **parameter real** `res = 5e3` from (0:inf);
- **parameter real** `percentage = 0.7` from [0:1];
- **parameter integer** `N = 4` from (0:inf);
- **parameter real** `poles[0:3] = { 1.0, 3.198, 4.554, 2.00 }`;
- **parameter string** `transistortype = "NPN"` from { "NPN", "PNP" };

# Variables

- **integer** a[1:64]; // an array of 64 integer values
- **real** float; // a variable to store real value
- **real** gain\_factor[1:30]; // array of 30 gain multipliers


# Signal Access on Nodes, Ports, Branches

- To **get (probe) values**: use access function in expression
  - $x$  gets voltage between  $a$  and ground:  $x = V(a)$
  - $x$  gets voltage between  $a$  and  $b$ :  $x = V(a,b)$
  - $x$  gets current between  $a$  and ground:  $x = I(a)$
  - $x$  gets current between  $a$  and  $b$ :  $x = I(a,b)$
- To **set (source) values**: use access function as target in contribution
  - set voltage between  $a$  and ground to  $x$ :  $V(a) <+ x$
  - set voltage between  $a$  and  $b$  to  $x$ :  $V(a,b) <+ x$
  - set current between  $a$  and ground to  $x$ :  $I(a) <+ x$
  - set current between  $a$  and  $b$  to  $x$ :  $I(a,b) <+ x$
 
# The Contribution Operator : '<+'

- *Accumulates potentials or flows to nodes, ports, and branches*
- Order of contribution is not significant

```
module rlc (a, b);  
  electrical a, b;  
  parameter R = 1 exclude 0;  
  parameter C = 1;  
  parameter L = 1 exclude 0;  
  
  analog begin  
    I(a,b) <+ V(a,b) / R;  
    I(a,b) <+ C*ddt(V(a,b));  
    I(a,b) <+ idt(V(a,b) / L;  
  end  
endmodule
```



# Assignment vs Contribution

- **Example1:**

```
module test(p,n) ;  
  inout p,n;    electrical p,n;  
  parameter integer a = 2;    real r;  
  analog    begin
```

```
    r=a; // Now r=2
```

```
    r=2*a; // The value of r is updated to r=4
```

```
    V(n) <+ a; // This equation contributes by a value a , V(n) =a=2;
```

```
    V(n) <+ 2*a; // A new contribution is added to V(n) , V(n) = a+2a =6;
```

```
  end  
endmodule
```

# Operators

Arithmetic Operators	+, -, *, **, /, %
Relational Operators	<, <=, >, >=
Equality Operators	==, !=, ===, !==
Logical Operators	!, &&,
Bit-Wise Operators	~, &,  , ^, ~^
Unary Reduction	&, ~&,  , ~ , ^, ~^
Shift Operators	>>, <<
Conditional Operators	?:
Concatenations	{ }

# Analog Operators

- **Differentiator: ddt()**  
Time derivative of its argument
- **Integrator: idt()**  
Time integral of its argument  
Optional initial condition
- **Circular integrator: idtmod()**  
Time integral of its argument passed through modulus operation
- **Time delay: absdelay()**  
Delayed version of its argument

# Standard mathematical functions

Verilog function style	Traditional Verilog-AMS function style	Equivalent C function	Description	Domain
<code>\$ln(x)</code>	<code>ln(x)</code>	<code>log(x)</code>	Natural logarithm	$x > 0$
<code>\$log10(x)</code>	<code>log(x)</code>	<code>log10(x)</code>	Decimal logarithm	$x > 0$
<code>\$exp(x)</code>	<code>exp(x)</code>	<code>exp(x)</code>	Exponential	All $x$
<code>\$sqrt(x)</code>	<code>sqrt(x)</code>	<code>sqrt(x)</code>	Square root	$x \geq 0$
-	<code>min(x, y)</code>	-	Minimum	All $x$ , all $y$
-	<code>max(x, y)</code>	-	Maximum	All $x$ , all $y$
-	<code>abs(x)</code>	-	Absolute	All $x$
<code>\$pow(x,y)</code>	<code>pow(x, y)</code>	<code>pow(x,y)</code>	Power ( $x^y$ )	if $x > 0$ , all $y$ ; if $x = 0$ , $y > 0$ ; if $x < 0$ , <code>int(y)</code>
<code>\$floor(x)</code>	<code>floor(x)</code>	<code>floor(x)</code>	Floor	All $x$
<code>\$ceil(x)</code>	<code>ceil(x)</code>	<code>ceil(x)</code>	Ceiling	All $x$

# Trigonometric and hyperbolic functions

Verilog function style	Traditional Verilog-AMS function style	Equivalent C function	Description	Domain
<code>\$sin(x)</code>	<code>sin(x)</code>	<code>sin(x)</code>	Sine	All $x$
<code>\$cos(x)</code>	<code>cos(x)</code>	<code>cos(x)</code>	Cosine	All $x$
<code>\$tan(x)</code>	<code>tan(x)</code>	<code>tan(x)</code>	Tangent	$x \neq n(\pi / 2)$ , $n$ is odd
<code>\$asin(x)</code>	<code>asin(x)</code>	<code>asin(x)</code>	Arc-sine	$-1 \leq x \leq 1$
<code>\$acos(x)</code>	<code>acos(x)</code>	<code>acos(x)</code>	Arc-cosine	$-1 \leq x \leq 1$
<code>\$atan(x)</code>	<code>atan(x)</code>	<code>atan(x)</code>	Arc-tangent	All $x$
<code>\$atan2(y,x)</code>	<code>atan2(y,x)</code>	<code>atan2(y,x)</code>	Arc-tangent of $y/x$	All $x$ , all $y$ ; $atan2(0,0) = 0$
<code>\$hypot(x,y)</code>	<code>hypot(x,y)</code>	<code>hypot(x,y)</code>	$\sqrt{x^2 + y^2}$	All $x$ , all $y$
<code>\$sinh(x)</code>	<code>sinh(x)</code>	<code>sinh(x)</code>	Hyperbolic sine	All $x$
<code>\$cosh(x)</code>	<code>cosh(x)</code>	<code>cosh(x)</code>	Hyperbolic cosine	All $x$
<code>\$tanh(x)</code>	<code>tanh(x)</code>	<code>tanh(x)</code>	Hyperbolic tangent	All $x$
<code>\$asinh(x)</code>	<code>asinh(x)</code>	<code>asinh(x)</code>	Arc-hyperbolic sine	All $x$
<code>\$acosh(x)</code>	<code>acosh(x)</code>	<code>acosh(x)</code>	Arc-hyperbolic cosine	$x \geq 1$
<code>\$atanh(x)</code>	<code>atanh(x)</code>	<code>atanh(x)</code>	Arc-hyperbolic tangent	$-1 < x < 1$

# If Statement (*SWITCH*)

## Example 1


```
if (x1 >= 2) begin
    x2= 5*x1;
end
else if (x1<5) begin
    x2= x1/2;
end
else begin
    x2 = x1;
end
```

## Example 2

```
if(analysis("ic")) begin
    x2= init_cond;
end
else if(analysis("tran")) begin
    x2= x1/2;
end
```


# Example: Resistor and Conductor

- Resistor (potential source branch)

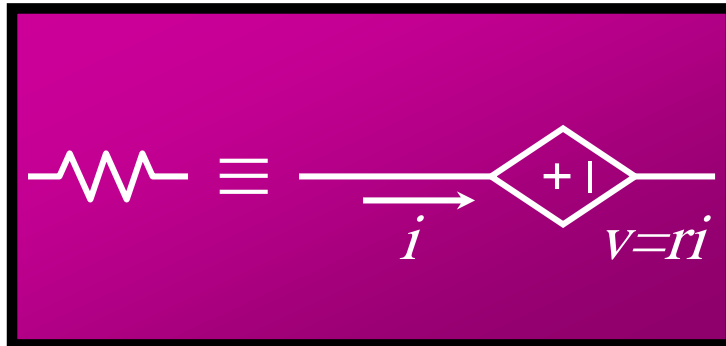

```
module res (a, b);  
electrical a, b;  
parameter real r = 1;  
  
analog  
     $V(a,b) <+ r*i(a,b);$   
endmodule
```


- Conductor (flow source branch)

 

```
module cond (a, b);  
electrical a, b;  
parameter real g = 1;  
  
analog  
     $i(a,b) <+ g*V(a,b);$   
endmodule
```


# Example: Capacitor and inductor

- Capacitor

 

```
module cap (a, b);  
  electrical a, b;  
  parameter c = 1;  
  
  analog  
    I(a,b) <+ C*ddt(V(a,b));  
endmodule
```

- inductor

 

```
module ind (a, b);  
  electrical a, b;  
  parameter L = 1;  
  
  analog  
    V(a,b) <+ L*ddt(I(a,b));  
endmodule
```

# Example: Multiplier


```
//VerilogA for a multiplier,  
`include "constants.vams"  
`include "disciplines.vams"  
module multiplier(in1,in2,out);  
input in1,in2;
```

```
output out;  
electrical in1,in2,out;  
analog begin  
V(out) <+ V(in1) * V(in2);  
end  
endmodule
```

# Inserting Verilog-A model into Cadence

- Open Cadence then change the editor:

editor="gedit"

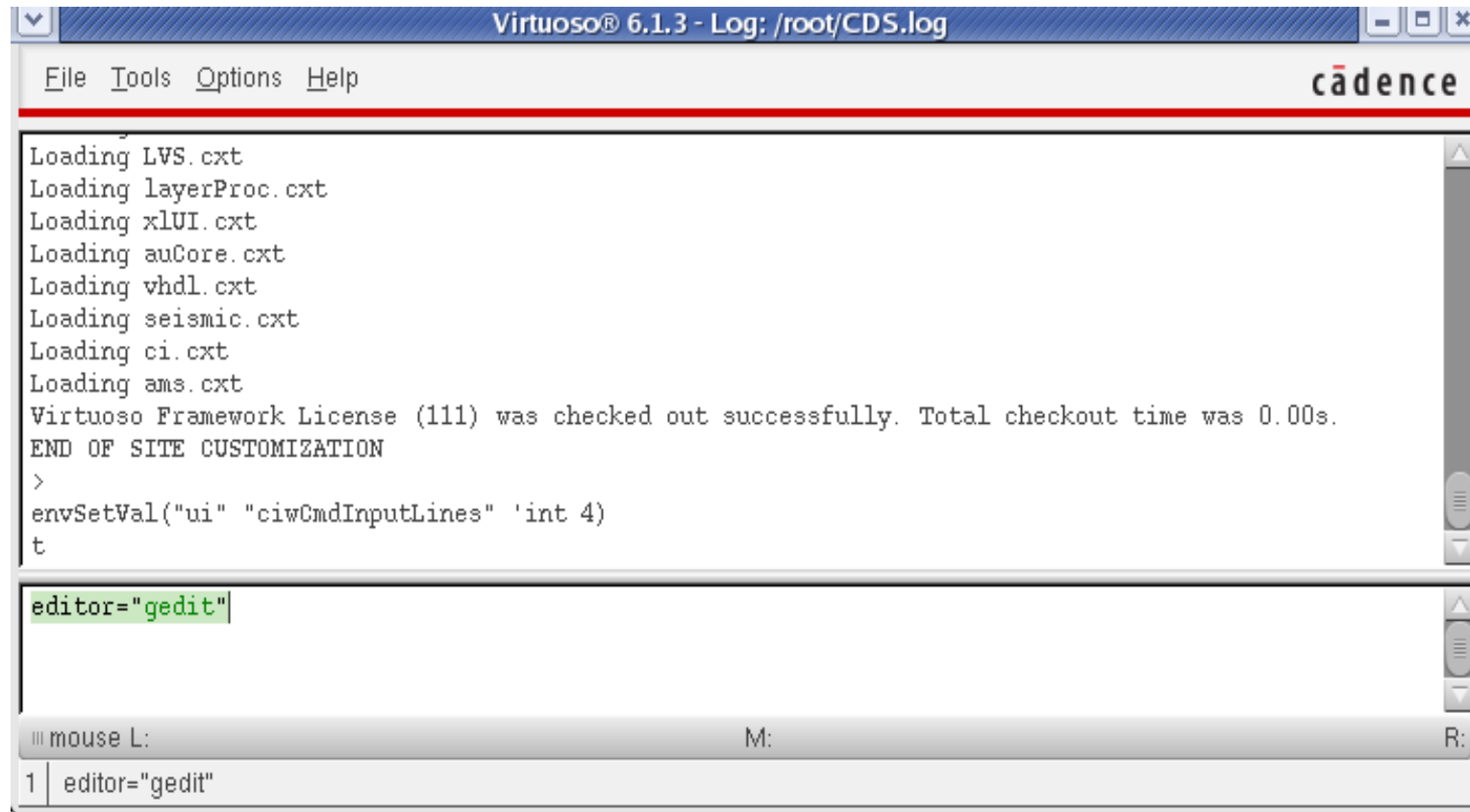


The screenshot shows the Cadence Virtuoso 6.1.3 command window. The title bar reads "Virtuoso® 6.1.3 - Log: /root/CDS.log". The menu bar includes "File", "Tools", "Options", and "Help". The main text area displays the following output:

```
Loading LVS.cxt
Loading layerProc.cxt
Loading xlUI.cxt
Loading auCore.cxt
Loading vhdL.cxt
Loading seismic.cxt
Loading ci.cxt
Loading ams.cxt
Virtuoso Framework License (111) was checked out successfully. Total checkout time was 0.00s.
END OF SITE CUSTOMIZATION
>
envSetVal("ui" "ciwCmdInputLines" 'int 4)
t
```

Below the main text area, the command `editor="gedit"` is entered and highlighted in green. At the bottom of the window, there is a status bar with "mouse L:", "M:", and "R:" indicators, and a command line showing `1 | editor="gedit"`.

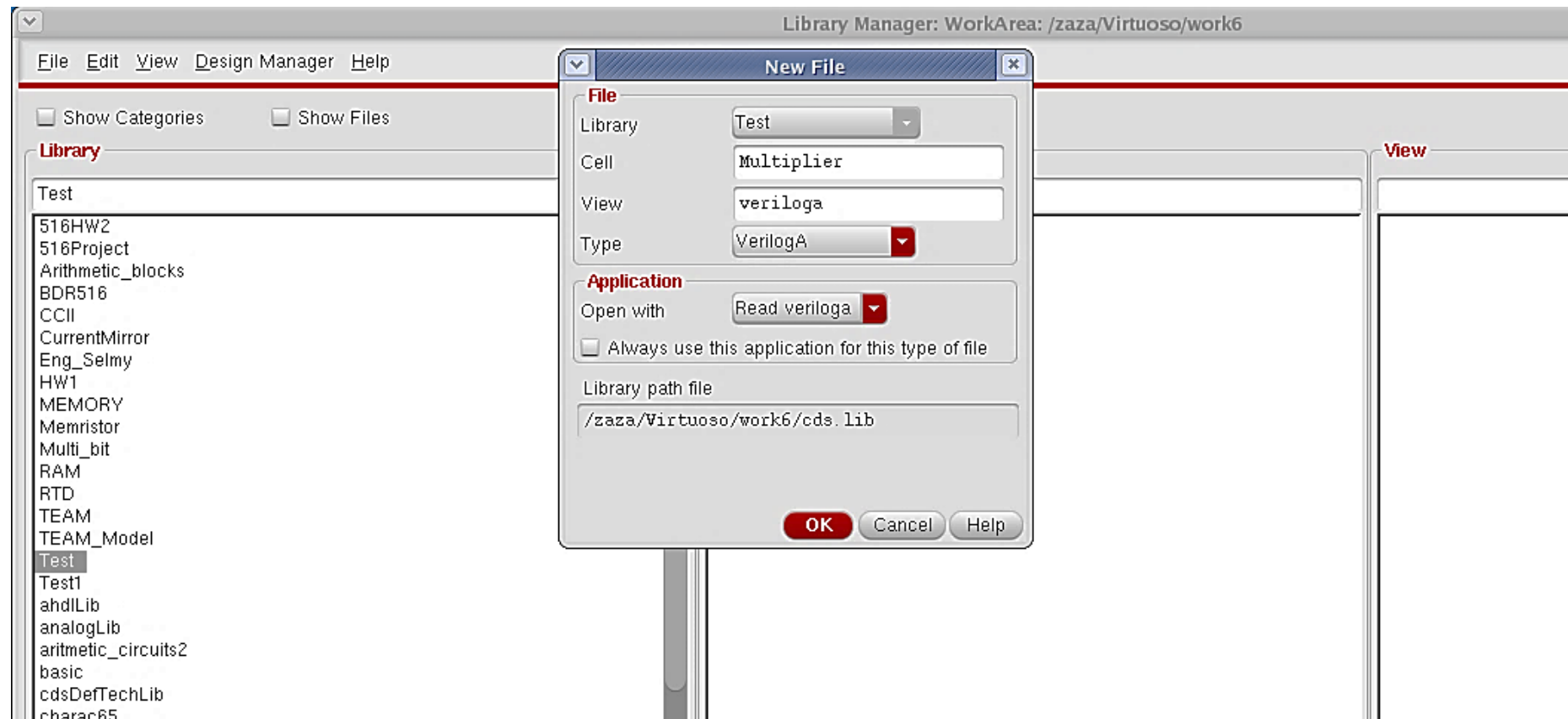
# Inserting Verilog-A model into Cadence

- From the library manager, create a “new cell view” with a type: “veriloga”



# Inserting Verilog-A model into Cadence

- Insert the VerilogA code:

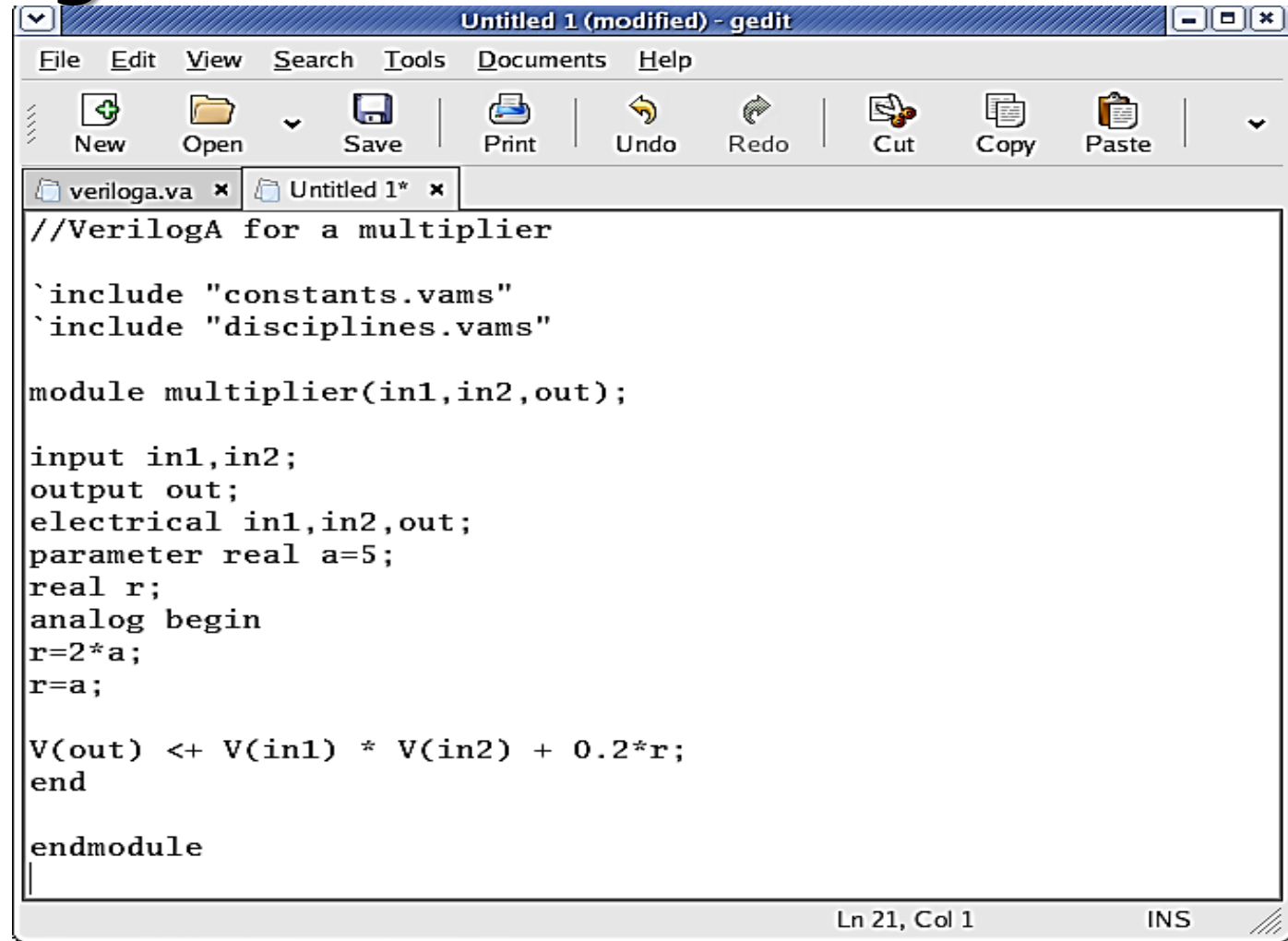

The screenshot shows a gedit text editor window titled "Untitled 1 (modified) - gedit". The window contains the following Verilog-A code:

```
//VerilogA for a multiplier

`include "constants.vams"
`include "disciplines.vams"

module multiplier(in1,in2,out);

input in1,in2;
output out;
electrical in1,in2,out;
parameter real a=5;
real r;
analog begin
r=2*a;
r=a;


V(out) <+ V(in1) * V(in2) + 0.2*r;
end

endmodule
```

The status bar at the bottom right of the editor shows "Ln 21, Col 1" and "INS".

# Inserting Verilog-A model into Cadence

- Choose highlight mode > verilog

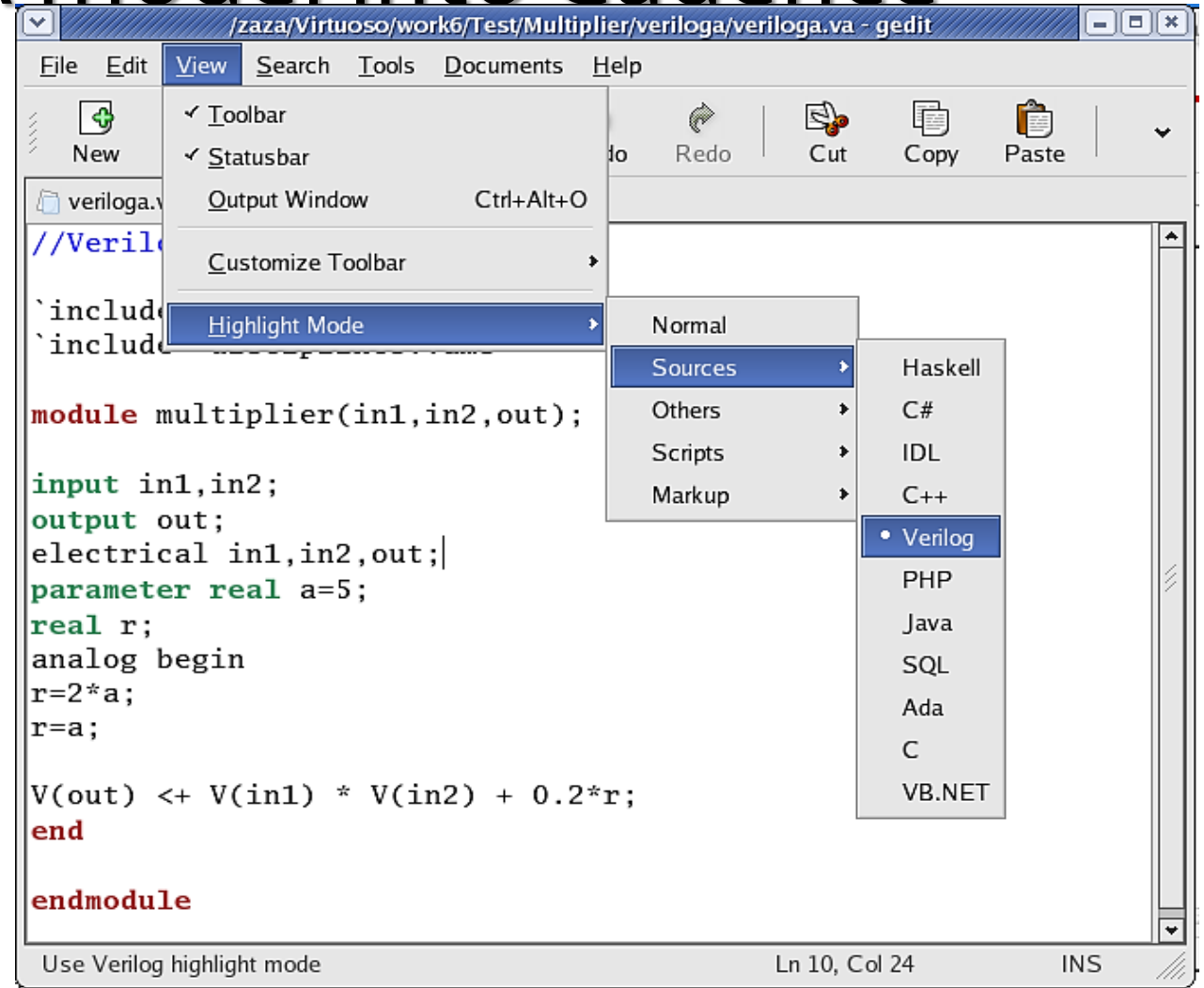


# Inserting Verilog-A model into Cadence

- Insert the VerilogA code, save the file, and close.
1. If the model does not has a syntax error, you will be asked to create a symbol.




 2. If the model has a syntax error, open the error log to identify errors and solve it.



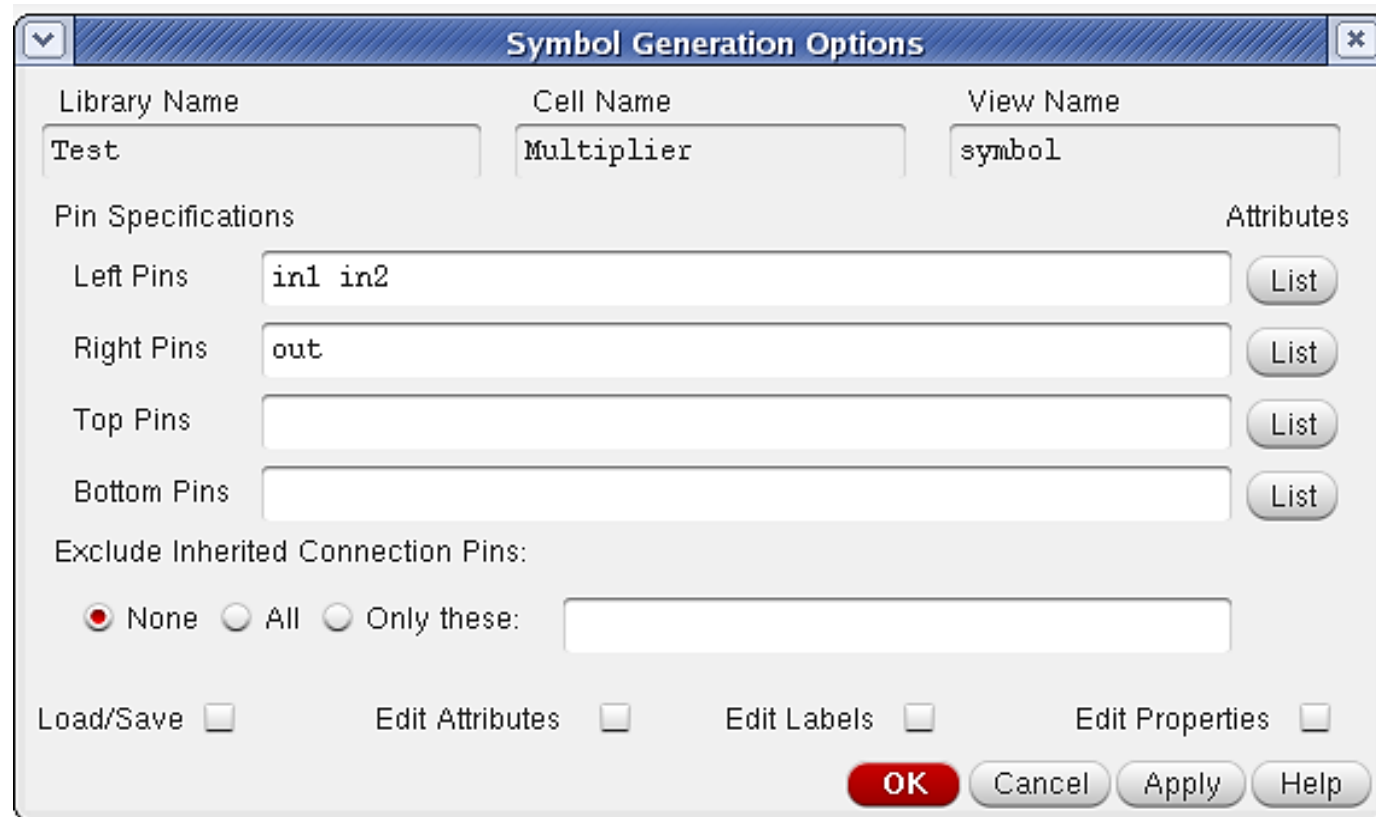
# Inserting Verilog-A model into Cadence

- Define the directions of the pins i.e. : left, right, top, or bottom



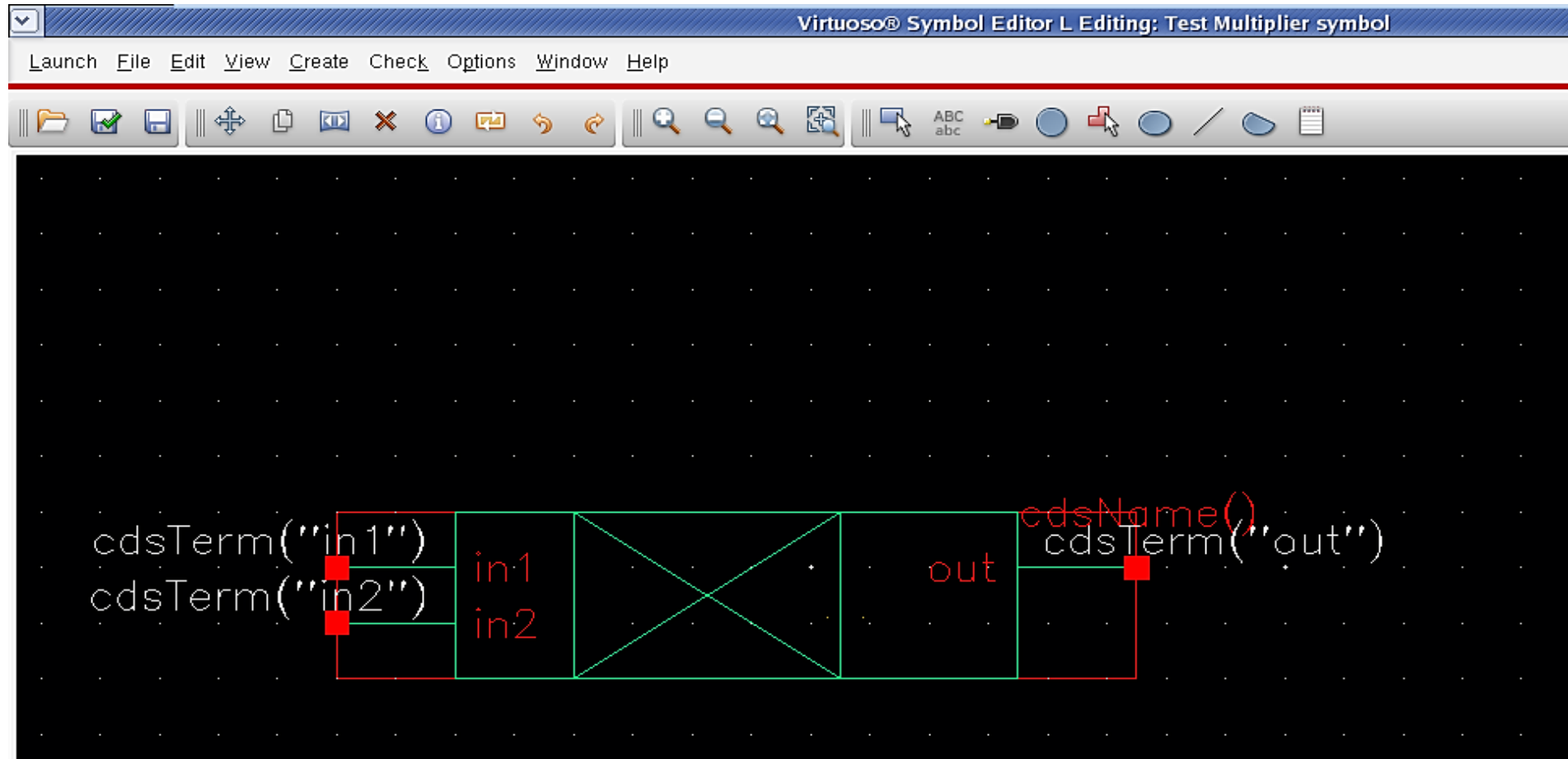
# Inserting Verilog-A model into Cadence

- Modify the symbol “optional”, then Check & Save



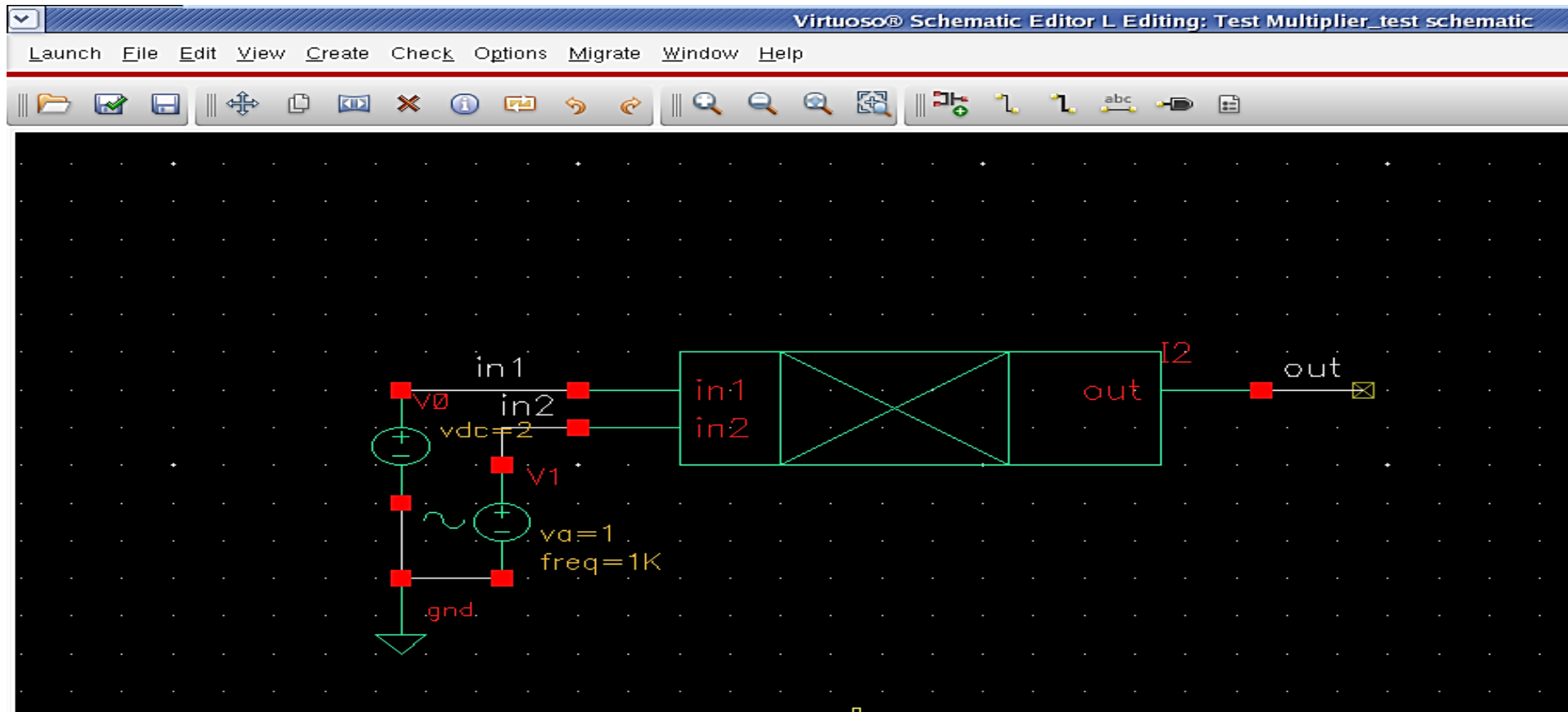
# Inserting Verilog-A model into Cadence


- Now you can test your model by creating a new cell view of type “Schematic”, and make a simple test circuit:







# Inserting Verilog-A model into Cadence

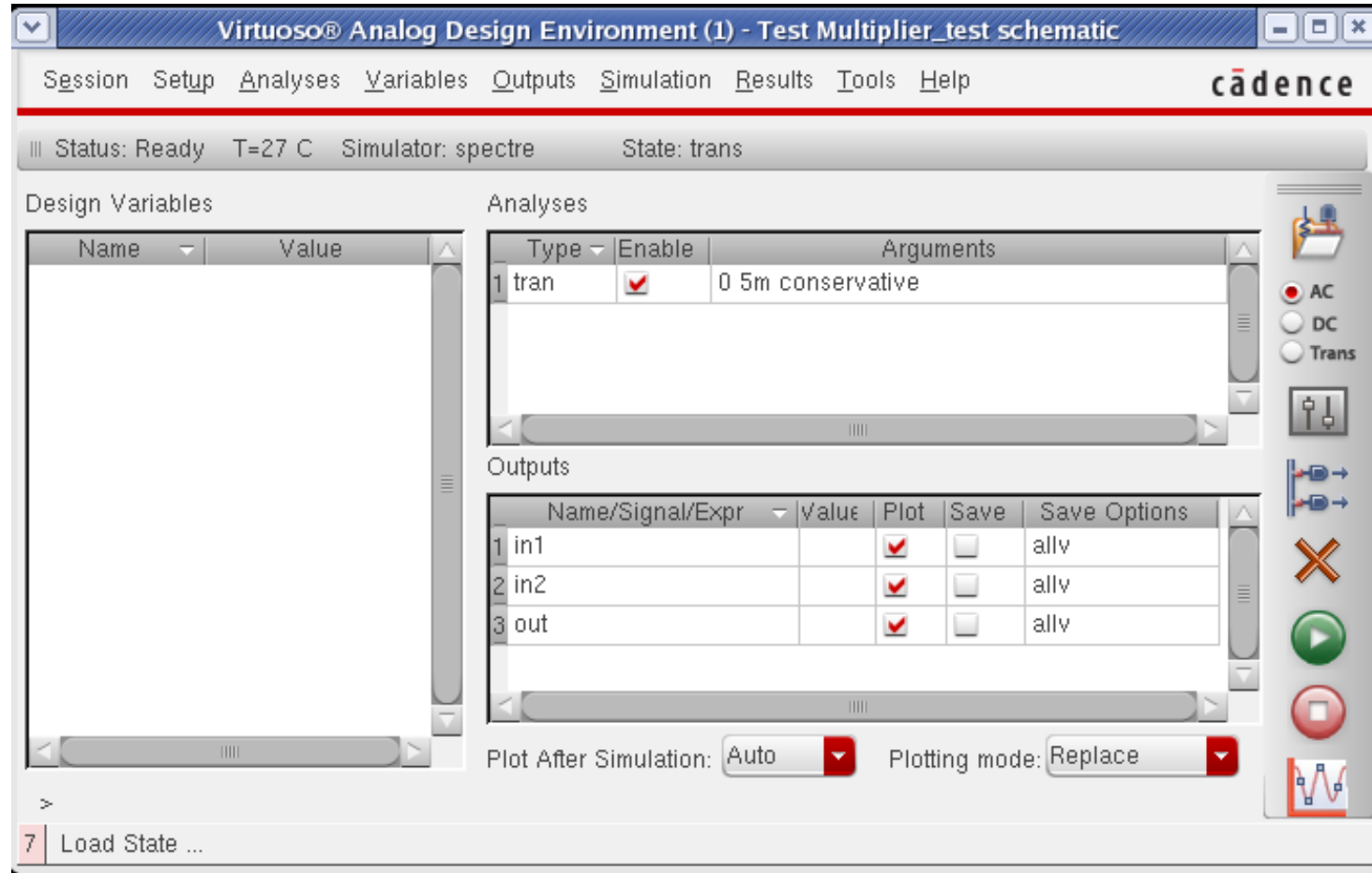

# Inserting Verilog-A model into Cadence

 

# Example B: TEAM Memristor model

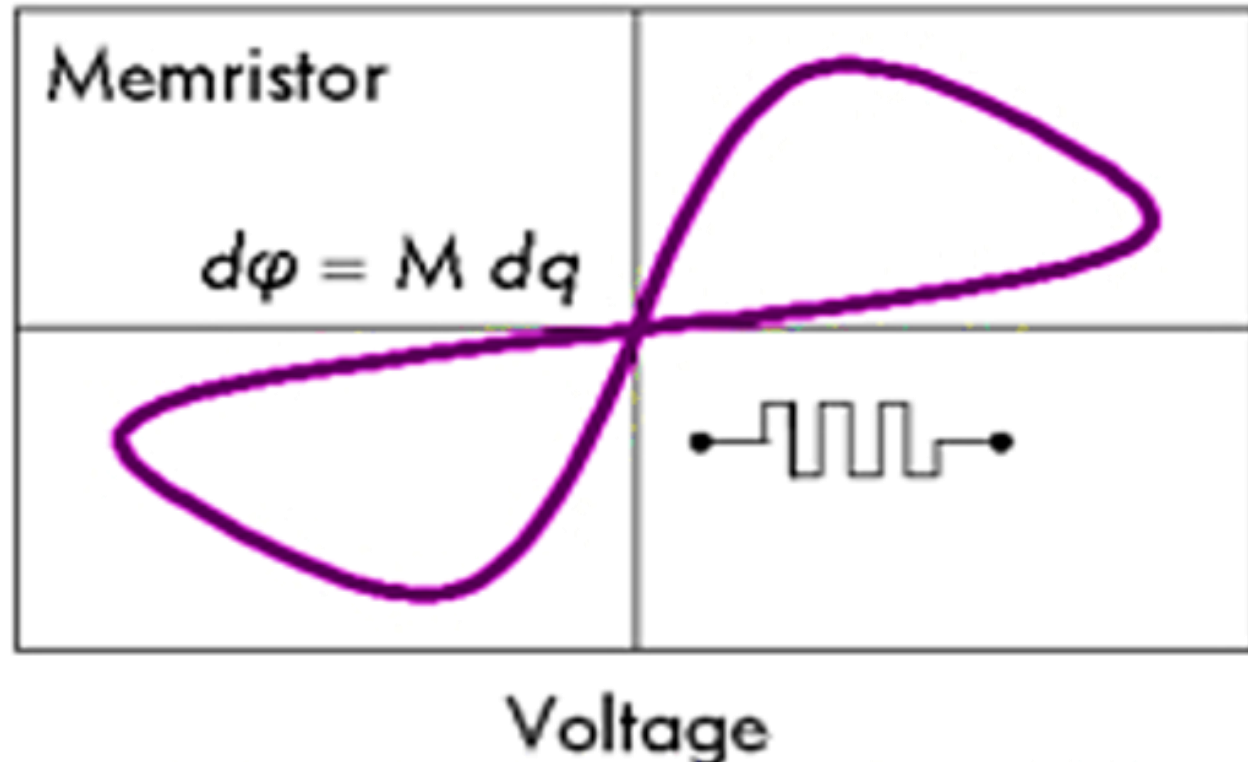  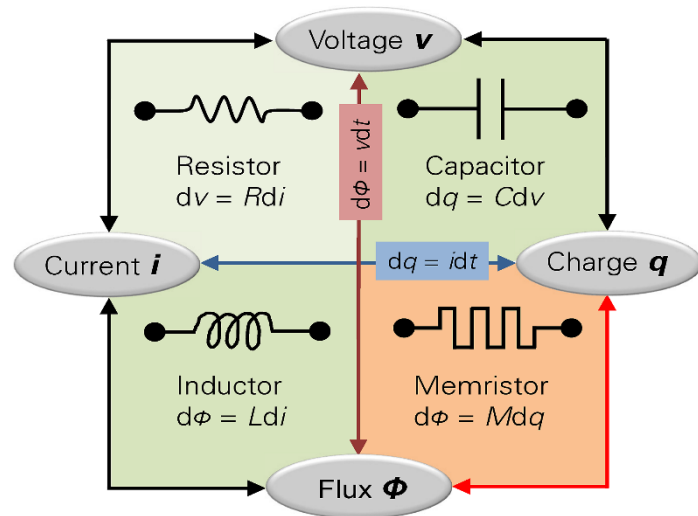

[http://webee.technion.ac.il/people/skva/Memristor%20Models/TCAS\\_memristor\\_model\\_paper\\_final.pdf](http://webee.technion.ac.il/people/skva/Memristor%20Models/TCAS_memristor_model_paper_final.pdf)

# Example B: TEAM Memristor model

**Note:** You can access the parameters' values from the schematic directly

The screenshot shows the 'Edit Object Properties' dialog box for a TEAM Memristor model. The dialog is divided into two main sections. The top section contains a table of properties and their values, with a 'Browse' button and a 'Reset Instance Labels Display' button. The bottom section contains a list of CDF parameters for the view, with a dropdown menu for the view name and a 'Display' column for each parameter.

Property	Value	Display
Library Name	TEAM	off
Cell Name	TEAM1	off
View Name	symbol	off
Instance Name	I0	off

CDF Parameter of view	Value	Display
model	2	off
window_type	0	off
dt	100e-13	off
init_state	0	off
Roff	2e+05	off
Ron	100	off
D	3e-09	off
uv	1e-13	off
w_multiplied	3.33e+08	off
p_coeff	2	off
J	1	off
p_window_noise	1e-18	off
treshold_voltage	0	off
f_off	3.5e-06	off

## *Some useful links*

- Verilog-AMS Manual

<http://www.accellera.org/images/downloads/standards/v-ams/VAMS-LRM-2-3-1.pdf>

- Verilog-A model library at

<http://www.designers-guide.org/VerilogAMS/>

# Questions



*Thank  
you*








# Operators

{ } { }	Concatenation, replication
unary +, unary -	Unary operators
+ - * / **	Arithmetic
%	Modulus
> >= < <=	Relational
!	Logical negation
&&	Logical and
	Logical or
==	Logical equality
!=	Logical inequality
===	Case equality
!==	Case inequality
~	Bitwise negation
&	Bitwise and
	Bitwise inclusive or
^	Bitwise exclusive or
~ or ~	Bitwise equivalence
&	Reduction and
~&	Reduction nand
	Reduction or

     
# Verilog-AMS

- **Combines Verilog, ...**
  - Discrete-event / discrete-value simulation
- **Verilog-A, ...**
  - Continuous-time / continuous-value simulation
  - Signal flow modeling
  - Conservative modeling
- **And some extras**
  - Discrete-event / continuous value simulation
  - Automatic interface element insertion


 
# Named Branches

- Named branches are explicitly declared
  - Useful when defining distinct *parallel potential branches*



```
module rlc (a, b);  
  electrical a, b;  
  parameter R = 1, C = 1, L = 1;  
  branch (a, b) res, cap, ind;  
  
  analog begin  
    V(res) <+ R*I(res);  
    I(cap) <+ C*ddt(V(cap));  
    V(ind) <+ L*ddt(I(ind));  
  end  
endmodule
```

# Example: Capacitor with Initial Condition

```
module cap (a, b);  
    electrical a, b;  
    parameter real c=0, ic=0;  
  
    analog begin  
        if (analysis("ic"))  
            V(a,b) <+ ic;  
        else  
            I(a,b) <+ ddt(c*V(a,b));  
        end  
    endmodule
```

## Examples:

```
module adc4 (out, rem, in);
    output [3:0] out; output rem;
    input in;
    electrical [3:0] out;
    electrical in, rem, rem_chain;

    adc2 hi2 (out[3:2], rem_chain, in);
    adc2 lo2 (out[1:0], rem, rem_chain);
endmodule

module adc2 (out, remainder, in);
    output [1:0] out; output remainder;
    input in;
    electrical [1:0] out;
    electrical in, remainder, r;

    adc hil (out[1], r, in);
    adc lol (out[0], remainder, r);
endmodule
```

# Accessing Net and Branch Signals

- Examples

$V_{in} = V(in);$

$CurrentThruBranch = I(myBranch);$

- Indirect branch assignment

An indirect branch assignment is useful when it is difficult to solve an equation. It has this format,

$$V(n) : V(p) == 0;$$

which can be read as "***find  $V(n)$  such that  $V(p)$  is equal to zero.***"

# Operator Precedence

[ ] bit-select or part-select

( ) parentheses

!, ~ logical and bit-wise  
negation

&, |, ~&, ~|, ^, ~^, ^~  
reduction operators

+, - unary arithmetic

{ } concatenation

\*, /, % arithmetic

+, - arithmetic

<<, >> shift

>, >=, <, <= relational

==, != logical equality

& bit-wise AND

^, ^~, ~^ bit-wise XOR and XNOR

| bit-wise OR

&& logical AND

|| logical OR

? : conditional

# Analog operators and equations

- Time derivative operator
- Time integral operator
- Circular integrator operator


Table 4-20—Analog operator arguments

Operator	Constant expression arguments	Dynamic expression arguments
absdelay	maxdelay	expr, td
ddt	abstol	expr
ddx	wrt_what	expr
idt	abstol	expr, ic, assert
idtmod	abstol	expr, ic, modulus, offset
laplace_zp laplace_zd laplace_np laplace_nd	poles, abstol, zero	expr
last_crossing		expr, dir
limexp		expr
slew		expr, max_pos_slew_rate, max_neg_slew_rate
transition	time_tol	expr, td, rise_time, fall_time
zi_zp zi_zd zi_np zi_nd	zeros, poles, T , t0	expr, t
 
# The Contribution Operator – '<+'

- *Accumulates potentials or flows to nodes, ports, and branches*
- Order of contribution is not significant

```
module rlc (a, b);  
  electrical a, b;  
  parameter R = 1 exclude 0;  
  parameter C = 1;  
  parameter L = 1 exclude 0;  
  
  analog begin  
    I(a,b) <+ V(a,b) / R;  
    I(a,b) <+ C*ddt(V(a,b));  
    I(a,b) <+ idt(V(a,b) / L;  
  end  
endmodule
```



# The Contribution Operator – '<+'

- Supports implicit equations
  - Solves for  $x$  when  $x <+ f(x)$

```
module diode (a, c);  
electrical a, c;  
parameter is = 1f from (0:inf);  
parameter rs = 0 from [0:inf);  
  
analog begin  
   $I(a,c) <+ is * (\$limexp((V(a,c) - rs * I(a,c)) / \$vt) - 1);$   
end  
endmodule
```



Limiting  
Exponential  
(helps convergence)

$I(a,c)$  on both sides  
makes eqn implicit

# Example: Controlled Sources

```
module vcvs (p, n, ps, ns);  
  electrical p, n, ps, ns;  
  output p, n; input ps, ns;  
  
  parameter gain = 1;  
  
  analog  
    V(p,n) <+ gain*V(ps,ns);  
endmodule
```

```
module vccs (p, n, ps, ns);  
  electrical p, n, ps, ns;  
  output p, n; input ps, ns;  
  
  parameter gain = 1;  
  
  analog  
    I(p,n) <+ gain*V(ps,ns);  
endmodule
```

```
module ccvs (p, n, ps, ns);  
  electrical p, n, ps, ns;  
  output p, n; input ps, ns;  
  
  parameter gain = 1;  
  
  analog  
    V(p,n) <+ gain*I(ps,ns);  
endmodule
```

```
module cccs (p, n, ps, ns);  
  electrical p, n, ps, ns;  
  output p, n; input ps, ns;  
  
  parameter gain = 1;  
  
  analog  
    I(p,n) <+ gain*I(ps,ns);  
endmodule
```

# Hysteretic Relay

```
module relay (pout, nout, pin, nin);  
voltage pout, nout, pin, nin;  
input pin, nin; output pout, nout;  
parameter real thresh = 0, hyst = 0;  
  
real offset;  
  
analog begin  
  @(cross(V(pin,nin) - thresh - offset, +1))  
    offset = -hyst;  
  @(cross(V(pin,nin) - thresh - offset, -1))  
    offset = hyst;  
  
  if (V(pin,nin) - thresh - offset > 0)  
    V(pout, nout) <+ 0;  
  
end  
endmodule
```

Switch Branch

# Event-Driven Modeling

- @ blocks
  - Blocks of code executed upon an event
- Event types

<i>Name</i>	<i>Generates events ...</i>
<i>cross()</i>	At analog signal crossings
<i>timer()</i>	Periodically or at specific times
<i>initial_step</i>	At beginning of simulation
<i>final_step</i>	At end of simulation

- Time of the Last Zero Crossing; last\_crossing()
-

# Example: Record Zero Crossing Times

```
module zero_crossings (in);  
  voltage in; input in;  
  parameter integer dir=1 from [-1:1] exclude 0;  
  integer fp; real last;  
  
  analog begin  
    @(initial_step)  
      fp = $fopen( "zero-crossings");  
      last = $last_crossing(V(in), dir);  
      @(cross(V(in), dir))  
        $fstrobe( fp, "%0.10e", last);  
      @(final_step)  
        $fclose(fp);  
  end  
endmodule
```

Record time  
of crossing

# Example: Noisy Diode

```
module diode (a, c);  
  electrical a, c;  
  branch (a, c) diode, cap;  
  parameter real is=1e-14, rs=0, tf=0, cjo=0, phi=0.7;  
  parameter real kf=0, af=1, ef=1;  
  
  analog begin  
    I(diode) <+ is*($limexp(V(diode)/$vt) - 1);  
    I(cap) <+ ddt(tf*I(diode) - 2*cjo*sqrt(phi * (phi * V(diode))));  
    I(diode) <+ white_noise( 2 * `P_Q * I(diode) );  
    I(diode) <+ flicker_noise( kf * pow(abs(I(diode)), af), ef);  
  end  
endmodule
```

## 4. Basic language features

Powerful syntax for declaring parameters with default and range:

```
parameter real r = 1000 from (0:inf);
```

Chained defaults:

```
parameter real l = 1u from (0:inf);
```

```
parameter real w = 1u from (0:inf);
```

```
parameter real rho = 1 from (0:inf);
```

```
parameter real r = rho*l/w from (0:inf);
```

## 4. Basic language features

All behavior in the **analog** block

```
analog begin  
    I(a,b) <+ V(a,b) / r;  
end
```

Use **begin** / **end** for multi-line blocks – like you would use braces { } in C

\*\*\* Emacs and VIM have "Verilog-mode" plug-ins that can highlight keywords and keep your indentation correct.

## 4. Basic language features

The contribution operator:

```
analog begin  
  I(a,b) <+ V(a,b) / r;  
  I(a,b) <+ white_noise(4*`P_K  
    *$temperature, "thermal");  
end
```

Not quite an assignment – all contributions to I are summed.

### 3. Simple examples

```
`include "disciplines.vams"  
  
module simplecap(a, b);  
  inout a, b;  
  electrical a, b;  
  parameter real c = 1000 from [0:inf);  
  (* desc = "charge" *) real q;  
  
  analog begin  
    q = c * V(a,b);  
    I(a,b) <+ ddt( q );  
  end  
endmodule
```

Always use  
ddt( charge )  
not C\*ddt(V)

# Example: Resistive RF Source

```
module port (p, m);  
  voltage p, m;  
  parameter real r=50, dc=0, mag=0, ampl=0, freq=0, phase=0;  
  analog begin  
    V(p,m) <+ 2*dc - r*I(p,m);  
    V(p,m) <+ 2*ac_stim(mag);  
    V(p,m) <+ white_noise(4*`P_K*r*$temperature);  
    if (analysis("tran"))  
      V(p,m) <+ 2*ampl*cos(2*`M_PI*freq*$abstime+phase);  
    bound_step(0.1 / freq);  
  end  
endmodule
```

