

Chapter 10 CMOS Bandgap References

§10-1 Basic Principles of Bandgap References (BGR)

$$V_{BE(on)} = mV_{therm} \ln(I_1 / I_S)$$

$$I_S = qAn_i^2 \bar{D}_n / Q_B$$

I_S : Reverse saturation current of a BJT

$$= Bn_i^2 \bar{D}$$

A : Area of a BJT

$$= B' n_i^2 T \bar{m}$$

Q_B : Base minority carrier charges

where B and B' are constants, indep. of T.

\bar{D} : Average diffusivity of carriers

$$\bar{m} = CT^{-n}$$

C : Constant, indep. of T.

n : Temp. exponent.

$$n_i^2 = ET^3 \exp(-V_{GO} / V_{therm})$$

E : Constant, indep. of T.

V_{GO} : Energy gap.

$$\Rightarrow V_{BE(on)} = mV_{therm} \ln[I_1 T^{-g} F \exp(V_{GO} / V_{therm})]$$

F : Constant , indep. of T.

$$g = 4 - n$$

$I_1 = GT^a$ where I_1 is the collector current and G is a temp.-indep. constant.

$$\Rightarrow V_{BE(on)} = V_{GO} - V_{therm} [(g - a) \ln T - \ln(FG)]$$

In general, the output voltage V_{out} is a sum of $V_{BE(on)}$, and KV_{therm} with a weighting factor K such that V_{out} is nearly indep. of T.

$$V_{BE(on)} + KV_{therm} = V_{out} = V_{GO} - mV_{therm} (g - a) \ln T + mV_{therm} [K + \ln(FG)] \dots\dots\dots(1)$$

$$\left. \frac{dV_{out}}{dT} \right|_{T=T_0} = 0 = \frac{mV_{thermo}}{T_0} [K + \ln(FG)] - \frac{mV_{thermo}}{T_0} (g - a) \ln T_0 - \frac{mV_{thermo}}{T_0} (g - a) + \frac{d}{dT} V_{GO}$$

$$\Rightarrow K + \ln(FG) = (g - a) \ln T_0 + (g - a) - \left(\frac{d}{dT} V_{GO} \right) \cdot \frac{T_0}{mV_{thermo}} \dots\dots(2)$$

Substituting (2) into (1), we have

$$V_{out} = V_{GO} + mV_{therm}(\mathbf{g} - \mathbf{a})(1 + \ln \frac{T_o}{T}) - T \frac{d}{dT} V_{GO}$$

$$V_{GO} = 1.16 - \frac{7.02 \times 10^{-4} \cdot T^2}{T + 1108}$$

$$\left. \frac{d}{dT} V_{GO} \right|_{T=T_o} = - \frac{14.04 \times 10^{-4} T_o (T_o + 1108) - 7.02 \times 10^{-4} \cdot T_o^2}{(T_o + 1108)^2}$$

$$= - \frac{14.04 \times 10^{-4} \cdot T_o}{T_o + 1108} + \frac{7.02 \times 10^{-4} \cdot T_o^2}{(T_o + 1108)^2}$$

$$\Rightarrow V_{out} = mV_{therm}(\mathbf{g} - \mathbf{a})(1 + \ln \frac{T_o}{T}) + 1.16 - \frac{7.02 \times 10^{-4} \cdot T^2}{T + 1108} - \frac{14.04 \times 10^{-4} \cdot T_o T}{T_o + 1108} + \frac{7.02 \times 10^{-4} \cdot T_o^2 \cdot T}{(T_o + 1108)^2}$$

If $\mathbf{g} = 3.2, m = 1, \mathbf{a} = 1, T_o = 25^\circ C$

$$\Rightarrow V_{out}(T) \Big|_{T=25^\circ C} = 1.16 + 2.2(0.0259) - \frac{21.06 \times 10^{-4} (298)^2}{298 + 1108} + \frac{7.02 \times 10^{-4} (298)^2}{(298 + 1108)^2}$$

$$= 1.093V$$

§10-2 Bipolar Bandgap Reference

Widlar bandgap reference

*Feedback element Q_4 is used to force Q_3 on.

* Q_4 also serves as a start-up circuit.

$$*V_{out} = I_2 R_2 + V_{BE3}$$

$$I_2 = I_3 \quad \text{if } I_{B2} = I_{B3}$$


$$I_3 = \frac{V_{BE1} - V_{BE2}}{R_3} = \frac{1}{R_3} mV_{therm} \left[\ln \left(\frac{I_1}{I_2} \right) + \ln \left(\frac{I_{S2}}{I_{S1}} \right) \right]$$



$$V_{out} = V_{BE3} + \left\{ \frac{R_2}{R_3} m \left[\ln \left(\frac{R_2}{R_1} \right) + \ln \left(\frac{I_{S2}}{I_{S1}} \right) \right] \right\} \cdot V_{therm}$$

$$I_1 / I_2 = R_2 / R_1 \quad \text{If } V_{BE1} = V_{BE3}$$

Adjust R_2 / R_3 , R_2 / R_1 and I_{S2} / I_{S1} to give a suitable K

 And Keep $I \cong I_2$ to obtain $I_{B2} \cong I_{B3}$ and $\frac{I_{S3}}{I_{S1}} = \frac{I_3}{I_1}$ to obtain $V_{BE1} = V_{BE3}$.



  


The operating point ④ is the desired operating point
=>Need a start-up circuit.

§10-3 CMOS Real Bandgap Reference (BGR)

§10-3.1 CMOS BGR via BJTs and Resistors


Version 1:

N-well CMOS, positive V_{REF}

 

Version 2:

N-well CMOS, Negative V_{REF}

 

Q_1, Q_2 : Substrate-well-source/drain parasitic vertical BJTs

$$V_{BE} = mV_{therm} \ln \frac{I_E}{I_S}$$

$$V_{REF} = \pm \left\{ V_{BE1} + \frac{R_2}{R_3} V_{therm} \left(\ln \frac{R_2}{R_1} + \ln \frac{I_{s2}}{I_{s1}} \right) + V_{OS} \left[\frac{R_3 + R_2}{R_3} \right] \right\}$$

Typical design values:

$$I_1 = 80 \mu A \quad I_2 = 8 \mu A$$

$$R_2 \approx \frac{0.6V}{8 \mu A} = 75K, \quad R_1 = \frac{R_2}{10} = 7.5K, \quad R_3 = \frac{60mV}{8 \mu A} = 7.5K$$

Large resistance → use well resistors

R1, R2, R3: n+/p+ diffusion resistors
 n+ - poly resistors
 well resistors

Both transistors are in the active region

Error analysis:

1. Error due to base resistances

$$V_{BE1} = V_{therm} \ln \frac{I_1}{I_S} + V_{therm} \ln \frac{1}{1 + \frac{1}{A_1}} + \frac{r_b I_1}{A_1}$$

$$\Delta V_{BE} = V_{therm} \ln A + V_{therm} \ln \frac{I_2}{I_1} + V_{therm} \ln \frac{1 + \frac{1}{A_2}}{1 + \frac{1}{A_1}} + r_b \left(\frac{I_2}{A_2} - \frac{I_1}{A_1} \right)$$

If \hat{a}_1, \hat{a}_2 are not large enough or r_b is too large,

→ ΔV_{BE} due to r_b and is large.

$$V_{REF} = \pm \left\{ V_{BE1} + V_{OS} \left(\frac{R_3 + R_2}{R_3} \right) + \frac{R_2}{R_3} V_{therm} \left(\ln \frac{R_2}{R_1} + \ln \frac{I_{s2}}{I_{s1}} + \ln \frac{1 + \frac{1}{A_2}}{1 + \frac{1}{A_1}} \right) + \frac{R_2}{R_3} r_b \left(\frac{I_2}{A_2} - \frac{I_1}{A_1} \right) \right\}$$

2. Error due to input offset voltage V_{OS}


$$V_{OS} = 10mV, \quad V_{OS} \left(1 + \frac{R_2}{R_3} \right) \approx 10V_{OS} = 100mV$$

TC error due to

$$V_{OS} : \frac{1}{V_{REF}} \frac{d}{dT} V_{REF} = \frac{\left(1 + \frac{R_2}{R_1} \right) V_{OS}}{V_{REF} T_0} = \frac{10 \times 10mV}{1.26V \times 300^\circ K} = 264 ppm / ^\circ C$$

 3. Error due to Bias current variation

$$V_{BE1} = V_{therm} \ln \frac{I_1}{I_{S1}} = V_{Threm} \ln \frac{V_{therm} \ln A}{R I_{S1}} \quad (R_3 = R_1)$$



$$= V_{therm} \ln \frac{V_{therm} \ln A}{R_1(T_O) I_{S1}} + V_{therm} \ln \frac{R_1(T_O)}{R_1(T)} \quad I_1 = I_2$$

$$\text{If } R_1 \text{ is indep. of } T \Rightarrow V_{BE} = V_{therm} \ln \frac{V_{therm} \ln A}{R_1(T_O) I_{S1}}$$

$$\text{If } R_1 \text{ depends on } T \Rightarrow V_{BE} = V_{therm} \ln \frac{V_{therm} \ln A}{R_1(T_O) I_{S1}} + V_{therm} \ln \frac{R_1(T_O)}{R_1(T)}$$

$$V_{BE} = V_{BE}|_{ideal} - V_{therm} \cdot \left(\frac{1}{R} \frac{dR}{dT} \Big|_{T_O} \right) (T - T_O) - V_{therm} \left(\frac{1}{2R} \frac{d^2 R}{dT^2} \Big|_{T_O} \right) (T - T_O)^2 + V_{therm} \left(\frac{1}{2R^2} \frac{dR}{dT} \Big|_{T_O} \right) (T - T_O)^2 - \dots$$

$\swarrow \quad \nwarrow \quad \swarrow \quad \nwarrow$
 $PTAT^2 \quad PTAT \quad PTAT^3 \quad PTAT$
 $\swarrow \quad \nwarrow$
 $PTAT^3 \quad PTAT$

If R is only linearly dependent on T, we still have $PTAT^2$ term

The $PTAT^2$ term can be cancelled via curvature compensations.

4. TC Error due to Base Resistance

$$\Delta V_{BE} = r_b \frac{I_2}{b_2}$$

$$\text{TC error} = \left(1 + \frac{R_2}{R_1} \right) \frac{r_b I_2}{V_{ref} b_2} \left(\frac{1}{r_b} \frac{dr_b}{dT} + \frac{1}{I_2} \frac{dI_2}{dT} - \frac{1}{b_2} \frac{db_2}{dT} \right)$$

Example : $r_b = 2K\Omega$, TC of $r_b = 1000 ppm/^{\circ}C$, $I_2 = 30\mu A$, $b = 150$,


TC of $b = 7000 ppm/^{\circ}C$

$$\Rightarrow \text{TC} = -8.6 ppm/^{\circ}C$$

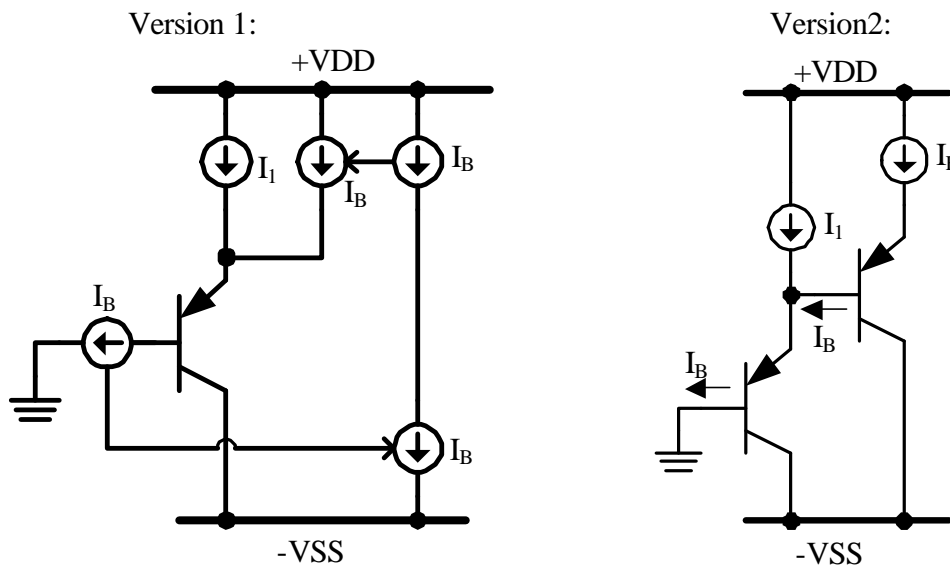5. Error due to base current

Base current cancellation technique


*To compensate for the different between the collector, emitter, or base current




Ref:1.IEEE J .Solid-State Circuits, vol.SC-18, pp634-640, DEC. 1983

2. IEEE J .Solid-State Circuits, vol.SC-19, pp1014-1021, DEC. 1984


The circuit to obtain V_{REF} from a BGR

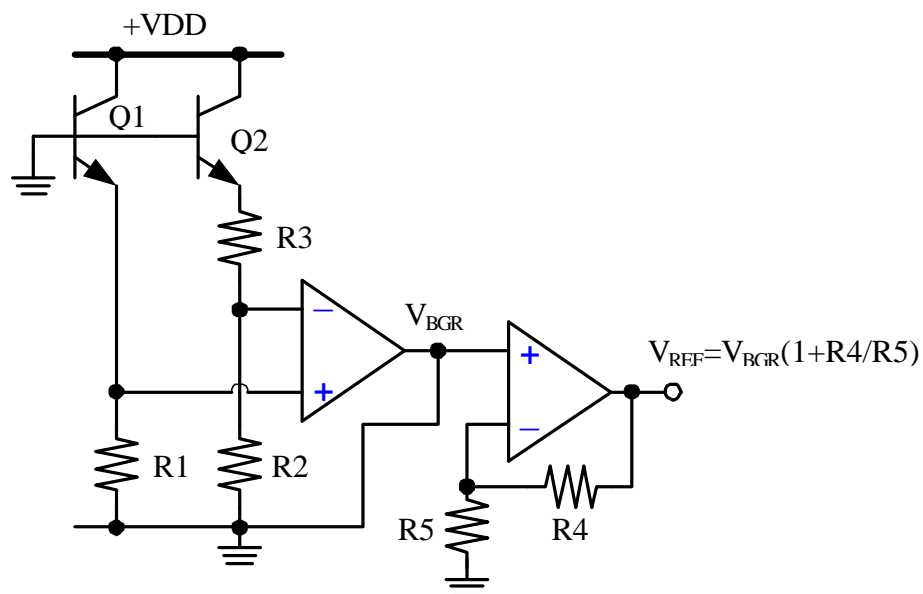


§ 10-3.2 Improved structure

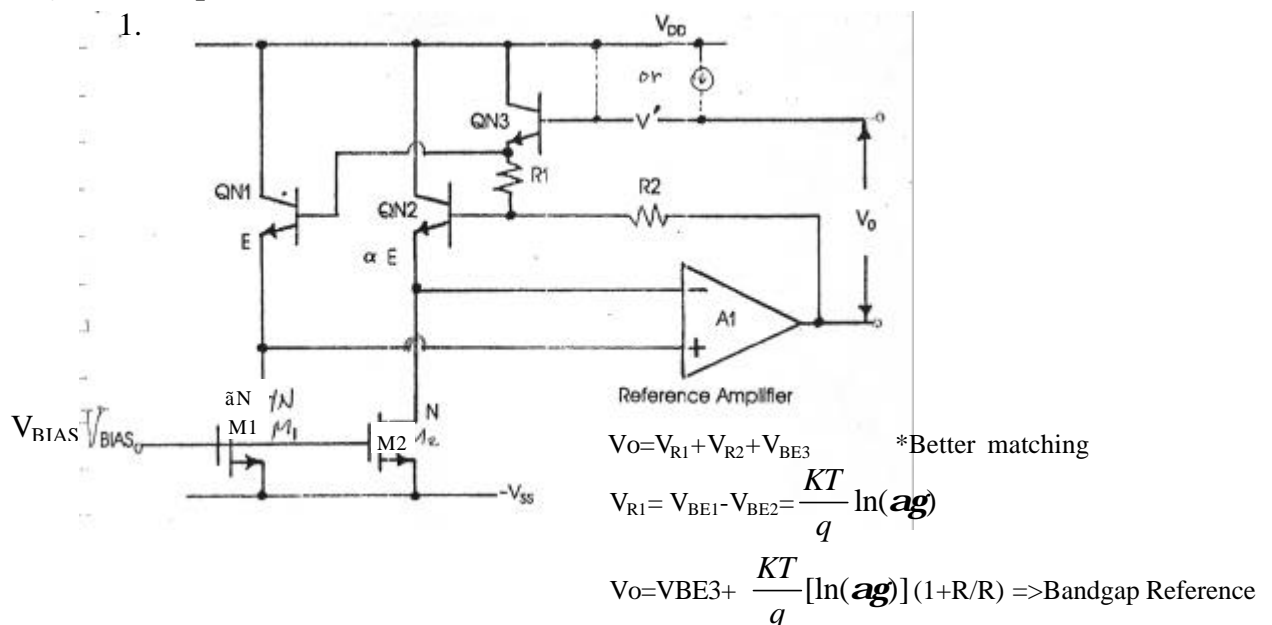



2.

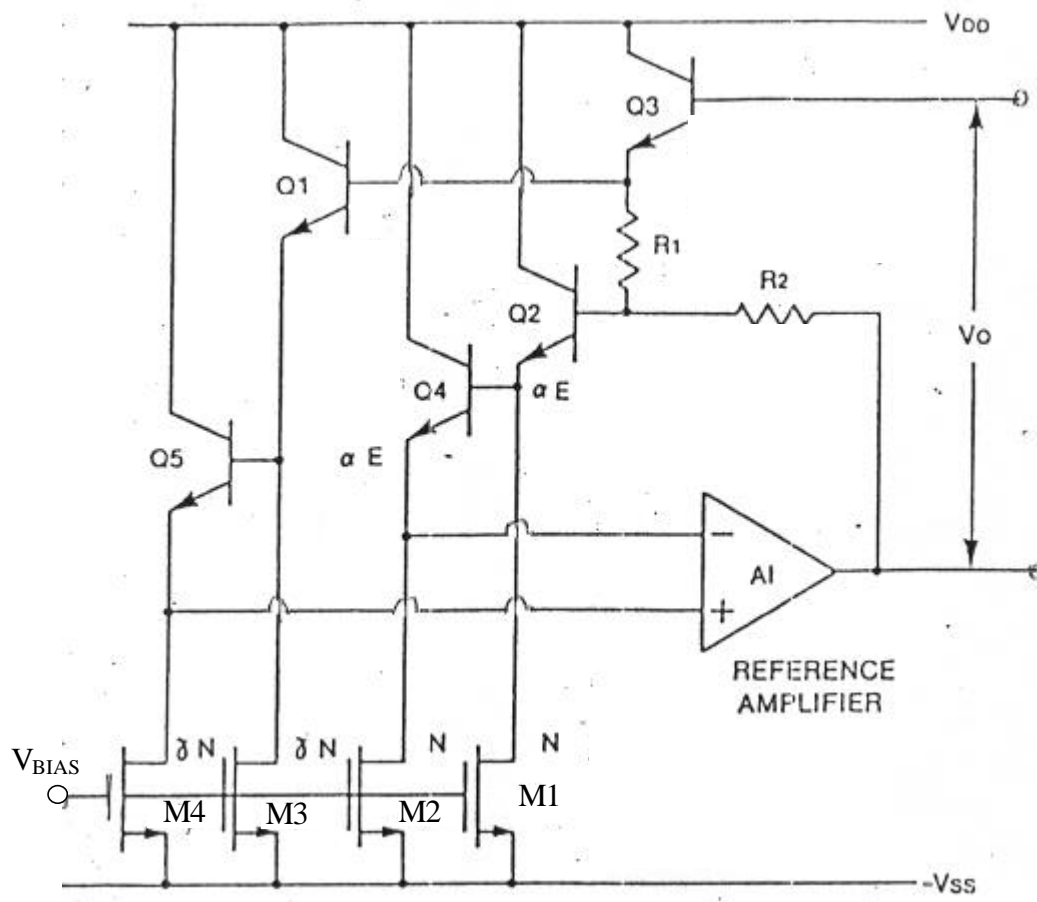


3.

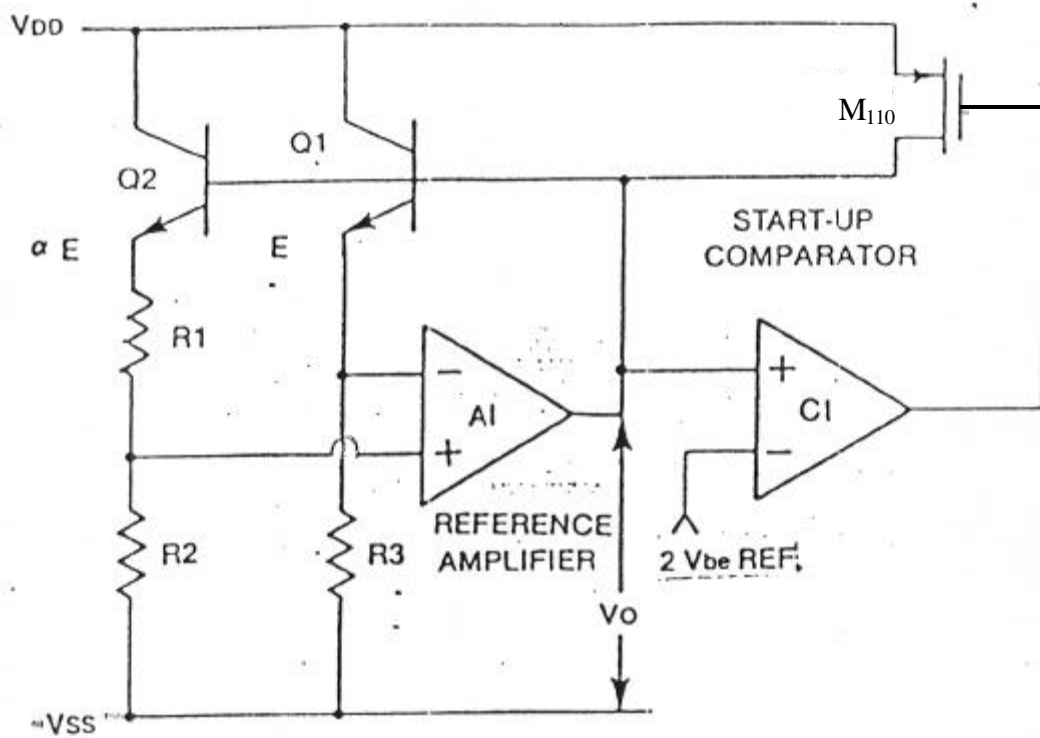

4.

 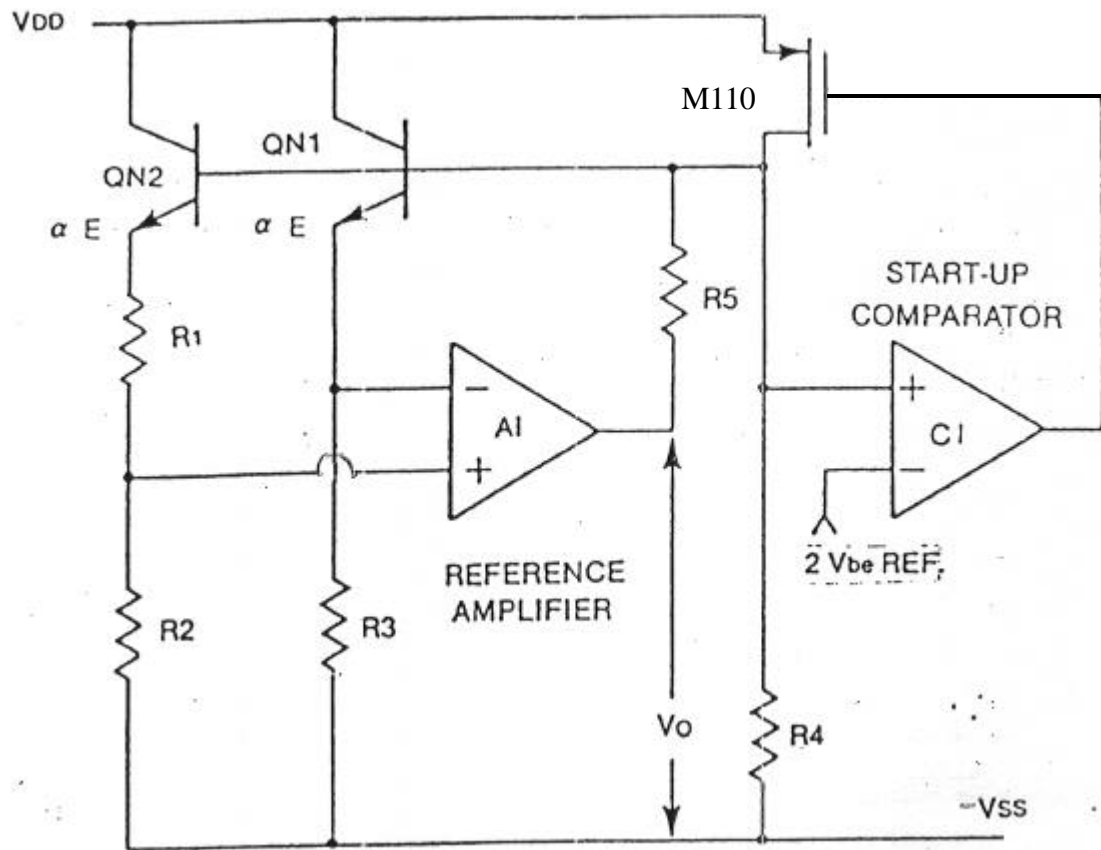

5.Low Power Supply Circuit:

 

*Low driving capability

Power supply limits:


	Low Possible	Voltage T=25°C
Bandgap reference Topology	PMOS Inputs	NMOS Inputs
	$V_{TP} \leq 1.0V$	$V_{TN} \leq 1.0V$
1	1.5v	2.2v
2	1.95v	2.95v
3	1.90v	-
5	2.5v	1.5v

§ 10-3.3 CMOS BGR via lateral Transistor


Ref:IEEE J .Solid-State Circuits, vol. SC-20, pp.1151-1157, DEC. 1985

Structure of a lateral BJT in CMOS:

A.

 


B.

 


Voltage reference via LBJT:

Conceptual circuit :

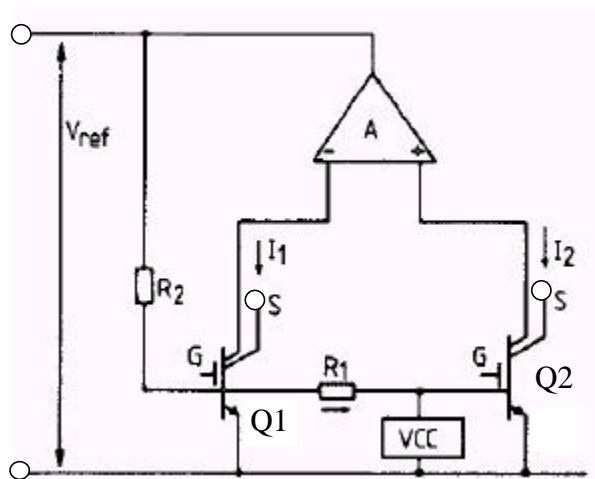

Symbol:

 

A:Current comparator



VCC:Voltage-controlled current source

G:A negative voltage is applied to cause accumulation.

Advantages:(1)The offset of the amplifier A has a negligible effect on V_{REF}

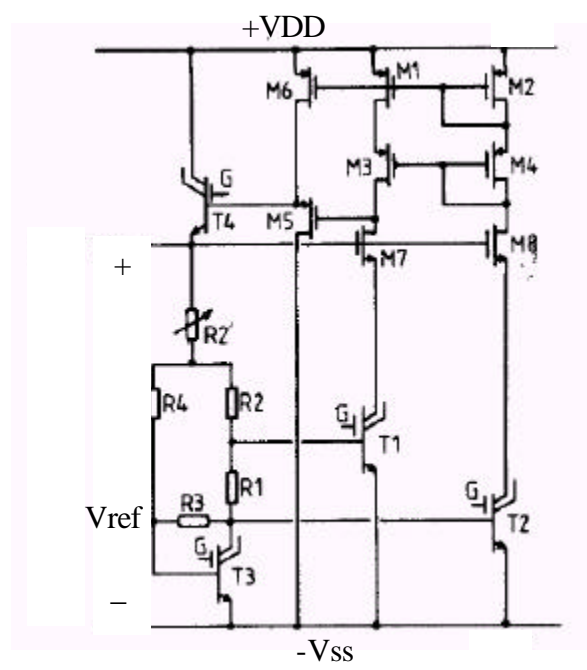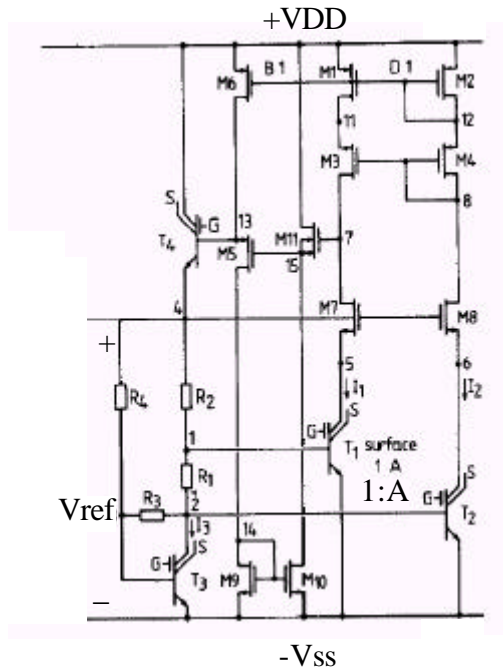(2)Simple structure.

Purpose of VCC : To provide a current path for $I_{R1} \gg I_{B1}, I_{B2}$



- * High supply voltage.
- * Two source followers+one emitter follower
in(A) current amp. \Rightarrow higher current gain

- * Low supply voltage
- * Low current gain in A
- * R2 is trimmable

R4,R3,T3:VCC

R3: To keep T3 from quasi-saturation

R4:To sense the output voltage and transform it into the collector current of T3.

- * All resistor are polysistors
- * Low output impedance.

Measured results:

V_{REF} mean :1.2285V ; standard deviation :150 μ V

Minimal supply voltage 2.2V

Supply current 79 μ A

Noise spectra $316nV/\sqrt{Hz}$ (white) ; $560nV/\sqrt{Hz}(\frac{1}{f},1KHz)$

PSRR(100Hz) 60dB

Load regulation ($\Delta V_{out}/I_{out}$) 3.6 μ V/A


Chip area 0.42 mm²

High PSRR BGR:

* R_1, R_2 may be p-well resistors and PSRR still high.

Experimental results:

V_{REF}	1.2281V (mean)
	350mV (σ)
Minimal Supply	1.7V
Supply Current	20mA
Noise Spectra	$500nV/\sqrt{Hz}$ (white)
	$1mV/\sqrt{Hz} (\frac{1}{f}, 1KHz)$
PSRR(100Hz)	77dB
Load Regulation	4.1mV/A
($\Delta V_{out}/I_{out}$)	
Chip area	0.18 mm ²

 

Curvature-Compensated BGR:


Ref: IEEE J. Solid-State Circuits, vol. sc-20, pp.1283-1285, Dec. 1985

§10-4 High-Precision Curvature-Compensated CMOS Bandgap Voltage References (BVR)

Ref: Int. J. of Analog ICs and Signal Processing, Kluwer, pp. 207-215, 1992

 
1. Type A structure

The circuit structure of the proposed BVR (Type A)




$$V_{out} = V_{BE3} + I_3 R_2 = V_{BE3} + r_3 \frac{R_2}{R_1} \left(\frac{kT}{q} \ln A^* + \Delta V_{sg} \right)$$

2. Type \bar{A} structure

 


3. Type B structure

 


4. Type C structure


The cascode structure of BVR (Type C):

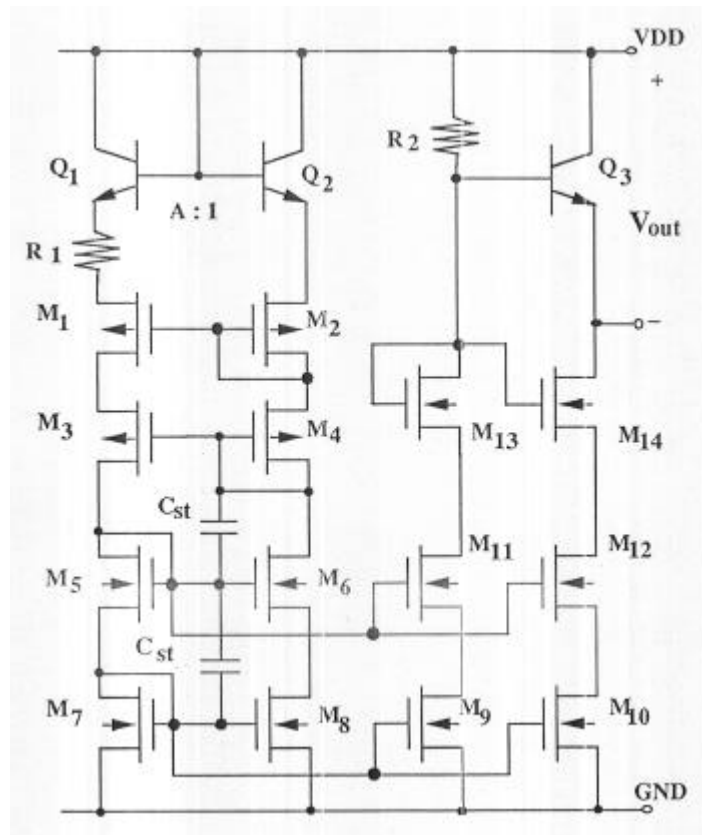

 
The variation of V_{sg} versus temperature



 
The simulated output voltages versus temperature in Type A and Type A \bar{B} VR



 
The variation of ΔV_{sg} versus MOS channel length in Type A BVR



 The Spice simulated output voltages versus temperature in Type C BVR



 The measured output voltages versus temperature in the fabricated cascaded-structure BVR(Type C)[3.5 μ m CMOS technology , $R_1=1K\Omega$ (external), $R_2=25.9K\Omega$ (external)]



- * Average temperature drift
 $5.5 \text{ ppm/}^{\circ}\text{C}$ $-60^{\circ}\text{C} \sim +150^{\circ}\text{C}$
 $5\text{V} \sim 15\text{V}$
- * At 25°C , average voltage drift $25 \mu\text{V/V}$
 $V_{\text{out}} = 1.1963\text{V} \sim 1.1965\text{V}$
 $5\text{V} \sim 15\text{V}$
- * 2 mil^2 , 0.8 mW at 5V

§10-5 CMOS Bandgap Reference with Sub-1-V Operation

Ref.: IEEE JSSC, vol.34, pp.670~674, May 1999

Concept: * Conventional BGR $V_{\text{ref}} = 1.25\text{V}$


Can't be operated below 1V supply.


* The built-in voltage V_f of the diode \rightarrow the current I_{2b}

The thermal voltage V_{therm} \rightarrow the current I_{2a}


$$(I_{2a} + I_{2b})R \rightarrow V_{\text{ref}} < 1\text{V}$$

1. Schematic of the proposed BGR

 

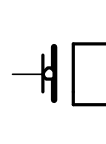 Native NMOS $V_{\text{THI}} = -0.2\text{V}$
 NMOS $V_{\text{THN}} = +0.7\text{V}$
 PMOS $V_{\text{THP}} = -1.0\text{V}$

 *The diode is realized by the parasitic $P^+/n\text{-well}/P\text{-substrate}$ BJT as



* C_1 and C_2 are used to stabilize the circuit.

*The control signal PONRST is used to initialize the BGR circuit when the power is turned on.

* $R_1 = R_2$

$V_a = V_b$

$I_1 = I_2 = I_3$ and $I_{1a} = I_{2a}$, $I_{1b} = I_{2b}$

$dV_f = V_{f1} - V_{f2} = V_{therm} \ln(N)$, $N = 100$


$$I_{2a} = \frac{dV_f}{R_3} \propto V_{therm}$$

$$I_{2b} = \frac{V_{f1}}{R_2} \propto V_f$$

$$I_3 = I_2 = I_{2a} + I_{2b}$$

$$V_{ref} = R_4 I_3 = \frac{R_4}{R_2} V_{f1} + \frac{R_4}{R_3} dV_f$$

2. Simulated V_{ref} characteristics

 

* $V_{ref} = 1.25V$ conventional BGR

* $V_{ref} = 0.84V$ proposed BGR


3. Minimum V_{DD}

$$\min V_1 \cong V_s \cong V_b - V_{THI} \cong V_f + |V_{THI}| \cong V_{DD} + V_{THP} = \min V_{DD} - |V_{THP}|$$

$$\Rightarrow \min V_{DD} = V_f + |V_{THI}| + |V_{THP}| \cong 0.8 \sim 1.0V$$

$$0.54 \quad -0.2 \quad -0.3$$

4. Measured results:

 

* $TC \cong 60 ppm/^{\circ}C$ $27^{\circ} \sim 125^{\circ}C$

Voltage drift (average) $\cong 600mV/V$ $2.2V \sim 4V$