

## Chapter 8 Advanced Design Techniques and Recent Design Examples of CMOS OP AMPs

### §8-1 Advanced Design Techniques of CMOS OP AMPs

#### §8-1.1 Improved PSRR and frequency compensation

$$\text{P.6-26} \quad \frac{\partial V_{out}}{\partial V_{ss}} \approx \frac{C_{gs}}{C_I} \left[ \frac{\partial I_o}{\partial V_{ss}} \frac{1}{2g_{m1}} + \frac{\partial V_{GS1}}{V_{ss}} \right] + \frac{C_{gd}}{C_I} \frac{1}{2g_{m3}} \frac{\partial I_o}{\partial V_{ss}}$$

$$\frac{\partial V_{out}}{\partial V_{DD}} \approx \frac{C_{gd}}{C_I} \left[ 1 - \frac{\partial I_o}{\partial V_{DD}} \frac{1}{2g_{m3}} \right] + \frac{C_{gs}}{C_I} \frac{1}{2g_{m1}} \frac{\partial I_o}{\partial V_{DD}}$$


Where  $I_o$  represents the input stage bias current.

If  $I_o$  is independent of  $V_{ss}$  and  $V_{DD}$

and the input devices have no body effect.

$$\implies \frac{\partial V_{out}}{\partial V_{ss}} \rightarrow 0 \quad \frac{\partial V_{out}}{\partial V_{DD}} \rightarrow -\frac{C_{gd}}{C_I}$$

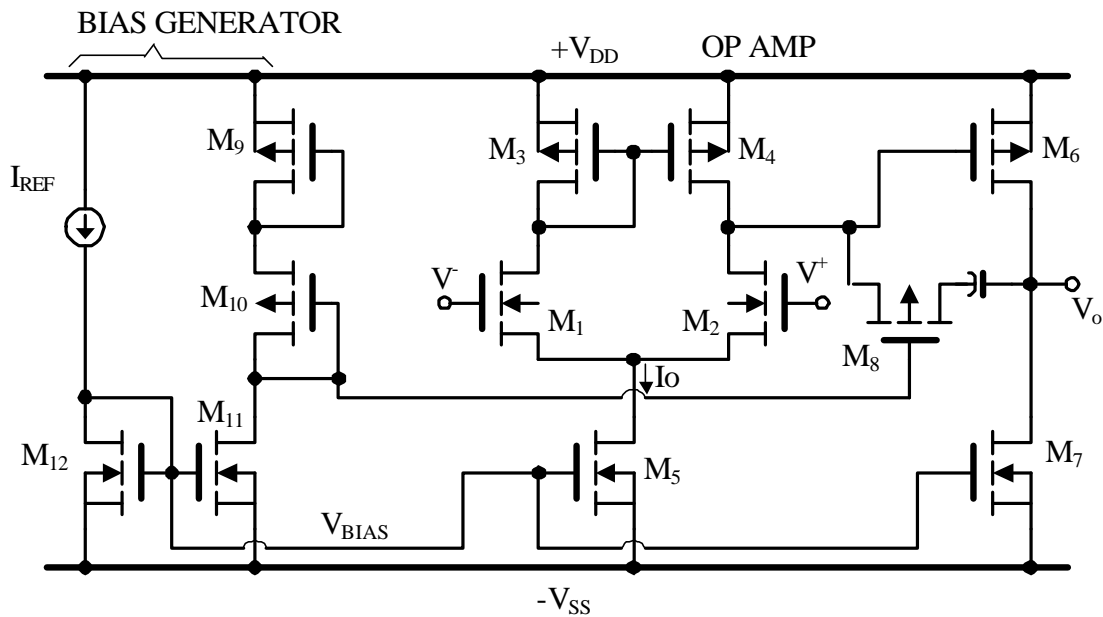Ref.: IEEE JSSC, vol. SC-15, pp.929-938, Dec. 1980




\*  $I_{REF}$  is generated by using the power supply independent current source.

\*  $V_{BIAS}$  is nearly independent of  $V_{DD}$  and  $V_{ss}$ .

\* It is better to use separate p-wells for  $M_1$  and  $M_2$  to avoid the body effect.

\*Tracking RC compensation

Conceptual circuits :

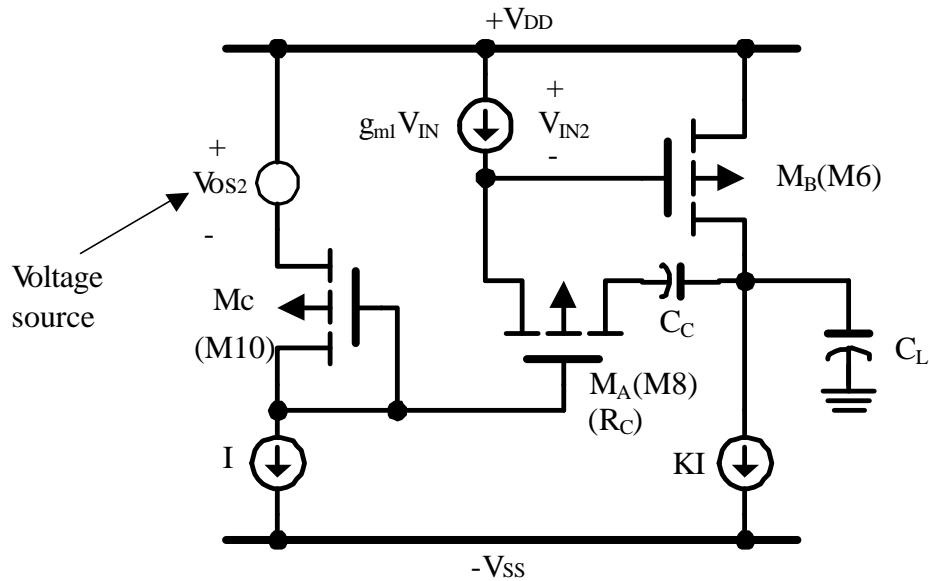

In the quiescent case ,  $V_{in2}=V_{os2}$

$$\text{If } (W/L)_A \approx [(W/L)_B \cdot (W/L)_C \cdot K]^{1/2} \frac{C_c}{C_c + C_L}$$

$$\Rightarrow R_{dsA} \approx \frac{C_c + C_L}{g_{m2} C_c} \approx R_c$$

The requires  $R_c$  is  $R_c = 1/g_{m2} [1 + (C_d + C_L)/C_c] \approx 1/g_{m2} [(C_c + C_L)/C_c]$

Thus LHP zero=LHP pole P2

and P3 becomes the second pole.

The stability considerations,

$$P_3 \geq A_{do} P_1$$


$$\text{or } C_c \geq \sqrt{\frac{g_{m1}}{g_{m2}}} c_1 c_L$$

allows a smaller  $g_{m2}$  and larger  $C_L$

\*  $R_{dsA} \approx R_c$  indep of temperature, process , and supply variations.

=>Tracking design to make sure that  $z=P_2$

=>No pole-zero doublet problem!

 


- \* M17,  $C_c$  : Tracking RC compensation.
- \* M9, M11: Sharing the separate n-well.
- \*  $V_{BIAS}$  is not strictly independent of  $V_{DD}$  and  $V_{SS}$ .

### §8-1.2 Improved frequency compensation technique.

Ref.: IEEE JSSC ,vol.sc-18, pp 629-633, Dec.1983

#### Grounded gate cascode compensation

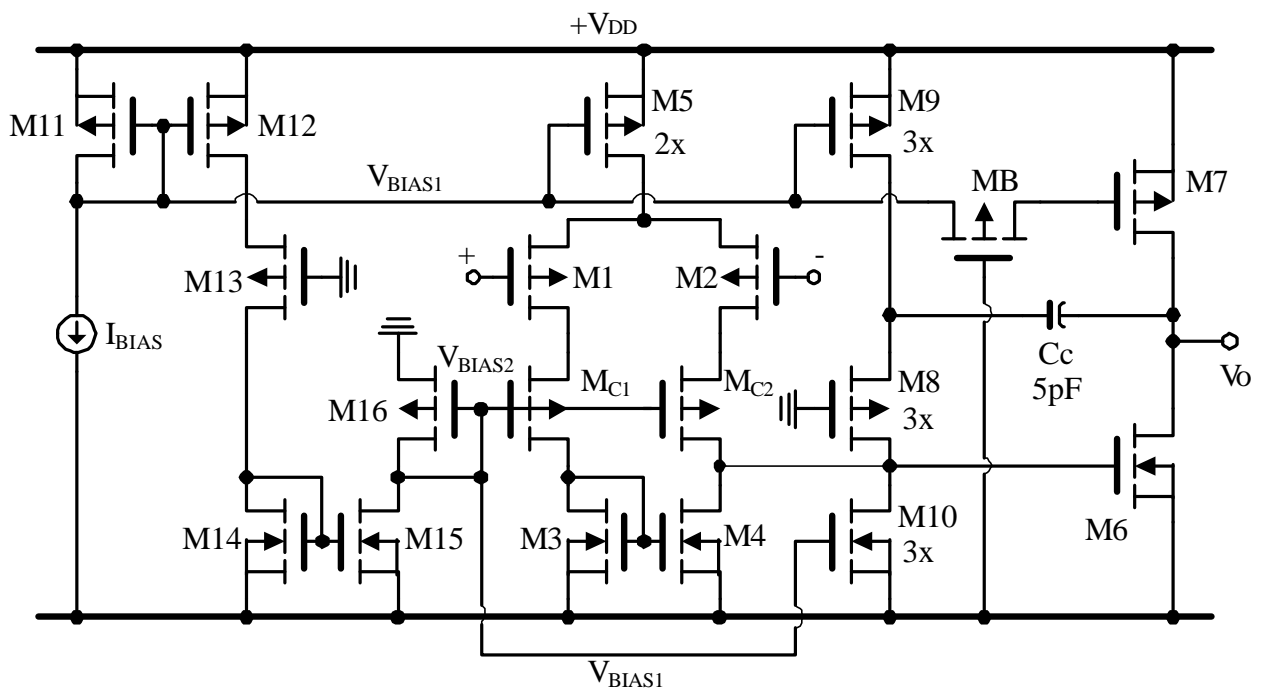


MB,Cgs7:low pass filter for high frequency noises.

M8,M9,M10:new compensation circuit.

M11~M16:Bias generator.

Conceptual circuits:

 

Net current in  $C_c$  ( $C_c \frac{d}{dt} V_o$ ) enters the second stage.


The input voltage  $V_i$  can't reach the node (A)

- ➔ \* Better PSRR ( no low-freq. zero ), especially PSRR
- \* Allow larger capacitive loads.
- \* Slight increase in complexity , random offset and noise.

### § 8-1.3 Improved cascode structure

 1. To improve gain:

Ref: IEEE JSSC , vol. SC-17, pp. 969-982, Dec. 1982




- \* Substantial reduction in input-stage common-mode range.
- \* Improved wilson current source is used as the load to improve the balance of the first stage.
 
## 2. Single-stage push-pull class AB CMOS OP AMP

Ref: IEEE JSSC , vol.sc-17, pp.969-982, Dec. 1982

- \* Inverting mode only. (+ grounded)
- \* Capable of high current driving and high voltage gain.
- \* Not a differential-amplifier-based OP AMP.




## 3. Cascoded CMOS OP AMP with high ac PSRR

Ref: (1) IEEE JSSC , vol. SC-19, pp.55-61, Feb. 1984

(2) IEEE JSSC , vol SC-19, pp. 919-925, Dec. 1984

### 1) Original version

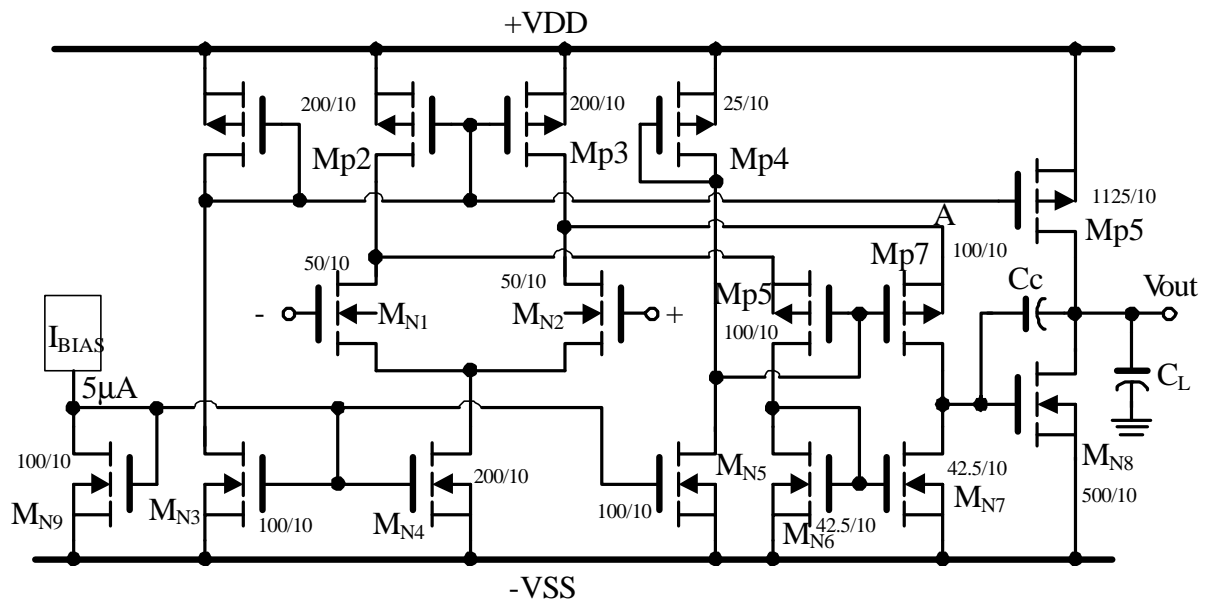

### Characteristics:

$$V_{DD}=V_{SS}=2.5V$$

Input offset voltage

5mV

Supply current

100μA

Output voltage range

$-V_{SS} \sim V_{DD}$

Input common mode range

$-V_{SS}+1.47V \sim V_{DD}$

CMRR @ 1KHz

99dB

Unity-gain frequency


1.0MHz

Slew rate

1.8 V/μsec

- \* Better input common-mode range.
- \*  $V_{ic} \rightarrow V_{DSN4} \rightarrow I_{DSN4} \rightarrow V_A \rightarrow M_{N8}$  is turned on  $\rightarrow V_{out} - V_{SS}$  voltage spike at  $V_{out}$ .
- \* The possible spike in the settling period.

## 2) Improved version

 


- \*  $M_{12}, M_{13}$  and  $M_{14}$  : Let the drain bias currents of  $M_{10}$  and  $M_{11}$  follow the change of  $I_{D7}$  under positive input common mode voltage.  
 $\Rightarrow$  No voltage spike at  $V_{out}$

Also serves as CMFB

- \* Better PSRR and input common-mode range.
- \*  $C_c$  is decoupled from the gate of the driver  $M_8$ .
 
## 4. Simple cascoded CMOS OP AMP


Ref.: IEEE JSSC, vol. SC-19, pp. 919~925, Dec. 1984



- \* Good PSRR
- \* Reduced input common range.  
 $\Rightarrow$  restrict its applications to those which use a virtual ground.

## 5. Single-stage cascode OTA

Ref.: IEEE JSSC , vol. SC-20 , pp.657~665 , June 1985

  $T_9, T_{10}$  : Cascode structure

\* Output conductance  $\downarrow$  without any noise penalty and with only a very small reduction of phase margin.

$\Rightarrow$  Gain  $\uparrow$  no any compensation is necessary.

\* Maximum output swing  $\downarrow$

## § 8-2 Advanced Design Techniques on High-frequency Non-differential-type CMOS OP AMPs

### 1. Single-ended push-pull CMOS OP AMP

\*Current-gain-based design

 


TABLE I

Parameter	Measured Value
DC-Open Circuit Gain	69dB
Unity Gain Bandwidth	70MHz
Phase Margin	40°
Slew Rate	200V / <b>msec</b>
PSRR (DC <sup>+</sup> )	68dB
PSRR (DC <sup>-</sup> )	66dB
Input Offset Voltage	10mV
CMRR (DC)	62dB
Output Voltage Swing	1.5V <sub>P</sub>
Output Resistance	3 MΩ
Input Referred Noise (@1KHz)	0.54 <b>nV</b> / $\sqrt{Hz}$
DC-Power Dissipation	1.1mWatt

$V_{DD} = +3V$  ;  $V_{CC} = -3V$  ;  $I_{B1} = 50 \text{ **nA**}$  ; CL=1pF

TABLE II

Bias Current	Unity-Gain Bandwidth	DC-Open Circuit Voltage Gain	DC-Power Dissipation
25 <b>nA</b>	50MHz	70dB	0.55mW
50 <b>nA</b>	70MHz	69dB	1.1mW
100 <b>nA</b>	100MHz	66dB	2.2mW



$$V_{DD} = +3V ; V_{CC} = -3V ; CL=1pF$$


## 2. Low output resistance CMOS OP AMP

\*  $C_L$  is a compensation capacitor

\* For low-resistance load

\* Smaller maximum output voltage swing.

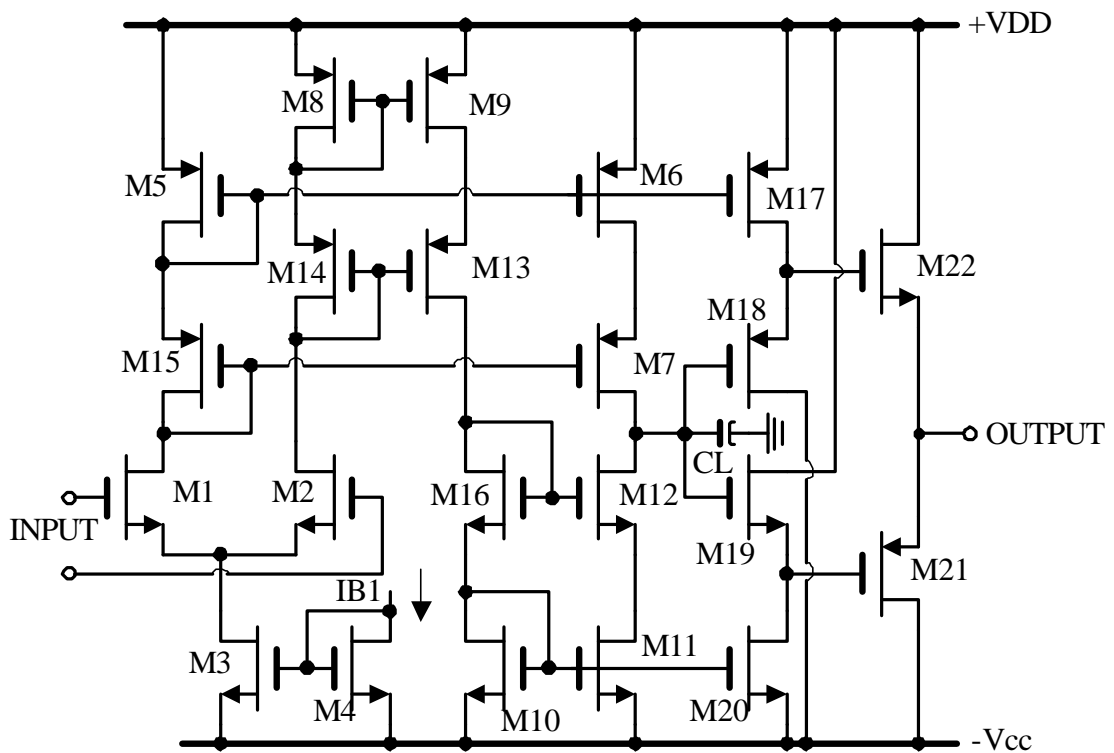
\*  $I_{B1} = 50 \mu A$ ,  $C_L = 1 pF$ ,  $f_u = 60 MHz$




## § 8-3 Advanced Design Techniques on High-drive MOS Power or Buffer OP AMPs

### § 8-3.1 Efficient Output Stages.

 A. CMOS output stage using a bipolar emitter follower and a low-threshold PMOS source follower.




 B. Complementary class B output stage using compound devices with common-source output MOS.




### § 8-3.2 High-drive power or buffer CMOS OP AMPs
 
## 1. Large swing CMOS power amplifier (National Semiconductor)



- \* Noninverting unity gain amplifier

 

$$V_{in} \cong V_{out}$$

$M_6$  provides the negative feedback

- \*  $A_1, M_6$  and  $A_2, M_{6A}$  form a class AB push-pull output stage.
- \* Full swing from  $+V_{DD}$  to  $-V_{SS}$
- \*  $M_9, M_{10}, M_{11}$ , and  $M_{12}$  form a current feedback to stabilize the bias current of  $M_6$  and  $M_{6A}$ .


Offset in  $A_1$ , e.g.  $V_{inA1}^- \uparrow \Rightarrow V_{outA1} \downarrow \Rightarrow I_{DM6} \uparrow$  and  $I_{DM9} \uparrow \Rightarrow I_{DM11} \uparrow$

and  $I_{DM12} \uparrow \Rightarrow V_{GSM8A} \uparrow$  and  $V_{inA2}^+ \downarrow \Rightarrow V_{out} \uparrow$ , i.e.

$V_{inA1}^+ \uparrow \Rightarrow V_{out} \downarrow \Rightarrow V_{inA1}^- \downarrow$  (virtual short between + and -)  $\Rightarrow V_{inA2}^- \downarrow$

through  $M_8 \Rightarrow$  All the bias voltage and current are restored to the normal values and the offset is absorbed by  $M_{8A}$ .

 Since the current feedback is not unity gain, some current variation in transistors  $M_6$  and  $M_{6A}$  still exists.



Large positive common mode range allows  $M_6$  to source large amount of current to the load. (because  $V_{in} \cong V_{out}$ )


The maximum  $V_{GS6}$  which  $M_1$  and  $M_2$  still in the saturation region is

$$V_{GS6 \max} = -(V_{DD} - (V_{IN} - V_{GS1} + V_{DSAT1})) = -(V_{CC} - V_{IN} + V_{TH1})$$

$$\Rightarrow V_{TH1} \uparrow \Rightarrow V_{GS6 \max} \uparrow \Rightarrow I_{DM6} \uparrow$$

(1). Threshold implant to increase  $V_{TH1}$

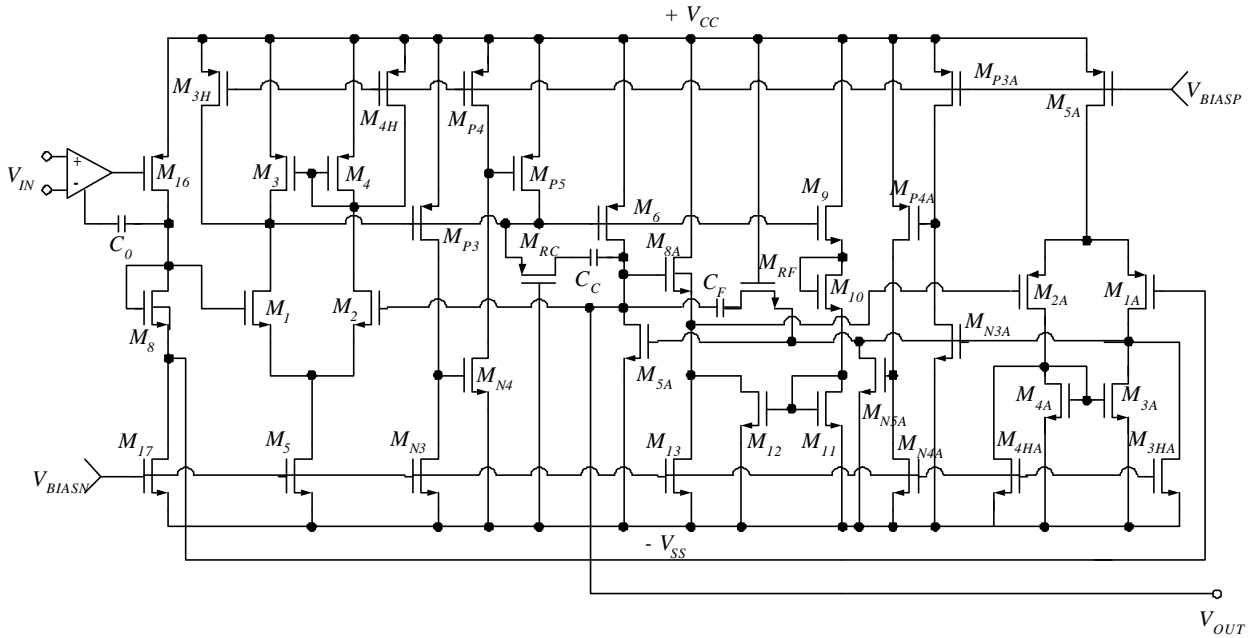(2). Negative substrate bias  $-V_{SS}$  to increase  $V_{TH1}$



- \* The input stage is not shown in the diagram.
- \*  $M_{16}, M_8, M_{17}$  form the second stage with  $C_D$  the Miller compensation capacitor.
- \* If  $V_{out} \rightarrow -V_{SS}, V_{DSM5} \rightarrow 0$  and  $I_{DSM5} \rightarrow 0$ .

$$\Rightarrow M_1, M_2, M_3 \text{ and } M_4 \text{ are off}$$

$$\Rightarrow M_{3H} \text{ and } M_{4H} \text{ are still on to keep } V_{GS6} \cong 0V.$$

Otherwise,  $M_6$  will be turned on.

Similarly,  $M_{3HA}$  and  $M_{4HA}$  turn off  $M_{6A}$  in the positive voltage swing

- \*  $M_{P3}, M_{N3}, M_{N4}, M_{P4}$  and  $M_{P5}$  are output short-circuit protection circuitry.

Normally,  $M_{P5}$  is off.

When  $I_{DM6} \cong 60mA$ ,  $I_{DMP3} \uparrow \Rightarrow I_{DMN4} \uparrow \Rightarrow V_{GSMP5} \uparrow$ .

$\Rightarrow I_{DM6}$  is limited to approximately 60 mA.

Table I  
POWER AMPLIFIER PREFORMANCE

Parameter	Simulation	Measured Results
Power dissipation( $\pm 5V$ )	7.0mW	5.0mW
$A_{vol}$	82dB	83dB
$F_u$	500KHz	420KHz
$V_{offset}$	0.4mV	1mV
PSRR+(dc)	85dB	86dB
(1KHz)	81dB	80dB
PSRR-(dc)	104dB	106dB
(1KHz)	98dB	98dB
THD $V_{IN}=3.3V_p$ $R_L=300\Omega$	0.03%	0.13%(1KHz)
$C_L=1000$ pF	0.08%	0.32%(4KHz)
$V_{IN}=4.0V_p$ $R_L=15$ k $\Omega$	0.05%	0.13%(1KHz)
$C_L=200$ pF	0.16%	0.20%(4KHz)
$T_{settling}$ (0.1%)	3.0us	<5.0us
Slew rate	0.8V/us	0.6V/us
1/f noise at 1KHz	N/A	130nV/Hz
Broad-band noise	N/A	49nV/Hz
Die area		1500mils <sup>2</sup>

TABLE II  
COMPONENT SIZES (  $\mu m$  nF )


MI6	184/9	M8A	481/6
MI7	66/12	M13	66/12
M8	184/6	M9	27/6
M1,M2	36/10	M10	6/22
M3,M4	194/6	M11	14/6
M3H,M4H	16/12	M12	140/6
M5	145/12	MP3	8/6
M6	2647/6	MN3	244/6
MRC	48/10	MP4	43/12
CC	11.0	MN4	12/6
M1A,M2A	88/12	MP5	6/6
M3A,M4A	196/6	MN3A	6/6
M3HA,M4HA	10/12	MP3A	337/6
M5A	229/12	MN4A	24/12
M6A	2420/6	MP4A	20/12
MRF	25/12	MN5A	6/6
CF	10.0		

Maximum loads :  $300\Omega$  and  $1000\text{pF}$  to ground.

Ref.:IEEE JSSC , vol.SC-18 , pp.624-629 , Dec.1983

## 2. High-performance CMOS power amplifier (Siemens AG)

(1). New input stage : 3 gain stages.

 

\*  $C_c$  is connected to the source of  $M_9$  to improve PSRR

\* Three poles and one zero :

$$Z = \frac{-2g_{m6}g_{m8}g_{m13}}{C_c g_{m6}g_{m13} + C_1 g_{m8}g_{m12}} \quad \text{LHP.}$$

$$P_1 \cong \frac{-g_{ds10}g_o}{g_{m13}C_c}$$

$$P_2, P_3 \cong \frac{-g_{m8}(C_c + C_o)}{2C_o C_c} \pm j \left[ \frac{g_{m8}g_{m13}}{C_o C_1} - \left( \frac{g_{m8}(C_o + C_c)}{2C_o C_c} \right)^2 \right]^{1/2}$$

where  $g_o \equiv g_{ds12} + g_{ds13}$


$$C_o = C_L + C_{db12} + C_{db13}$$

$$C_1 = C_{gs13} + C_{db11} + C_{db9} + C_{gd9}$$

Design guidelines for stability :

$$g_{m8} \text{ large , } g_{m13} \gg g_{m6}$$

(2). Output stage

 


Class AB source follower

\* One pole and one zero at high frequencies.

\* Not full swing


- \* The quiescent current in  $M_1$  and  $M_2$  will vary widely with variations in  $V_{os1}$  and  $V_{os2}$ .
- \* Suitable common-mode range of the two amplifiers  $A_1$  and  $A_2$  are required.
- \* Large phase shift at high frequencies due to  $A_1$  and  $A_2 \Rightarrow$  stability problem.

 - \*  $M_1$  and  $M_2$  are turned off in the quiescent state by building a small offset voltage into  $A_1$  and  $A_2 \Rightarrow M_3$ - $M_6$  control the output quiescent currents.
- \*  $M_2$  ( $M_1$ ) sinks (sources) approximately 95% of the required currents.
- \*  $M_1$  and  $M_2$  provide a high-frequency feed-forward path.



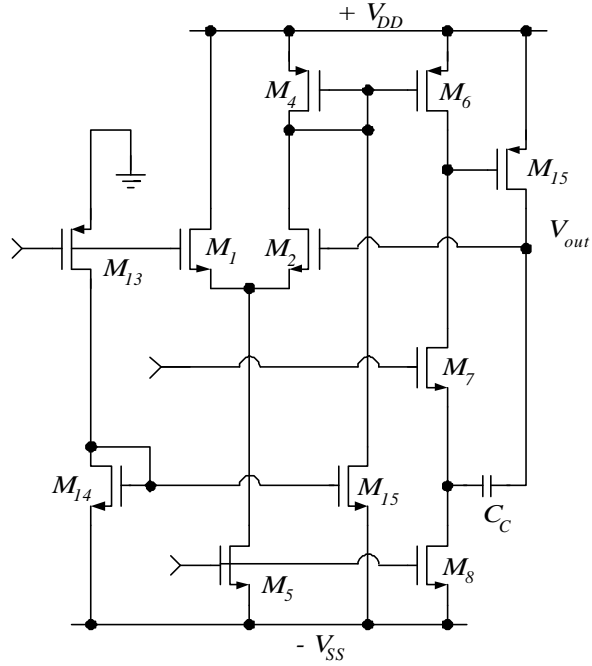Still has a smaller swing limited by  $M_5, M_6$ .





- \*  $M_{13}$ ,  $M_{14}$  and  $M_{15}$  form a circuit to turn off  $M_{15}$  when  $V_{out} < V_{TP13}$  (negative)
- \*  $C_c$  : compensation.
- \* Three poles and one zeros.

$$Z_1 \approx -\frac{g_{m7} + g_{mbs7}}{C_c + C_{gs7}}$$

$$P_1 \approx \frac{-g_L}{C_L + C_c \frac{g_{m15}}{g_{ds6}}}$$

$$P_2, P_3 \approx -\frac{g_{m7}(C_c + C_L)}{2C_c C_L} \pm j \left[ \frac{g_{m7} g_{ds6} (C_L + C_c \frac{g_{m15}}{g_{ds6}})}{C_c C_L C_1} - \left( \frac{g_{m7}(C_c + C_L)}{2C_c C_L} \right)^2 \right]^{\frac{1}{2}} \quad \text{where}$$

$$C_1 = C_{gs9} + C_{db6} + C_{db7} + C_{gd7}$$

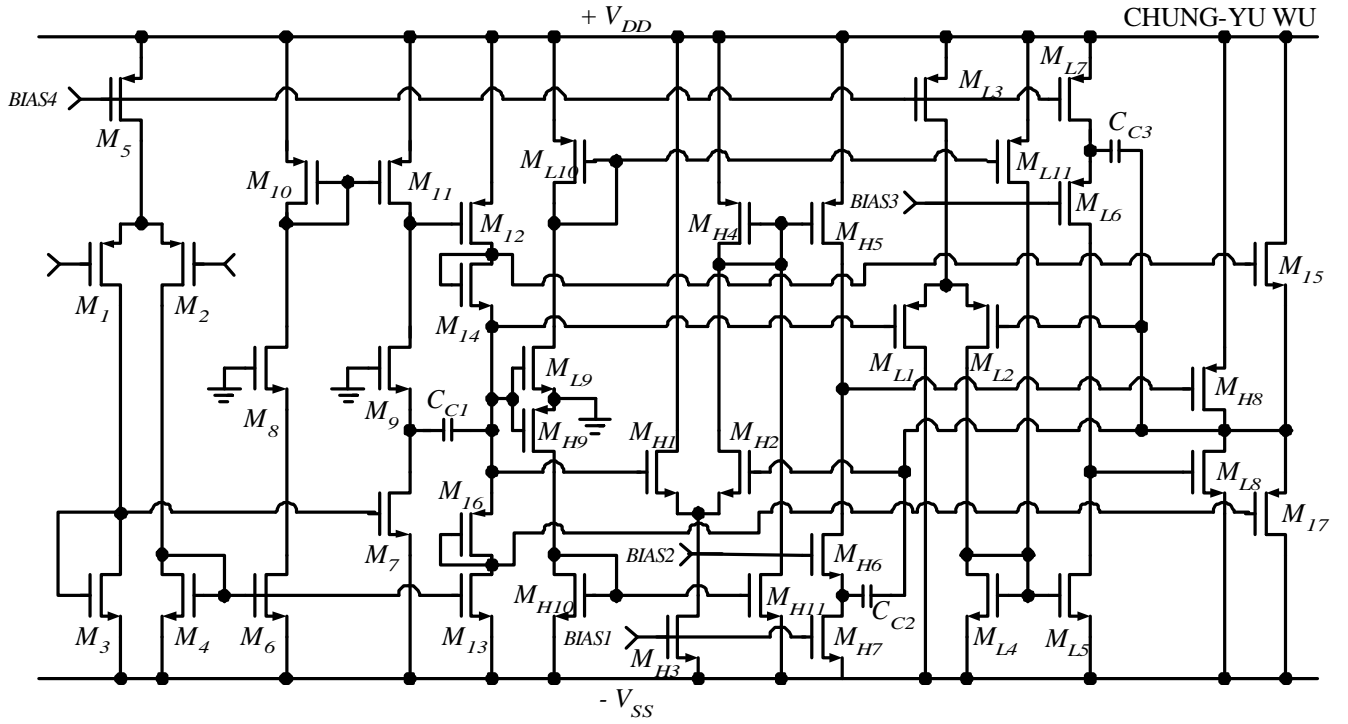


TABLE I Component Sizes

M1	400/15	MH1	48/10	ML1	48/6
M2	400/15	MH2	50/10	ML2	50/6
M3	150/10	MH3	500/15	ML3	300/15
M4	150/10	MH4	300/6	ML4	150/5
M5	100/15	MH5	300/6	ML5	100/5
M6	150/10	MH6	200/5	ML6	300/6
M7	150/10	MH7	250/15	ML7	100/15
M8	300/5	MH8	700/6	ML8	400/5
M9	300/5	MH9	15/6	ML9	5/5
M10	300/10	MH10	10/15	ML10	5/15
M11	300/10	MH11	20/15	ML11	15/15
M12	1200/10	Cc1	20pf		
M13	600/10	Cc2	4pf		
M14	200/5	Cc3	4pf		
M15	200/5				
M16	600/6				
M17	600/6				

TABLE II  
POWER AMPLIFIER PERFORMANCE SUMMARY  
(First Revision)


parameter	Measured Results
Supplies	$\pm 5V$
Open-Loop Gain	93dB
Bandwidth	1.2MHz
Power Dissipation $\bar{x}$	12.7 mW
$\phi$	1.76mW
Output Swing ( $R_L=200\Omega$ )	$\pm 3.1V$
PSRR+ at DC	93dB
1 kHz	91dB
10 kHz	76dB
100 kHz	60dB
PSRR- at DC	102dB
1 kHz	89dB
10 kHz	75dB
100 kHz	53dB
Slew Rate	1.5V/ $\mu$ s
Input Common Mode Range	+3.3V
	-5.5V
Die Area (51 m CMOS)	1000 mils <sup>2</sup>
Harmonic Distortion (3 kHz) $V_{in}=3 V_p$ $R_L=200\Omega$	
HD2	-73dB
HD3	-78dB

Maximum Loads : 1000pF and 200 $\Omega$ to ground.

Ref.: IEEE JSSC , vol. sc-20, pp.1200-1205, Dec. 1985.

### 3. Efficient Unity-gain CMOS buffer for driving large $C_L$ .

High-drive OTA buffer

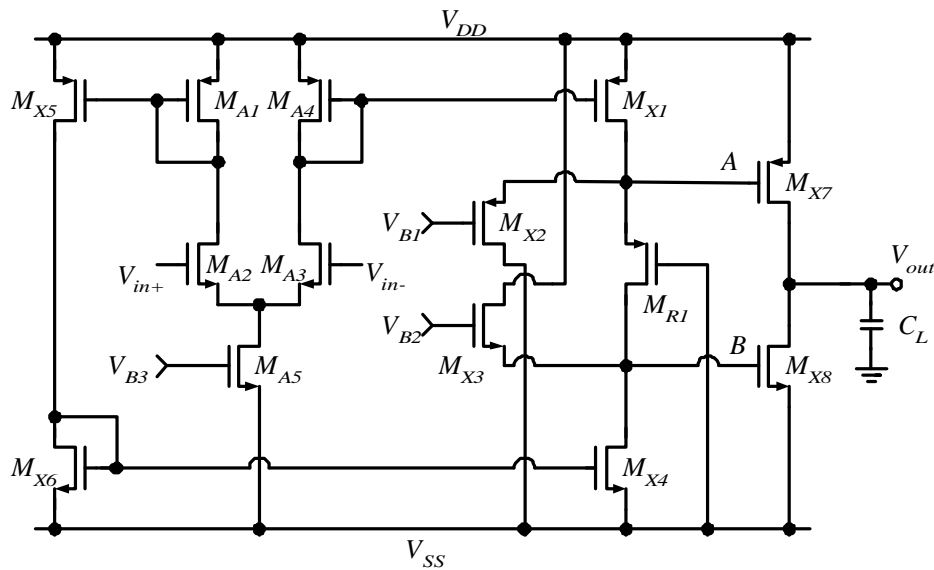

Bias stage

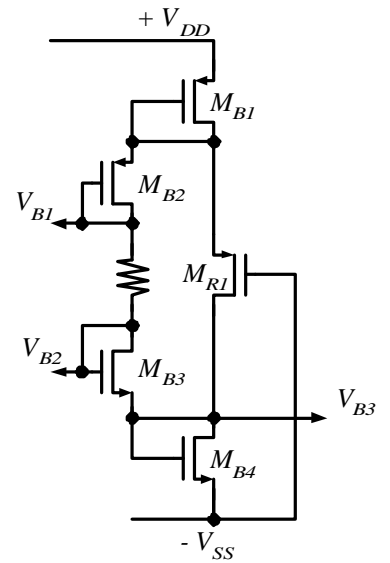


TABLE I  
TRANSISTORS' DIMENSIONS

TRANSISTOR	W ( $\mu\text{m}$ )	L ( $\mu\text{m}$ )
MX1, MX5	225	3
MX2	75	3
MX3	30	3
MX4, MX6	90	3
MR1	6	21
MA1, MA4	45	3
MA2, MA3	450	3
MA5	36	3
MX7	600	3
MX8	240	3

\*  $M_{R1}$  has a low W/L and is operated in the linear region

$\Rightarrow$  like a linear resistor.

\*  $M_{X2}$  and  $M_{X3}$

Quiescent operation:

✧  $M_{X2}$  and  $M_{X3}$  are on.

$\Rightarrow$  Keep  $V_{GSMX7}$  and  $V_{GSMX8}$  low to reduce dc power.

⇒ Provide a low-impedance level at node A and B. CHUNG-YU WU

The low-order poles created by the Miller cap. of  $M_{X7}$  and  $M_{X8}$  can be avoid

\* If  $V_{in} \ll 0$

$M_{X3}$ - $M_{X6}$  are turned off and  $M_{X1}$  and  $M_{X2}$  are on

⇒ Node A has a high voltage ⇒  $M_{X7}$  off.

$V_B = V_A$  because of  $M_{R1} \Rightarrow M_{X8}$  on.

\* In the bias circuit,  $M_{R2} \leftrightarrow M_{R1}$ ,  $M_{B1} \leftrightarrow M_{X1}$ ,  $M_{B2} \leftrightarrow M_{X2}$ ,  $M_{B3} \leftrightarrow M_{X3}$ ,  $M_{B4} \leftrightarrow M_{X4}$ .

In the quiescent case,  $V_{GSMX1} \approx V_{GSMX7}$  and  $V_{GSMX4} \approx V_{GSMX8}$

⇒ The current in  $M_{B1}$  and  $M_{B4}$  controls that in  $M_{X1}$  and  $M_{X4}$  and  $M_{X7}$  and  $M_{X8}$ .

\*  $R_{BIAS}$  controls the current through  $M_{B2}$  and  $M_{B3}$ .

⇒ i.e. the current through  $M_{X2}$  and  $M_{X3}$ .

Characteristics:

3  $\mu\text{m}$  CMOS area: 100mils<sup>2</sup>.

$C_L \geq 100\text{pF}$  and  $R_L \geq 10\text{ k}\Omega$  : stable.

$C_L=5000\text{pF} \Rightarrow f \approx 100\text{kHz}$ .

TABLE II  
BUFFER' S PERFORMANCE

PARAMETER	MEASURED VALUE	SPICE
Supply Voltage	$\pm 2.5\text{ V}$	$\pm 2.5\text{ V}$
Supply Current	285 $\mu\text{A}$	270 $\mu\text{A}$
Voffset	< 10 mV	5 mV
Voltage Gain	+ 1.00 V/V	+ 1.00 V/V
$F_{3\text{dB}}$ ( $C_L=100\text{pF}$ )	6 MHz	8 MHz
Gain Peaking	0.4 dB	0
$R_{o\text{CL}}$	330 $\Omega$	270 $\Omega$
CMRR	80 dB	84 dB
Input CM Range	$\pm 1.8\text{ V}$	$\pm 1.7\text{ V}$
SR ( $C_L=5\text{nF}$ )	$\pm 0.9\text{ V}/\mu\text{s}$	$\pm 1.0\text{ V}/\mu\text{s}$

$T_{\text{settling}}$ (to 1%)	3.9 $\mu\text{s}$	4 $\mu\text{s}$
-------------------------------	-------------------	-----------------

Input Noise Density $F = 1 \text{ kHz}$	$270 \text{ V} / \sqrt{H_Z}$	NA
$F = 50 \text{ kHz}$	$70 \text{ V} / \sqrt{H_Z}$	NA

Ref.: IEEE JSSC, vol. sc-21, pp.464-469, June 1986.

#### § 8-4 Advanced Design Techniques on Fully differential type CMOS OP AMPs

##### 1. Low-noise chopper-stabilized OP AMP

Techniques for the reduction of  $1/f$  noise:

1) Use large device geometries.

Possibly too large chip area.

2) Use buried channel devices

Not a standard technology.


3) Transform the noise to a higher frequency range

So that it does not contaminate the signal.

a. The correlated double sampling (CDS) method


b. The chopper stabilization method

##### a. CDS method

 

$\Rightarrow$  Noise reduction

##### b. Chopper stabilization method

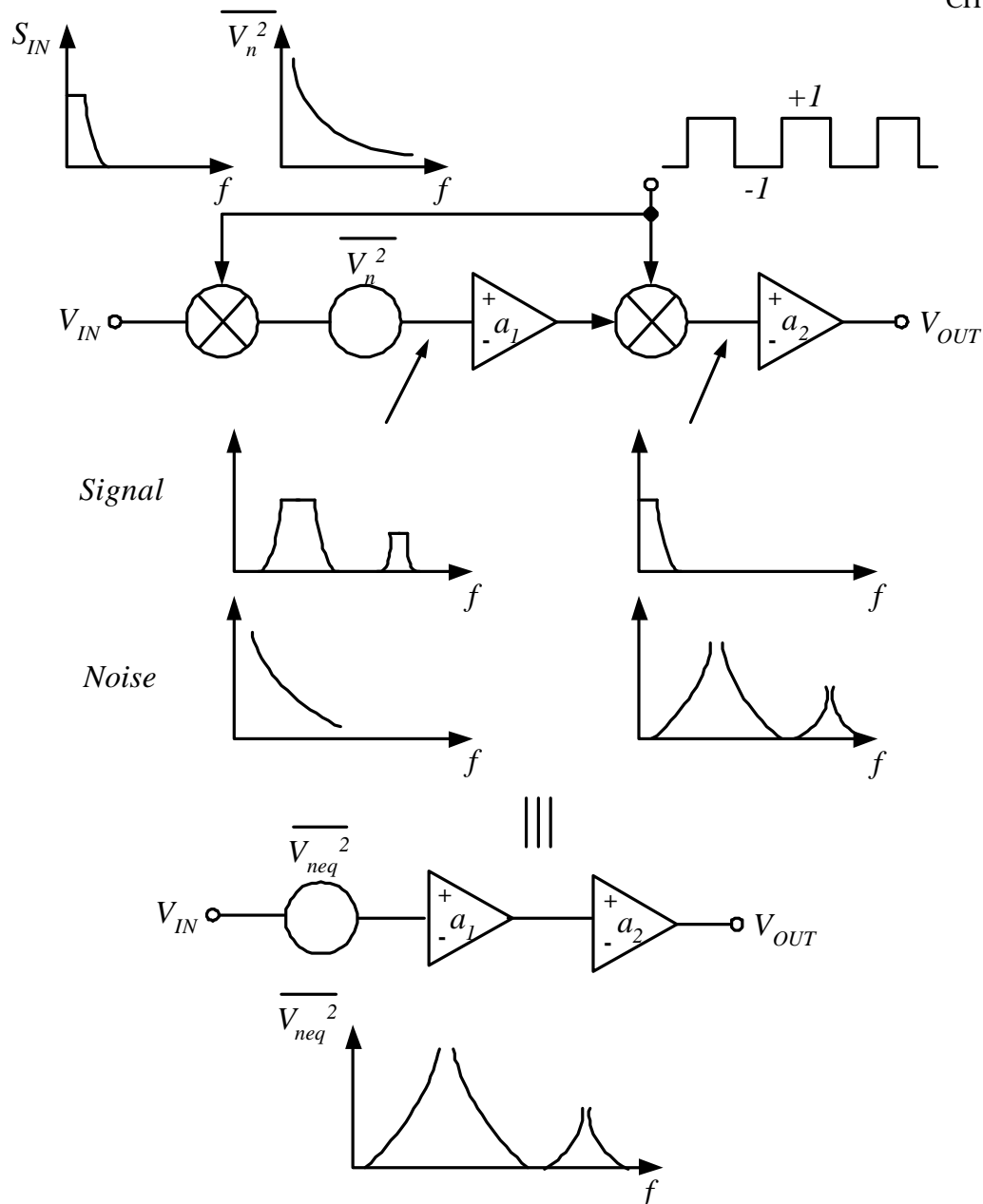

- \* If the chopper frequency is much higher than the signal bandwidth, the  $1/f$  noise in the signal band will be greatly reduced.


Example: Fully differential class AB chopper stabilized OP AMP with DCMFB circuit.

Major advantage of fully differential OP AMPs:

1. Improvement of PSRR
2. Improvement of dynamic range
3. double the output swing
4. Reduction on the sensitivity to clock and supply noise.

Disadvantage:

 1. Larger area, mainly due to interconnection
2. Additional design complexity
3. Increase power dissipation.



M43-M46, M47-M54: the input chopper and the output chopper.

M29-M42, C1-C4 : DCMFB circuit

Device	W(um)	L(um)	Device	W(um)	L(um)
M1	25	3	M19	7	3.5
M2	25	3	M20	7	3.5
M3	25	3	M21	17.5	3.5
M4	25	3	M22	17.5	3.5
M5	25	3	M23	7	3.5
M6	25	3	M24	7	3.5

8 - 25

CHUNG-YU WU

M7	25	3	M25	3.5	3.5
M8	25	3	M26	3.5	3.5




M9	10	3.5	M27	3	7
M10	10	3.5	M28	3	7
M11	4	3.5	M29	12	3.5
M12	4	3.5	M30	12	3.5
M13	17.5	3.5	M31	16	3.5
M14	17.5	3.5	M32	18	3.5
M15	7	3.5	M33-M34	7	3
M16	7	3.5	M55	7	3
M17	17.5	3.5	M56	7	3
M18	17.5	3.5			

Ref: IEEE JSSC vol.sc-21, pp.57-64 Feb.1986


## 2. Fully differential folded cascode amplifier(National Semiconductor)

For internal OP AMPs, high output impedance is O.K.

⇒ simple 2-stage or single-stage OP AMP.

 

TWO-STAGE

 

SINGLE-STAGE


CASCODE

### DOMINANT AND NONDOMINANT POLE LOCATIONS FOR THE TWO-AND SINGLE-STAGE AMPLIFIERS

	Dominant pole location	Nondominant pole location
Two-stage amplifier	$\frac{1}{r_o C_c g_m r_o}$	$\frac{g_m}{C_L}$
One-stage amplifier	$\frac{1}{r_o C_L g_m r_o}$	$\frac{g_m}{C_p}$

In general, the higher the 2<sup>nd</sup> pole frequency, the faster the settling response.

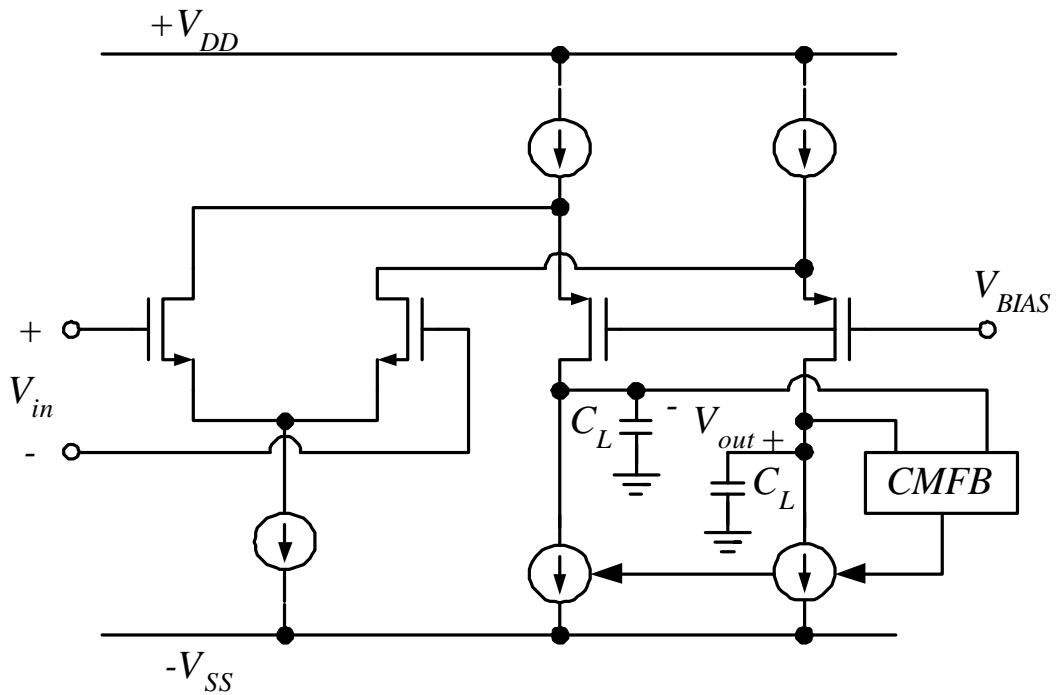
⇒ Single-stage cascode amp. has a faster settling behavior.




CMFB: Common-mode feedback circuitry
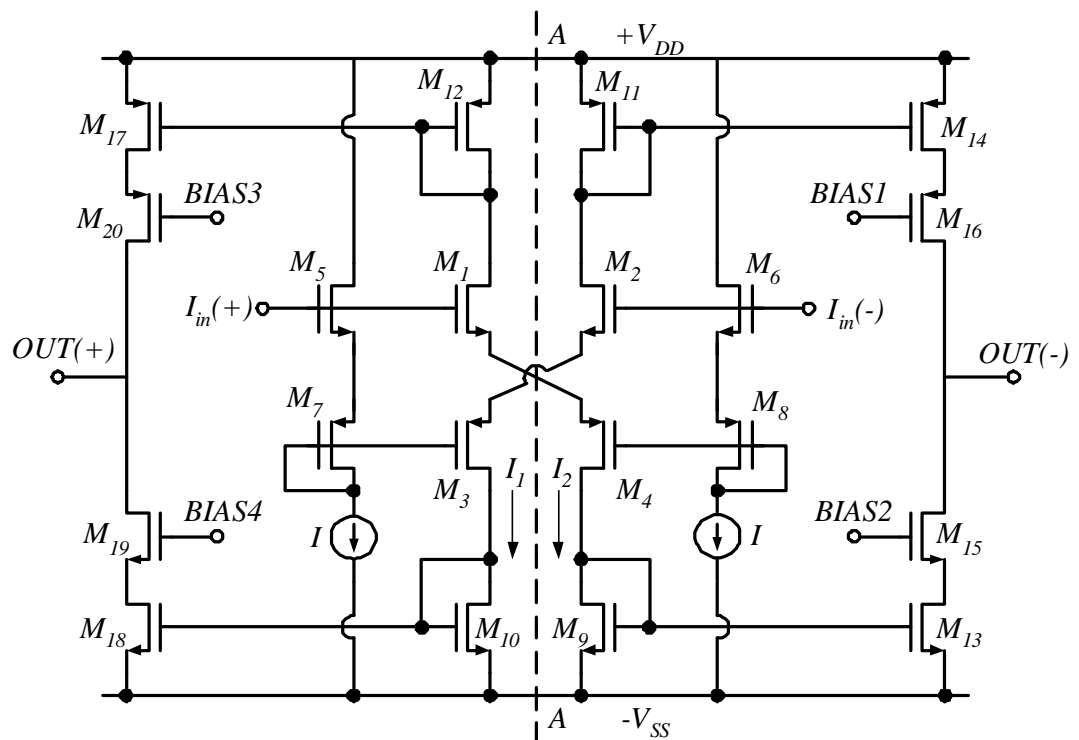
### 3. High-performance micropower fully differential OP AMP.


Simplified schematic of the class AB amplifier:



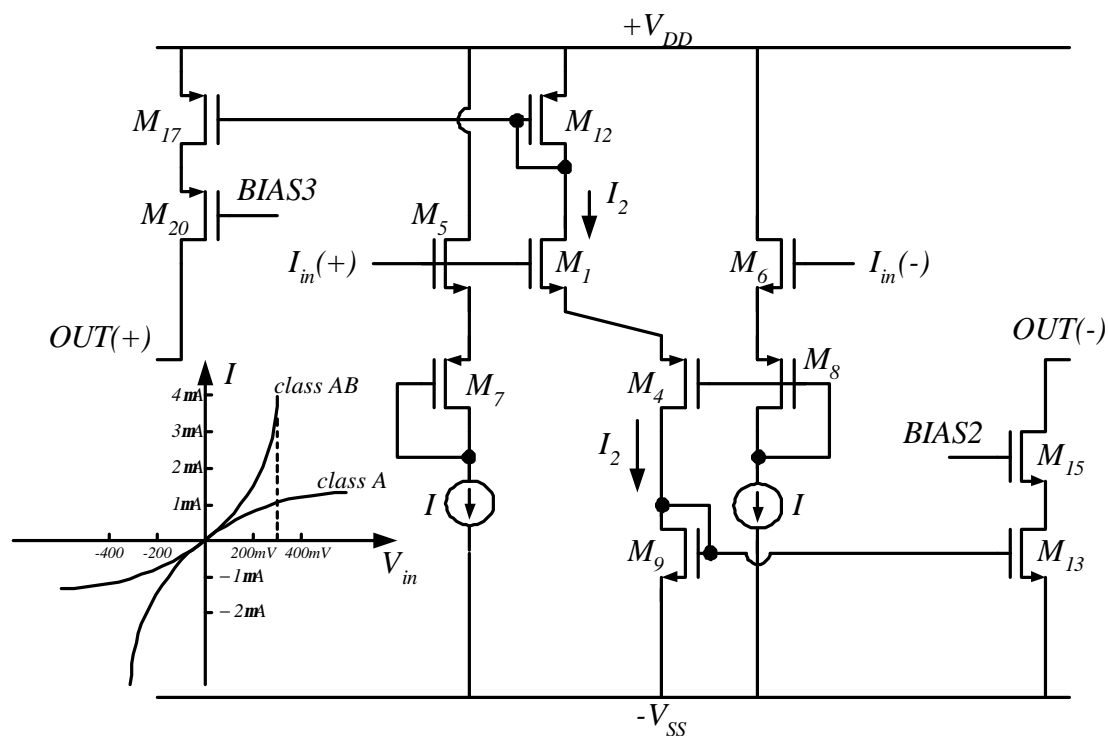


Active portion of the amplifier for a positive input signal.

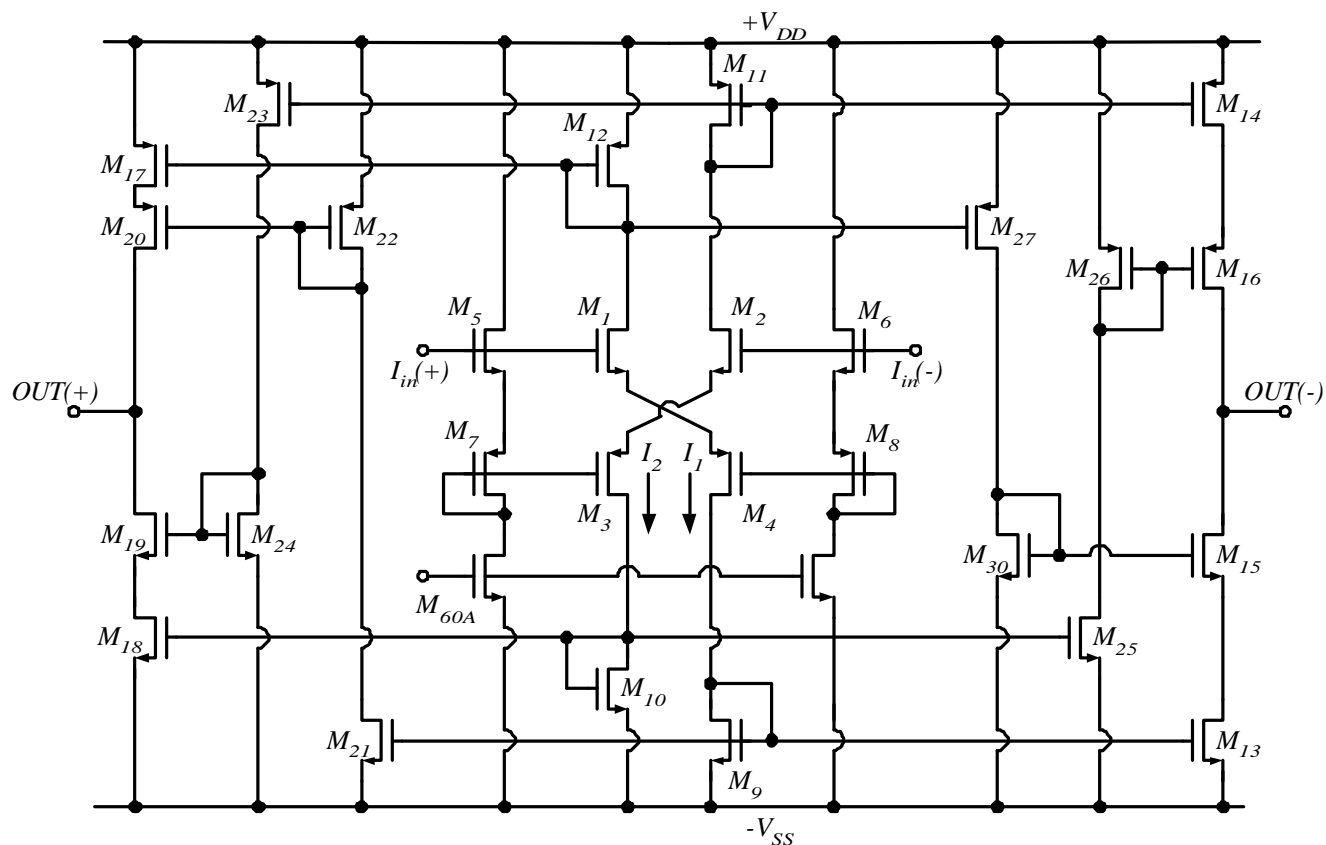Detailed schematic of the entire amplifier without CMFB:



 - \* NMOS dynamically biased current mirror:



If  $I_9 = I_{30}$ ,  $V_{GS9} = V_{GS13} = V_{GS15}$

$$V_{DS13} = V_{GS30} - V_{GS9}$$

Set  $V_{DG13} = -V_{TH} \Rightarrow V_{GS30} = 2V_{GS9} - V_{TH}$

Design  $\left(\frac{W}{L}\right)_{30}$ , such that  $V_{GS30} = 2V_{GS9} - V_{TH}$

$\Rightarrow M_{13}$  is always sat. at the edge of the linear region.

⇒ Output swing ↑

\* Dynamic CMFB is used.

## AMPLIFIER DEVICE SIZES

DEVICE	Z( $\mu$ m)	L( $\mu$ m)
M1	180	6
M2	180	6
M3	140	6
M4	140	6
M5	150	6
M6	150	6
M7	200	6
M8	200	6
M9	22	10
M10	22	10

M11	29	7
M12	29	7
M13	22	10
M14	29	7
M15	22	6
M16	29	6
M17	29	7
M18	22	10
M19	22	6
M20	29	6
M21	20	9
M22	6	12
M23	28	6
M24	6	14
M25	20	9
M26	6	12
M27	28	6
M30	6	14


#### AMPLIFIER SPECIFICATIONS

CORE AMPLIFIER SPECIFICATIONS (0-5 Volts Supply) 100 $\mu$ W Quiescent Power Dissipation	
DIFFERENTIAL GAIN	>10.000★
UNITY GAIN FREQUENCY	2 MHz★
NOISE	140 nV/ $\sqrt{Hz}$ 1KHz 50 nV/ $\sqrt{Hz}$ white
OUTPUT SWING	0.5 Volts from Supply★
AREA	300 <i>mils</i> <sup>2</sup>

★inferred from filter measurement

Ref: IEEE JSSC, vol. SC-20, pp.1122-1132, Dec. 1985

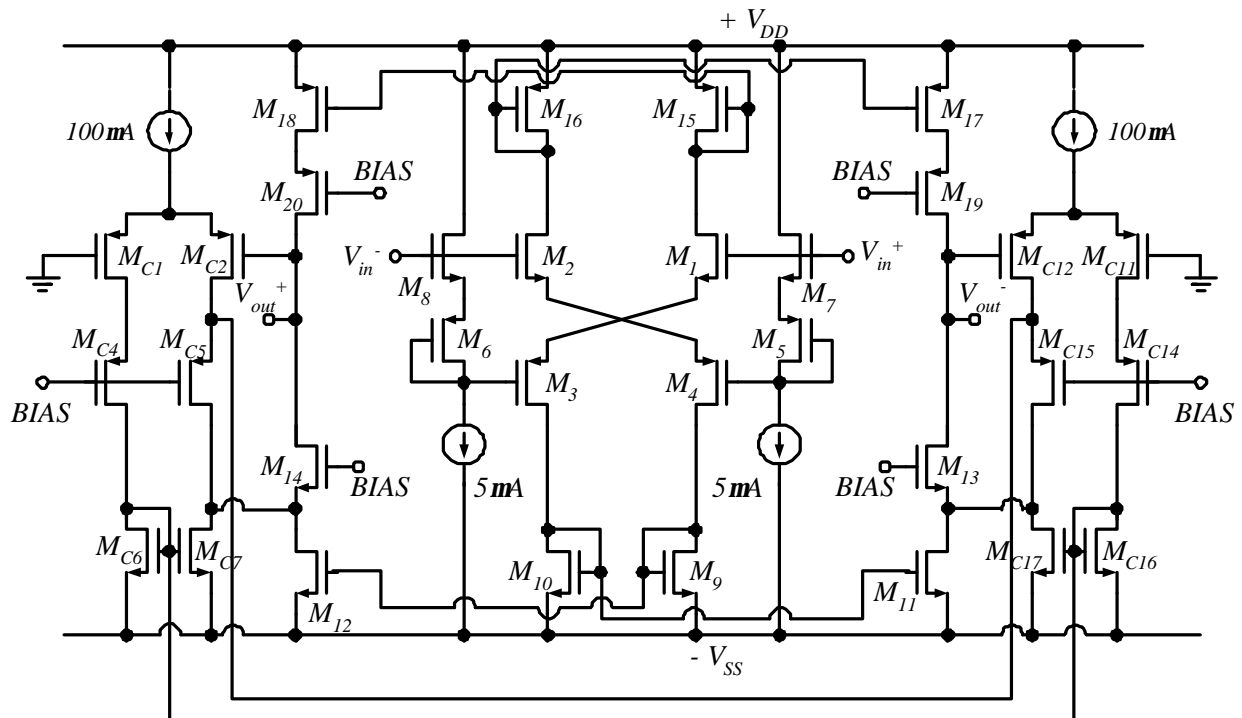4. Fully differential class AB OP AMP with CMFB circuit



Characteristics:

Technology	: 5um, P-well CMOS, double-poly cap.		
Open loop gain	: 1180	unity-gain freq	: 10Mhez
CMRR	: 61db	power consumption	: 2.3mw
Area	: 290 mils <sup>2</sup>	power supply	: $\pm 5V$

Ref: IEEE JSSC ,vol.sc-20 , pp.1103-1112 , Ddec,1985


## § 8-5 Recent Design Examples of CMOS OP AMPs

### § 8-5.1 Fast-settling CMOS OP AMP for SC Circuit with 90-dB DC Gain

Reference : IEEE JSSC, vol.25, no.6, pp.1379-1384, Dec 1990.

#### 1. Gain boosting
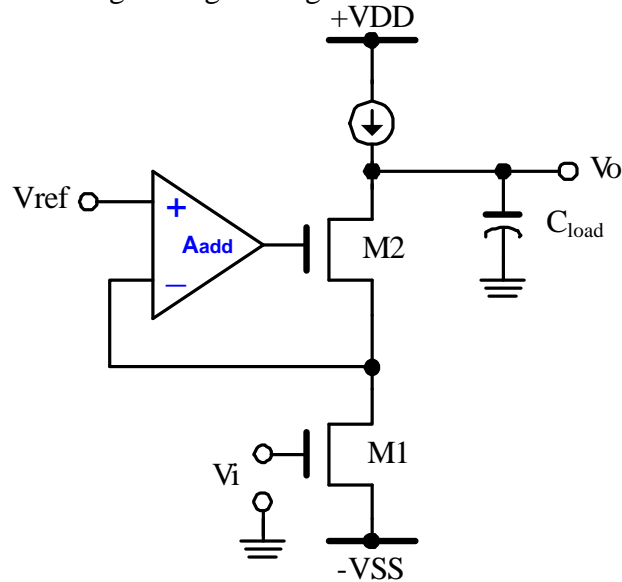
##### 1) Cascode gain stage with gain enhancement




$$R_{out} = [g_{m2}r_{o2}(A_{add} + 1) + 1]r_{o1} + r_{o2}$$


$$A_{tot} = g_{m1}r_{o1}[g_{m2}r_{o2}(A_{add} + 1) + 1]$$

$$A_{orig} = g_{m1}g_{m2}r_{o1}r_{o2}$$
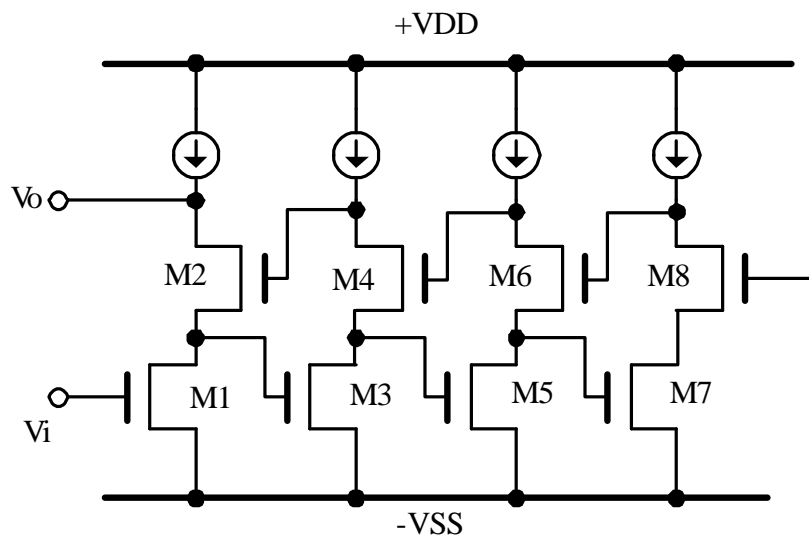
##### 2) Repetitive implementation of gain enhancement



#### 2. High-frequency behavior

 

$\omega_3$  : Upper 3-dB frequency of  $A_{orig}$

$\omega_5$  : Unity-gain frequency of  $A_{tot}$

$\omega_2$  : Upper 3-dB frequency of  $A_{add}$

$\omega_4$  : Unity-gain frequency of  $A_{add}$

$\omega_1$  : Upper 3-dB frequency of  $A_{tot}$

$\omega_5$  : Unity-gain frequency of  $A_{orig}$

We want  $\omega_5|_{A_{orig}} = \omega_5|_{A_{tot}}$

$\omega_2 > \omega_1 \Rightarrow$  The bandwidth is determined by  $\omega_1$ , i.e.  $R_{out}$  and  $C_{load}$ .

$\Rightarrow \omega_4 > \omega_3$

But  $\omega_4 < \omega_5$  for easy design of  $A_{add}$ .

$A_{add}$  and M2 forms a close loop with the dominant pole of  $\omega_2$  and the second pole at the source of M2, i.e.  $\omega_6$

The stability consideration requires  $\omega_4 < \omega_6$

$\Rightarrow$  The safe range of  $\omega_4$  is

$$\omega_3 < \omega_4 < \omega_6$$

\* The repetitive usage of the gain-enhancement techniques yields a decoupling of the op-amp gain and unity-gain frequency  $f_u$ . That is: gain  $\uparrow$  without  $f_u \downarrow$ .

### 3. Settling behavior


1. Total output impedance  $Z_{tot}$

$$Z_{tot} = Z_{load} // Z_{out}$$

$Z_{load}$ : impedance of  $C_{load}$

$Z_{out}$ : output impedance of the amplifier

$$Z_{out} \cong Z_{orig} (A_{add} + 1)$$

 



$\omega_2$  : Upper-3dB freq. Of  $A_{add}$   
 $\rightarrow$  the same for  $Z_{out}$

$\omega_4$  : Unity-gain freq. Of  $A_{add}$

For  $\omega > \omega_4$ ,  $A_{add} < 1 \rightarrow Z_{out} \rightarrow Z_{orig}$

$\rightarrow$  A zero is formed at  $\omega_4$  for  $Z_{out}$

$Z_{total} = Z_{load} \parallel Z_{out} \rightarrow$  A pole-zero doublet is formed around  $\omega_4$


$\rightarrow$  The same doublet of  $A_{total}$

### 3. Design technique for fast settling

The time constant of the doublet,  $\frac{1}{\omega_{PZ}}$ , must be smaller than the main close-loop time

constant,  $\frac{1}{\beta\omega_{unity}}$ . where  $\beta$  is the feedback factor.


The safe range for the  $\omega_4$ .

 

$$\beta\omega_5 < \omega_4 < \omega_6$$

doublet

### 4. CMOS OP AMP circuit

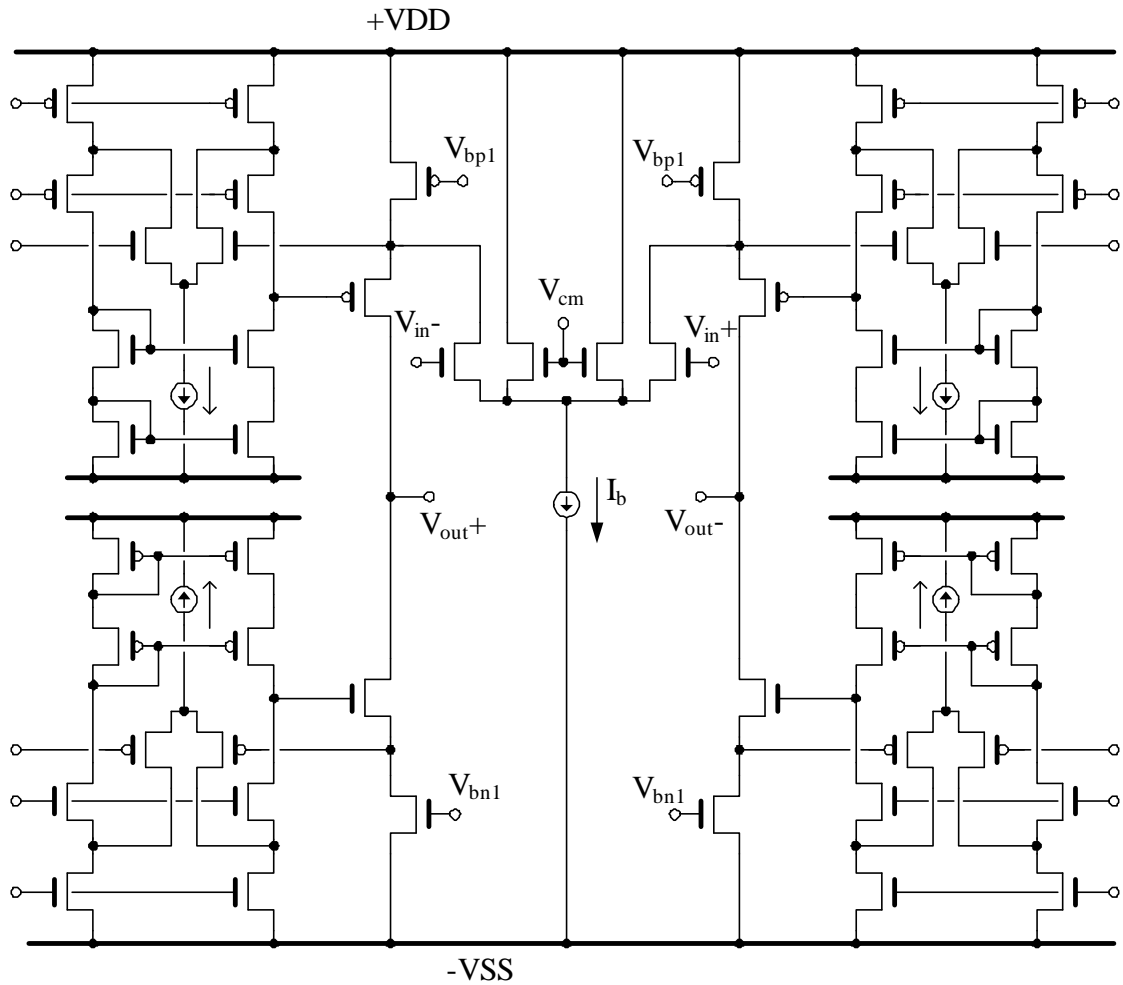

MAIN CHARACTERISTICS OF THE OP AMP

Gain enh.	on	Off
DC-gain	90dB	46dB
Unity-gain freq.	116MHz	120MHz
Load cap.	16pF	16pF
Phase margin	64deg.	63deg
Power cons.	52mW	45mW
Output-swing	4.2V	4.2V
Supply voltage	5.0V	5.0V
Settling time	61.5ns	-
0.1% , $\Delta V_o = 1V$		



### § 8-5.2 1V Rail-to-Rail CMOS OP AMPs

Ref.: IEEE JSSC vol.35, no.1, pp.33-44 Jan. 2000
 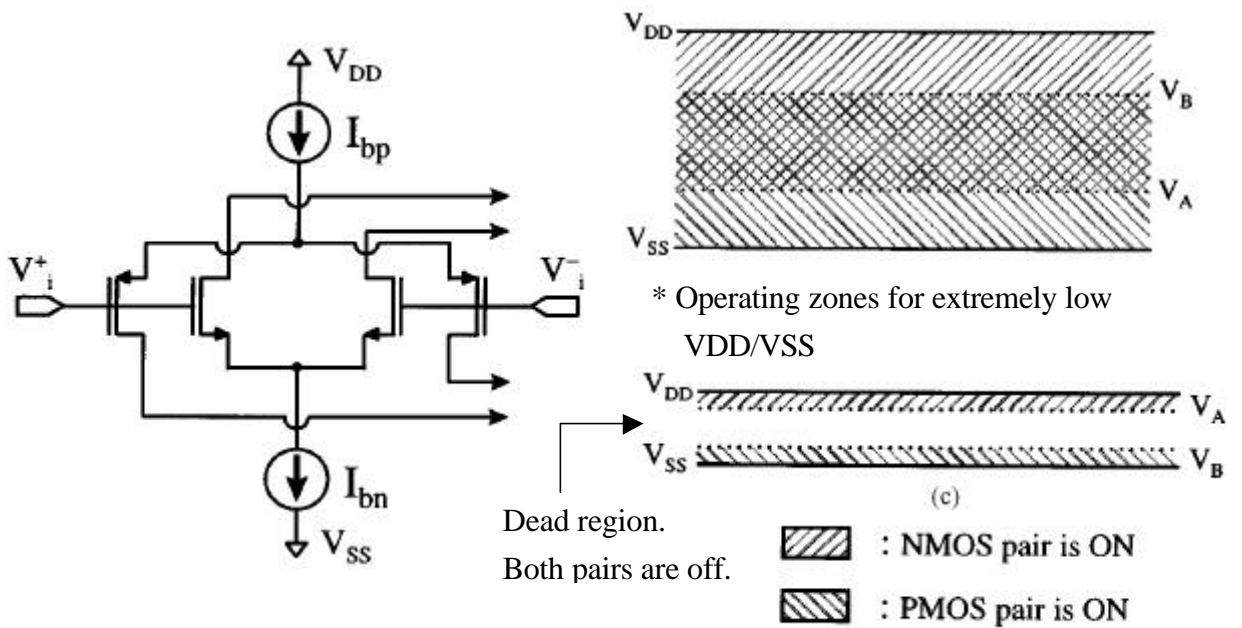
## 1. Typical input stage for rail-to-rail amplifiers

\* Parallel-connected complementary differential pairs.

\* Operating zones for low  $V_{DD}/V_{SS}$



## 2. Dynamic level-shifting current generator

$$V_{i,n,cm} = V_{i,cm} + IR$$

$$V_{i,p,cm} = V_{i,cm} - IR$$

\* The input resistance over the entire voltage range is infinite and no loading effect or input current over the previous stage.


Usually mismatches cause negligible input current.

\* The symmetrical topology ensures very high CMRR


$$CMRR = \frac{1}{RG_m} \left( \frac{\Delta R}{R} + \frac{\Delta G_m}{G_m} \right)^{-1}$$

$$\text{where } G_m = \Delta I / \Delta V_{i,cm}$$

### Circuit implementation

 

 
### 3. Rail-to-rail very LV CMOS OP AMP with input dynamic level-shifting circuit



MAIN TRANSISTOR ASPECT RATIOS (IN  $\mu\text{m}$ ) AND ELEMENT VALUES OF THE AMPLIFIER BASED ON COMPLEMENTARY PAIRS

M1A,M1B	400/5	M15	700/2
M2A,M2B	200/5	R1-R4	30 $K\Omega$
M1,M2	400/2	$R_M$	5 $K\Omega$
M3,M4	200/2	$C_M$	10pF
M5-M8	400/5	$I_{bn} = I_{bp}$	10 $\mu\text{A}$
M9-M12	500/5	$I_o$	40 $\mu\text{A}$

## 4. Input CM adapter

 

$$V_x = A[2V_{ref} - (V_{i,p}^+ + V_{i,p}^-)]$$

$$= 2A(V_{ref} - V_{i,p,cm})$$


$$I = G_m V_x$$

$$\Rightarrow V_{i,p,cm} \cong V_{ref} + \frac{V_{i,cm}}{2RG_m A}$$


$$V_{i,p,dm} = V_{i,dm}$$

\* $V_{i,cm}$  is degraded by A and  $V_{i,p,cm} \cong V_{ref}$

Circuit implementation:

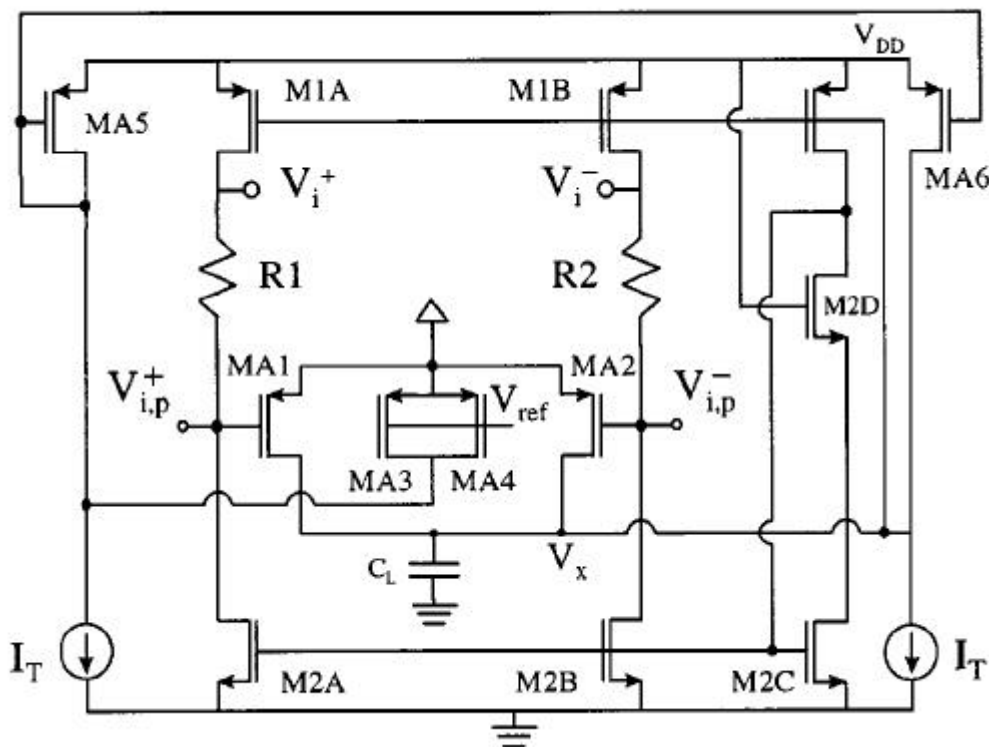
 
## 5. Very LV CMOS OP AMP with a single differential pair and the input CM adapter.



Main transistor ratios(in  $\mu\text{m}$ ) and element values of the amplifier based on a single input pair

M1A M1B	1000/6	M6	1600/2
M2A M2B	600/4	M7-M10	300/4
MA1-MA4	50/2	M11	700/2
MA5-MA6	300/4	R1-R2	15K $\Omega$
M2D	150/2	RM	5K $\Omega$
M1,M2	200/2	CM	5pF
M3-M5	400/2	Is=Ir/2	10 $\mu\text{A}$

#### 6.Measured results

Experimental performance of amplifiers( $V_{\text{supply}}=1\text{V}$ ,technology:1.2 $\mu\text{m}$  CMOS,  $C_L=15\text{pF}$ )

Parameter	Dynamic-shifting amp	CM adapter amp
Active die area	0.81mm <sup>2</sup>	0.26 mm <sup>2</sup>
Ido(supply current)	410uA	208uA
DC gain	87dB	70.5dB
unity-gain frequency	1.9Mhz	2.1Mhz
Phase margin	61°	73°
SR+	0.8V/us	0.9V/us
SR-	1V/us	1.7V/us
THD( <a href="#">0.5Vpp@1kHz</a> )	-54dB	-77dB
THD( <a href="#">0.5Vpp@40kHz</a> )	-32dB	-57dB
Vni(@1KHz)	267nV/ $\sqrt{Hz}$	359nV/ $\sqrt{Hz}$
Vni(@10KHz)	91nV/ $\sqrt{Hz}$	171nV/ $\sqrt{Hz}$
Vni(@1MHz)	74nV/ $\sqrt{Hz}$	82nV/ $\sqrt{Hz}$
CMRR	62dB	58dB
PSRR+	-54.4dB	-56.7dB
PSRR-	-52.1dB	-51.5dB

#### §8-5.3 1.5V High Drive Capability CMOS OP AMP

Ref.: IEEE JSSC vol.34, no.2, pp. 248-252, Feb. 1999

1. Folded-mirror differential input stage

$$V_{CM} \leq V_{GS6,7} + V_{THn} = 2V_{THn} + \Delta V_{6,7}$$

$$V_{CM} \geq V_{DSsat5} + V_{GS1,2} = 2V_{THn} + \Delta V_5 + \Delta V_{1,2}$$


$$CMR = V_{THn} - \Delta V_5$$

$\Delta V$  : overdrive voltage.


CMR is independent of supply voltage.

For  $V_{DD}=1.5V$ ,  $CMR=0.6 \sim 0.7V$

 CMR of the conventional NMOS-input differential pair is 0.3-0.5V



2. Output Stage

 

Input section : M1A-M4A ,  $I_{B1}$  ,  $I_{B2}$

Output section: M5A-M6A and M7A-M8A

M5A, M8A sat

M6A, M7A off.

For low input levels , M6A and M7A off  $\rightarrow$  Class A operation.

For large positive input signals,

$I_{D1A}=I_{B1} \rightarrow$  M3A and M5A OFF

$\rightarrow V_A - V_{SS}$

$\rightarrow M_{6A}$  is turned on to supply most of the output current.


But M7A remains cutoff.

The current of M8A is increased.

For large negative input signals,  $M_{7A}$  supplies most of the output current.

$(W/L)_{5A,8A} \ll (W/L)_{6A,7A}$  for low dc power dissipation and high drive.

## 3. Overall LV CMOS OP AMP.

 

$$\text{Dominant pole : } W_{p1} \approx \frac{1}{r_{o5,7} \{ (g_{m8} r_{o8,9})^2 [g_{m5A,8A} (r_{o5A} \parallel r_{o8A})] \} C_c}$$

$$\text{Gain-bandwidth product: } W_{GBW} \approx \frac{g_{m1,2}}{C_{c1}}$$

Hybrid nested Miller compensation:  $C_{C1}, C_{C2}, C_{C3A,B}$

The inner amplifier  $M_8, M_9, M_{1A} \sim M_{8A}$  contributes the nondominant poles.

\* The two-stage OP AMP  $M_1 \sim M_9$  has a gain-bandwidth product of  $\frac{g_{m1,2}}{C_{c2}}$

and the gain of  $\frac{g_{m1,2}}{sC_{c2}}$  at high frequency. The gain of  $M_1 \sim M_7$  at high frequency is

$$\frac{g_{m1,2}}{sC_{c1}}. \text{ Thus the gain of the gain stage } M_8 \text{ and } M_9 \text{ is approximately equal to } \frac{C_{C1}}{C_{C2}}.$$

\* The open-loop gain of the inner amplifier is

$$A_{in} \cong - \left( \frac{C_{C1}}{C_{C2}} \right) \left( \frac{g_{m1A,2A}}{g_{m3A,4A}} \right) 2g_{m5A,8A} (r_{o5A} \parallel r_{o8A})$$

$$\text{Dominant pole : } w_{p1in} \cong \frac{g_{m3A,4A}}{g_{m5A,8A} (r_{o5A} \parallel r_{o8A}) C_{C3A,B}}$$

$$\text{Second pole : } w_{p2in} \cong \frac{2g_{m5A,8A}}{C_L}$$



Gain-bandwidth product :  $\omega_{GBWin} \cong 2 \frac{C_{C1}}{C_{C2}} \frac{g_{m1A,2A}}{C_{C3A,B}}$   
or the second pole of the  
whole amplifier

Design consideration :

To obtain a maximally flat Butterworth response without gain peaking, we have the unity-gain frequency equal to one half of the second-pole frequency.

$$\omega_{GBWin} = \omega_{uin} = \frac{1}{2} \omega_{P2in}$$

$$\omega_{GBW} = \omega_u = \frac{1}{2} \omega_{uin} = \frac{1}{2} \omega_{GBWin}$$

Reference : IEEE JSSC, vol.27, pp.1709-1716, Dec. 1992.

Setting  $2C_{C3A,B} = C_{C2}$ , we have

$$C_{C1} = 2 \frac{g_{m1,2}}{g_{m5A,8A}} C_L$$

$$C_{C2} = 2C_{C3A,B} = \sqrt{2g_{m1,2}g_{m1A,2A}} \cdot \frac{C_L}{g_{m5A,8A}}$$

Component values :

M1,M2,M3,M9,M1A,M2A,M10	60/2
M4,M5,M11,M12,M13	20/2
M6,M7	15/2
M8	90/2
M3A	5/1.2
M4A	15/1.2
M5A	30/1.2
M7A	120/1.2
M6A	360/1.2
M8A	90/1.2
M14,M16	10/1.2
M15,MC	30/2
$C_{C1}$	4pF
$C_{C2}$	6pF
$C_{C3A},C_{C3B}$	2pF
$I_{BIAS}$	5uA
$V_{TH}$	0.8V

Experimental results:

MEASURED MAIN PERFORMANCE

Open-Loop Gain	68dB
GBW	1MHz
Phase Margin	$65^{\circ}$
Gain Margin	16dB
Settling Time(0.1%), $\Delta V = 200mV$	400ns
Slew Rate	1 V/ $\mu$ s
<a href="#">THD@1kHz</a> $V_{out} = 0.5V$ RL=500 Closed-Loop Gain=20dB	-57dB
<a href="#">PSRR+@1kHz</a>	75dB
PSRR- @1kHz	75dB
CMRR @1kHz	95dB
Offset	< 8mv
Power Dissipation	280 $\mu$ W
Die Size	0.08 $mm^2$
Technology	1.2 $\mu$ m CMOS
Loading	50pF    500