

VERILOG

Hardware Description Language

1

About Verilog

- **Along with VHDL, Verilog is among the most widely used HDLs.**
- **Main differences:**
 - **VHDL was designed to support system-level design and specification.**
 - **Verilog was designed primarily for digital hardware designers developing FPGAs and ASICs.**
- **The differences become clear if someone analyzes the language features.**

2

- **VHDL**
 - Provides some high-level constructs not available in Verilog (user defined types, configurations, etc.).
- **Verilog**
 - Provides comprehensive support for low-level digital design.
 - Not available in native VHDL
 - Range of type definitions and supporting functions (called packages) needs to be included.

3

Concept of Verilog “Module”

- In Verilog, the basic unit of hardware is called a module.
 - Modules cannot contain definitions of other modules.
 - A module can, however, be instantiated within another module.
 - Allows the creation of a *hierarchy* in a Verilog description.

4

Basic Syntax of Module Definition

```
module module_name (list_of_ports);  
  
    input/output declarations  
  
    local net declarations  
  
    Parallel statements  
  
endmodule
```

5

Example 1 :: simple AND gate

```
module simpleand (f, x, y);  
    input x, y;  
    output f;  
    assign f = x & y;  
endmodule
```

6

Example 2 :: two-level circuit

```
module two_level (a, b, c, d, f);  
    input a, b, c, d;  
    output f;  
    wire t1, t2;  
    assign t1 = a & b;  
    assign t2 = ~ (c | d);  
    assign f = t1 ^ t2;  
endmodule
```

7

Example 3 :: a hierarchical design

```
module add3 (s, cy3, cy_in, x, y);  
    input [2:0] x, y;  
    input cy_in;  
    output [2:0] s;  
    output cy3;  
    wire [1:0] cy_out;  
    add B0 (cy_out[0], s[0], x[0], y[0], cy_in);  
    add B1 (cy_out[1], s[1], x[1], y[1], cy_out[0]);  
    add B2 (cy3, s[2], x[2], y[2], cy_out[1]);  
endmodule
```

8

Specifying Connectivity

- There are two alternate ways of specifying connectivity:
 - Positional association
 - The connections are listed in the same order
 - `add A1 (c_out, sum, a, b, c_in);`
 - Explicit association
 - May be listed in any order
 - `add A1 (.in1(a), .in2(b), .cin(c_in),
 .sum(sum), .cout(c_out));`

9

Variable Data Types

- A variable belongs to one of two data types:
 - Net
 - Must be continuously driven
 - Used to model connections between continuous assignments & instantiations
 - Register
 - Retains the last value assigned to it
 - Often used to represent storage elements

10

Net data type

- Different 'net' types supported for synthesis:
 - *wire, wor, wand, tri, supply0, supply1*
- 'wire' and 'tri' are equivalent; when there are multiple drivers driving them, the outputs of the drivers are shorted together.
- 'wor' / 'wand' inserts an OR / AND gate at the connection.
- 'supply0' / 'supply1' model power supply connections.

11

```
module using_wire (A, B, C, D, f);  
  input  A, B, C, D;  
  output f;  
  wire  f;          // net f declared as 'wire'  
  
  assign f = A & B;  
  assign f = C | D;  
endmodule
```

12

```

module using_wired_and (A, B, C, D, f);
  input  A, B, C, D;
  output f;
  wand  f;          // net f declared as 'wand'

  assign f = A & B;
  assign f = C | D;
endmodule

```

13

```

module using_supply_wire (A, B, C, f);
  input  A, B, C;
  output f;
  supply0 gnd;
  supply1 vdd;
  nand  G1 (t1, vdd, A, B);
  xor   G2 (t2, C, gnd);
  and   G3 (f, t1, t2);
endmodule

```

14

Register data type

- Different 'register' types supported for synthesis:
 - **reg, integer**
- The 'reg' declaration explicitly specifies the size.
 - reg x, y; // single-bit register variables**
 - reg [15:0] bus; // 16-bit bus, bus[15] MSB**
- For 'integer', it takes the default size, usually 32-bits.
 - **Synthesizer tries to determine the size.**

15

Other differences:

- In arithmetic expressions,
 - An 'integer' is treated as a 2's complement signed integer.
 - A 'reg' is treated as an unsigned quantity.
- General rule of thumb
 - 'reg' used to model actual hardware registers such as counters, accumulator, etc.
 - 'integer' used for situations like loop counting.

16


```

module simple_counter (clk, rst, count);
  input  clk, rst;
  output count;
  reg [31:0] count;

  always @(posedge clk)
  begin
    if (rst)
      count = 32'b0;
    else
      count = count + 1;
  end
endmodule

```

17

- When 'integer' is used, the synthesis system often carries out a data flow analysis of the model to determine its actual size.

- Example:

```

wire [1:10] A, B;
integer    C;
C = A + B;

```

→ The size of C can be determined to be equal to 11 (10 bits plus a carry).

18

Specifying Constant Values

- A value may be specified in either the 'sized' or the 'un-sized' form.
 - Syntax for 'sized' form:
`<size>'<base><number>`
- Examples:
 - `8'b01110011` // 8-bit binary number
 - `12'hA2D` // 1010 0010 1101 in binary
 - `12'hCx5` // 1100 xxxx 0101 in binary
 - `25` // signed number, 32 bits
 - `1'b0` // logic 0
 - `1'b1` // logic 1

19

Parameters

- A *parameter* is a constant with a name.
- No size is allowed to be specified for a parameter.
 - The size gets decided from the constant itself (32-bits if nothing is specified).
- Examples:
 - `parameter HI = 25, LO = 5;`
 - `parameter up = 2b'00, down = 2b'01,`
`steady = 2b'10;`

20

Logic Values

- The common values used in modeling hardware are:
 - 0 :: Logic-0 or FALSE
 - 1 :: Logic-1 or TRUE
 - x :: Unknown (or don't care)
 - z :: High impedance
- Initialization:
 - All unconnected nets set to 'z'
 - All register variables set to 'x'

21

- Verilog provides a set of predefined logic gates.
 - They respond to inputs (0, 1, x, or z) in a logical way.
 - Example :: AND

0 & 0 → 0	0 & x → 0
0 & 1 → 0	1 & z → x
1 & 1 → 1	z & x → x
1 & x → x	

22

Primitive Gates

- **Primitive logic gates (instantiations):**

```
and    G (out, in1, in2);  
nand   G (out, in1, in2);  
or     G (out, in1, in2);  
nor    G (out, in1, in2);  
xor    G (out, in1, in2);  
xnor   G (out, in1, in2);  
not    G (out1, in);  
buf    G (out1, in);
```

23

- **Primitive Tri-State gates (instantiation)**

```
bufif1 G (out, in, ctrl);  
bufif0 G (out, in, ctrl);  
notif1 G (out, in, ctrl);  
notif0 G (out, in, ctrl);
```

24

Some Points to Note

- For all primitive gates,
 - The output port must be connected to a net (a wire).
 - The input ports may be connected to nets or register type variables.
 - They can have a single output but any number of inputs.
 - An optional delay may be specified.
 - *Logic synthesis tools ignore time delays.*

25

```
`timescale 1 ns / 1ns
module exclusive_or (f, a, b);
    input a, b;
    output f;
    wire t1, t2, t3;
    nand #5 m1 (t1, a, b);
    and #5 m2 (t2, a, t1);
    and #5 m3 (t3, t1, b);
    or #5 m4 (f, t2, t3);
endmodule
```

26

Hardware Modeling Issues

- The values computed can be held in
 - A 'wire'
 - A 'flip-flop' (edge-triggered storage cell)
 - A 'latch' (level-sensitive storage cell)
- A variable in Verilog can be of
 - 'net data type'
 - Maps to a 'wire' during synthesis
 - 'register' data type
 - Maps either to a 'wire' or to a 'storage cell' depending on the context under which a value is assigned.

27

```
module reg_maps_to_wire (A, B, C, f1, f2);  
  input  A, B, C;  
  output f1, f2;  
  wire   A, B, C;  
  reg    f1, f2;  
  always @(A or B or C)  
  begin  
    f1 = ~(A & B);  
    f2 = f1 ^ C;  
  end  
endmodule
```

The synthesis system
will generate a wire
for f1

28

```

module a_problem_case (A, B, C, f1, f2);
  input  A, B, C;
  output f1, f2;
  wire   A, B, C;
  reg    f1, f2;
  always @(A or B or C)
  begin
    f2 = f1 ^ f2;
    f1 = ~(A & B);
  end
endmodule

```

The synthesis system
will not generate a
storage cell for f1

29

```

// A latch gets inferred here
module simple_latch (data, load, d_out);
  input  data, load;
  output d_out;

  always @(load or data)
  begin
    if (!load)
      t = data;
    d_out = !t;
  end
endmodule

```

Else part missing; so
latch is inferred.

30

Verilog Operators

- Arithmetic operators

`*, /, +, -, %`

- Logical operators

`!` → logical negation

`&&` → logical AND

`||` → logical OR

- Relational operators

`>, <, >=, <=, ==, !=`

- Bitwise operators

`~, &, |, ^, ~^`

31

- Reduction operators (operate on all the bits within a word)

`&, ~&, |, ~|, ^, ~^`

→ accepts a single word operand and produces a single bit as output

- Shift operators

`>>, <<`

- Concatenation `{ }`

- Replication `{ { } }`

- Conditional

`<condition> ? <expression1> : <expression2>`

32


```

module operator_example (x, y, f1, f2);
  input    x, y;
  output f1, f2;
  wire [9:0] x, y;  wire [4:0] f1;  wire f2;

  assign f1 = x[4:0] & y[4:0];
  assign f2 = x[2] | ~f1[3];
  assign f2 = ~& x;
  assign f1 = f2 ? x[9:5] : x[4:0];
endmodule

```

33

```

// An 8-bit adder description

module parallel_adder (sum, cout, in1, in2, cin);
  input  [7:0] in1, in2;  input  cin;
  output [7:0] sum;       output cout;

  assign #20 {cout, sum} = in1 + in2 + cin;
endmodule

```

34

Some Points

- The presence of a 'z' or 'x' in a *reg* or *wire* being used in an arithmetic expression results in the whole expression being unknown ('x').
- The logical operators (!, &&, | |) all evaluate to a 1-bit result (0, 1 or x).
- The relational operators (>, <, <=, >=, ~=, ==) also evaluate to a 1-bit result (0 or 1).
- Boolean *false* is equivalent to 1'b0
Boolean *true* is equivalent to 1'b1.

35

Some Valid Statements

```
assign outp = (p == 4'b1111);  
if (load && (select == 2'b01)) .....  
assign a = b >> 1;  
assign a = b << 3;  
assign f = {a, b};  
assign f = {a, 3'b101, b};  
assign f = {x[2], y[0], a};  
assign f = { 4{a} }; // replicate four times  
assign f = {2'b10, 3{2'b01}, x};
```

36

Description Styles in Verilog

- Two different styles of description:
 1. Data flow
 - Continuous assignment
 2. Behavioral
 - Procedural assignment
 - ❖ Blocking
 - ❖ Non-blocking

37

Data-flow Style: Continuous Assignment

- Identified by the keyword “assign”.

```
assign a = b & c  
assign f[2] = c[0];
```
- Forms a static binding between
 - The ‘net’ being assigned on the LHS,
 - The expression on the RHS.
- The assignment is continuously active.
- Almost exclusively used to model combinational logic.

38

- A Verilog module can contain any number of continuous assignment statements.
- For an “assign” statement,
 - The expression on RHS may contain both “register” or “net” type variables.
 - The LHS must be of “net” type, typically a “wire”.
- Several examples of “assign” illustrated already.

39

```
module generate_mux (data, select, out);  
  input [0:7] data;  
  input [0:2] select;  
  output out;  
  
  assign out = data [ select];  
endmodule
```

Non-constant index in
expression on RHS
generates a MUX

40

```

module generate_decoder (out, in, select);
    input in;
    input [0:1] select;
    output [0:3] out;

    assign out [select] = in;
endmodule

```

Non-constant index in
expression on LHS
generates a decoder

41

```

module generate_set_of_MUX (a, b, f, sel);
    input [0:3] a, b;
    input sel;
    output [0:3] f;

    assign f = sel ? a : b;
endmodule

```

Conditional operator
generates a MUX

42

```

module level_sensitive_latch (D, Q, En);
  input D, En;
  output Q;

  assign Q = en ? D : Q;
endmodule

```

Using “assign” to describe sequential logic

43

Behavioral Style: Procedural Assignment

- The procedural block defines
 - A region of code containing *sequential* statements.
 - The statements execute in the order they are written.
- Two types of procedural blocks in Verilog
 - The “always” block
 - A continuous loop that never terminates.
 - The “initial” block
 - Executed once at the beginning of simulation (used in Test-benches).


44

- A module can contain any number of “always” blocks, all of which execute concurrently.
- Basic syntax of “always” block:

```

always @ (event_expression)
begin
    statement;
    statement;
end

```



- The @(event_expression) is required for both combinational and sequential logic descriptions.

45

- Only “reg” type variables can be assigned within an “always” block. Why??
 - The sequential “always” block executes only when the event expression triggers.
 - At other times the block is doing nothing.
 - An object being assigned to must therefore remember the last value assigned (not continuously driven).
 - So, only “reg” type variables can be assigned within the “always” block.
 - Of course, any kind of variable may appear in the event expression (reg, wire, etc.).

46

Sequential Statements in Verilog

1. **begin**
 sequential_statements
 end
 2. **if (expression)**
 sequential_statement
 [else
 sequential_statement]
 3. **case (expression)**
 expr: sequential_statement

 default: sequential_statement
 endcase
- begin...end**
not required
if there
is only 1 stmt.

47

4. **forever**
 sequential_statement
5. **repeat (expression)**
 sequential_statement
6. **while (expression)**
 sequential_statement
7. **for (expr1; expr2; expr3)**
 sequential_statement

48

8. # (time_value)

- Makes a block suspend for “time_value” time units.

9. @ (event_expression)

- Makes a block suspend until event_expression triggers.

49

// A combinational logic example

```
module mux21 (in1, in0, s, f);  
  input in1, in0, s;  
  output f;  
  reg f;  
  
  always @ (in1 or in0 or s)  
    if (s)  
      f = in1;  
    else  
      f = in0;  
endmodule
```

50

// A sequential logic example

```
module dff_negedge (D, clock, Q, Qbar);
  input D, clock;
  output Q, Qbar;
  reg Q, Qbar;

  always @ (negedge clock)
    begin
      Q = D;
      Qbar = ~D;
    end
endmodule
```

51

// Another sequential logic example

```
module incomp_state_spec (curr_state, flag);
  input  [0:1] curr_state;
  output [0:1] flag;
  reg     [0:1] flag;

  always @ (curr_state)
    case (curr_state)
      0, 1 : flag = 2;
      3    : flag = 0;
    endcase
endmodule
```

The variable 'flag' is not assigned a value in all the branches of case.
→ Latch is *inferred*

52

// A small change made

```
module incomp_state_spec (curr_state, flag);
  input  [0:1] curr_state;
  output [0:1] flag;
  reg     [0:1] flag;

  always @ (curr_state)
    flag = 0;
    case (curr_state)
      0, 1 : flag = 2;
      3    : flag = 0;
    endcase
endmodule
```

'flag' defined for all
values of curr_state.
→ Latch is *avoided*

53

```
module ALU_4bit (f, a, b, op);
  input [1:0] op;    input [3:0] a, b;
  output [3:0] f;    reg  [3:0] f;

  parameter ADD=2'b00, SUB=2'b01,
            MUL=2'b10, DIV=2'b11;

  always @ (a or b or op)
    case (op)
      ADD : f = a + b;
      SUB : f = a - b;
      MUL : f = a * b;
      DIV : f = a / b;
    endcase
endmodule
```

54

```

module priority_encoder (in, code);
  input [0:3] in;
  output [0:1] code;
  reg [0:1] code;
  always @ (in)
    case (1'b1)
      input[0] : code = 2'b00;
      input[1] : code = 2'b01;
      input[2] : code = 2'd10;
      input[3] : code = 2'b11;
    endcase
endmodule

```

55

Blocking & Non-blocking Assignments

- Sequential statements within procedural blocks (“always” and “initial”) can use two types of assignments:
 - Blocking assignment
 - Uses the ‘=’ operator
 - Non-blocking assignment
 - Uses the ‘=>’ operator

56

Blocking Assignment (using '=')

- Most commonly used type.
- The target of assignment gets updated before the next sequential statement in the procedural block is executed.
- A statement using blocking assignment blocks the execution of the statements following it, until it gets completed.
- Recommended style for modeling combinational logic.

57

Non-Blocking Assignment (using '<=')

- The assignment to the target gets scheduled for the end of the simulation cycle.
 - Normally occurs at the end of the sequential block.
 - Statements subsequent to the instruction under consideration are not blocked by the assignment.
- Recommended style for modeling sequential logic.
 - Can be used to assign several 'reg' type variables synchronously, under the control of a common clock.

58

Some Rules to be Followed

- Verilog synthesizer ignores the delays specified in a procedural assignment statement.
 - May lead to functional mismatch between the design model and the synthesized netlist.
- A variable cannot appear as the target of *both* a blocking and a non-blocking assignment.
 - Following is not permissible:

```
value = value + 1;  
value <= init;
```

59

// Up-down counter (synchronous clear)

```
module counter (mode, clr, ld, d_in, clk, count);  
  input mode, clr, ld, clk;   input [0:7] d_in;  
  output [0:7] count;        reg [0:7] count;  
  always @ (posedge clk)  
    if (ld)  
      count <= d_in;  
    else if (clr)  
      count <= 0;  
    else if (mode)  
      count <= count + 1;  
    else  
      count <= count + 1;  
endmodule
```

60

// Parameterized design:: an N-bit counter

```
module counter (clear, clock, count);  
  parameter N = 7;  
  input clear, clock;  
  output [0:N] count;      reg [0:N] count;  
  
  always @ (negedge clock)  
    if (clear)  
      count <= 0;  
    else  
      count <= count + 1;  
endmodule
```

61

// Using more than one clocks in a module

```
module multiple_clk (clk1, clk2, a, b, c, f1, f2);  
  input clk1, clk2, a, b, c;  
  output f1, f2;  
  reg f1, f2;  
  always @ (posedge clk1)  
    f1 <= a & b;  
  always @ (negedge clk2)  
    f2 <= b ^ c;  
endmodule
```

62

// Using multiple edges of the same clock

```
module multi_phase_clk (a, b, f, clk);  
  input a, b, clk;  
  output f;  
  reg f, t;  
  always @ (posedge clk)  
    f <= t & b;  
  always @ (negedge clk)  
    t <= a | b;  
endmodule
```

63

A Ring Counter Example

```
module ring_counter (clk, init, count);  
  input clk, init;    output [7:0] count;  
  reg [7:0] count;  
  always @ (posedge clk)  
  begin  
    if (init)  
      count = 8'b10000000;  
    else begin  
      count    = count << 1;  
      count[0] = count[7];  
    end  
  end  
endmodule
```

64

A Ring Counter Example (Modified--1)

```
module ring_counter_modi1 (clk, init, count);
input clk, init;    output [7:0] count;
reg [7:0] count;
always @ (posedge clk)
begin
    if (init)
        count = 8'b10000000;
    else begin
        count    <= count << 1;
        count[0] <= count[7];
    end
end
endmodule
```

65

A Ring Counter Example (Modified – 2)

```
module ring_counter_modi2 (clk, init, count);
input clk, init;    output [7:0] count;
reg [7:0] count;
always @ (posedge clk)
begin
    if (init)
        count = 8'b10000000;
    else
        count = {count[6:0], count[7]};
endmodule
```

66

About “Loop” Statements

- Verilog supports four types of loops:
 - ‘while’ loop
 - ‘for’ loop
 - ‘forever’ loop
 - ‘repeat’ loop
- Many Verilog synthesizers supports only ‘for’ loop for synthesis:
 - Loop bound must evaluate to a constant.
 - Implemented by unrolling the ‘for’ loop, and replicating the statements.

67

Modeling Memory

- Synthesis tools are usually not very efficient in synthesizing memory.
 - Best modeled as a component.
 - Instantiated in a design.
- Implementing memory as a two-dimensional register file is inefficient.

68

```

module memory_example (en, clk, adbus, dbus,
                      rw);

    parameter N = 16;
    input  en, rw, clk;
    input [N-1:0] adbus;
    output [N-1:0] dbus;
    .....
    ROM Mem1 (clk, en, rw, adbus, dbus);
    .....
endmodule

```

69

Modeling Tri-state Gates

```

module bus_driver (in, out, enable);
    input enable;      input [0:7] in;
    output [0:7] out;  reg [0:7] out;

    always @ (enable or in)
        if (enable)
            out = in;
        else
            out = 8'bz;
endmodule;


```

70


Modeling Finite State Machines

- Two types of FSMs

- Moore Machine

 

- Mealy Machine

 


71

Moore Machine : Example 1

- Traffic Light Controller

 - Simplifying assumptions made
- Three lights only (RED, GREEN, YELLOW)
- The lights glow cyclically at a fixed rate
 - Say, 10 seconds each
 - The circuit will be driven by a clock of appropriate frequency



72

```

module traffic_light (clk, light);
    input clk;
    output [0:2] light;    reg [0:2] light;
    parameter S0=0, S1=1, S2=2;
    parameter RED=3'b100, GREEN=3'b010,
               YELLOW=3'b001;

    reg [0:1] state;
    always @ (posedge clk)
        case (state)
            S0: begin                // S0 means RED
                    light <= YELLOW;
                    state <= S1;
                end

```

73

```

            S1: begin                // S1 means YELLOW
                    light <= GREEN;
                    state <= S2;
                end
            S2: begin                // S2 means GREEN
                    light <= RED;
                    state <= S0;
                end
            default: begin
                    light <= RED;
                    state <= S0;
                end
        endcase
    endmodule

```

74

- **Comment on the solution**
 - **Five flip-flops are synthesized**
 - Two for 'state'
 - Three for 'light' (outputs are also latched into flip-flops)
 - **If we want non-latched outputs, we have to modify the Verilog code.**
 - Assignment to 'light' made in a separate 'always' block.
 - Use blocking assignment.

75

```

module traffic_light_nonlatched_op (clk, light);
  input clk;
  output [0:2] light;   reg [0:2] light;
  parameter S0=0, S1=1, S2=2;
  parameter RED=3'b100, GREEN=3'b010,
             YELLOW=3'b001;
  reg [0:1] state;
  always @ (posedge clk)
    case (state)
      S0:    state <= S1;
      S1:    state <= S2;
      S2:    state <= S0;
      default: state <= S0;
    endcase

```

76

```


always @ (state)
  case (state)
    S0:    light = RED;
    S1:    light = YELLOW;
    S2:    light = GREEN;
    default: light = RED;
  endcase
endmodule

```

77

Moore Machine: Example 2

- Serial parity detector

 

78

```

module parity_gen (x, clk, z);
  input x, clk;
  output z;    reg z;
  reg even_odd; // The machine state
  parameter EVEN=0, ODD=1;

  always @ (posedge clk)
    case (even_odd)
      EVEN: begin
        z <= x ? 1 : 0;
        even_odd <= x ? ODD : EVEN;
      end

```

79

```

      ODD: begin
        z <= x ? 0 : 1;
        even_odd <= x ? EVEN : ODD;
      end
    endcase
endmodule


```

- If no output latches need to be synthesized, we can follow the principle shown in the last example.

80

Mealy Machine: Example

 - Sequence detector for the pattern '0110'.



81

// Sequence detector for the pattern '0110'

```
module seq_detector (x, clk, z)
```

```
  input x, clk;
```

```
  output z;      reg z;
```

```
  parameter S0=0, S1=1, S2=2, S3=3;
```

```
  reg [0:1] PS, NS;
```

```
  always @(posedge clk)
```

```
    PS <= NS;
```

82

```

always @ (PS or x)
case (PS)
  S0: begin
    z  = x ? 0 : 0;
    NS = x ? S0 : S1;
  end;
  S1: begin
    z  = x ? 0 : 0;
    NS = x ? S2 : S1;
  end;
  S2: begin
    z  = x ? 0 : 0;
    NS = x ? S3 : S1;
  end;

```

83

```


    S3: begin
      z  = x ? 0 : 1;
      NS = x ? S0 : S1;
    end;
  endcase
endmodule

```

84

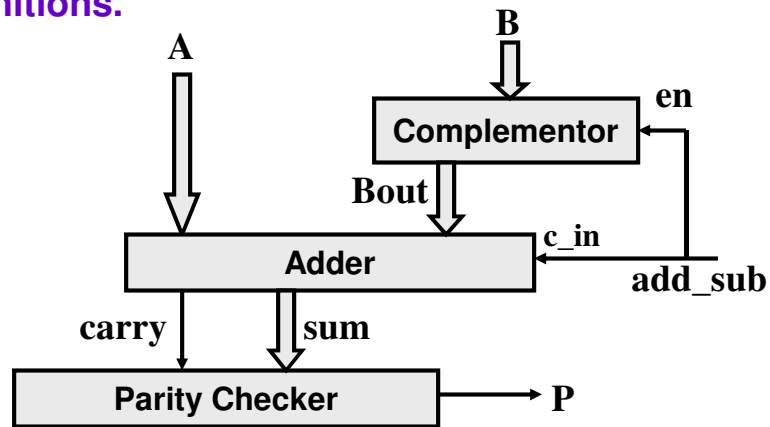Example with Multiple Modules

- A simple example showing multiple module definitions.



85

```
module complementor (Y, X, comp);  
  input [7:0] X;  
  input comp;  
  output [7:0] Y;  reg [7:0] Y;  
  
  always @ (X or comp)  
    if (comp)  
      Y = ~X;  
    else  
      Y = X;  
endmodule
```

86

```

module adder (sum, cy_out, in1, in2, cy_in);
  input [7:0] in1, in2;
  input cy_in;
  output [7:0] sum;    reg [7:0] sum;
  output cy_out;      reg cy_out;

  always @ (in1 or in2 or cy_in)
    {cy_out, sum} = in1 + in2 + cy_in;
endmodule

```

87

```

module parity_checker (out_par, in_word);
  input [8:0] in_word;
  output out_par;

  always @ (in_word)
    out_par = ^ (in_word);
endmodule

```

88

```
// Top level module
module add_sub_parity (p, a, b, add_sub);
    input [7:0] a, b;
    input add_sub;    // 0 for add, 1 for subtract
    output p;        // parity of the result
    wire [7:0] Bout, sum; wire carry;

    complementor M1 (Bout, B, add_sub);
    adder M2 (sum, carry, A, Bout, add_sub);
    parity_checker M3 (p, {carry, sum});
endmodule
```

89

Memory Modeling Revisited

- Memory is typically included by instantiating a pre-designed module.
- Alternatively, we can model memories using two-dimensional arrays.
 - Array of register variables.
 - Behavioral model of memory.
 - Mostly used for simulation purposes.
 - For small memories, even for synthesis.

90

Typical Example

```
module memory_model ( ..... )  
  
    reg [7:0] mem [0:1023];  
  
endmodule
```

91

How to Initialize memory

- By reading memory data patterns from a specified disk file.
 - Used for simulation.
 - Used in test benches.
- Two Verilog functions are available:
 1. \$readmemb (filename, memname, startaddr, stopaddr)
Data read in binary format.
 2. \$readmemh (filename, memname, startaddr, stopaddr)
Data read in hexadecimal format.

92

An Example

```
module memory_model ( ..... )
    reg [7:0] mem [0:1023];
    initial
        begin
            $readmemh ("mem.dat", mem);
        end
endmodule
```

93

A Specific Example :: Single Port RAM with Synchronous Read-Write

```
module ram_1 (addr, data, clk, rd, wr, cs)
    input [9:0] addr;  input  clk, rd, wr, cs;
    inout [7:0] data;
    reg [7:0] mem [1023:0];  reg [7:0] d_out;

    assign data = (cs && rd) ? d_out ; 8'bz;
    always @ (posedge clk)
        if (cs && wr && !rd) mem [addr] = data;
    always @ (posedge clk)
        if (cs && rd && !wr) d_out = mem [addr];
endmodule
```

94

A Specific Example :: Single Port RAM with Asynchronous Read-Write

```
module ram_2 (addr, data, rd, wr, cs)
    input [9:0] addr;  input rd, wr, cs;
    inout [7:0] data;
    reg [7:0] mem [1023..0];  reg [7:0] d_out;

    assign data = (cs && rd) ? d_out ; 8'bz;
    always @ (addr or data or rd or wr or cs)
        if (cs && wr && !rd) mem [addr] = data;
    always @ (addr or rd or wr or cs)
        if (cs && rd && !wr) d_out = mem [addr];
endmodule
```

95

A Specific Example :: ROM/EPROM


```
module rom (addr, data, rd_en, cs)
    input [2:0] addr;  input rd_en, cs;
    output [7:0] data;
    reg [7:0] data;
    always @ (addr or rd_en or cs)
        case (addr)
            0: 22;
            1: 45;
            .....
            7: 12;
        endcase
endmodule
```

96

Verilog Test Bench

- **What is test bench?**
 - A Verilog procedural block which executes only once.
 - Used for simulation.
 - Testbench generates clock, reset, and the required test vectors.

97

 

98

How to Write Testbench?

- **Create a dummy template**
 - Declare inputs to the module-under-test (MUT) as “reg”, and the outputs as “wire”
 - Instantiate the MUT.
- **Initialization**
 - Assign some known values to the MUT inputs.
- **Clock generation logic**
 - Various ways to do so.
- **May include several simulator directives**
 - Like \$display, \$monitor, \$dumpfile, \$dumpvars, \$finish.

99

- **\$display**
 - Prints text or variables to stdout.
 - Syntax same as “printf”.
- **\$monitor**
 - Similar to \$display, but prints the value whenever the value of some variable in the given list changes.
- **\$finish**
 - Terminates the simulation process.
- **\$dumpfile**
 - Specify the file that will be used for storing the waveform.
- **\$dumpvars**
 - Starts dumping all the signals to the specified file.

100

Example Testbench

```
module shifter_toplevel;
  reg clk, clear, shift;
  wire [7:0] data;

  shift_register S1 (clk, clear, shift, data);
  initial
  begin
    clk = 0; clear = 0; shift = 0;
  end
  always
    #10 clk = !clk;
endmodule
```

101

Testbench: More Complete Version

```
module shifter_toplevel;
  reg clk, clear, shift;
  wire [7:0] data;

  shift_register S1 (clk, clear, shift, data);
  initial
  begin
    clk = 0; clear = 0; shift = 0;
  end
  always
    #10 clk = !clk;
```

contd..

102

```

initial
begin
    $dumpfile ("shifter.vcd");
    $dumpvars;
end
initial
begin
    $display ("\ttime, \tclk, \tclr, \tsft, \tdata);
    $monitor ("%d, %d, %d, %d, %d", $time,
        clk, reset, clear, shift, data);

end
initial
    #400 $finish;
***** REMAINING CODE HERE *****
endmodule

```

103

A Complete Example

```

module testbench;
    wire w1, w2, w3;
    xyz m1 (w1, w2, w3);
    test_xyz m2 (w1, w2, w3);
endmodule

```

```

module xyz (f, A, B);
    input A, B; output f;
    nor #1 (f, A, B);
endmodule

```

contd..

104

```
module test_xyz (f, A, B);  
  input f;  
  output A, B;  
  reg A, B;  
  initial  
    begin  
      $monitor ($time, "A=%b", "B=%b", f=%b",  
                A, B, f);  
  
      #10 A = 0; B = 0;  
      #10 A = 1; B = 0;  
      #10 A = 1; B = 1;  
      #10 $finish;  
    end  
endmodule
```

105